

(a)

$$dU = dq \times V \quad \dots \mathbf{1}$$

$$dU = \frac{dq}{dt} \times dt \times V \quad \dots \mathbf{1}$$

$$P = \frac{dU}{dt} = \frac{dq}{dt} \times V = I \times V \quad \dots \mathbf{1}$$

$$R \equiv V/I, I = V/R \quad \dots \mathbf{0.5}$$

$$P = I \times V = \frac{V^2}{R} \quad \dots \mathbf{0.5}$$


(b)

$$P = \frac{V^2}{R} \quad \dots \mathbf{1}$$

$$R = \frac{10^2}{2500} = 0.04 \text{ } (\Omega) \quad \dots \mathbf{1}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{0.04} \quad \dots \mathbf{2}$$
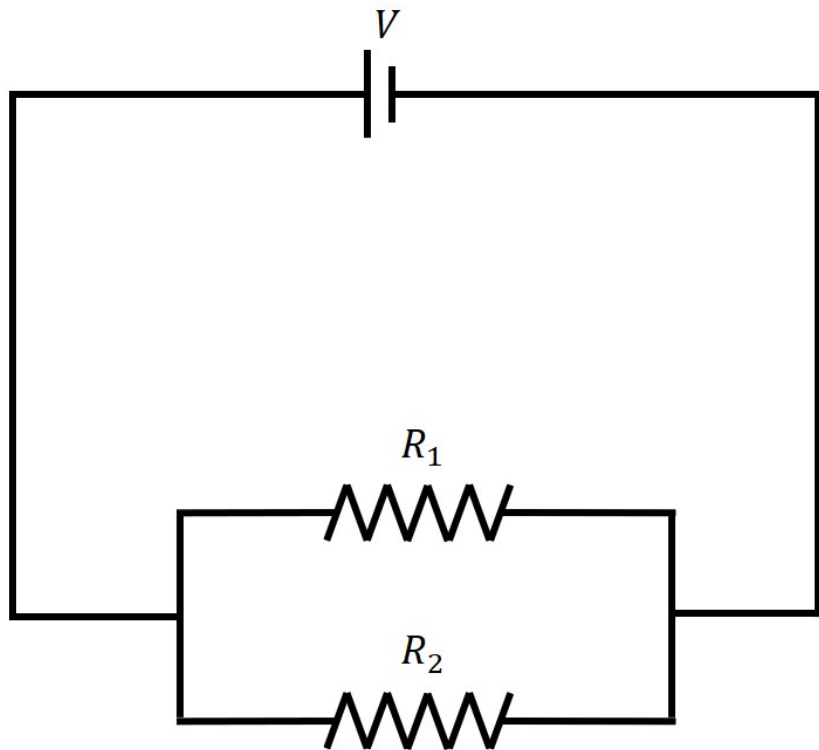
$$R_1 = R_2 = 0.08 \text{ } (\Omega) \quad \dots \mathbf{2}$$



Q.2 Figure 2. shows a parallel-plate capacitor of plate area $A = 12 \text{ m}^2$ and plate separation $3d = 6 \text{ m}$. The left half of the gap is filled with material of dielectric constant $\kappa_1 = 5$. The top, middle and bottom of the right half are filled with materials, with the same thickness d , of permittivity constants $\epsilon_2 = 2 \cdot \epsilon_0$, $\epsilon_3 = 4 \cdot \epsilon_0$ and $\epsilon_4 = 8 \cdot \epsilon_0$, respectively. The vacuum permittivity is $\epsilon_0 \text{ (F} \cdot \text{m}^{-1}\text{)}$. What is the capacitance? (10 points)

$$C_1 = \frac{(\kappa_1 \epsilon_0) \cdot (A/2)}{3d} = \frac{(5 \epsilon_0) \cdot (12/2)}{6} = 5 \epsilon_0 \text{ F} \quad (2)$$

$$C_2 = \frac{\epsilon_2 \cdot (A/2)}{d} = \frac{(2 \epsilon_0) \cdot (12/2)}{2} = 6 \epsilon_0 \text{ F} \quad (2)$$

$$C_3 = \frac{\epsilon_3 \cdot (A/2)}{d} = \frac{(4 \epsilon_0) \cdot (12/2)}{2} = 12 \epsilon_0 \text{ F} \quad (2)$$

$$C_4 = \frac{\epsilon_4 \cdot (A/2)}{d} = \frac{(8 \epsilon_0) \cdot (12/2)}{2} = 24 \epsilon_0 \text{ F} \quad (2)$$

$$C = 5 \epsilon_0 + \frac{1}{\frac{1}{6 \epsilon_0} + \frac{1}{12 \epsilon_0} + \frac{1}{24 \epsilon_0}} = \epsilon_0 \cdot \left(5 + \frac{24}{4+2+1} \right) = \frac{59}{7} \epsilon_0 \text{ F} \quad (2)$$

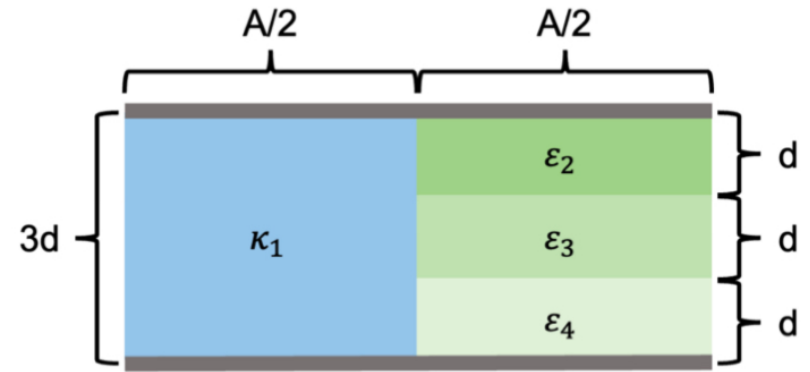


Figure 2