

Answers without **supporting work** or **necessary unit** will not be given full credit. If the meaning of the question isn't clear, please ask TA! You have **25mins** to complete this mini-test.

**Q.1** Figure 1. shows a disk with surface charge density  $\sigma = \frac{10}{3\pi} \text{ Cm}^{-2}$  and four points with different charge ( $q_1 = 10C$ ,  $q_2 = 27C$ ,  $q_3 = 9C$ ,  $q_4 = -6C$ ), the radius of disk  $R = 5m$  and the distance between origin and the center of disk is  $12m$ . What is the electric potential at origin? (10 points)

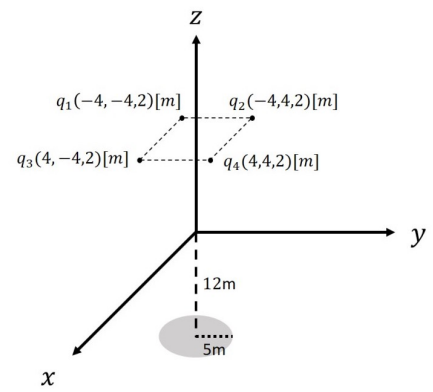


Figure 1

**Q.2** Figure 2. shows a symmetrical Wheatstone Bridge capacitor. The capacitance of  $C_1 = 3 F$ ,  $C_2 = 5 F$  and  $C_3 = 15 F$ . What is the equivalent capacitance  $C_{eq}$  of this circuit when system reaches equilibrium? (10 points)

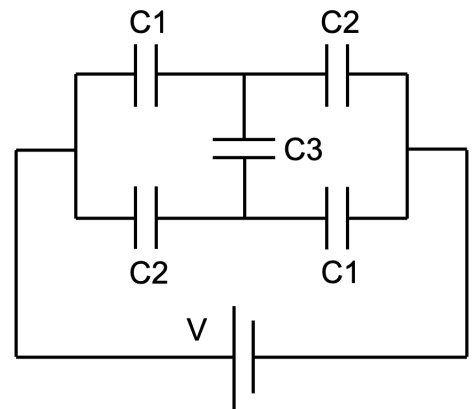


Figure 2