

An aerial photograph of a city grid, overlaid with various colors (green, purple, red, blue) to represent different zones or data. The grid lines are clearly visible, and the colors are applied in a somewhat irregular, block-like pattern.

## CHAPTER 3

# MOS Transistor Theory




# Outline

- 1. Introduction**
2. Ideal I-V Characteristics
3. Nonideal I-V Effects
4. C-V Characteristics
5. DC Transfer Characteristics
6. Switch-level RC Delay Models




# Introduction

- MOS Transistor symbols

– nMOS symbols

   


– pMOS symbols

   


# MOS Structure


– Accumulation Mode

 

– Depletion Mode

 

– Inversion Mode

 

# nMOS Operation Regions

- Cutoff


- $V_{gs} < V_t$  : no channel

- Linear

- $V_{gs} > V_t$ ,  $V_{gd} > V_t$  :  
linear resistor

- Saturation

 - $V_{gs} > V_t$ ,  $V_{gd} < V_t$  :  
channel pinchoff





# Outline

1. Introduction
- 2. Ideal I-V Characteristics**
3. Nonideal I-V Effects
4. C-V Characteristics
5. DC Transfer Characteristics
6. Switch-level RC Delay Models

# MOS Channel Charge

3- 7

  

$\text{SiO}_2$  Gate Oxide  
(Good insulator,  $\epsilon_{\text{ox}} = 3.9\epsilon_0$ )

Average gate to channel potential:

$$V_{gc} = (V_{gs} + V_{gd})/2 = V_{gs} - V_{ds}/2$$

$$Q_{\text{channel}} = C_g (V_{gc} - V_t) = C_g (V_{gs} - \frac{1}{2}V_{ds} - V_t)$$

$$C_g = \epsilon_{\text{ox}} WL/t_{\text{ox}} = C_{\text{ox}} WL$$

$$v = \mu E, E = V_{ds} / L, I_{ds} = \frac{Q_{\text{channel}}}{t_{\text{channel}}}, t_{\text{channel}} = \frac{L}{v}$$

# Ideal I-V Equations

$$Q_{channel} = C_{ox} WL \left( V_{gs} - \frac{1}{2} V_{ds} - V_t \right)$$

$$v = \mu E, E = V_{ds} / L,$$

$$\frac{L}{v} = \frac{L}{\mu E} = \frac{L^2}{\mu V_{ds}}$$


$$I_{ds} = \frac{Q_{channel}}{t_{channel}}, t_{channel} = \frac{L}{v}$$

- Ideal I-V equation

$$I_{ds} = \frac{Q_{channel}}{t_{channel}} = \frac{Q_{channel}}{L / v}$$

$$= \mu C_{ox} \frac{W}{L} \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

 
$$= \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$




$I_{ds} = \left\{ \begin{array}{l} \\ \\ \end{array} \right.$	$0$	$V_{gs} < V_t$	<b>cutoff</b>
	$\beta (V_{gs} - V_t - V_{ds}/2) V_{ds}$	$V_{ds} < V_{dsat} (= V_{gs} - V_t)$	<b>linear</b>
	$\frac{\beta}{2} (V_{gs} - V_t)^2$	$V_{ds} > V_{dsat} (= V_{gs} - V_t)$	<b>saturation</b>



# Ideal I-V Characteristics

 

• nMOS I-V

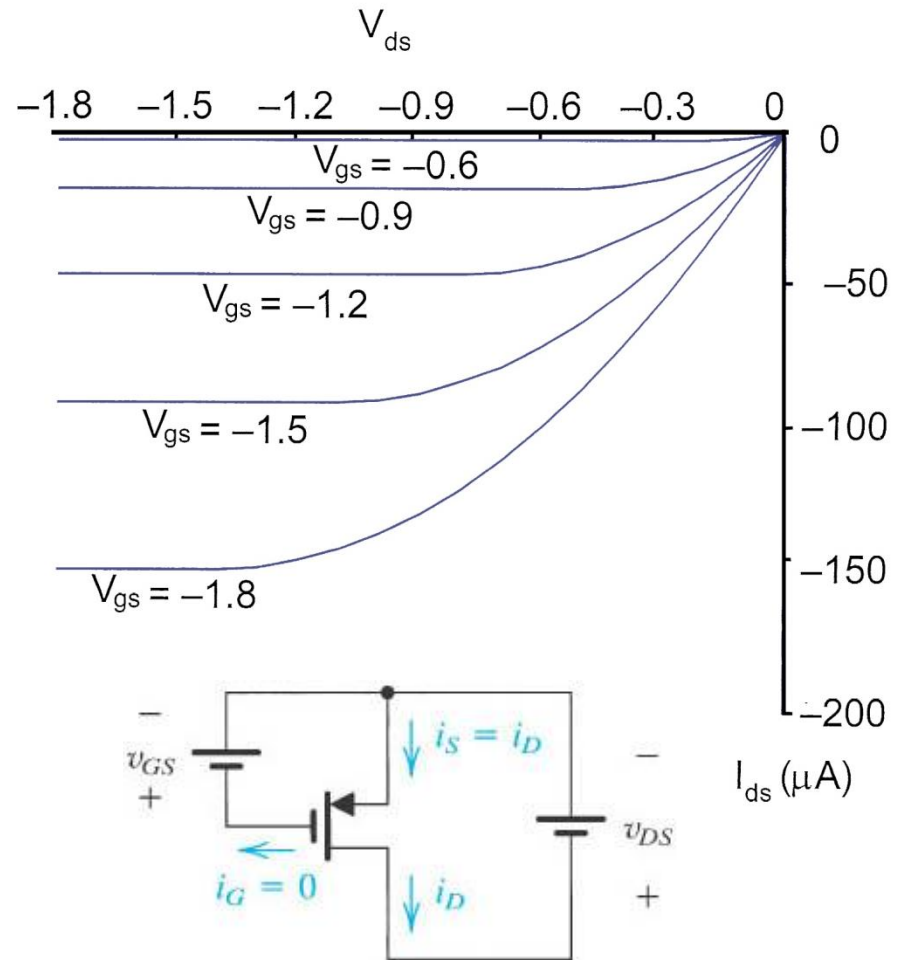

• pMOS I-V

# Outline

1. Introduction
2. Ideal I-V Characteristics
- 3. Nonideal I-V Effects**
4. C-V Characteristics
5. DC Transfer Characteristics
6. Switch-level RC Delay Models

# Nonideal I-V Effects

- **Velocity saturation**: at high  $V_{ds} \nearrow$ , the carrier velocity is not proportional to lateral field.  $I_{ds}$  decrease  $\searrow$ .
- **Mobility degradation**: at high  $V_{gs} \nearrow$ , the carrier scatter more and mobility decrease.  $I_{ds}$  decrease  $\searrow$ .
- **Channel length modulation effect**: at high  $V_{ds} \nearrow$ , depletion of S/D  $\nearrow$ , effective  $L \searrow$ .  $I_{ds}$  increase  $\nearrow$ .
- **Subthreshold conduction**:  $V_{gs} < V_t$ ,  $I_{ds}$  is exponentially dropoff instead of abruptly becoming zero.
- **Drain/Source leakage**: reverse diode junction leakage.
- **Non-zero gate current  $I_g$** : carriers tunneling effect.
- **Body effect**: threshold voltage  $V_t$  is influence by  $V_{bs}$  (body-to-source voltage).

# Velocity Saturation

- **Carrier velocity** : non-linearly proportional to lateral electrical field before velocity saturation


$$v = \mu E_{lat} / (1 + E_{lat} / E_{sat})$$

$v$  : carrier velocity

$\mu$  : mobility

$E_{lat} = V_{ds} / L$  : lateral electrical field

$E_{sat} = v_{sat} / \mu$

 

- $I_{ds}$  will saturate due to velocity saturation, it depends on channel length  $L$  and applied  $V_{ds}$ .

$$I_{ds} = \frac{Q_{channel}}{t_{channel}} = \frac{Q_{channel}}{L / v_{sat}} = C_{ox} W (V_{gs} - V_t) v_{sat}$$


# $\alpha$ -Power Law Model

- **$\alpha$ -Power Law Model**: piece-linear model to illustrate MOSs I-V characteristic with velocity saturation.

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ I_{dsat} \frac{V_{ds}}{V_{dsat}} & V_{ds} < V_{dsat} & \text{linear} \\ I_{dsat} & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

$$I_{dsat} = P_c \frac{\beta}{2} (V_{gs} - V_t)^\alpha, \quad V_{dsat} = P_v (V_{gs} - V_t)^{\alpha/2}$$


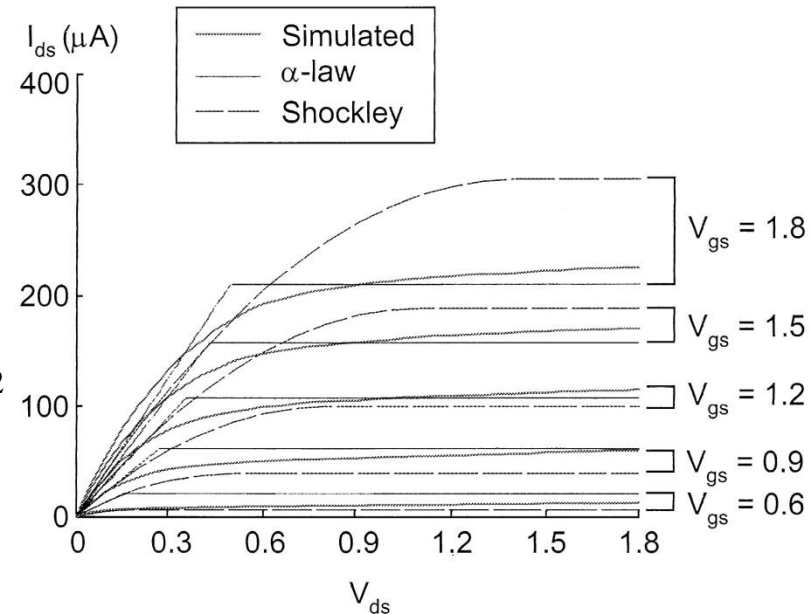
Empirical parameters:  $P_c, P_v, \alpha$



- **Because of  $\mu_p < \mu_n$** , pMOS experience less velocity saturation than nMOS, therefore  $\alpha_p > \alpha_n$
- **Mobility degradation** is modeled by a  $\mu_{\text{eff}} < \mu$ , and the it can be included in the parameter  $\alpha$
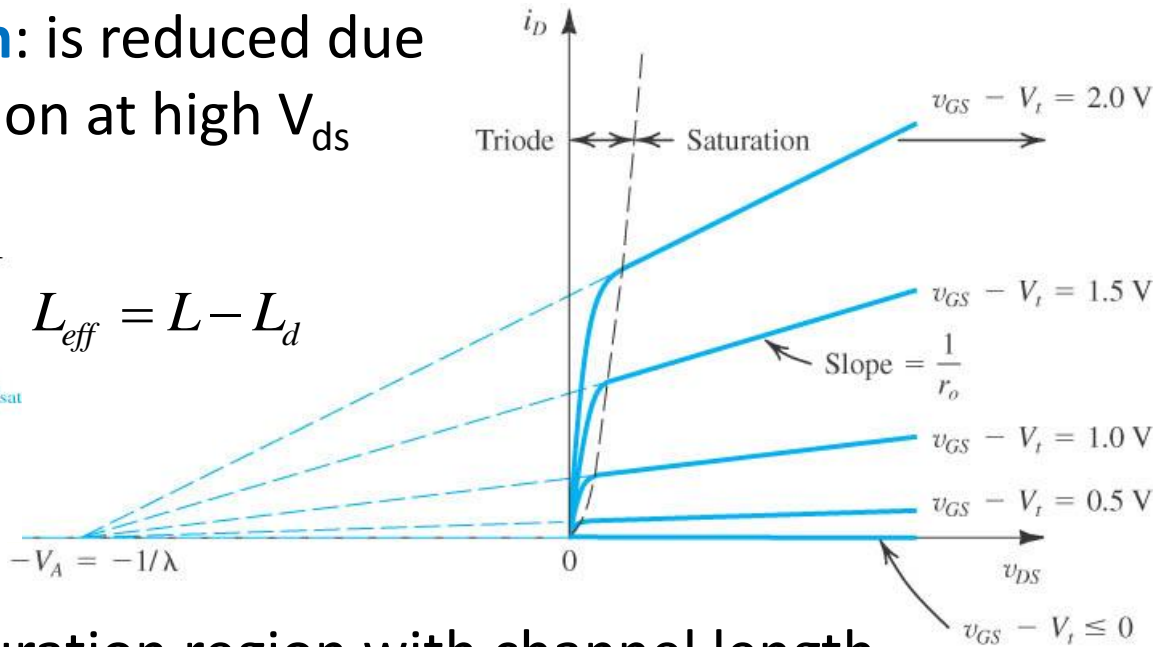 
# Channel Length Modulation

- **Effective channel length:** is reduced due to the wider depletion region at high  $V_{ds}$



- The I-V equation at saturation region with channel length modulation effect.  $\lambda'$  is the empirical parameter

$$I_{ds} = \beta \frac{(V_{gs} - V_t)^2}{2} (1 + \lambda V_{ds}), \lambda = \lambda' / L$$

- With shorter  $L \searrow$ ,  $\lambda \nearrow$ , result in **output resistance**  $\searrow$ , then MOSFET's **intrinsic gain**  $\searrow$

# Body Effect

- The threshold voltage  $V_t$  is increased by positive  $V_{sb}$ .
- $V_{sb} < 0$ ,  $V_t \searrow$ , OFF leakage  $\nearrow \rightarrow$  Design tradeoff

$$V_t = V_{t0} + \gamma[\sqrt{2\phi_s + V_{sb}} - \sqrt{2\phi_s}], \quad \phi_s = 2v_T \ln \frac{N_A}{n_i}$$

$V_{t0}$  : the threshold voltage for  $V_{sb} = 0$

$\phi_f$  : fabrication-process parameter

$$\gamma = \frac{t_{ox}}{\epsilon_{ox}} \sqrt{2qN_A \epsilon_{si}} = \frac{\sqrt{2qN_A \epsilon_{si}}}{C_{ox}}$$

$\gamma$  : Body-effect parameter  
(fabrication-process parameter)

$N_A$  : Doping concentration of p-type substrate

$\epsilon_s$  : permittivity of silicon =  $11.7 \epsilon_0$


# Subthreshold Conduction

- Leakage current at subthreshold region  $V_{gs} < V_t$  : weak inversion

$$I_{ds} = I_{ds0} e^{\frac{V_{gs}-V_t}{nV_T}} \left( 1 - e^{\frac{-V_{ds}}{V_T}} \right)$$

$$I_{ds0} = \beta v_T^2 e^{1.8}$$

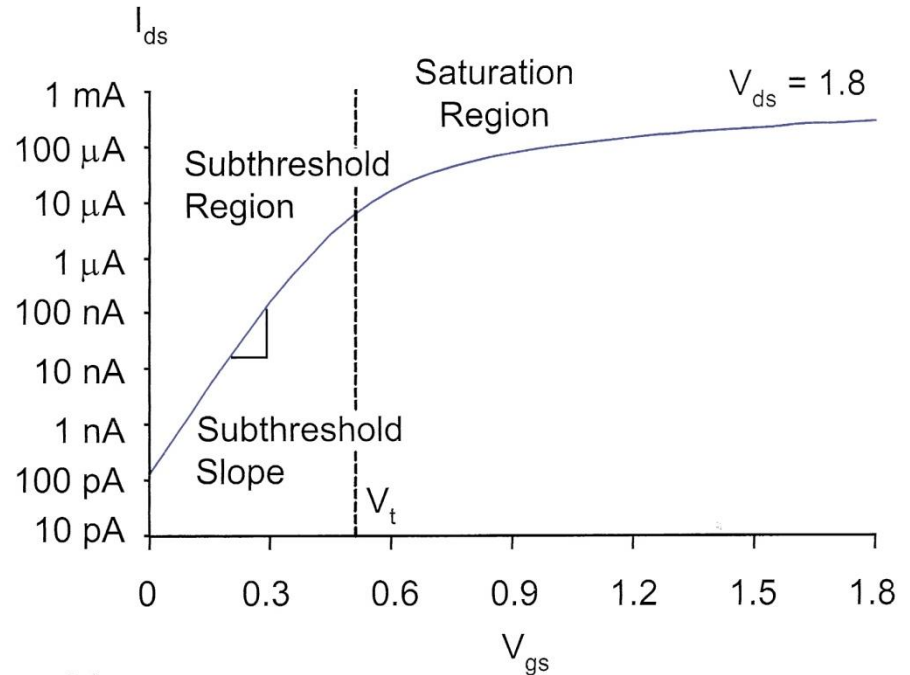- Leakage current = 0, when  $V_{ds} = 0$ . It increase exponentially with  $V_{gs}$ .




- Drain-Induced Barrier Lowering (DIBL)** : the  $V_t$  will be reduced by a positive  $V_{ds}$ . It will worsen the leakage at subthreshold. It acts like channel length modulation effect at active mode.

$$V'_t = V_t - \eta V_{ds}$$



# Junction Leakage

3- 17

 


- S/D junction leakage from a reverse-biased diode

$$I_D = I_S \left( e^{\frac{V_D}{V_T}} - 1 \right)$$

- Junction leakage used to be the storage time limitation. In modern transistor with shorter length, subthreshold leakage far exceed junction leakage.

# Tunneling

 


- Gate leakage: from carriers' tunneling through gate oxide. It is exponentially reverse proportional to gate oxide.
- Hi-K (dielectric constant) gate insulator is used to reduce it.

 
# Temperature Dependence

3- 19

- $T \nearrow \mu \searrow: \mu(T) = \mu(T_r) \left( \frac{T}{T_r} \right)^{-k_\mu}$



 - $T \nearrow V_t \searrow: V_t(T) = V_t(T_r) - k_{vt} (T - T_r)$





- $T \nearrow I_{OFF} \nearrow I_{ON} \searrow$

- $T \nearrow I_{dsat} \searrow$

- $T \searrow$  The circuit performance is improved: subthreshold leakage  $\searrow$ , saturation velocity  $\nearrow$ , mobility  $\nearrow$ , junction capacitance  $\searrow$ . But breakdown voltage  $\searrow$ .

# Geometry Dependence

3- 20

  

- Effective channel length and width

$$L_{eff} = L_{drawn} + X_L - 2L_D \quad X_L, X_W : \text{Poly over-etch}$$

$$W_{eff} = W_{drawn} + X_W - 2W_D \quad L_D, W_D : \text{Source-drain lateral diffusion}$$

- Use identical and same orientation MOSFET to get a good matching. ex. Current mirror

# Outline



1. Introduction
2. Ideal I-V Characteristics
3. Nonideal I-V Effects
- 4. C-V Characteristics**
5. DC Transfer Characteristics
6. Switch-level RC Delay Models

# C-V Characteristics



- **Gate capacitance:** with advance technology,  $t_{ox} \searrow$ ,  $L \searrow$ ,  $C_{permicron}$  keeps constant.

$$C_g = C_{ox}WL = C_{permicron}W$$
 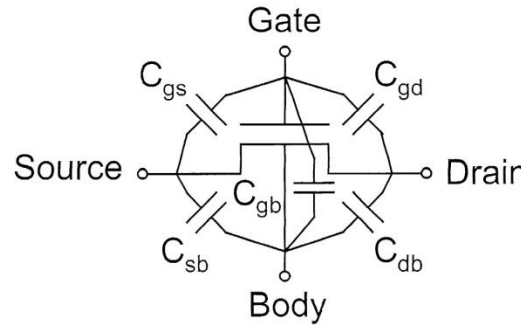
$$C_{permicron} = C_{ox}L = \frac{\epsilon_{ox}}{t_{ox}}L$$



  - **Parasitic capacitance:**  $C_{db}$  and  $C_{sb}$  are from reverse p-n junction and proportional to S/D area.



# MOS Gate Capacitance Model

- **Gate capacitance:** it varies with channel behavior at different operation region

**Table 2.1** Approximation of intrinsic MOS gate capacitance


Parameter	Cutoff	Linear	Saturation
$C_{gb}$	$C_0$	0	0
$C_{gs}$	0	$C_0/2$	$2/3 C_0$
$C_{gd}$	0	$C_0/2$	0
$C_g = C_{gs} + C_{gd} + C_{gb}$	$C_0$	$C_0$	$2/3 C_0$

$$C_0 = C_{ox}WL$$

- **S/D overlap capacitance:**  $C_{gs(overlap)}$  &  $C_{gd(overlap)}$  are from S/D lateral diffusion, don't confused with  $C_{gs}$  &  $C_{gd}$

$$C_{gs(overlap)} = C_{gsol}W$$



$$C_{gd(overlap)} = C_{gdol}W$$

 

# $C_{gc}$ vs. $V_{gs}$ & $V_{ds}$

- $C_{gc}$  vs.  $V_{gs}$

- $C_{gc}$  vs.  $V_{ds}$

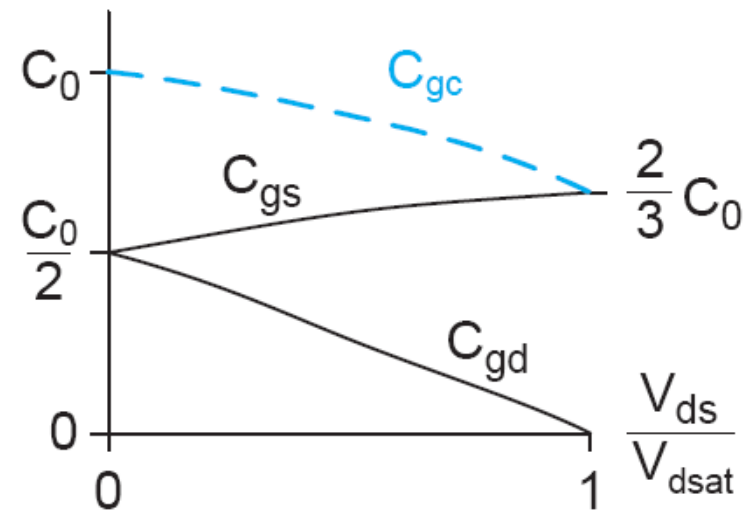 




 
# Gate Capacitance vs. $V_{ds}$

3- 25

- **Long channel device:**  $C_{gd}$  will become near 0 at saturation




 - **Short channel device:** more  $C_{gd(overlap)}$  and  $C_{gs(overlap)}$  factor



# Data-Dependent Gate Capacitance


3- 26

 

# Outline

1. Introduction
2. Ideal I-V Characteristics
3. Nonideal I-V Effects
4. C-V Characteristics
- 5. DC Transfer Characteristics**
6. Switch-level RC Delay Models



# CMOS Inverter DC Characteristic I

 

**Table 2.2** Relationships between voltages for the three regions of operation of a CMOS inverter


	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

# CMOS Inverter DC Characteristic II

  

- $I_{ds}$  vs.  $V_{ds}$  (nMOS & pMOS)
- For pMOS,  $I_d, V_{gs}, V_{ds}, V_{th} < 0$
- pMOS I-V as load-line of nMOS input device.

$I_{dsn}, |I_{dsp}|$


 


# CMOS Inverter DC Characteristic III

3- 30

- $V_{in} - V_{out}$  DC transfer curve
- Rail-to-rail operation

  - $V_{in} - I_{DD}$  DC transfer curve
- Dynamic power dissipation



# DC Response

- DC Response:  $V_{out}$  vs.  $V_{in}$  for a gate

- Ex: Inverter

– When  $V_{in} = 0$   $\rightarrow V_{out} = V_{DD}$

– When  $V_{in} = V_{DD}$   $\rightarrow V_{out} = 0$


– In between,  $V_{out}$  depends on transistor size and current

– By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

– We could solve equations

 – But graphical solution gives more insight



# Transistor Operation


- Current depends on region of transistor behavior
- For what  $V_{in}$  and  $V_{out}$  are nMOS and pMOS in
  - Cutoff?
  - Linear?
  - Saturation?



# nMOS Operation

3- 33


<b>Cutoff</b>	<b>Linear</b>	<b>Saturated</b>
$V_{gsn} <$	$V_{gsn} >$	$V_{gsn} >$
	$V_{dsn} <$	$V_{dsn} >$

 

# nMOS Operation

3- 34

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

 


# nMOS Operation

3- 35

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


# nMOS Operation

3- 33

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$


$$V_{dsn} = V_{out}$$

 

# pMOS Operation

3- 37


Cutoff	Linear	Saturated
$V_{gsp} >$	$V_{gsp} <$	$V_{gsp} <$
	$V_{dsp} >$	$V_{dsp} <$

 

# pMOS Operation

3- 38

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$

 

# pMOS Operation


3- 39

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_{out} - V_{DD}$$

$$V_{tp} < 0$$

 

# pMOS Operation


3- 40

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{tp} < 0$$


$$V_{dsp} = V_{out} - V_{DD}$$

 



 
# I-V Characteristics

- Make pMOS is wider than nMOS such that  $\beta_n = \beta_p$




# Current vs. $V_{out}$ , $V_{in}$

 

# Load Line Analysis


3- 43

- For a given  $V_{in}$ :
  - Plot  $I_{dsn}$ ,  $I_{dsp}$  vs.  $V_{out}$
  - $V_{out}$  must be where |currents| are equal in

 


# Load Line Analysis

- $V_{in} = 0$

 


# Load Line Analysis

- $V_{in} = 0.2V_{DD}$

 

# Load Line Analysis


- $V_{in} = 0.4V_{DD}$

 

# Load Line Analysis


3- 47

- $V_{in} = 0.6V_{DD}$

 

# Load Line Analysis


- $V_{in} = 0.8V_{DD}$

 




# Load Line Analysis

- $V_{in} = V_{DD}$


 


# Load Line Summary

 
  
# DC Transfer Curve


- Transcribe points onto  $V_{in}$  vs.  $V_{out}$  plot



# Operating Regions

- Revisit transistor operating regions


Region	nMOS	pMOS
A		
B		
C		
D		
E		

 

# Operating Regions

- Revisit transistor operating regions


Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 

# CMOS Inverter Operation

**Table 2.3** Summary of CMOS inverter operation

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 


# Beta Ratio Effect

- $\beta$  parameters and ratio

$$\beta_p = \mu_p C_{ox} (W/L)_p$$

$$\beta_n = \mu_n C_{ox} (W/L)_n$$
 
$$\beta \text{ ratio} = \beta_p / \beta_n$$



- $\beta$  ratio = 1: largest noise margin
  - $\because \mu_n > \mu_p$ , choose  $(W/L)_p > (W/L)_n$  to make  $\beta$  ratio = 1
- $\beta$  ratio > 1: HI-skewed inverter, switching threshold  $> 0.5V_{DD}$
- $\beta$  ratio < 1: LO-skewed inverter, switching threshold  $< 0.5V_{DD}$

# Noise Margin I

- Noise margin definition
  - The allowable noise voltage on the input that the output wont be corrupted.

$$NM_L = V_{IL} - V_{OL}$$


$$NM_H = V_{OH} - V_{IH}$$

$V_{IH}$  = minimum HIGH input voltage

$V_{IL}$  = maximum LOW input voltage

$V_{OH}$  = minimum HIGH output voltage

$V_{OL}$  = maximum LOW output voltage

 



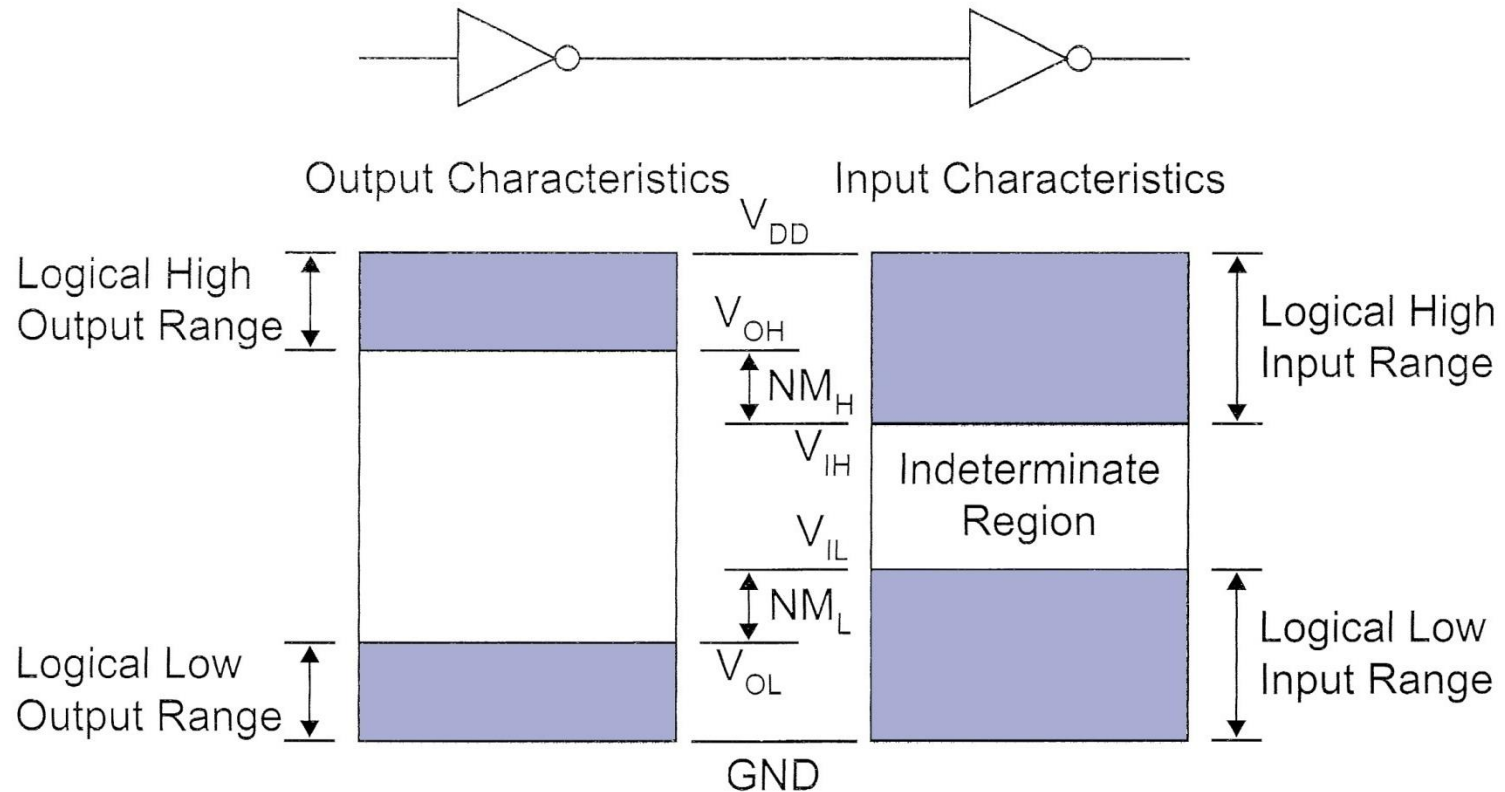
# Noise Margin II

- *Indeterminate region (forbidden zone)*


$$V_{IL} < V_{in} < V_{IH} : output = \text{unknown logic level}$$


 
# $\beta$ Ratio and Noise Margin

3- 58



- $\beta$  ratio  $> 1$ 
  - Switching threshold  $> 0.5V_{DD}$
  - $V_{IH} \nearrow NM_H \searrow$
  - $V_{IL} \nearrow NM_L \nearrow$
- $\beta$  ratio  $< 1$ 
  - Switching threshold  $< 0.5V_{DD}$
  - $V_{IH} \searrow NM_H \nearrow$
  - $V_{IL} \searrow NM_L \searrow$
  - Noise is scaled with  $V_{DD}$
  - $V_{DD} \searrow$ , smaller NM is acceptable.


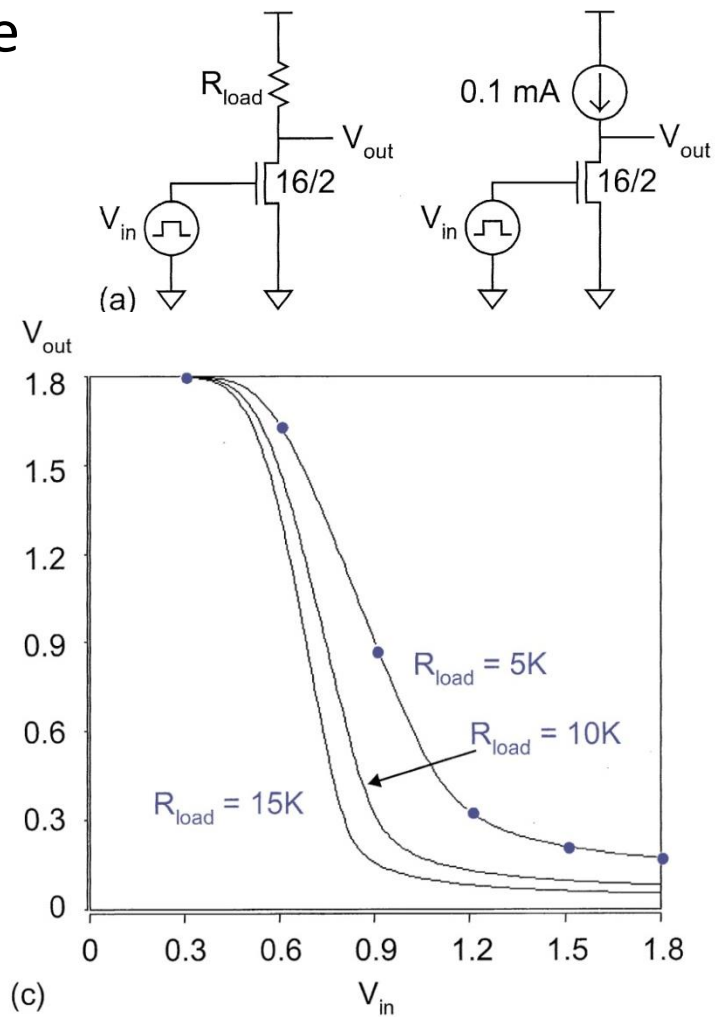 
# Ratioed Inverter Transfer Function I

3- 59





- nMOS inverters with resistive or constant current load
  - Transfer function depends on the ratio of pull-down to the pull-up transistor (*static load*).


    
# Ratioed Inverter Transfer Function II







3- 60

- Pseudo-nMOS inverters with turn-ON pMOS as load
  - Turn-ON pMOS is made by a depletion mode nMOS in pure nMOS process.
  - **Dissipating static power when  $V_o = \text{LOW}$**
  - **Poor NM but smaller area & input capacitance loading**


      
# Pass Transistor DC Characteristic





- Threshold drop
  - nMOS : **can NOT** pass “1”
  - pMOS : **can NOT** pass “0”
  - Need to consider **BODY EFFECT**.
- ON resistance depends on  $V_{in}$ 
  - Need to **BOOST** gate voltage with small  $V_{DD}$


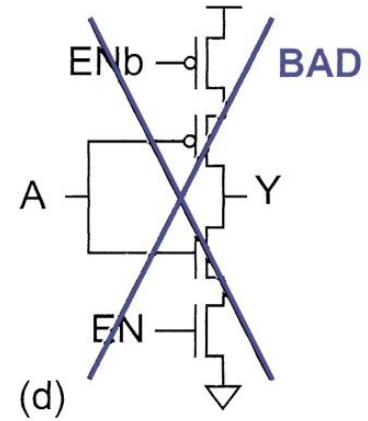   
# Tristate Inverter

3- 62

- Inverter + transmission gate
  - For the same size n and p devices, it is approximately half the speed of complementary CMOS inverter.
  - The structure in (d) is suffered from A's toggle in tristate.
  - Need to consider **BODY EFFECT**.



# Outline

1. Introduction
2. Ideal I-V Characteristics
3. Nonideal I-V Effects
4. C-V Characteristics
5. DC Transfer Characteristics
- 6. Switch-level RC Delay Models**

# Effective Resistance $R$

- **$R$ : effective resistance** of unit nMOS (minimum  $W$  &  $L$ )
  - An pMOS has resistance  $2R$ (or  $3R$ ) because of smaller mobility
  - **In linear region**, it is inverse proportional to  $W/L$  and  $V_{gs}$



$$R = \left( \frac{\partial I_{ds}}{\partial V_{ds}} \right)^{-1} = \frac{1}{\beta(V_{gs} - V_t)} = \frac{1}{\mu C_{ox}} \frac{L}{W} \frac{1}{(V_{gs} - V_t)}$$

- **$C$ : gate capacitance** of unit transistor (nMOS & pMOS)
  - It is proportional to gate area  $W*L$
- **$C$ : junction capacitance** of S/D of unit transistor
  - It is proportional to gate width  $W$
- nMOS of  $k$  times unit width has resistance  $R/k$ , gate capacitance  $kC$  and S/D capacitance  $kC$ .


  
# RC Circuit Model

- pMOS of  $k$  times unit width has resistance  $2R/k$ , gate capacitance  $kC$  and S/D capacitance  $kC$ 
  - nMOS parasitic capacitors are referred to GND (p-body) and pMOS parasitic capacitors are referred to VDD (n-well)




# Inverter Propagation Delay

- Fanout-of-1 Inverter

- Choose pMOS width size to be x2~x3 of that of nMOS

$$t_{pd} = R \bullet (6C) = 6RC$$

 

# R of Transmission Gate

3- 67

- Effective resistance of transmission gate is the parallel combination of nMOS and pMOS
  - It depends on the signal to be pass
  - pMOS pass 0 weakly with larger resistance  $4R$
  - nMOS pass 1 weakly with larger resistance  $2R$
  - Usually choose same size of nMOS/pMOS in transmission gate
  - Increase MOS size  $\rightarrow R \searrow C \nearrow$ : need to check the tradeoff

