



CHAPTER 4

Circuit Characterization and Performance Estimation I

Outline

- 1. Delay Estimation**
2. Logical Effort and Transistor Sizing
3. Power Dissipation
4. Interconnect
5. Wire Engineering
6. Design Margin
7. Reliability
8. Scaling

Transient Response

- DC analysis tells us V_{out} if V_{in} is constant
- Transient analysis tells us $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations
- Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa


Inverter Step Response

- Find step response of inverter driving load cap


$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$
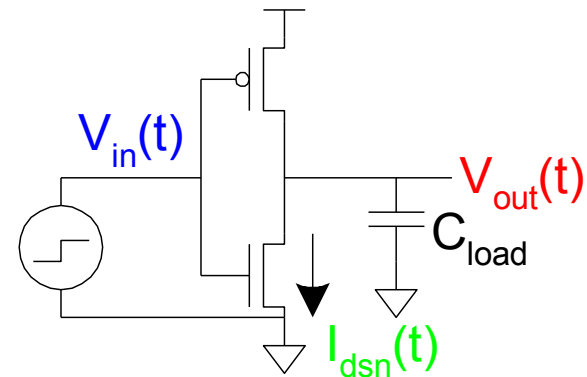
$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$



 
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V_t)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Definitions (1/3)


- t_{pdr} : *maximum rising propagation delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{pdf} : *maximum falling propagation delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- t_r : *rise time*
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- t_f : *fall time*
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$

Delay Definitions (2/3)

 


Delay Definitions (3/3)

 - t_{cdr} : *minimum rising contamination delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{cdf} : *minimum falling contamination delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{cd} : *average contamination delay*
 - $t_{cd} = (t_{cdr} + t_{cdf})/2$



Simulated Inverter Delay

 - Solving differential equations by hand is too difficult
- SPICE simulator solves the equations numerically
 - Use more accurate I-V models too
- But accurate simulations take time




Delay Estimation I

- Estimate delay easily
 - Not as accurate as simulation
 - Easier to ask “What if?”
- The step response usually looks like a 1st order RC response with a decaying exponential
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use effective resistance R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

Delay Estimation II



- **Critical path** : the signal path with the slowest (most critical) timing, it can be affected at 4 main levels.
- The **architectural/micro-architectural** level
 - Tradeoff of pipeline stages, number of execution units, and size of memory, **it's the level with the most impact factor.**
- The **logic** level
 - Tradeoff of functional block types, number of gate in the cycle, fan-in and fan-out number.
- The **circuit** level
 - Choosing transistor size and CMOS logic styles.
- The **layout** level
 - Determine floor plan, wire length, and check parasitic

Critical Path



 


RC Delay Models

  
- Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width



Example: Inverter

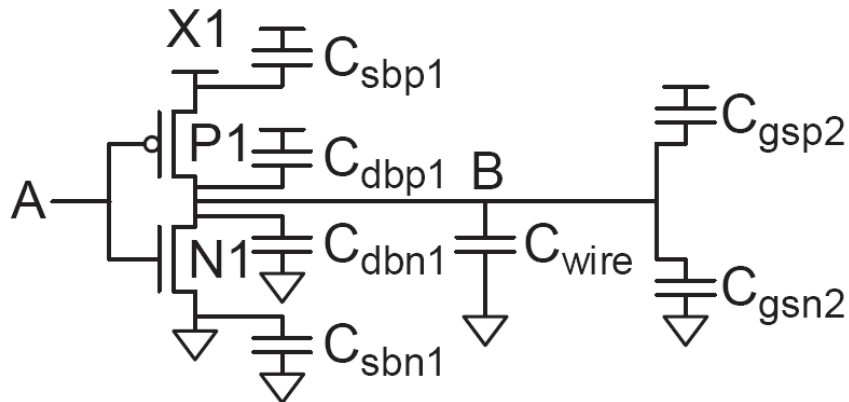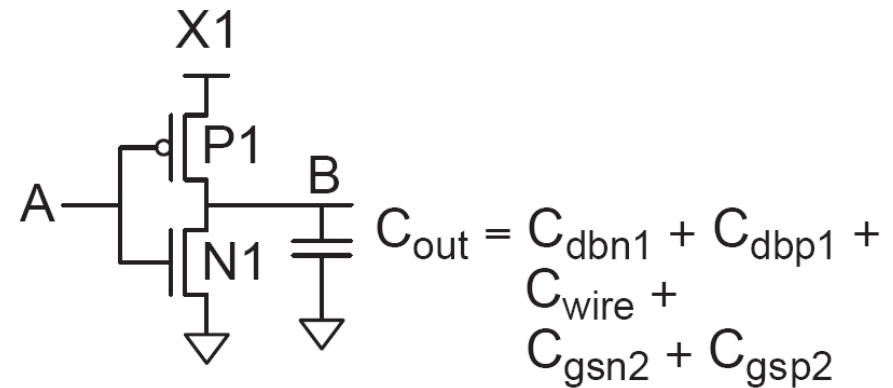 


Example: Inverter

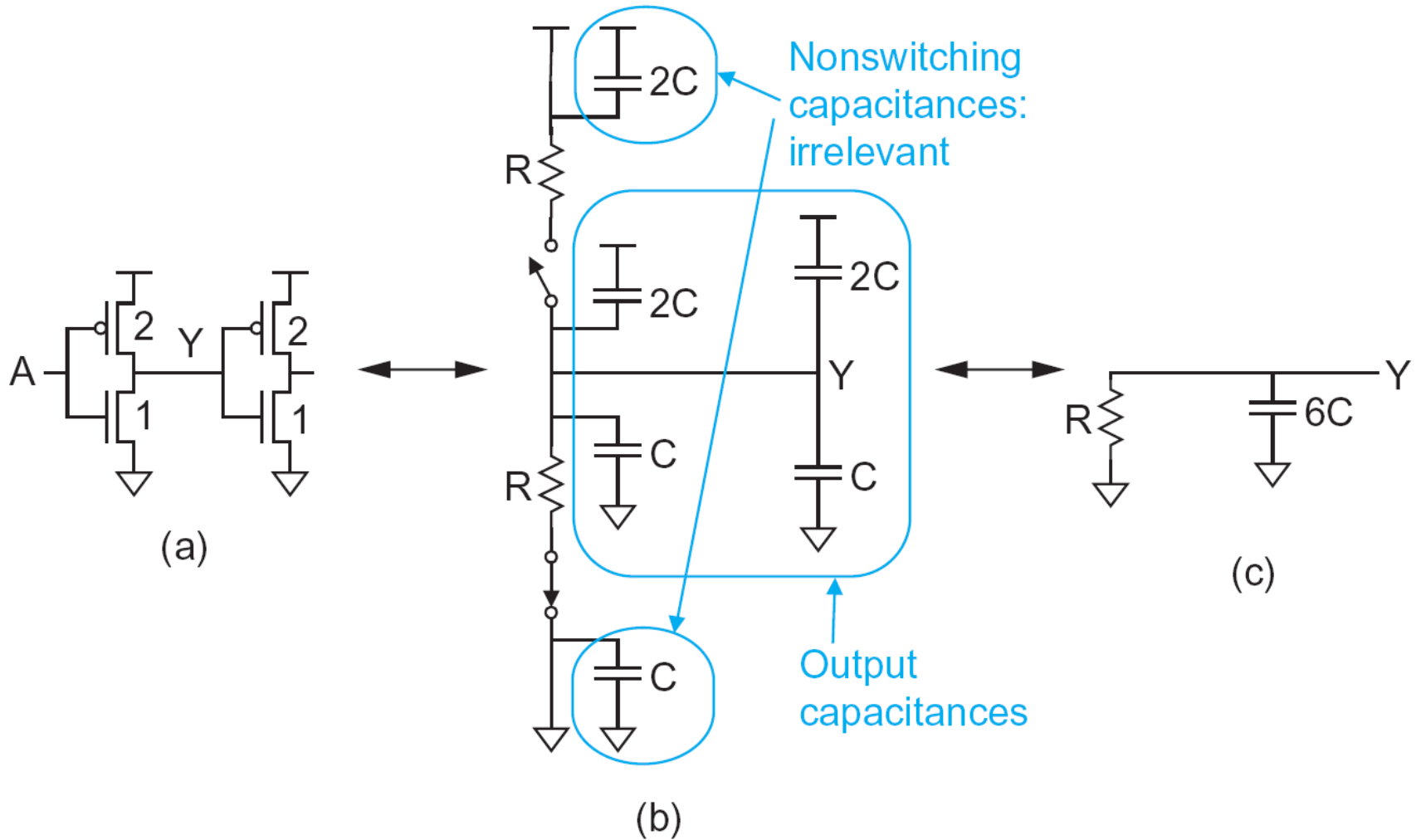

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances **equal to a unit inverter (R)**




3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




3-input NAND Caps

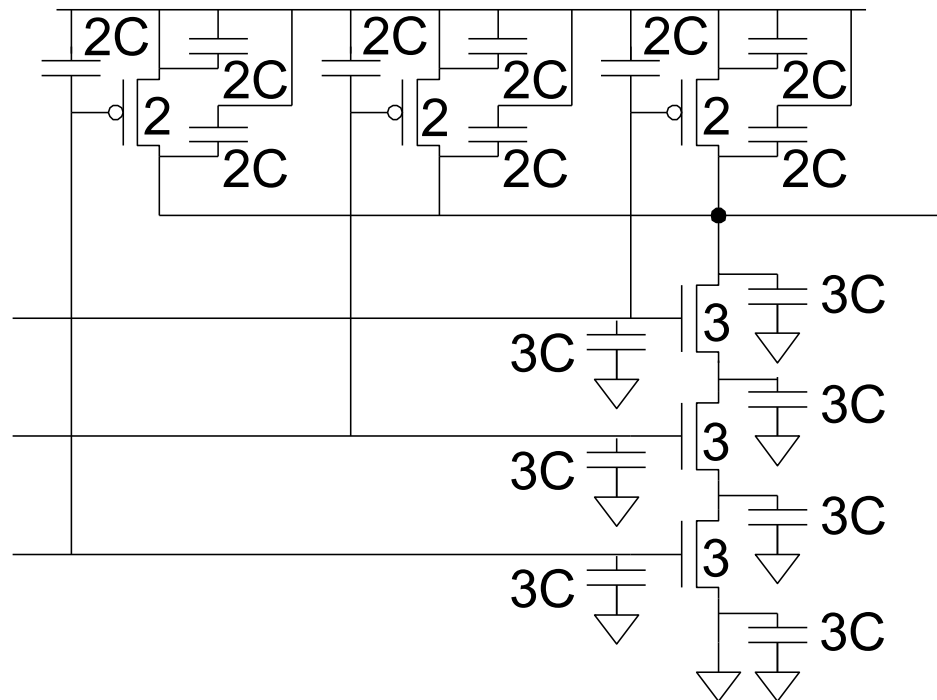- Annotate the 3-input NAND gate with gate and diffusion capacitance.





3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Delay of 3-input NAND

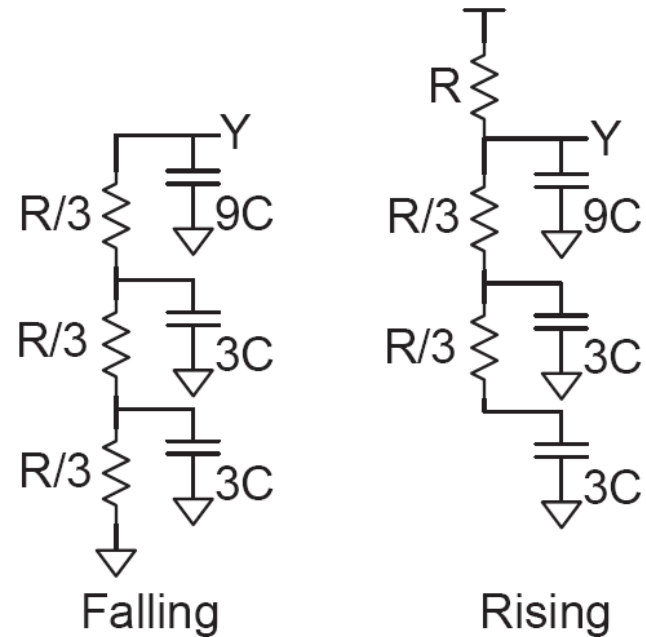 

Elmore Delay Model


- On transistors look like resistors
- Pullup or pulldown network can be modeled as RC ladder
- Elmore delay model of an RC ladder
 
$$t_{pd} = \sum_i R_{n-i} C_i = \sum_{i=1}^N C_i \sum_{j=1}^N R_j$$




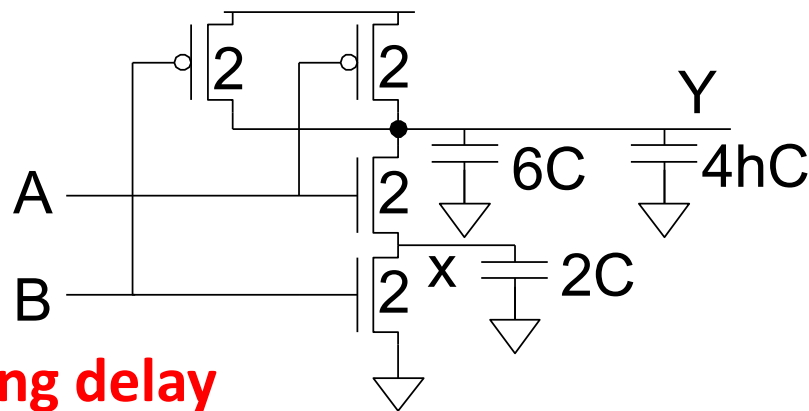Example: 2-input NAND


- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates



 
rising delay
(A=1, B=1->0 only 1 pMOS ON)



falling delay
(A=1, B=0->1, X,Y=1->0)

 


$$t_{pdr} = (6 + 4h) RC$$

 

$$t_{pdf} = (2C) \left(\frac{R}{2} \right) + [(6 + 4h)C] \left(\frac{R}{2} + \frac{R}{2} \right) = (7 + 4h) RC$$

Contamination Delay

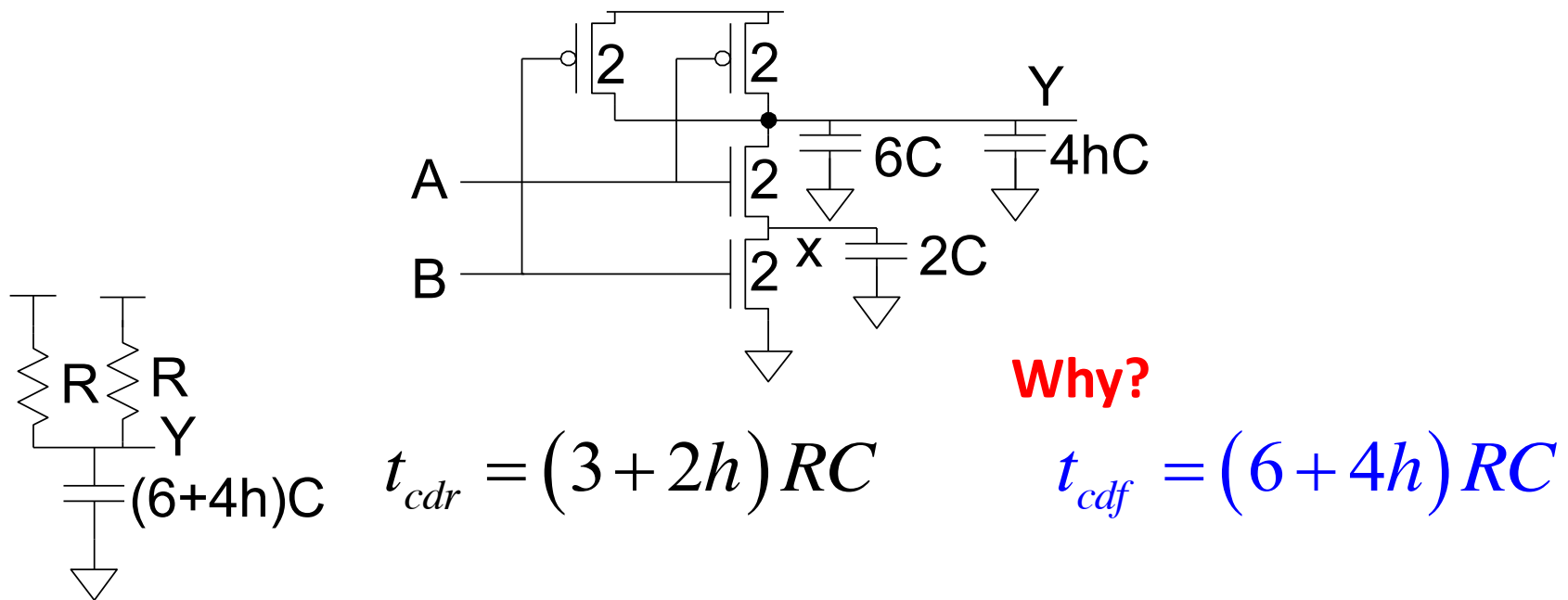
- Best-case (contamination) delay can be substantially less than propagation delay
- Example: If both inputs fall simultaneously



Latest input should be connected to transistor closest to the output



Diffusion Capacitance

 - Good layout minimizes diffusion area
- Example: NAND3 layout shares diffusion contact
 - Reduce output capacitance by $2C$
 - Merged un-contacted diffusion might help too



Layout Comparison

- Which layout is better

  

Delay Components

- Parasitic delay
 - 6 or 7 RC
 - Independent of load

$$t_{pdr} = (6 + 4h)RC$$

$$t_{pdf} = (7 + 4h)RC$$


- Effort delay
 - 4h RC
 - Proportional to load capacitance

Outline

 1. Delay Estimation
- 2. Logical Effort and Transistor Sizing**
3. Power Dissipation
4. Interconnect
5. Wire Engineering
6. Design Margin
7. Reliability
8. Scaling


Introduction

- Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries



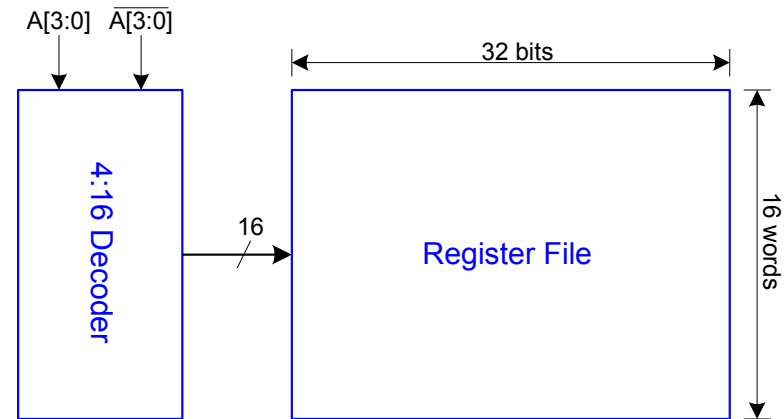Example

- Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC$$

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- *Effort delay* $f = gh$ (or *stage effort*)
 - Again has two components

Propagation Delay in a Logic Gate

4- 32

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (or stage effort)

- Again has two components

- g : *logical effort*

- Measures relative ability of gate to deliver current

- $g \equiv 1$ for inverter

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)

- Again has two components

- h : *electrical effort* = C_{out} / C_{in}

- Ratio of output to input capacitance

- Sometimes called fanout

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$


- Delay has two components

$$d = f + p$$


- Parasitic delay p
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

Computing Logical Effort

 
- The ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current
- Measure from delay vs. fanout plots or
- Estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 


$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Delay Plots


$$d = f + p$$
$$= gh + p$$

 

Delay Plots

$$d = f + p$$
$$= gh + p$$

- What about NOR2?

 

Catalog of Gates

- Logic effort of common gates

$$g_i = \frac{C_{in-i}}{C_{in-inv}} = \frac{C_{in-i}}{3C}$$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	(n+2)/3
NOR		5/3	7/3	9/3	(2n+1)/3
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

Catalog of Gates


- Parasitic delay of common gates
 - In multiples of $P_{inv}(\sim 1)$

$$p_i = \frac{C_{p-i}}{C_{p-inv}} = \frac{C_{p-i}}{3C}$$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logic Effort: $g = 1$

Electrical Effort: $h = 1$


Parasitic Delay: $p = 1$

Stage Delay: $d = 2$

Frequency: $f_{osc} = \frac{1}{2Nd} = \frac{1}{4N}$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter
 - *FO4 delay for a process (ps) is $\frac{1}{3}$ to $\frac{1}{2}$ of the channel length (nm). Ex. 180nm : FO4 = 60~90ps \rightarrow highly sensitive to process, voltage, temperature variation.*



Logic Effort: $g = 1$
Electrical Effort: $h = 4$
Parasitic Delay: $p = 1$
Stage Delay: $d = 5$

Multistage Logic Networks

- Logic effort generalizes to multistage networks

- Path logical effort


$$G = \prod g_i$$

- Path electrical effort

$$H = C_{out-path} / C_{in-path}$$

- Path effort

$$F = \prod f_i = \prod g_i h_i$$

 

Paths that Branch

- No! Consider paths that branch

$$G = 1$$


$$H = 90/5 = 18$$

$$GH = 18$$

$$h_1 = (15+15)/5 = 6$$

$$h_2 = 90/15 = 6$$

$$F = g_1g_2h_1h_2 = 36 = 2GH$$

 

Branching Effort

- Accounts for branching between stages in path

– *Branching effort*
$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

Note:

– *Path ranching effort*
$$B = \prod b_i \quad \prod h_i = BH$$

- Now we compute path effort

$$F = GBH$$

Multistage Delays

- Path effort delay

$$D_F = \sum f_i$$

- Path parasitic delay

$$P = \sum p_i$$

- Path delay

$$D = \sum d_i = D_F + P$$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logic effort
 - Find fastest possible delay
 - Doesn't require calculating gate size

Gate Size

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate with given load it drives
- Check work by verifying input cap spec is met

 
Example: 3-stage path

- Select gate size x and y for least delay from A to B



Example: 3-stage path

4- 49

 

Logical effort

$$G = (4/3)(5/3)(5/3) = 100/27$$

Electrical effort

$$H = 45/8$$

Branching effort

$$B = 3 * 2 = 6$$

Path effort

$$F = GBH = 125$$

Best stage effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic delay

$$P = 2 + 3 + 2 = 7$$

Delay


$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$

Example: 3-stage path

- Work backward for sizes

- $y = 45 * (5/3) / 5 = 15$


- $x = (15 * 2) * (5/3) / 5 = 10$

 

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fast
- Example: Drive 64-bit datapath with unit inverter


D =

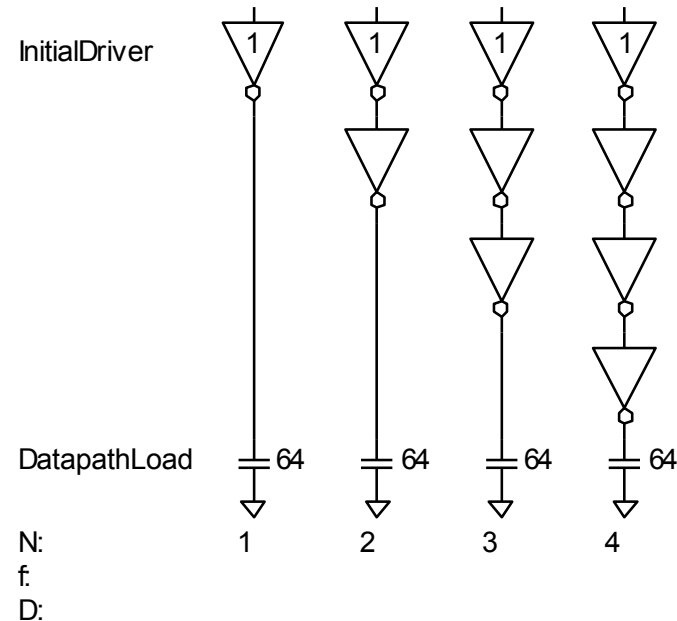

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fast
- Example: Drive 64-bit datapath with unit inverter

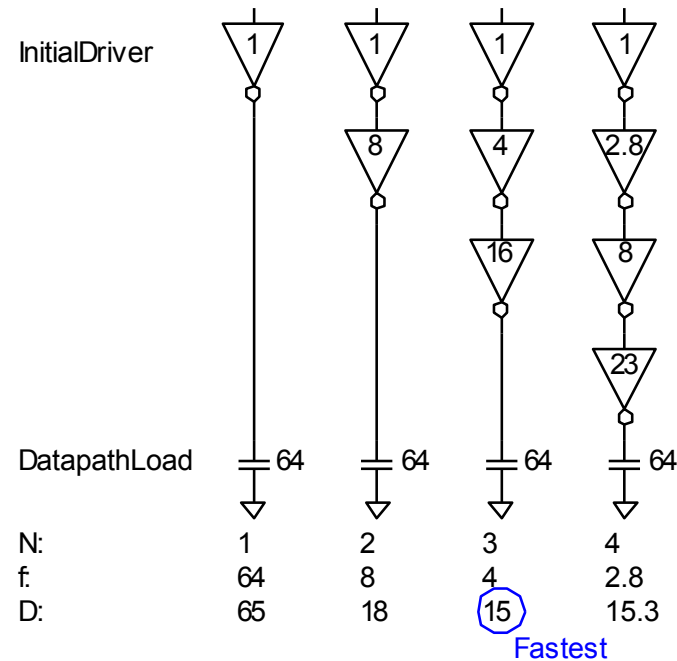
$$D = NF^{1/N} + P$$
$$= N(64)^{1/N} + N$$



Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

- $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv}=0$), we define
$$\rho = 2.718 (e)$$
- For $p_{inv}=1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 
- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay with 15% of optimal
 - 4 is a convenient choice

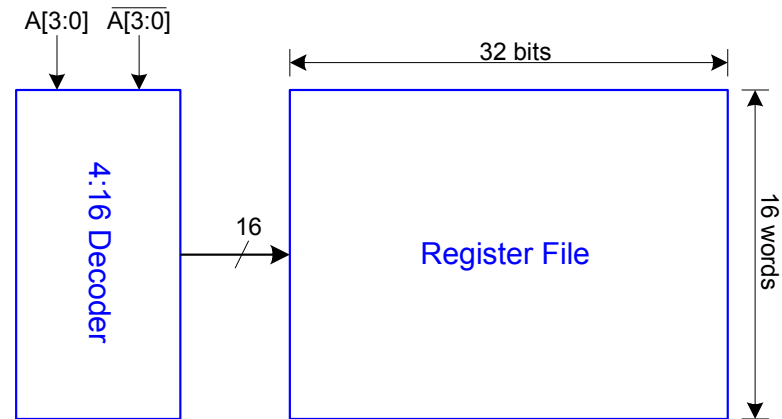Example, Revisited

- Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Number of Stages

- Decoder effort is mainly electrical and branching

Electrical Effort: $H =$

Branching Effort: $B =$

- If we neglect logical effort (assume $G = 1$)

Path Effort: $F =$

Number of Stages: $N =$

Number of Stages

- Decoder effort is mainly electrical and branching

Electrical Effort: $H = (32 * 3) / 10 = 9.6$

Branching Effort: $B = 8$


- If we neglect logical effort (assume $G = 1$)

Path Effort: $F = GBH = 76.8$

Number of Stages: $N = \log_4 F = 3.1$

- Try a 3-stage design

3 Stage 4:16 Decoder

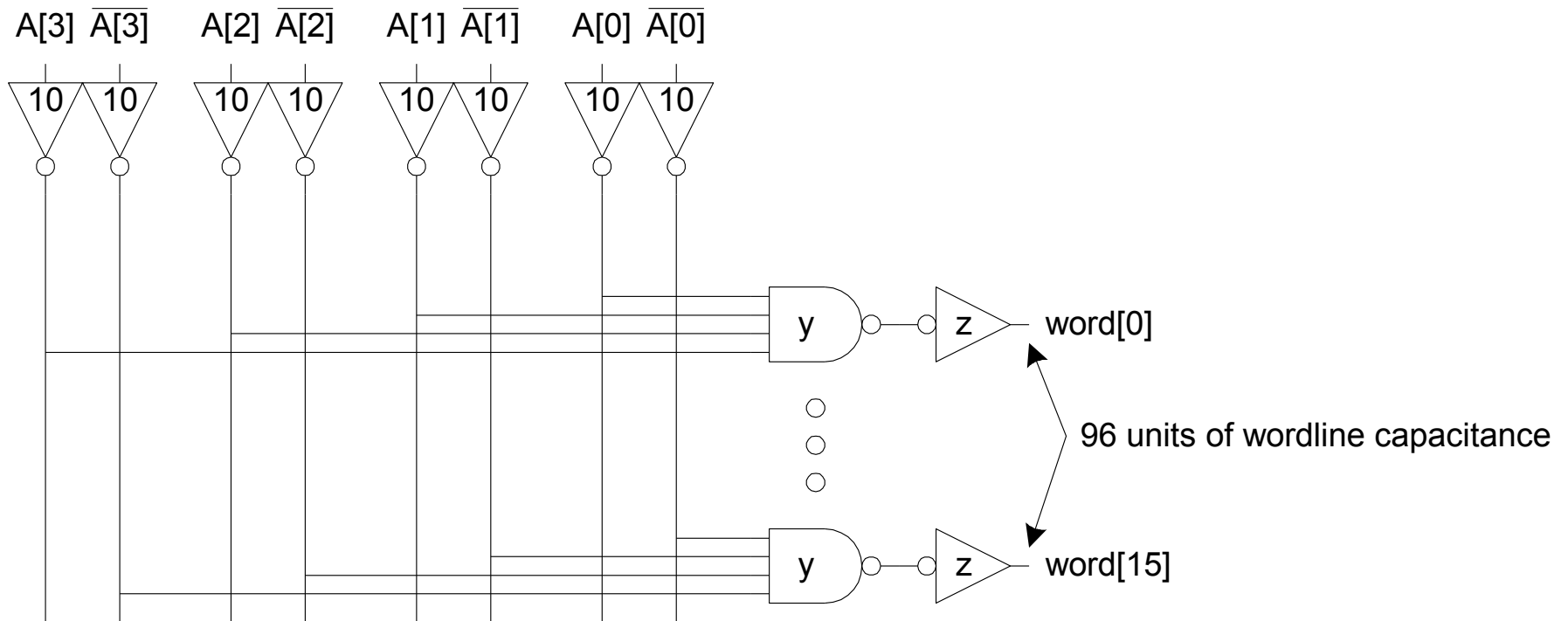

Gate Sizes & Delay

Logical Effort: $G =$


Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$

$y =$

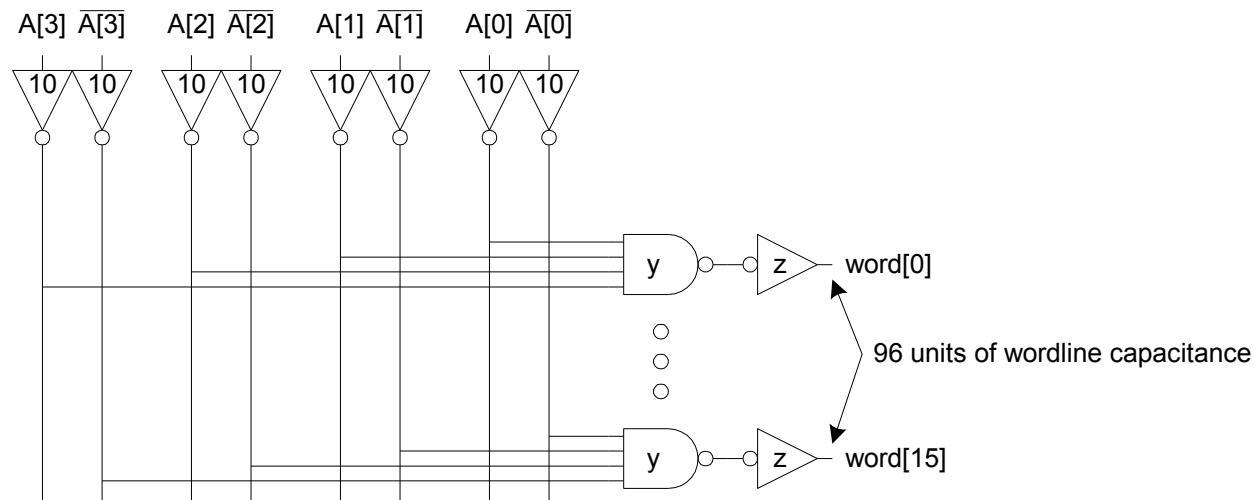

Gate Sizes & Delay


Logical Effort: $G = 1 * 6/3 * 1 = 2$

Path Effort: $F = GBH = 154$

Stage Effort: $\hat{f} = F^{1/3} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

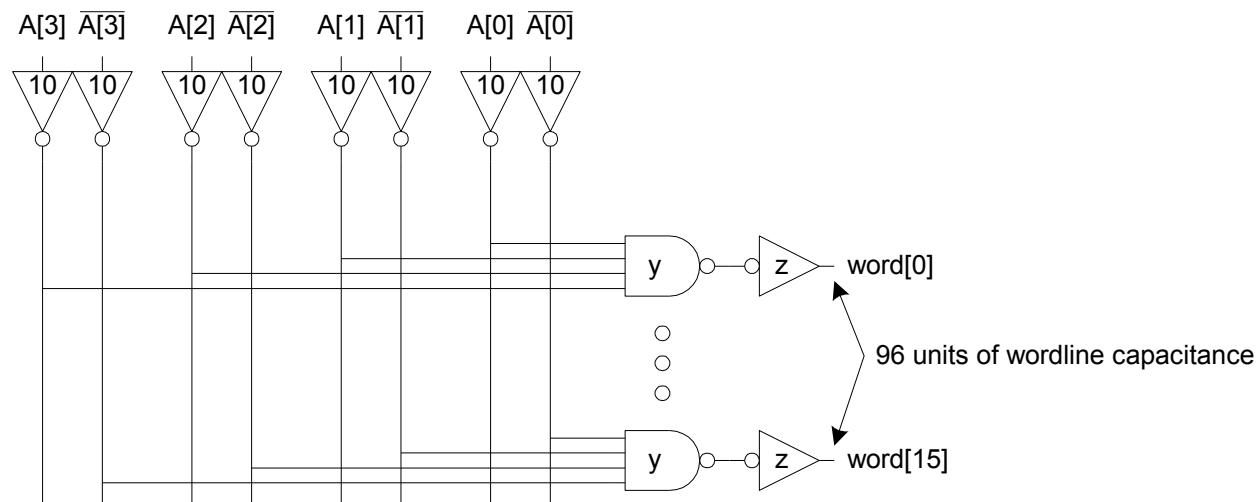Gate sizes: $z = 96 * 1 / 5.36 = 18$ $y = 18 * 2 / 5.36 = 6.7$



Comparison

- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

1) Compute path effort

$$F = GBH$$

2) Estimate best number of stages

$$N = \log_4 F$$

3) Sketch path with N stages

4) Estimate least delay

$$D = NF^{\frac{1}{N}} + P$$

5) Determine best stage effort

$$\hat{f} = F^{\frac{1}{N}}$$

6) Find gate sizes

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects, velocity saturation & body effect ...
- No Interconnect account
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master