



CHAPTER 5

Combinational Circuit Design

Outline

- 1. Static CMOS**
2. Ratioed Circuits
3. Cascode Voltage Switch Logic
4. Dynamic Circuits
5. Pass-Transistor Circuits
6. Circuit Pitfalls

Static CMOS


- Bubble Pushing
- Compound Gates
- Logical Effort Example
- Input Ordering
- Asymmetric Gates
- Skewed Gates
- Best P/N ratio

Example 1

5- 4


```
module mux(input  s, d0, d1,  
           output y);  
  
    assign y = s ? d1 : d0;  
endmodule
```

1) Sketch a design using AND, OR, and NOT gates.

 

Example 2

 2) Sketch a design using NAND, NOR, and NOT gates.
Assume $\sim S$ is available.





Bubble Pushing

- Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic
 - Remember DeMorgan's Law





$$\overline{A \cdot B} = \overline{A} + \overline{B}$$
  
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$




Bubble Pushing

- $Y = AB + CD$

    

Example 3

 3) Sketch a design using one compound gate and one NOT gate. Assume $\sim S$ is available.





Compound Gates

- Logical Effort of compound gates

unit inverter

$$Y = \overline{A}$$

 
 


$$g_A = 3/3$$

$$p = 3/3$$

AOI21

$$Y = \overline{A \bullet B + C}$$

  

$$g_A = 6/3$$



$$g_B = 6/3$$

$$g_C = 5/3$$

$$p = 7/3$$

AOI22
  
$$Y = \overline{A \bullet B + C \bullet D}$$



$$g_A = 6/3$$

$$g_B = 6/3$$



$$g_C = 6/3$$

$$g_D = 6/3$$

$$p = 12/3$$

Complex AOI
  
$$Y = \overline{A \bullet (B + C) + D \bullet E}$$



$$g_A = 5/3$$

$$g_B = 8/3$$

$$g_C = 8/3$$



$$g_D = 8/3$$

$$g_E = 8/3$$

$$p = 16/3$$

  Example 4

- The multiplexer has a maximum input capacitance of 16 units on each input. It must drive a load of 160 units. Estimate the delay of the NAND and compound gate designs.



$$H = 160 / 16 = 10$$

$$B = 1$$

$$N = 2$$

NAND Solution


$$P = 2 + 2 = 4$$

$$G = (4 / 3) \bullet (4 / 3) = 16 / 9$$


$$F = GBH = 160 / 9$$

$$\hat{f} = \sqrt[N]{F} = 4.2$$

$$D = N\hat{f} + P = 12.4\tau$$

 

DeMorgan's Law

 

Compound Solution


$$P = 4 + 1 = 5$$

$$G = (6 / 3) \bullet (1) = 2$$

$$F = GBH = 20$$

$$\hat{f} = \sqrt[N]{F} = 4.5$$


$$D = N\hat{f} + P = 14\tau$$

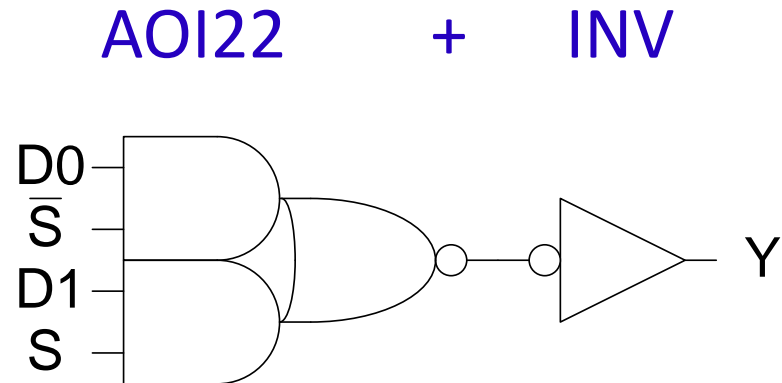


Example 5

- Annotate your designs with transistor sizes that achieve this delay.

NAND solution

 


Compound solution

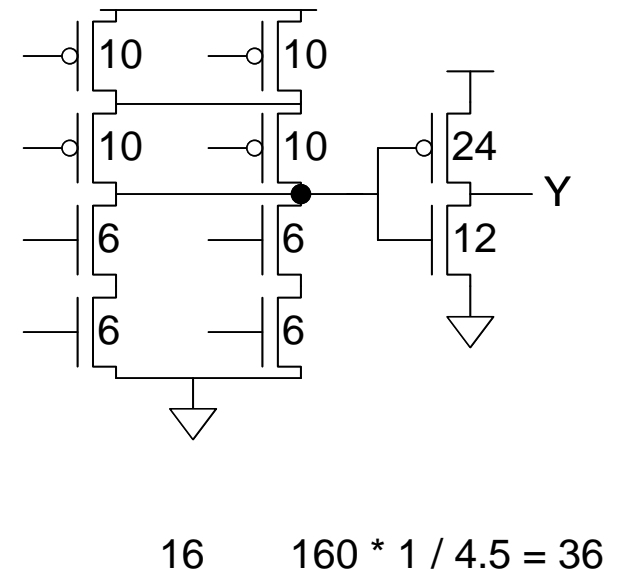


Input Order

 - Our parasitic delay model was too simple
 - Calculate parasitic delay for Y falling
 - If A arrives latest? 2τ
 - If B arrives latest? 2.33τ



Inner & Outer Inputs

 - *Outer* input is closest to rail (B)
- *Inner* input is closest to output (A)





- If input arrival time is known
 - Connect latest input to inner terminal

VTC is Data-Dependent

- The threshold voltage of M_2 is higher than M_1 due to **body effect** (γ)


$$V_{Tn1} = V_{Tn0} \quad V_{Tn2} = V_{Tn0} + \gamma(\sqrt{|2\phi_F| + V_{int}} - \sqrt{|2\phi_F|})$$

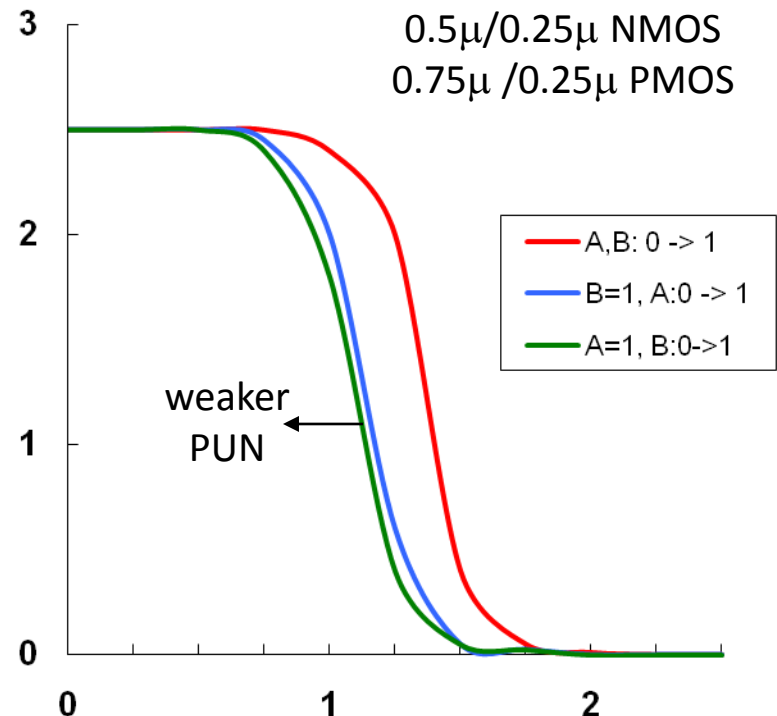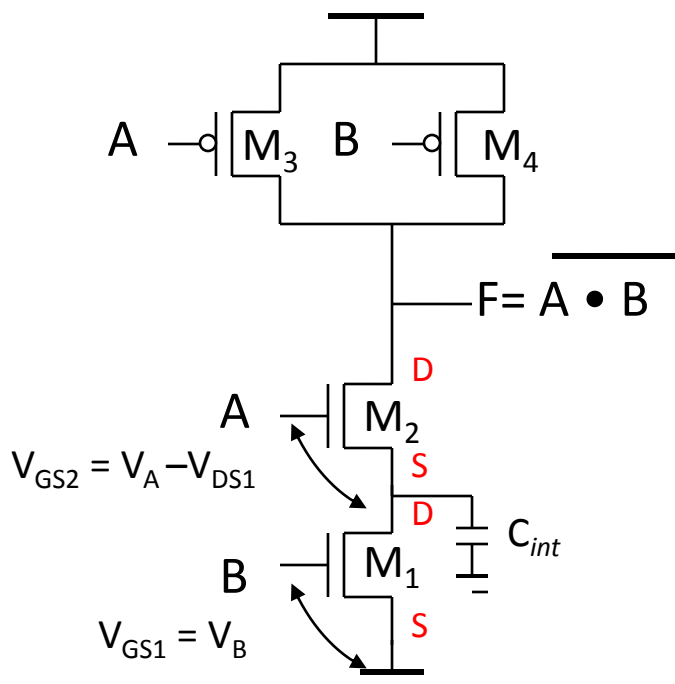since V_{SB} of M_2 is not zero (when $V_B = 0$) due to the presence of C_{int}





Symmetric Gates

- Inputs can be made perfectly symmetric

 


Asymmetric Gates

  - Asymmetric gates favor one **input** over another
- Ex: suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same
 - $g_A = 10/9$
 - $g_B = 2$
 - $g_{\text{total}} = g_A + g_B = 28/9$
- Asymmetric gate approaches $g = 1$ on critical input
- But total logical effort goes up



Skewed Gates

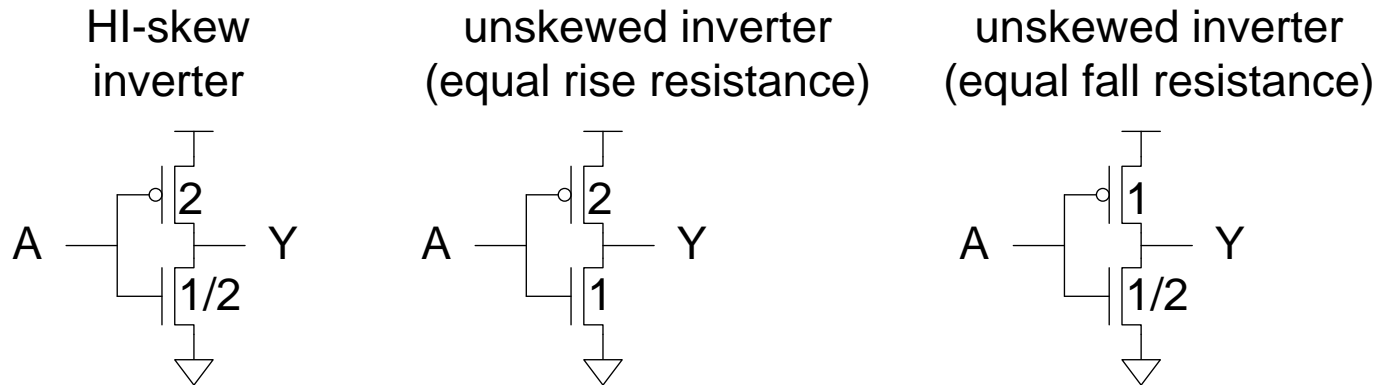- Skewed gates favor one edge over another
- Ex: suppose rising output of inverter is most critical
 - Downsize noncritical nMOS transistor



- Calculate logical effort by comparing to unskewed inverter with same effective R on that edge.
 - $g_u = 2.5 / 3 = 5/6$
 - $g_d = 2.5 / 1.5 = 5/3$

HI- and LO-Skew

- Def: Logical effort of a skewed gate **for a particular transition** is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition.
- Skewed gates reduce size of noncritical transistors
 - HI-skew gates favor rising output (small nMOS)
 - LO-skew gates favor falling output (small pMOS)
- Logical effort is smaller for favored direction
- But larger for the other direction




Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

  
 


LO-skew

   


Asymmetric Skew

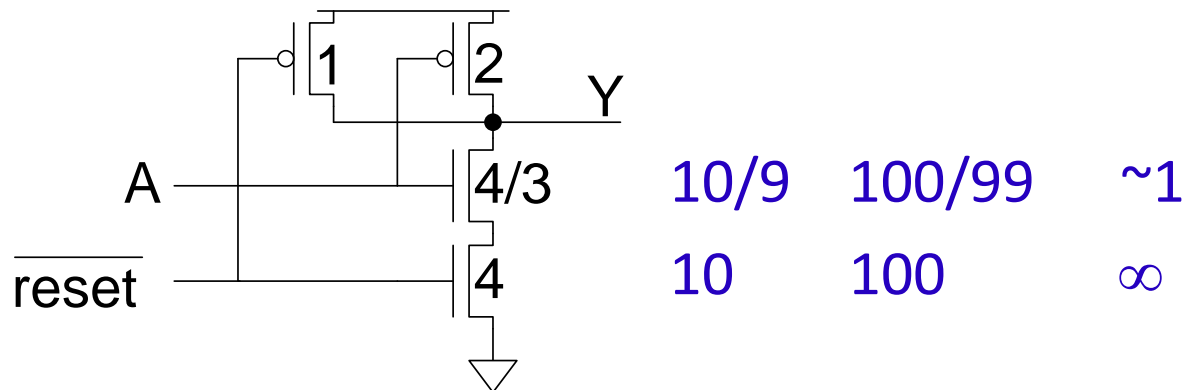 - Combine asymmetric and skewed gates
 - Downsize noncritical transistor on unimportant input
 - Reduces parasitic delay for critical input



Best P/N Ratio

 - We have selected P/N ratio for unit rise and fall resistance ($\mu = 2-3$ for an inverter).
- Alternative: choose ratio for **least average delay**
- Ex: inverter



– Delay driving identical inverter

– $t_{pdf} = (P+1)$

– $t_{pdr} = (P+1)(\mu/P)$

– $t_{pd} = (P+1)(1+\mu/P)/2 = (P + 1 + \mu + \mu/P)/2$

– Differentiate t_{pd} w.r.t. P


– Least delay for $P = \sqrt{\mu}$

P/N Ratios


- In general, best P/N ratio is **sqrt of that giving equal delay.**
 - Only improves average delay slightly for inverters
 - But significantly decreases area and power

Inverter


fastest
P/N ratio

 

NAND2

 

NOR2

 

Observations

- For speed:
 - NAND vs. NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages

Outline

1. Static CMOS
- 2. Ratioed Circuits**
3. Cascode Voltage Switch Logic
4. Dynamic Circuits
5. Pass-Transistor Circuits
6. Circuit Pitfalls

Introduction

- What makes a circuit fast?

- $I = C \, dV/dt \quad \rightarrow \quad t_{pd} \propto (C/I) \, \Delta V$

- low capacitance

- high current

- small swing


- Logical effort is proportional to C

- pMOS are the enemy!

- High capacitance for a given current



- Can we take the pMOS capacitance off the input?

 - Various circuit families try to do this...




Pseudo-nMOS

  - In the old days, nMOS processes had no pMOS
 - Instead, use pull-up transistor that is always ON
- In CMOS, use a pMOS that is always ON
 - *Ratio* issue, Make pMOS about 1/3~1/6 effective strength of pulldown network




Pseudo-nMOS Gates

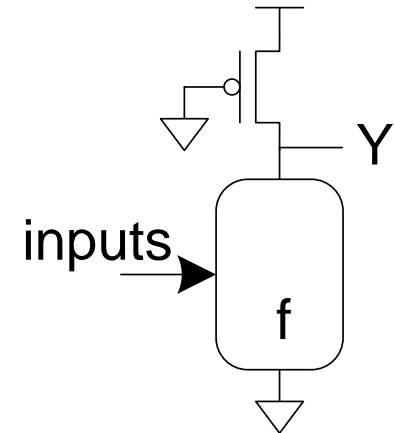
- Design for unit current on output to compare with unit inverter.
- Choose pMOS size between $1/3 \sim 1/6$ the effective width (pick $1/3$)




Inverter

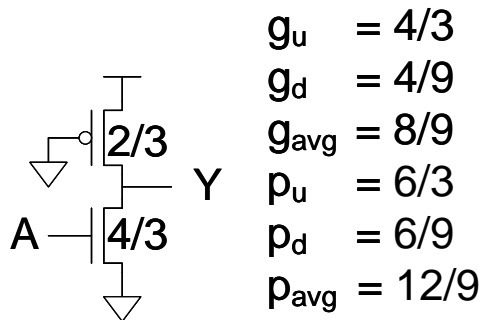

NAND2

 

NOR2

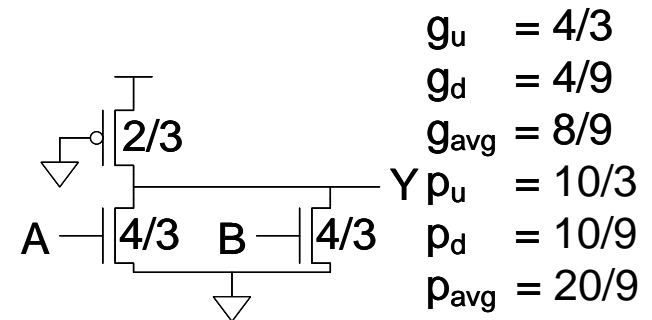


Inverter : $I_u = (1/3)I$, $C_{inv-u} = 1$, $g_u = (4/3)/1$, $p_u = (2/3+4/3)/1$

$I_d = I$, $C_{inv-d} = 3$, $g_d = (4/3)/3$, $p_d = (2/3+4/3)/3$

Pseudo-nMOS Design


- Ex: Design a k-input AND gate using INV+ pseudo-nMOS NOR. Find the delay driving a fanout of H

 - $G = 1 * 8/9 = 8/9$
- $F = GBH = 8H/9$
- $P = 1 + (4+8k)/9 = (8k+13)/9$
- $N = 2$
- $D = NF^{1/N} + P = \frac{4\sqrt{2H}}{3} + \frac{8k + 13}{9}$



Pseudo-nMOS Power

 - Pseudo-nMOS draws power whenever $Y = 0$
 - Called static power $P = I \cdot V_{DD}$
 - A few mA / gate * 1M gates would be a problem
 - This is why nMOS went extinct!
- Use pseudo-nMOS sparingly for wide NORs
- Turn off pMOS when not in use




Outline

1. Static CMOS
2. Ratioed Circuits
- 3. Cascode Voltage Switch Logic**
4. Dynamic Circuits
5. Pass-Transistor Circuits
6. Circuit Pitfalls

Cascode Voltage Switch Logic

5- 33

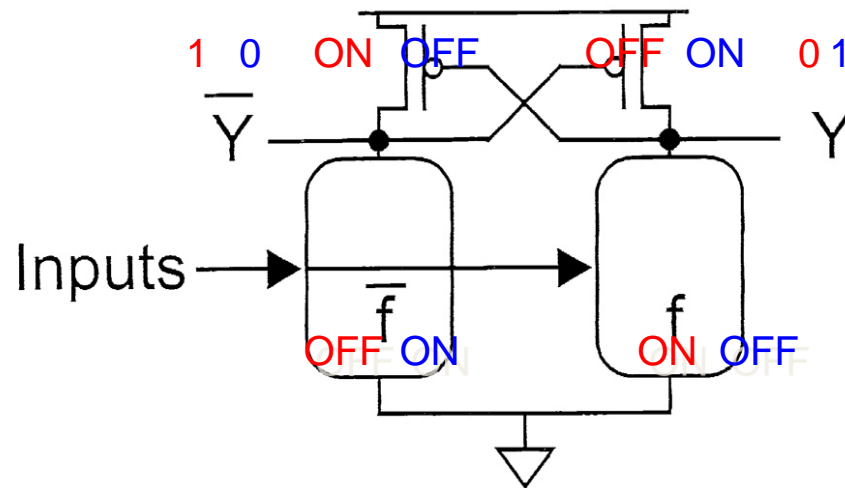- Differential Cascode Voltage Switching Logic (DCVS, DCVSL)
 - Seeks the performance of ratioed circuits without the static power consumption
 - Use both true and complementary input signals and compute both true and complementary outputs



Outline



1. Static CMOS
2. Ratioed Circuits
3. Cascode Voltage Switch Logic
- 4. Dynamic Circuits**
5. Pass-Transistor Circuits
6. Circuit Pitfalls

Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of N requires 2N devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires only N + 2 transistors
 - takes a sequence of **precharge** and conditional **evaluation** phases to realize logic functions




Dynamic Logic

  - *Dynamic* gates uses a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*



The Foot

  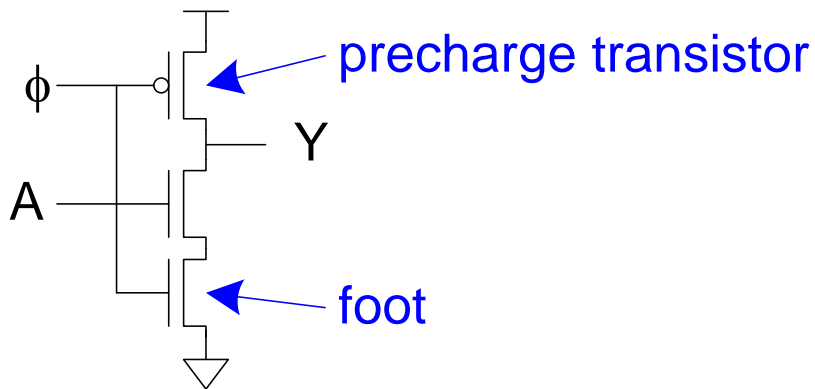
- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.




Logical Effort

Inverter



unfooted

 



footed

 

NAND2

  

NOR2

  

Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L

Properties of Dynamic Gates



- Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
 - should be smaller in area than static complementary CMOS
- Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- Nonratioed - sizing of the devices is not important for proper functioning (only for performance)
- Faster switching speeds
 - reduced load capacitance due to lower number of transistors per gate (C_{int}) so a reduced logical effort
 - reduced load capacitance due to smaller fan-out (C_{ext})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L
 - Ignoring the influence of precharge time on the switching speed of the gate, $t_{pLH} = 0$ but the presence of the evaluation transistor slows down the t_{pHL}

Properties of Dynamic Gates, con't

5- 42

- Power dissipation should be better
 - consumes only dynamic power – no short circuit power consumption since the pull-up path is not on when evaluating
 - lower C_L - both C_{int} (since there are fewer transistors connected to the drain output) and C_{ext} (since there the output load is one per connected gate, not two)
 - by construction can have at most one transition per cycle – **no glitching**
- But power dissipation can be significantly **higher** due to
 - higher transition probabilities
 - extra load on CLK
- PDN starts to work as soon as the input signals exceed V_{Tn} , so set V_M , V_{IH} and V_{IL} all equal to V_{Tn}
 - low noise margin (NM_L)
- Needs a precharge clock

Dynamic Behavior

  


#Trns	V_{OH}	V_{OL}	V_M	NM_H	NM_L	t_{pHL}	t_{pLH}	t_p
6	2.5V	0V	V_{Tn}	$2.5 - V_{Tn}$	V_{Tn}	110ps	0ns	83ps

Gate Parameters are Time Independent


5- 44

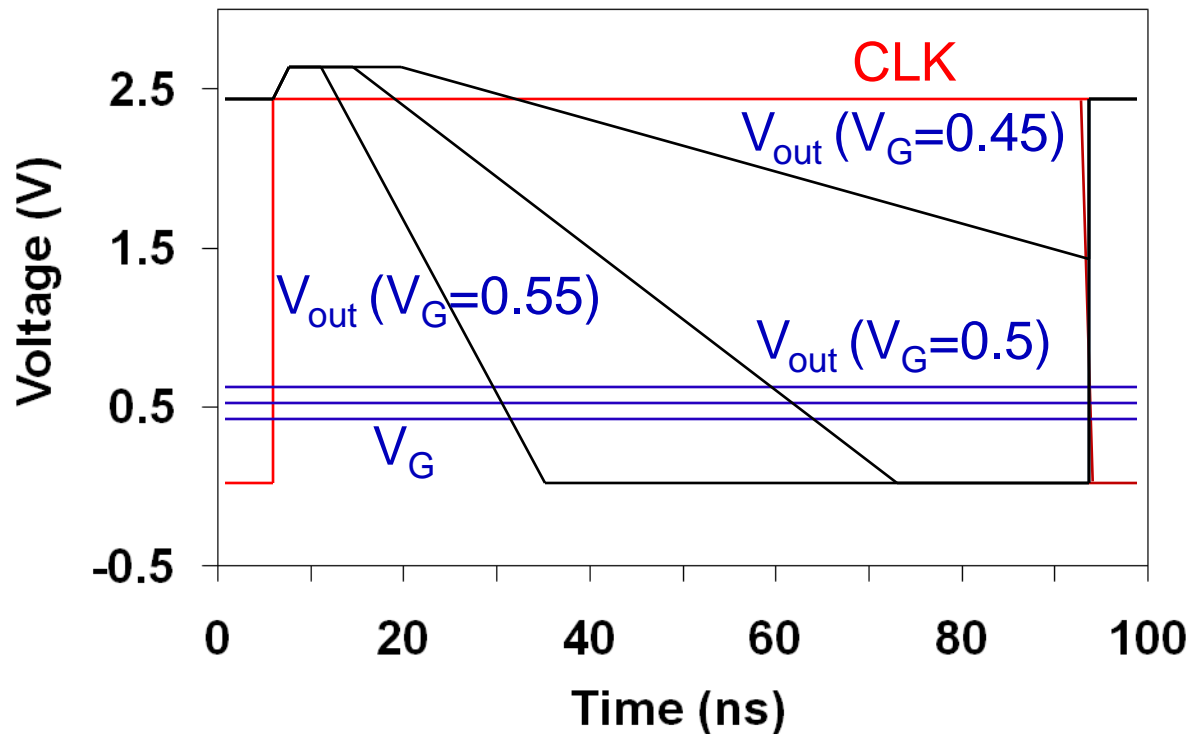- The amount by which the output voltage drops is a strong function of the input voltage and the **available evaluation time**.
 - Noise needed to corrupt the signal has to be larger if the evaluation time is short – i.e., the switching threshold is truly time independent.



Power Consumption of Dynamic Gate

5- 45

 

Power only dissipated when previous $Out = 0$

Dynamic Power is Data Dependent

5- 46

Dynamic 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$



Then **transition probability**

$$\begin{aligned} P_{0 \rightarrow 1} &= P_{\text{out}=0} \times P_{\text{out}=1} \\ &= 3/4 \times 1 = 3/4 \end{aligned}$$

Switching activity can be **higher** in dynamic gates!

$$P_{0 \rightarrow 1} = P_{\text{out}=0}$$


Issues 1: Charge Leakage

 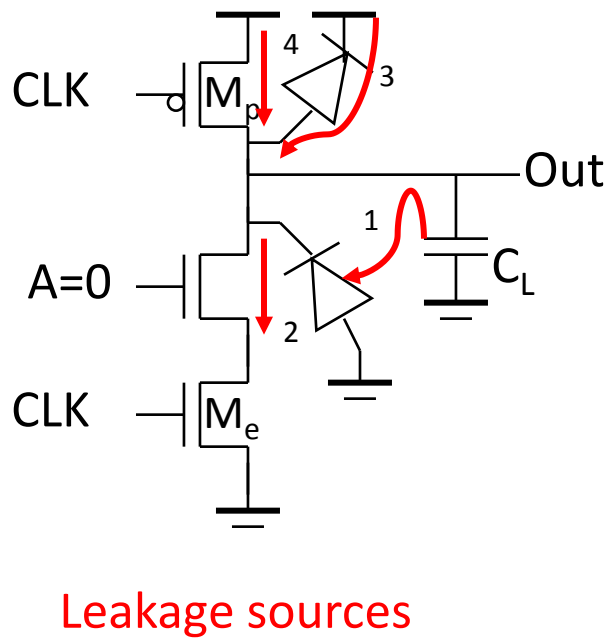

Minimum clock rate of a few kHz

Impact of Charge Leakage

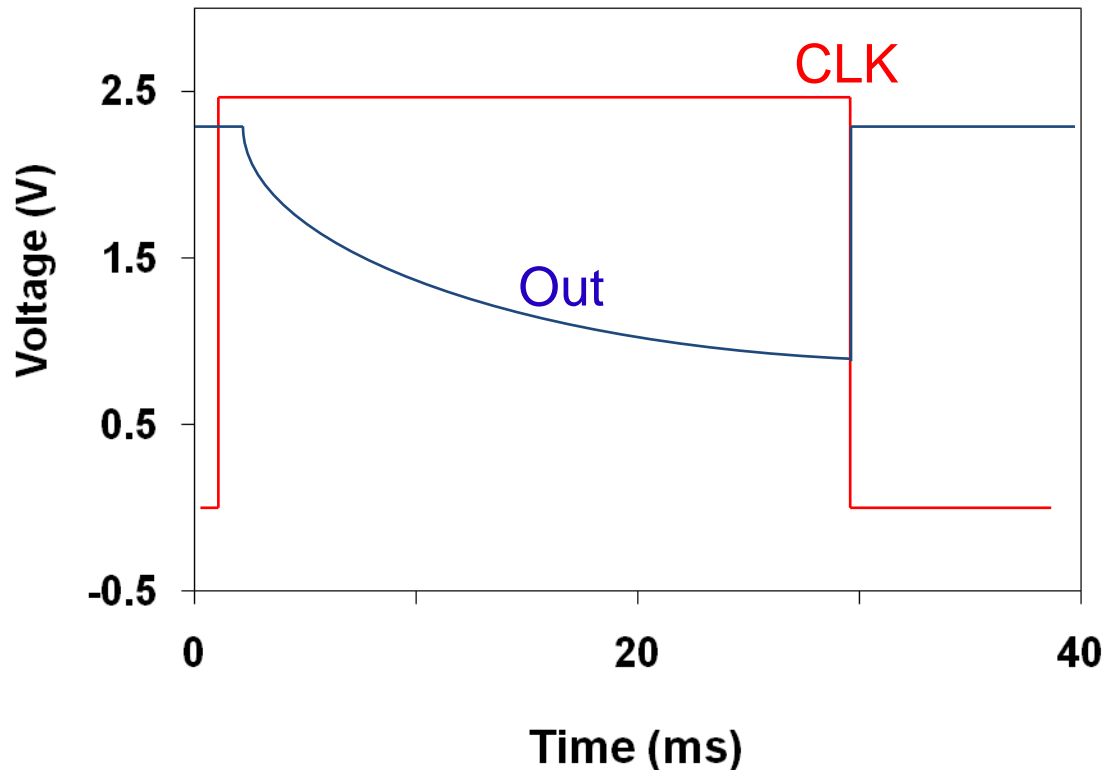
- Output settles to an intermediate voltage determined by a resistive divider of the pull-up and pull-down networks
 - Once the output drops below the switching threshold of the fan-out logic gate, the output is interpreted as a low voltage.



A Solution to Charge Leakage

5- 49

 
- **Keeper** compensates for the charge lost due to the pull-down leakage paths.



Same approach as level restorer for pass transistor logic


Summary: Leakage

- Dynamic node floats high during evaluation
 - Transistors are leaky ($I_{OFF} \neq 0$)
 - Dynamic value will leak away over time
 - Formerly miliseconds, now nanoseconds!
- Use keeper to hold dynamic node
 - Must be weak enough not to fight evaluation

 

Issues 2: Charge Sharing


 
- Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to static power consumption by downstream gates and possible circuit malfunction.



- When $\Delta V_{out} = -V_{DD} (C_a / (C_a + C_L))$ the drop in V_{out} is large enough to be below the switching threshold of the gate it drives causing a malfunction.

Charge Sharing

  
- Dynamic gates suffer from charge sharing



$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$

Charge Sharing Example

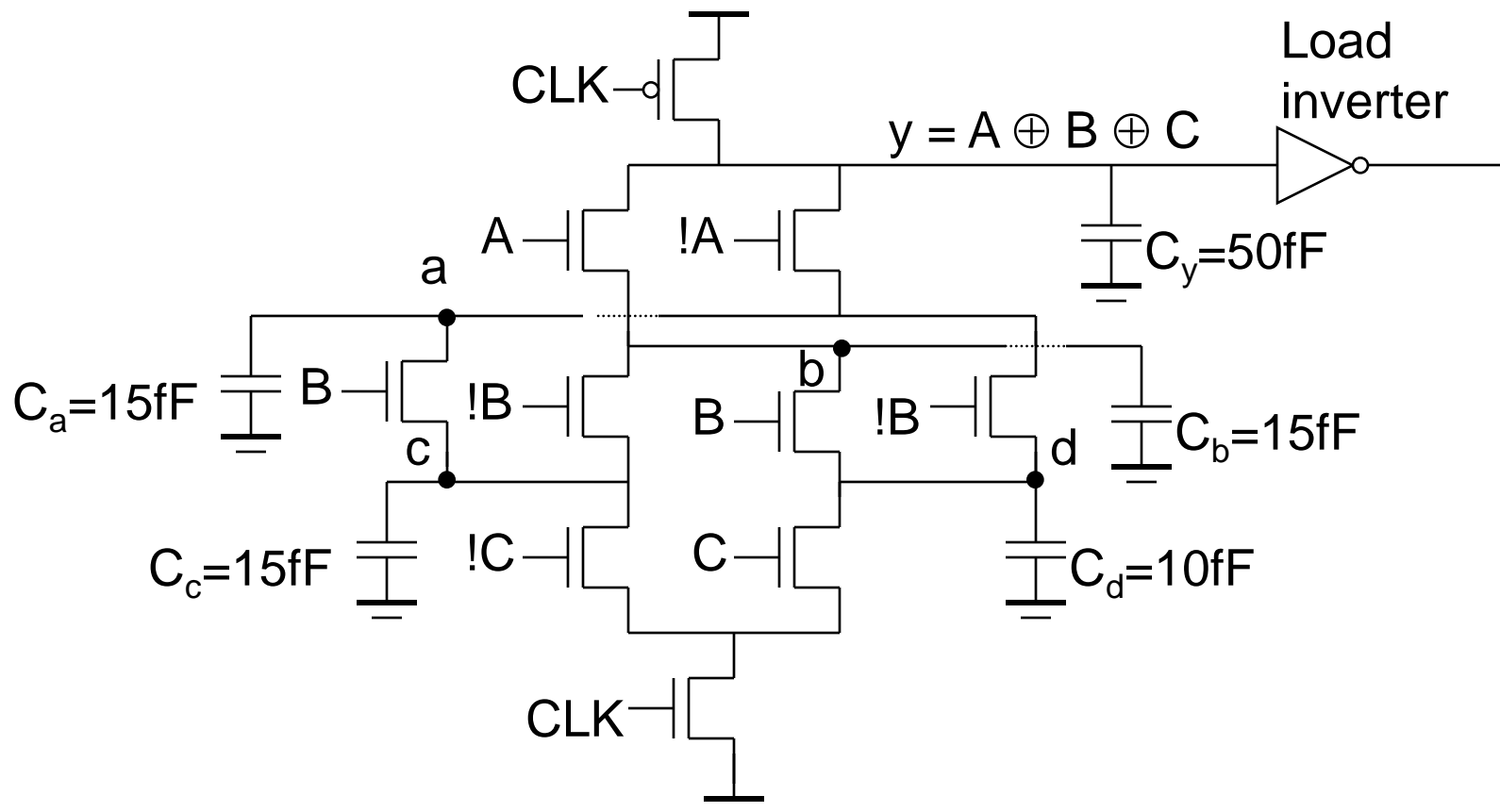
What is the worst case voltage drop on y ? (Assume all inputs are low during precharge and that all internal nodes are initially at 0V.)



Charge Sharing Example

5- 54

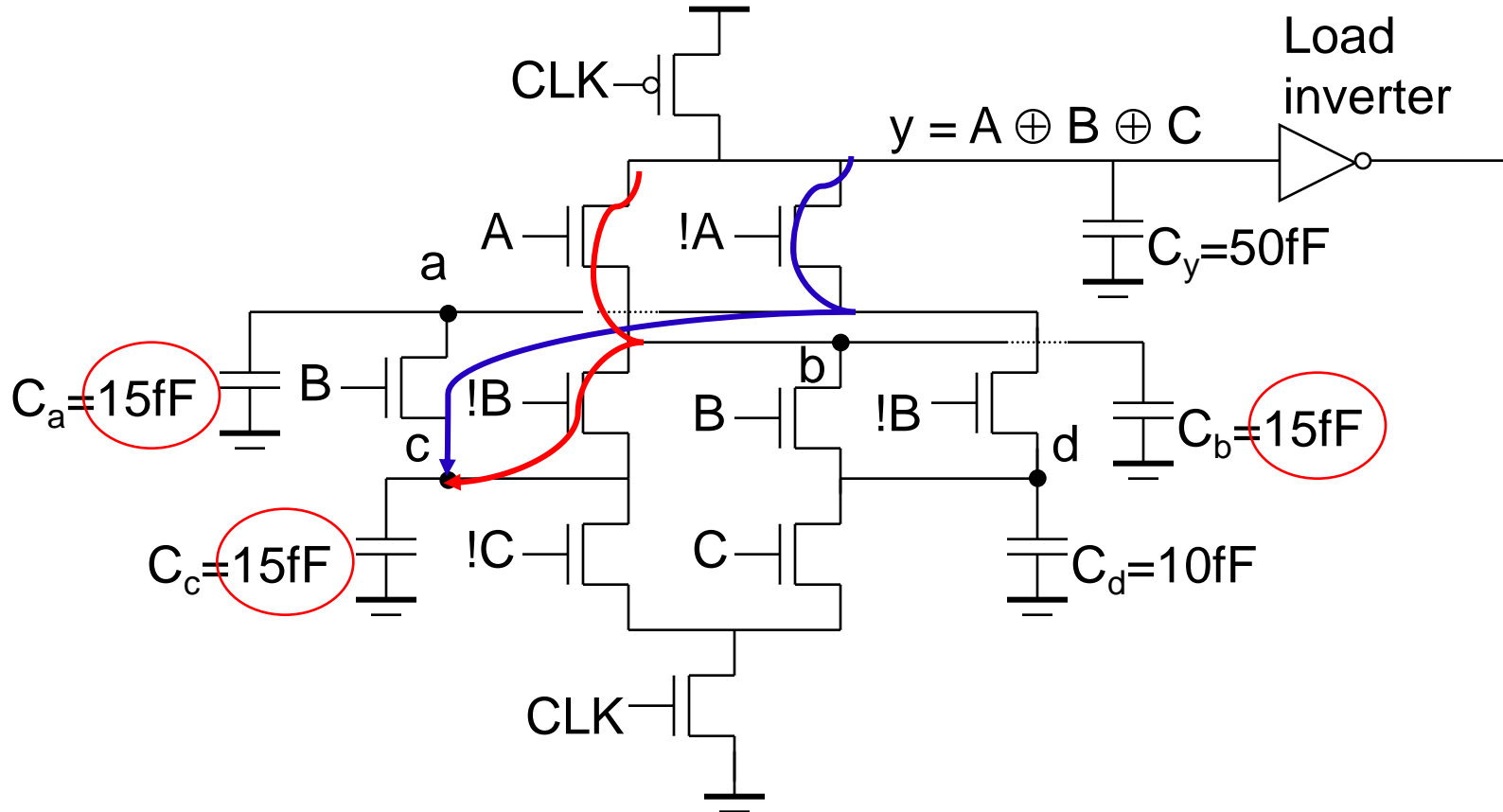
What is the worst case voltage drop on y ? (Assume all inputs are low during precharge and that all internal nodes are initially at 0V.)



$$\Delta V_{\text{out}} = -V_{\text{DD}} \left(\frac{C_a + C_c}{(C_a + C_c) + C_y} \right) = -2.5\text{V} * \left(\frac{30}{30+50} \right) = -0.94\text{V}$$

Solution to Charge Redistribution


5- 55

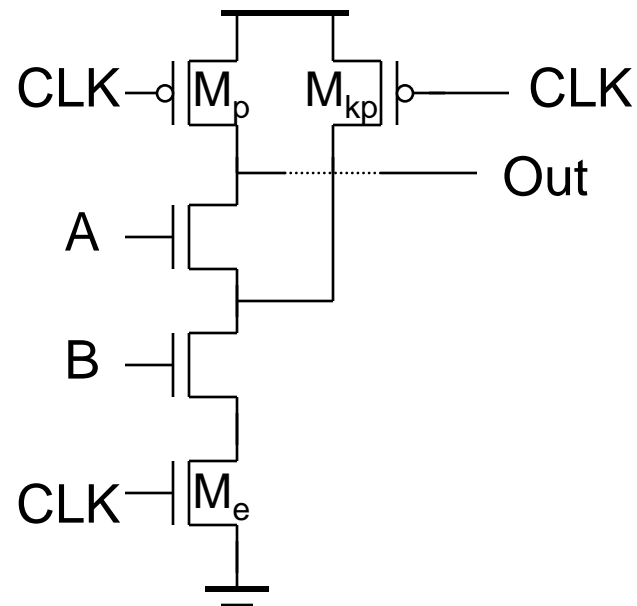

Precharge internal nodes using a clock-driven transistor
(at the cost of increased area and power)

Secondary Precharge


- Solution: add secondary precharge transistors
 - Typically need to precharge every other node
- Big load capacitance C_Y helps as well

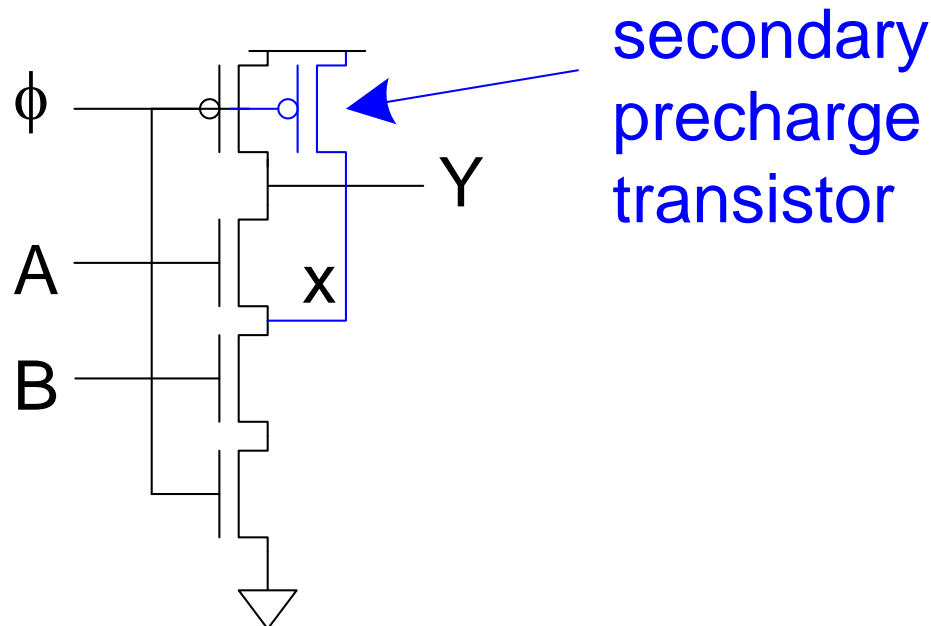

Issues 3: Backgate Coupling


5- 57

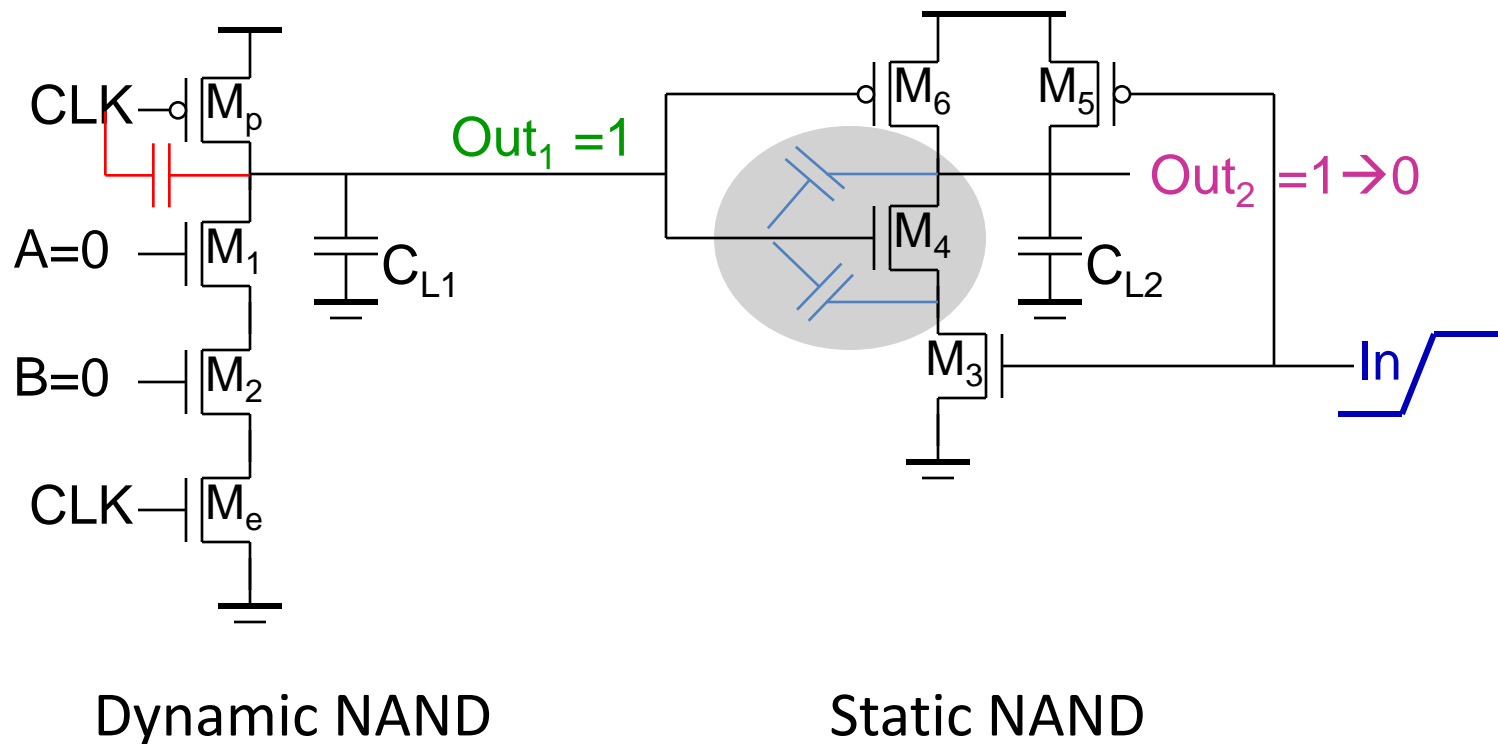- Susceptible to crosstalk due to 1) high impedance of the output node and 2) backgate capacitive coupling
 - Out_2 capacitively couples with Out_1 through the gate-source and gate-drain capacitances of M_4





Backgate Coupling Effect

 - Capacitive coupling means Out_1 drops significantly so Out_2 doesn't go all the way to ground




Clock Feedthrough

  

Issues 5: Cascading Gates

5- 61

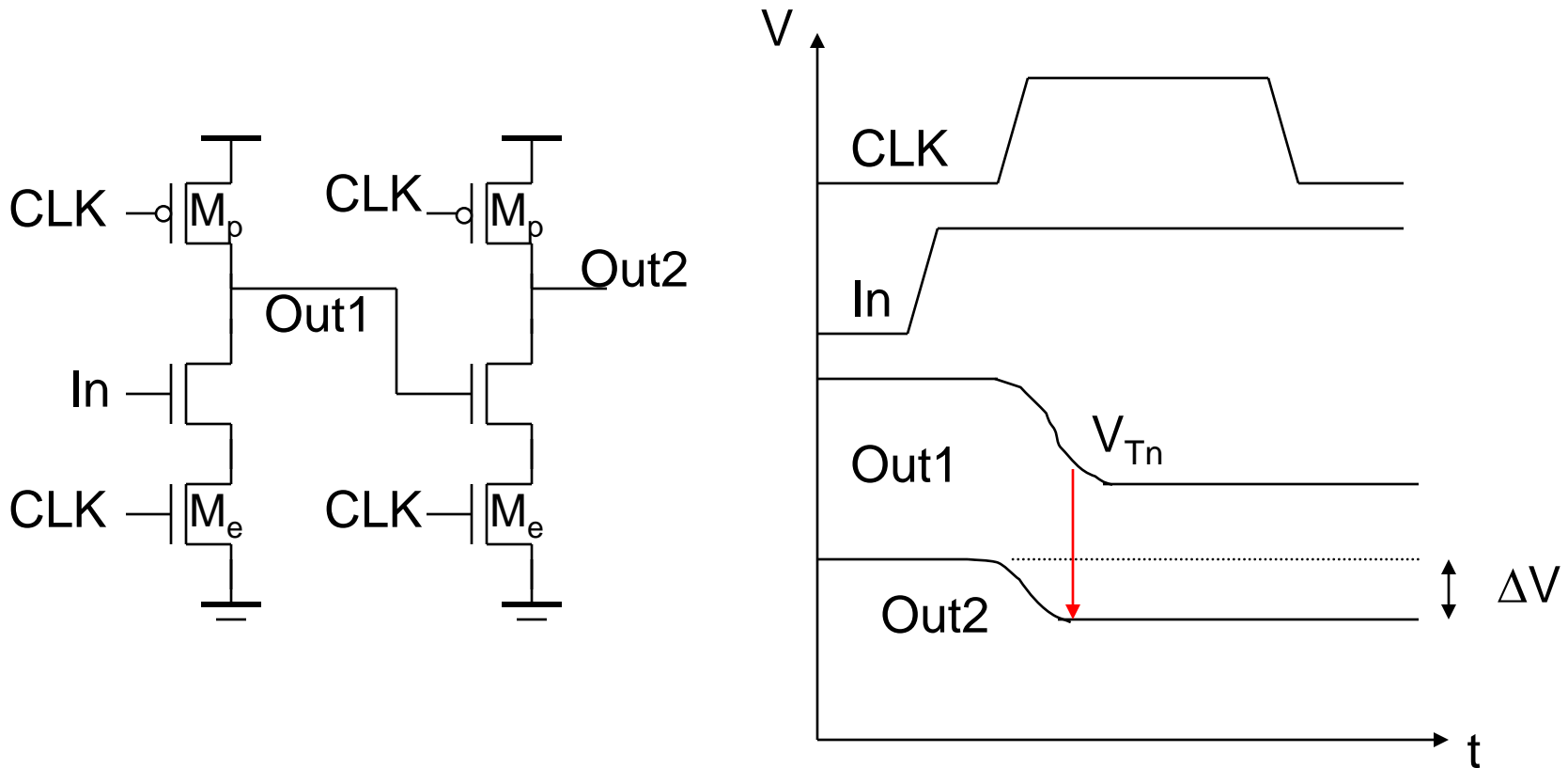

Only a single 0 \rightarrow 1 transition allowed at the inputs during the evaluation period!

Monotonicity



- Dynamic gates require *monotonically rising* inputs during evaluation

– 0 -> 0

– 0 -> 1



– 1 -> 1

– But not 1 -> 0

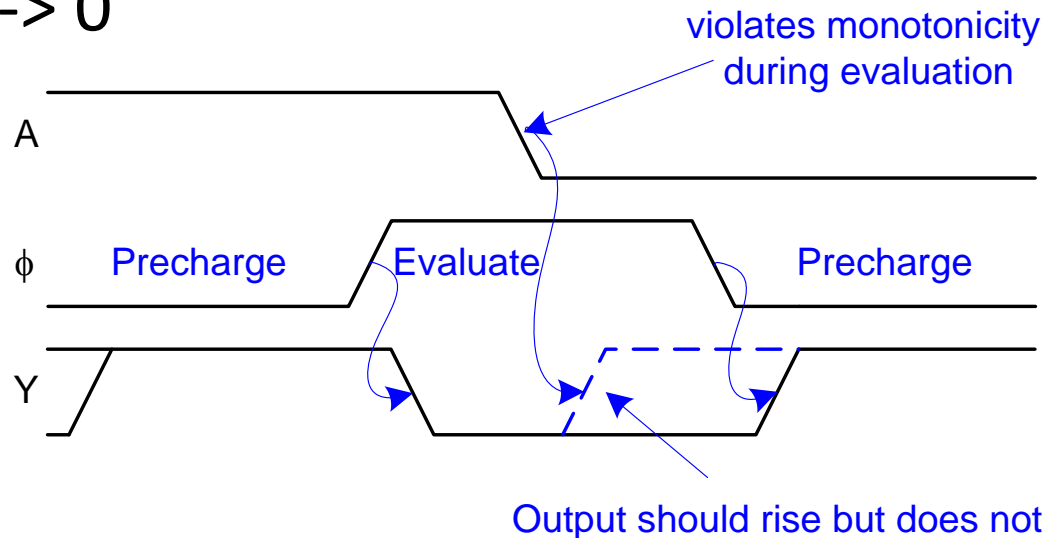 



Monotonicity Woes

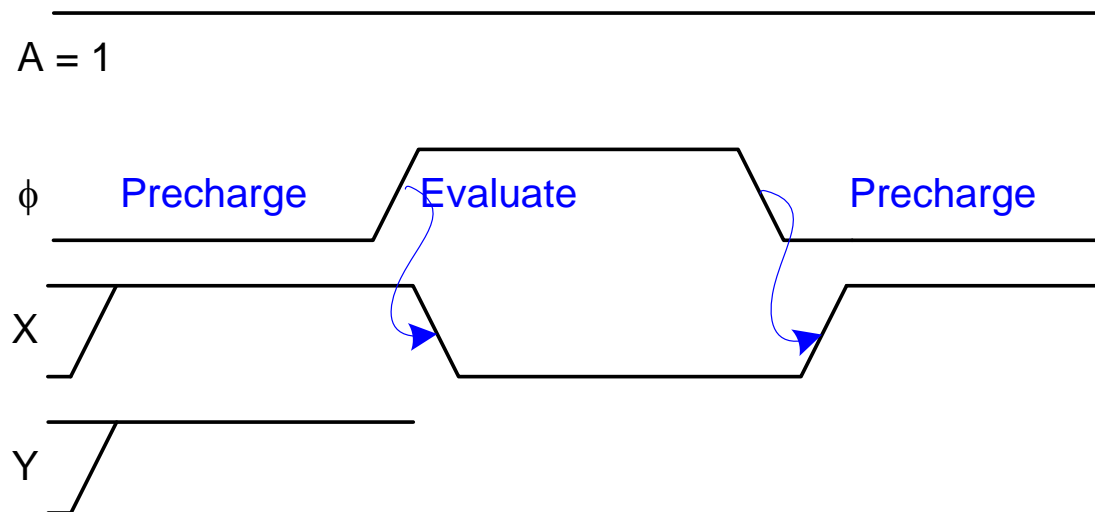 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!






Monotonicity Woes

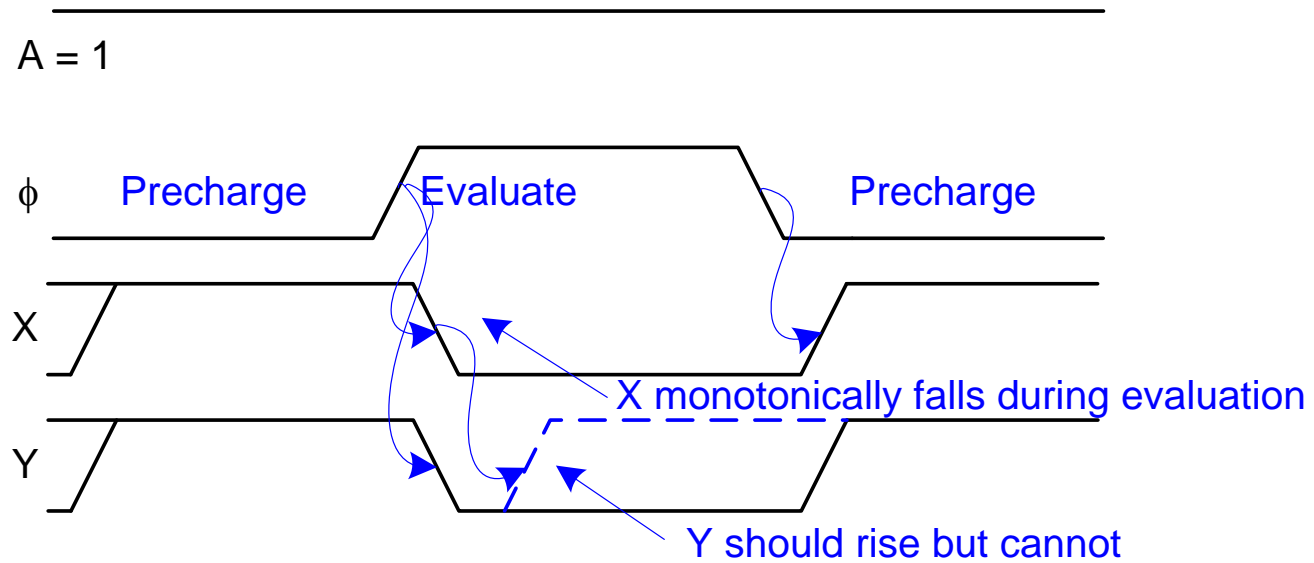 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




Domino Gates

 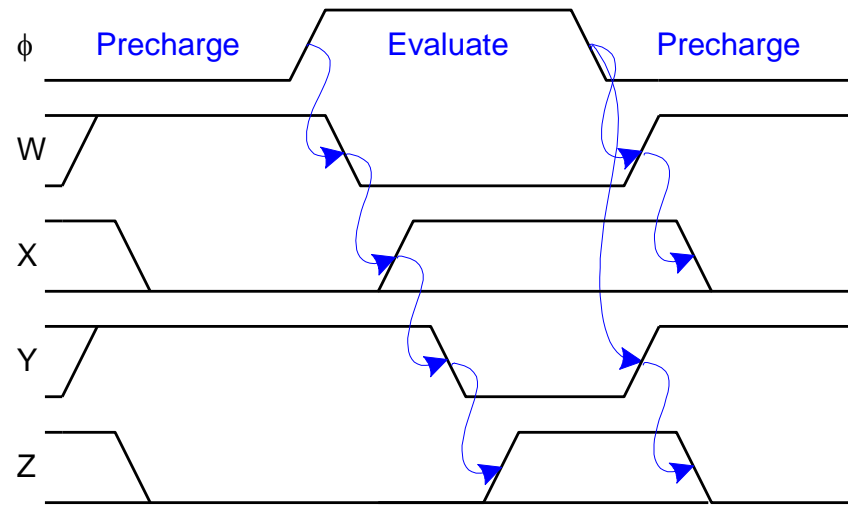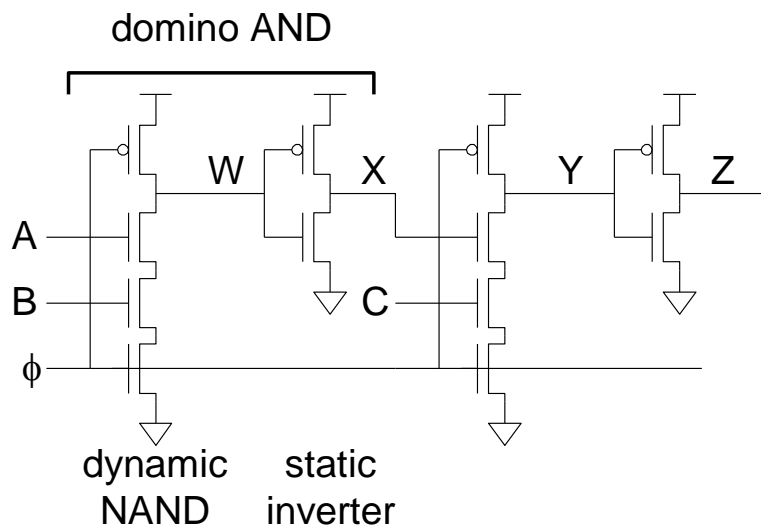- Follow dynamic stage with inverting static gate
 - Dynamic / static pair is called **domino gate**
 - Produces monotonic outputs



Domino Optimizations

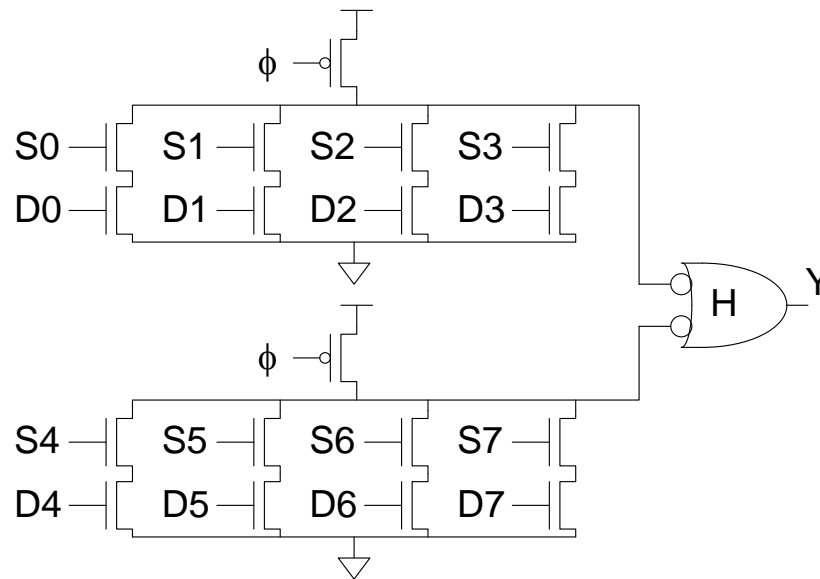
- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially, precharge in parallel
- Thus evaluation is more critical than precharge
- HI-skewed static stages can perform logic



Dual-Rail Domino


- Domino only performs noninverting functions:
 - AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
 - Takes true and complementary inputs
 - Produces true and complementary outputs

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

 

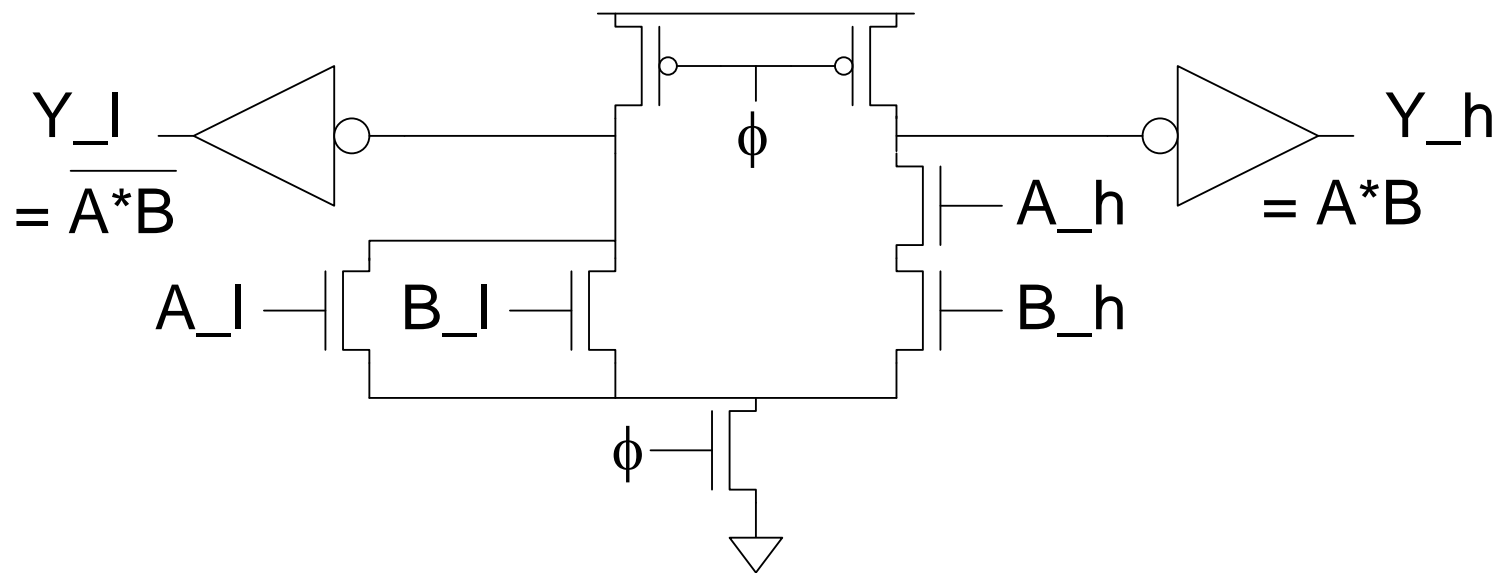
Example: AND/NAND

- Given A_h, A_l, B_h, B_l
- Compute $Y_h = A * B, Y_l = \sim(A * B)$
- Pulldown networks are conduction complements



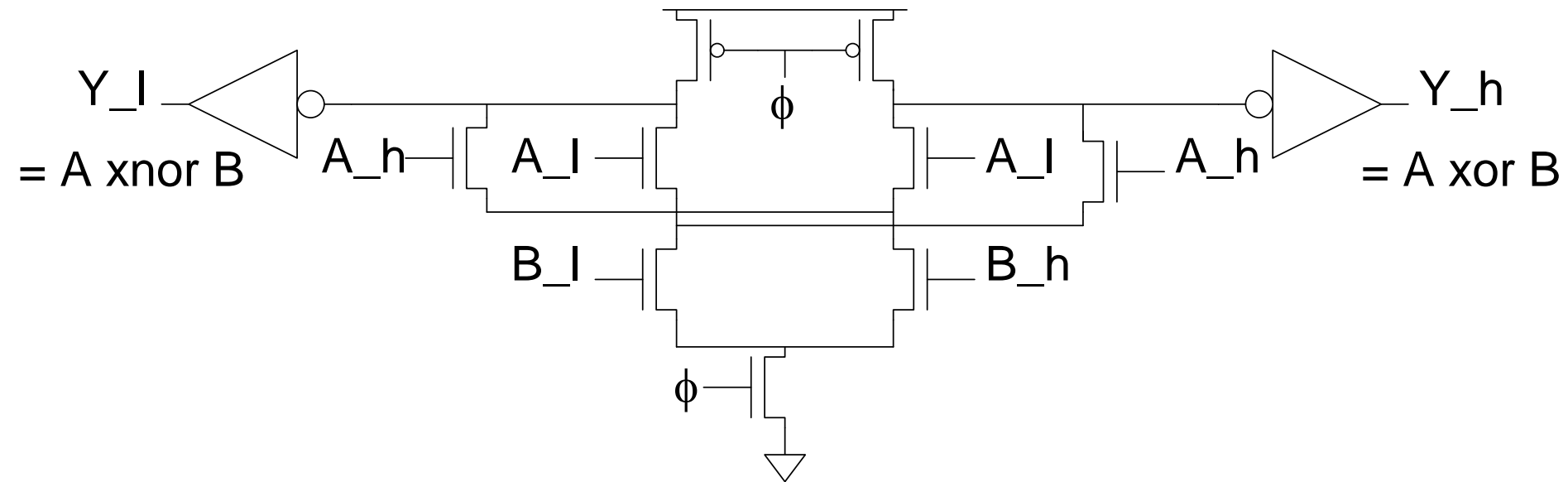Example: XOR/XNOR

- Sometimes possible to share transistors



Noise Sensitivity

- Dynamic gates are very sensitive to noise
 - Inputs: $V_{IH} \approx V_{tn}$
 - Outputs: floating output susceptible noise
- Noise sources
 - Capacitive crosstalk
 - Charge sharing
 - Power supply noise
 - Feedthrough noise
 - And more!

Domino Summary

- Domino logic is attractive for high-speed circuits
 - 1.5 – 2x faster than static CMOS
 - But many challenges:
 - Monotonicity
 - Leakage
 - Charge sharing
 - Noise
- Widely used in high-performance microprocessors



Outline

5- 72

  1. Static CMOS
2. Ratioed Circuits
3. Cascode Voltage Switch Logic
4. Dynamic Circuits
- 5. Pass-Transistor Circuits**
6. Circuit Pitfalls

Pass Transistor Circuits


- Use pass transistors like switches to do logic
- Inputs drive diffusion terminals as well as gates
- CMOS + Transmission Gates:
 - 2-input multiplexer
 - Gates should be restoring




NMOS Transistors in Series/Parallel

5- 74

 - Primary inputs drive both gate and source/drain terminals
- NMOS switch closes when the gate input is high



$X = Y$ if A and B

 


$X = Y$ if A or B

- Remember - NMOS transistors pass a **strong 0** but a **weak 1**


PMOS Transistors in Series/Parallel

5- 75

 - Primary inputs drive both gate and source/drain terminals
- PMOS switch closes when the gate input is low


 
$$X = Y \text{ if } \overline{A} \text{ and } \overline{B} = \overline{A + B}$$





$$X = Y \text{ if } \overline{A} \text{ or } \overline{B} = \overline{A \cdot B}$$

- Remember - PMOS transistors pass a **strong** 1 but a **weak** 0



Pass Transistor (PT) Logic

5- 76

  

- Gate is static – a low-impedance path exists to both supply rails under all circumstances
- **N** transistors instead of **2N**
- No static power consumption
- Ratioless
- Bidirectional (versus unidirectional)

VTC of PT AND Gate

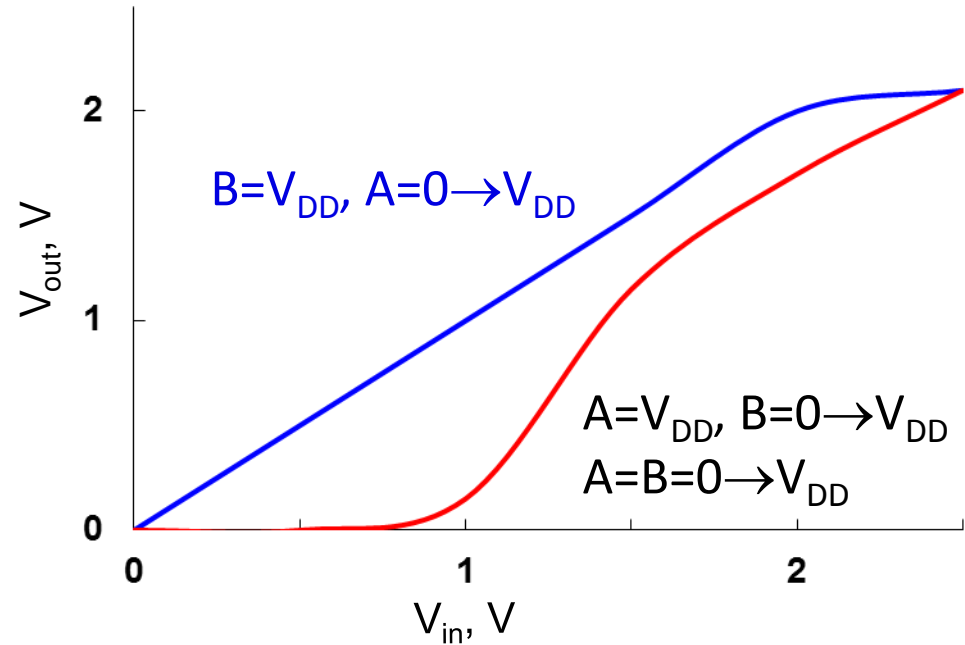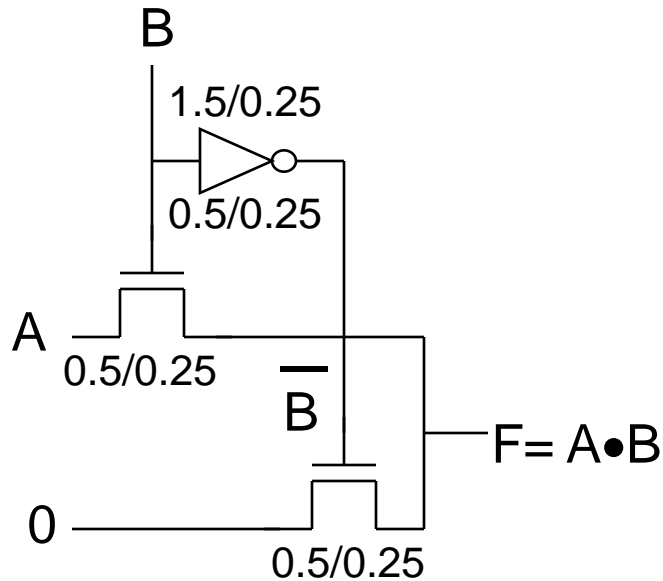


- Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)

NMOS Only PT Driving an Inverter

5- 78

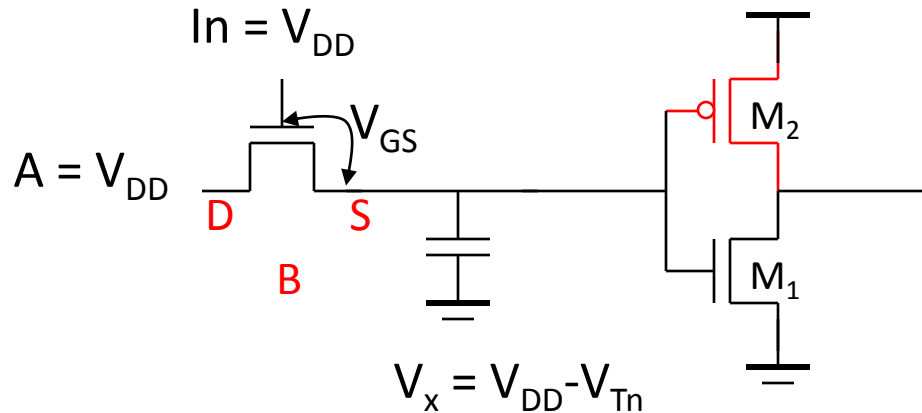- V_x does not pull up to V_{DD} , but $V_{DD} - V_{Tn}$





- Threshold voltage drop causes static power consumption (M_2 may be weakly conducting forming a path from V_{DD} to GND)
- Notice V_{Tn} increases for pass transistor due to **body effect** (V_{SB})

Voltage Swing of PT Driving an Inverter


5- 79

- **Body effect** – large V_{SB} at x - when pulling high (B is tied to GND and S charged up close to V_{DD})
- So the voltage drop is even worse

$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{|2\phi_f| + V_x} - \sqrt{|2\phi_f|}))$$

  

Cascaded NMOS Only PTs

 



Swing on $y = V_{DD} - V_{Tn1} - V_{Tn2}$

Swing on $y = V_{DD} - V_{Tn1}$

- Pass transistor gates should **never** be cascaded as on the left
- Logic on the right suffers from static power dissipation and reduced noise margins

Restorer Circuit Transient Response

  - Restorer has speed and power impacts: increases the capacitance at x, slowing down the gate; increases t_r (but decreases t_f)



$W/L_n = 0.50/0.25$


$W/L_2 = 1.50/0.25$

$W/L_1 = 0.50/0.25$

Time, ps

Solution 2: Multiple V_T Transistors




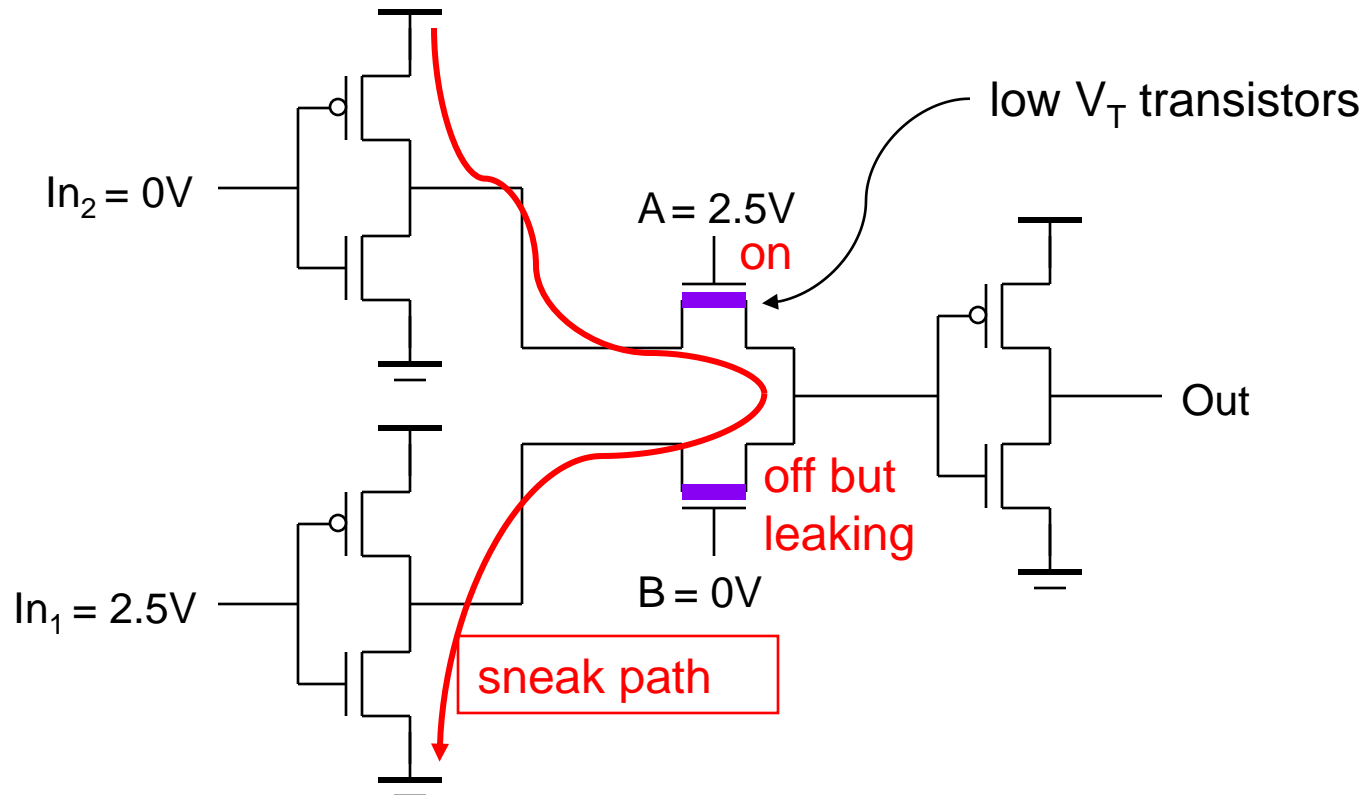
- Technology solution: Use (near) **zero** V_T devices for the NMOS PTs to eliminate *most* of the threshold drop (body effect still in force preventing full swing to V_{DD})



- Impacts static power consumption due to subthreshold currents flowing through the PTs (even if V_{GS} is below V_T)


Solution 3: Transmission Gates (TGs)

- Most widely used solution
- **Full swing** *bidirectional* switch controlled by the gate signal C, $A = B$ if $C = 1$

    

Solution 4: CPL

 - **C**omplementary **P**ass-transistor **L**ogic
 - Dual-rail form of pass transistor logic
 - Avoids need for ratioed feedback
 - Optional cross-coupling for rail-to-rail swing



Outline

1. Static CMOS
2. Ratioed Circuits
3. Cascode Voltage Switch Logic
4. Dynamic Circuits
5. Pass-Transistor Circuits
- 6. Circuit Pitfalls**


Introduction

- Circuit Pitfalls
 - Detective puzzle
 - Given circuit and symptom, diagnose cause and recommend solution
 - All these pitfalls have caused failures in real chips
- Noise Budgets
- Reliability

Threshold Drop

- Circuit

- 2:1 multiplexer

 

- Symptom

- Mux works when selected D is 0 but not 1.
- Or fails at low V_{DD} .
- Or fails in SF corner.


- Principle: Threshold drop

- X never rises above $V_{DD} - V_t$
- V_t is raised by the body effect
- The threshold drop is most serious as V_t becomes a greater fraction of V_{DD} .

- Solution: Use transmission gates, not pass transistors

Leakage

- Circuit
 - Latch

 


- Symptom
 - Load a 0 into Q
 - Set $\phi = 0$
 - Eventually Q spontaneously flips to 1

□ Principle: Leakage

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge

□ Solution: Stabilize node with feedback

 
- Or periodically refresh node (requires fast clock, not practical processes with big leakage)



Leakage

- Circuit

- Domino AND gate

 


- Symptom

- Precharge gate ($Y=0$)
- Then evaluate
- Eventually Y spontaneously flips to 1

- Principle: Leakage

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge


- Solution: Keeper

 

Ratio Failure

- Circuit

- Pseudo-nMOS OR

 

- Symptom

- When only one input is true, $Y = 0$.
- Perhaps only happens in SF corner.

- Principle: Ratio Failure


- nMOS and pMOS fight each other.
- If the pMOS is too strong, nMOS cannot pull X low enough.

- Solution: Check that ratio is satisfied **in all corners**

Ratio Failure

- Circuit

- Latch

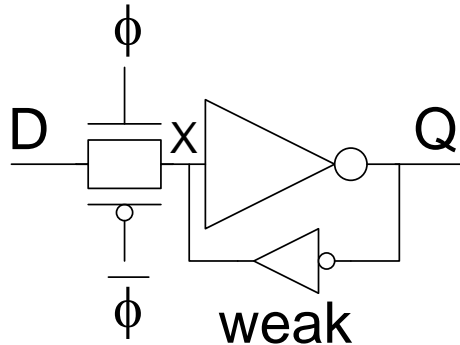

- Symptom


- Q stuck at 1.
- May only happen for certain latches where input is driven by a small gate located far away.

- Principle: Ratio Failure (again)

- Series resistance of D driver, wire resistance, and t_{gate} must be much less than weak feedback inverter.

- Solutions: Check relative strengths

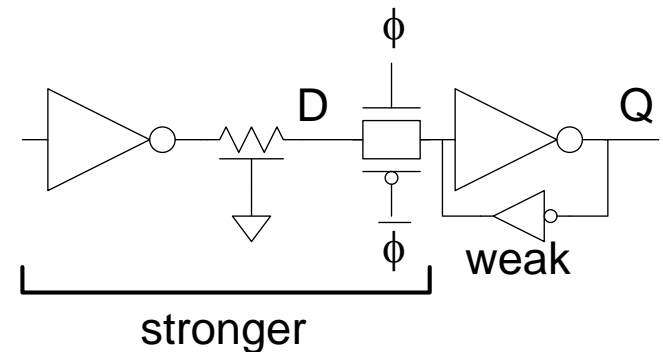
- Avoid unbuffered diffusion inputs where driver is unknown



Charge Sharing

- Circuit

- Domino AND gate

 

- Symptom

- Precharge gate while $A = B = 0$, so $Z = 0$
- Set $\phi = 1$
- A rises
- Z is observed to sometimes rise


- Principle: Charge Sharing

- If X was low, it shares charge with Y

- Solutions: Limit charge sharing

$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$

 
- Safe if $C_Y \gg C_X$
- Or precharge node X too



Charge Sharing

- Circuit

- Dynamic gate
+ latch

 

- Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls


- Principle: Charge Sharing

- If Y was low, it shares charge with X

- Solution: Buffer dynamic nodes before driving transmission gate

Diffusion Input Noise

- Circuit
 - Latch

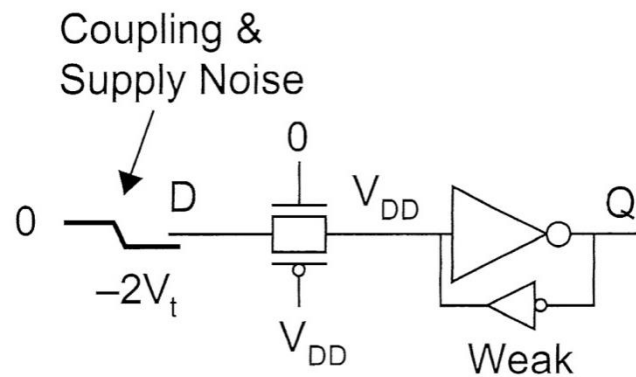


- Symptom
 - Q changes while latch is opaque
 - Especially if D comes from a far-away driver

❑ Principle: Diffusion Input Noise Sensitivity



- If $D < -V_t$, transmission gate turns on
- Most likely because of power supply noise or coupling on D

❑ Solution: Buffer D locally

 


Hot Spot

  - Nonuniform power dissipation (even within overall power budget)



Minority Carrier Injection

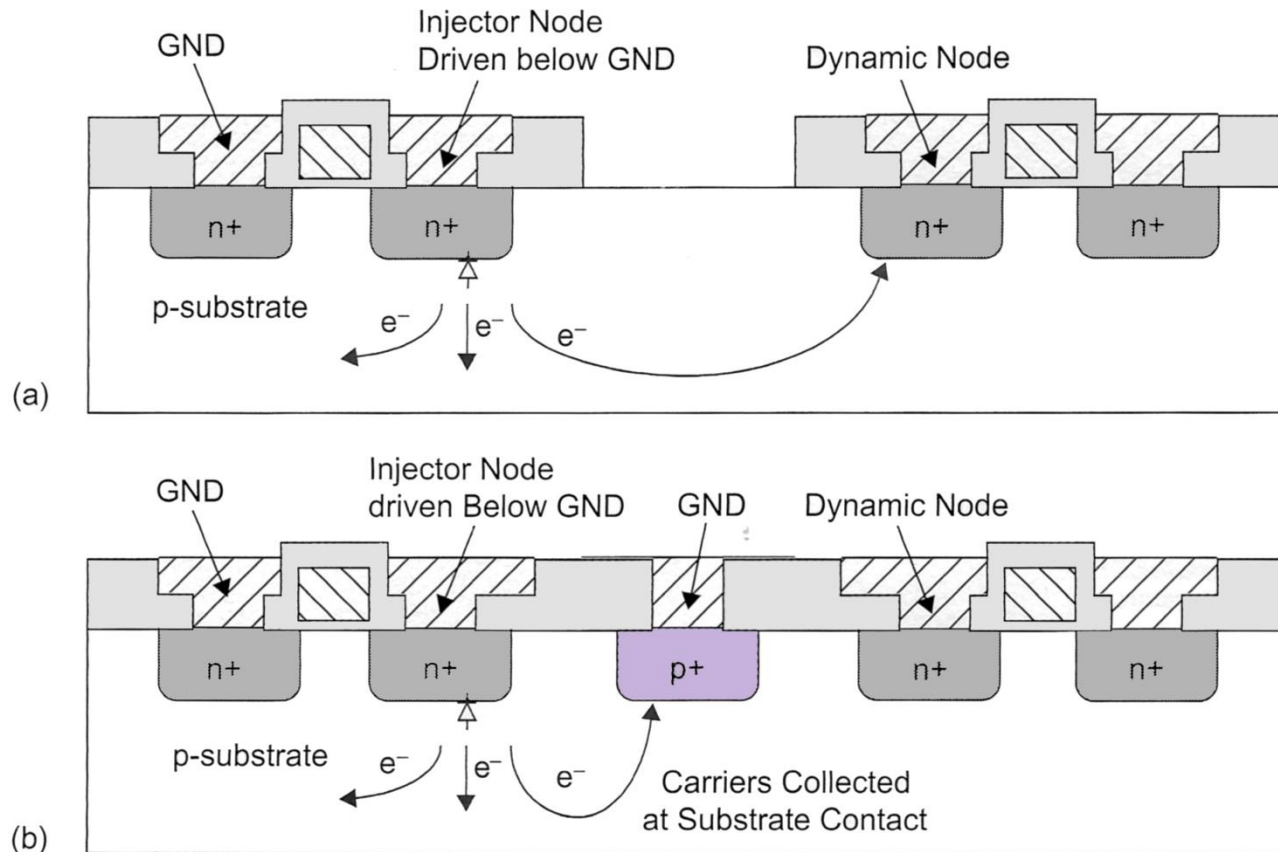- Minority injection caused by forward biased p-n junction
- Solution: Use guard ring to collect the excess minority



Back-Gate Coupling

- Dynamic gates drive multiple-input static CMOS gates
- Solution : Drive input closer to the rail

