

An aerial photograph of a city grid, overlaid with various colored rectangles in shades of purple, green, and red, representing different zones or data points.

## CHAPTER 6


# Sequential Circuit Design

# Outline


- 1. Sequencing**
2. Sequencing Element Design
3. Max and Min-Delay
4. Time Borrowing
5. Clock Skew
6. Two-Phase Clocking
 
# Sequencing

- *Combinational logic*
  - output depends on current inputs
- *Sequential logic*
  - output depends on current and previous inputs
  - Requires separating previous, current, future
  - Called *state* or *tokens*
  - Ex: FSM, pipeline



Finite State Machine

 

Pipeline

# Sequencing Cont.

- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
  - Light pulses (tokens) are sent down cable
  - Next pulse sent before first reaches end of cable
  - No need for hardware to separate pulses
  - But *dispersion* sets min time between pulses
- This is called *wave pipelining* in circuits
- In most circuits, dispersion is high
  - Delay fast tokens so they don't catch slow ones.

# Sequencing Overhead

- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
  - Called sequencing overhead
- Some people call this clocking overhead
  - But it applies to asynchronous circuits too
  - Inevitable side effect of maintaining sequence

# Outline

1. Sequencing
- 2. Sequencing Element Design**
3. Max and Min-Delay
4. Time Borrowing
5. Clock Skew
6. Two-Phase Clocking

# Static vs Dynamic Storage


- Static storage
  - preserve state as long as the power is on
  - have positive feedback (**regeneration**) with an internal connection between the output and the input
  - useful when updates are infrequent (clock gating)
- Dynamic storage
  - store state on parasitic capacitors
  - only hold state for short periods of time (milliseconds)
  - require periodic refresh
  - usually simpler, so higher speed and lower power

# Sequencing Elements

- **Latch:** level sensitive
  - a.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
  - a.k.a. master-slave flip-flop, D flip-flop, D register

- **Timing Diagrams**

- Transparent
- Opaque
- Edge-trigger

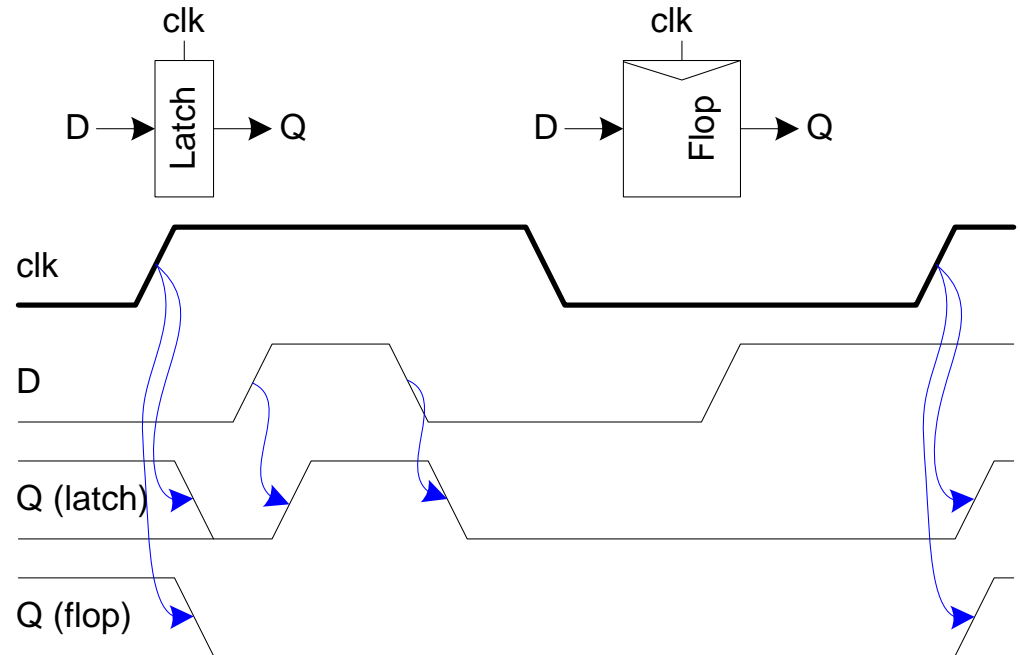




# Latches vs Flipflops

- Latches
  - **level sensitive** circuit that passes inputs to Q when the clock is high (or low) - **transparent** mode
  - input sampled on the falling edge of the clock is held stable when clock is low (or high) - **hold** mode
- Flipflops (edge-triggered)
  - **edge sensitive** circuits that sample the inputs on a clock transition
    - positive edge-triggered:  $0 \rightarrow 1$
    - negative edge-triggered:  $1 \rightarrow 0$
  - built using latches (e.g., master-slave flipflops)
 
# Latch Design


- Pass Transistor Latch
- Pros
  - + Tiny
  - + Low clock load
- Cons
  - $V_t$  drop (not rail-to-rail)
  - Nonrestoring
  - Backdriving
  - Output noise sensitivity
  - Dynamic (floating when opaque)
  - Diffusion input



Used in 1970's
 
# Latch Design


- Transmission gate
  - + No  $V_t$  drop
  - Requires inverted clock


 
# Latch Design



6- 12

- Inverting buffer
  - + Restoring
  - + No backdriving
  - + Fixes either
    - Output noise sensitivity
    - Or diffusion input
  - Inverted output



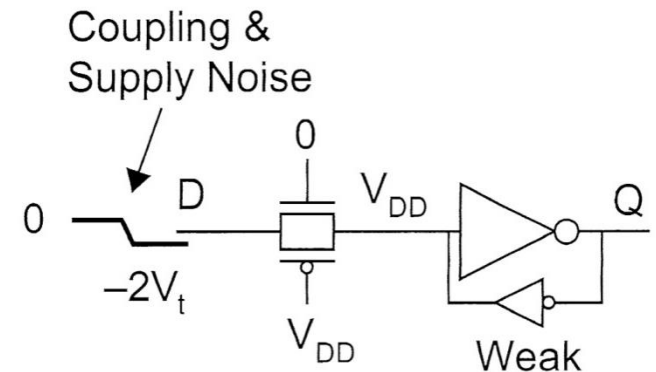 
# Latch Design

- Tristate feedback
  - + Static
  - Backdriving risk
  - Diffusion input
- Noise on diffusion input
  - Noise couple will turn ON the “OFF” transmission gate and destroy the output
- Static latches are now essential



 
# Latch Design

- Buffered input
  - + Fixes diffusion input
  - + Noninverting
  - Output noise backdriving



 
# Latch Design

- Buffered output  
+ No backdriving
- Widely used in standard cells
  - + Very robust (most important)
  - Rather large
  - Rather slow (1.5 – 2 FO4 delays)
  - High clock loading


 
# Latch Design

- Datapath latch
  - + Smaller, faster
  - Unbuffered input
  - Need careful input noise control







   
# Clocked CMOS : C<sup>2</sup>MOS


- C<sup>2</sup>MOS latch
  - + Smaller
  - Slower

D toggle will cause charge sharing noise while opaque.



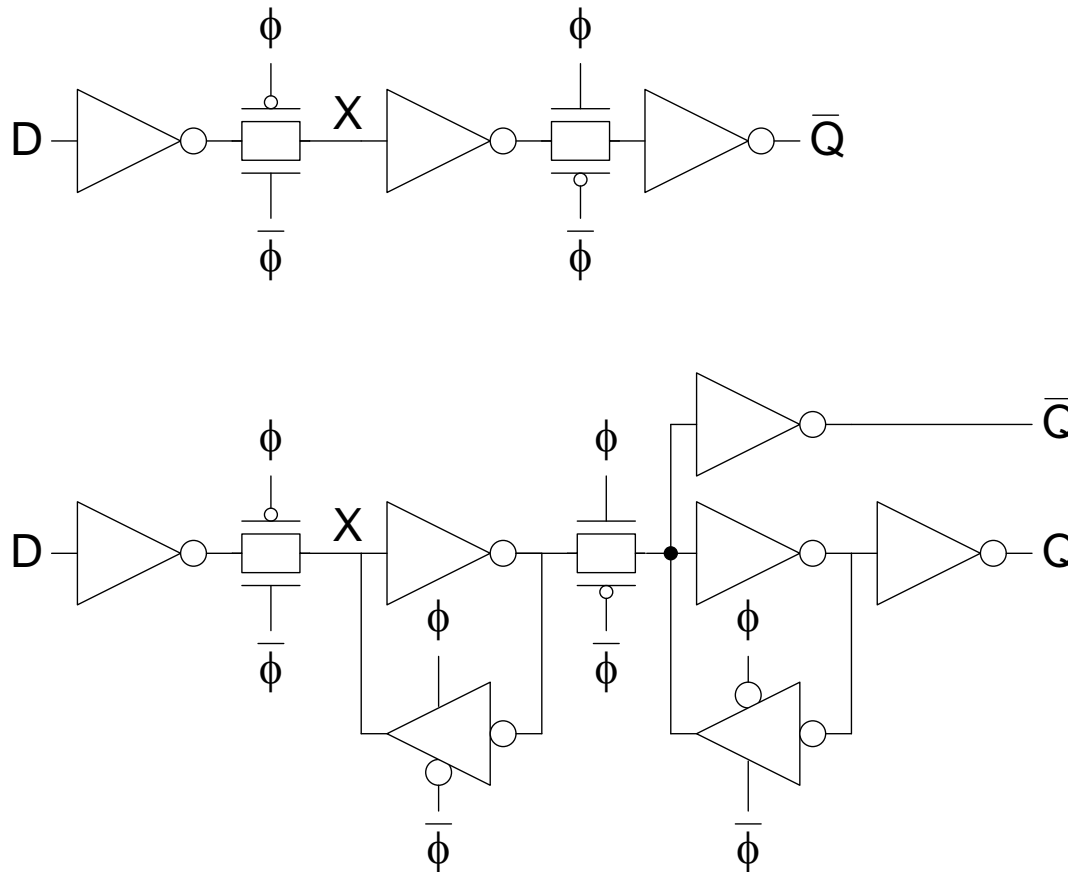
# Flip-Flop Design

- Flip-flop is built as pair of back-to-back latches



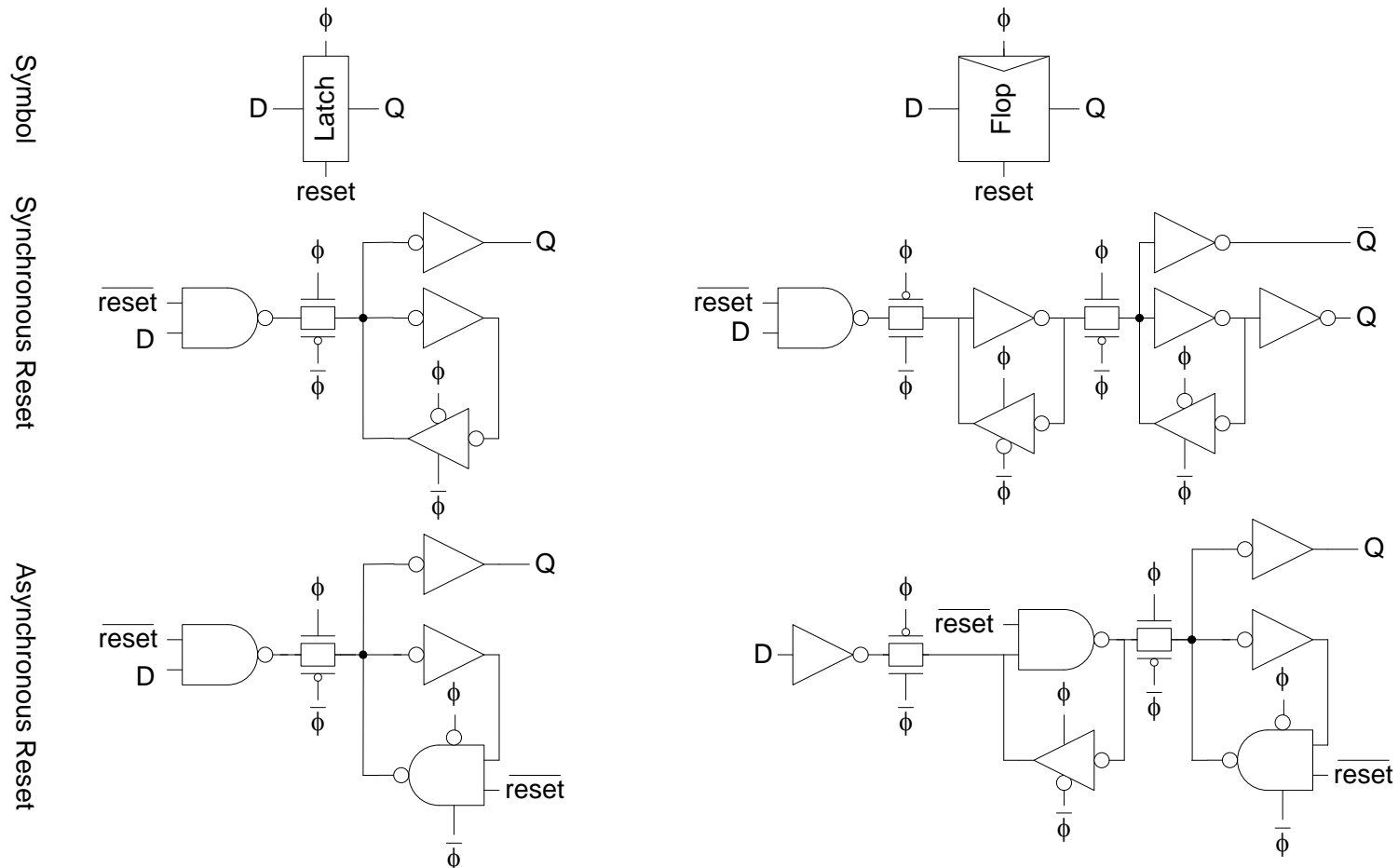
# Reset

- Force output low when reset asserted
- Synchronous vs. asynchronous


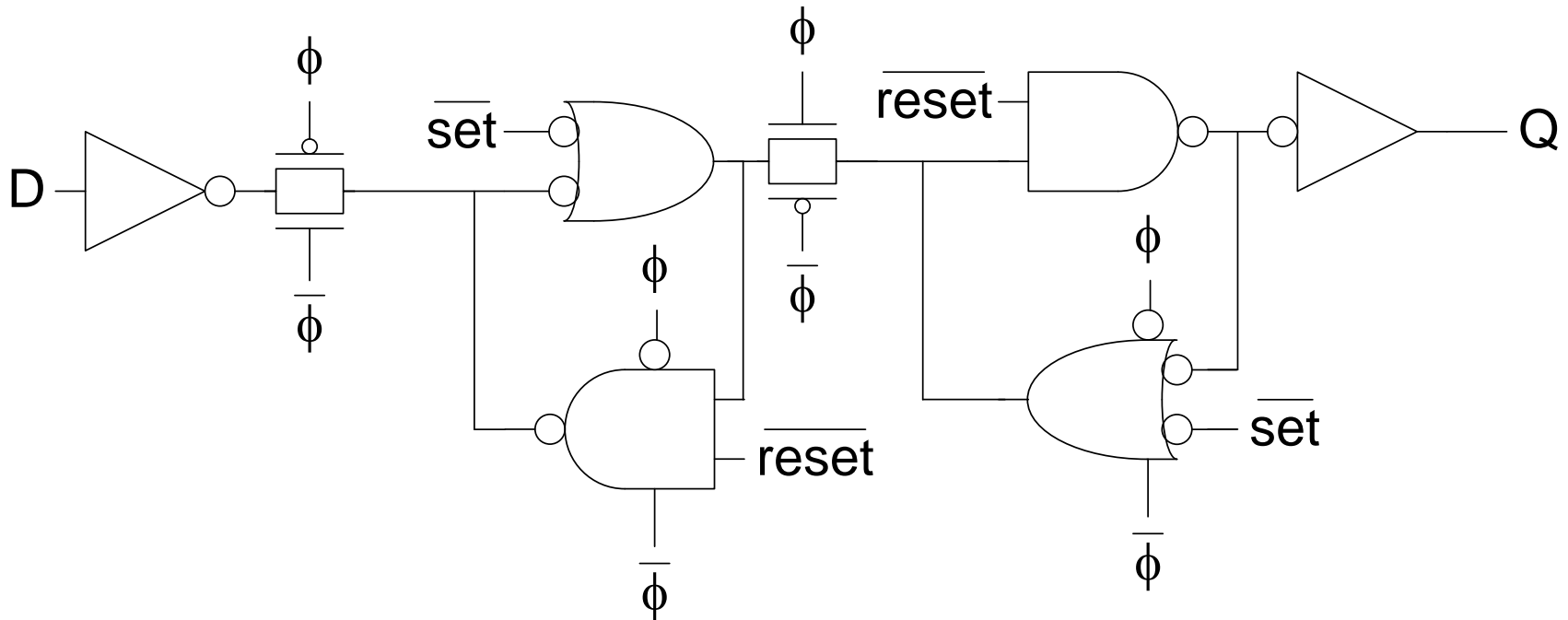
# Set / Reset



- Set forces output high when enabled
- Flip-flop with asynchronous set and reset





# Enable

- Enable: ignore clock when  $en = 0$ 
  - Mux: increase latch D-Q delay
  - Clock Gating: increase en setup time, skew



Symbol

  

Multiplexer Design

  


Clock Gating Design

  


# Sequencing Methods

- Flip-flops

 



- 2-Phase Latches

- Pulsed Latches




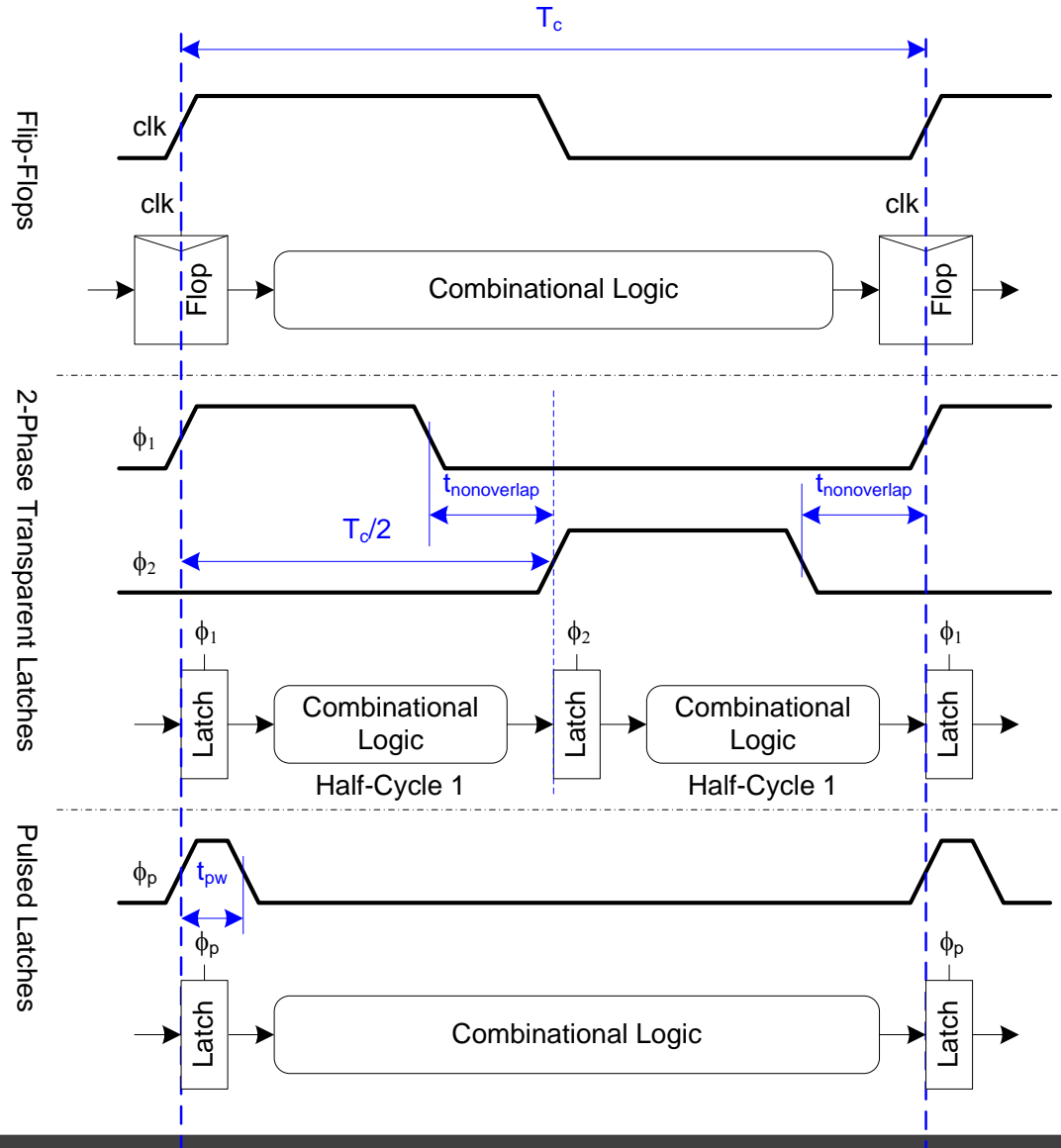


# Timing Diagrams

## Contamination and Propagation Delays

  

$t_{pd}$	Logic Prop. Delay
$t_{cd}$	Logic Cont. Delay
$t_{pcq}$	Latch/Flop Clk-Q Prop Delay
$t_{ccq}$	Latch/Flop Clk-Q Cont. Delay
$t_{pdq}$	Latch D-Q Prop Delay
$t_{cdq}$	Latch D-Q Cont. Delay
$t_{setup}$	Latch/Flop Setup Time
$t_{hold}$	Latch/Flop Hold Time

    


# Outline


1. Sequencing
2. Sequencing Element Design
- 3. Max and Min-Delay**
4. Time Borrowing
5. Clock Skew
6. Two-Phase Clocking



# Sequential Logic

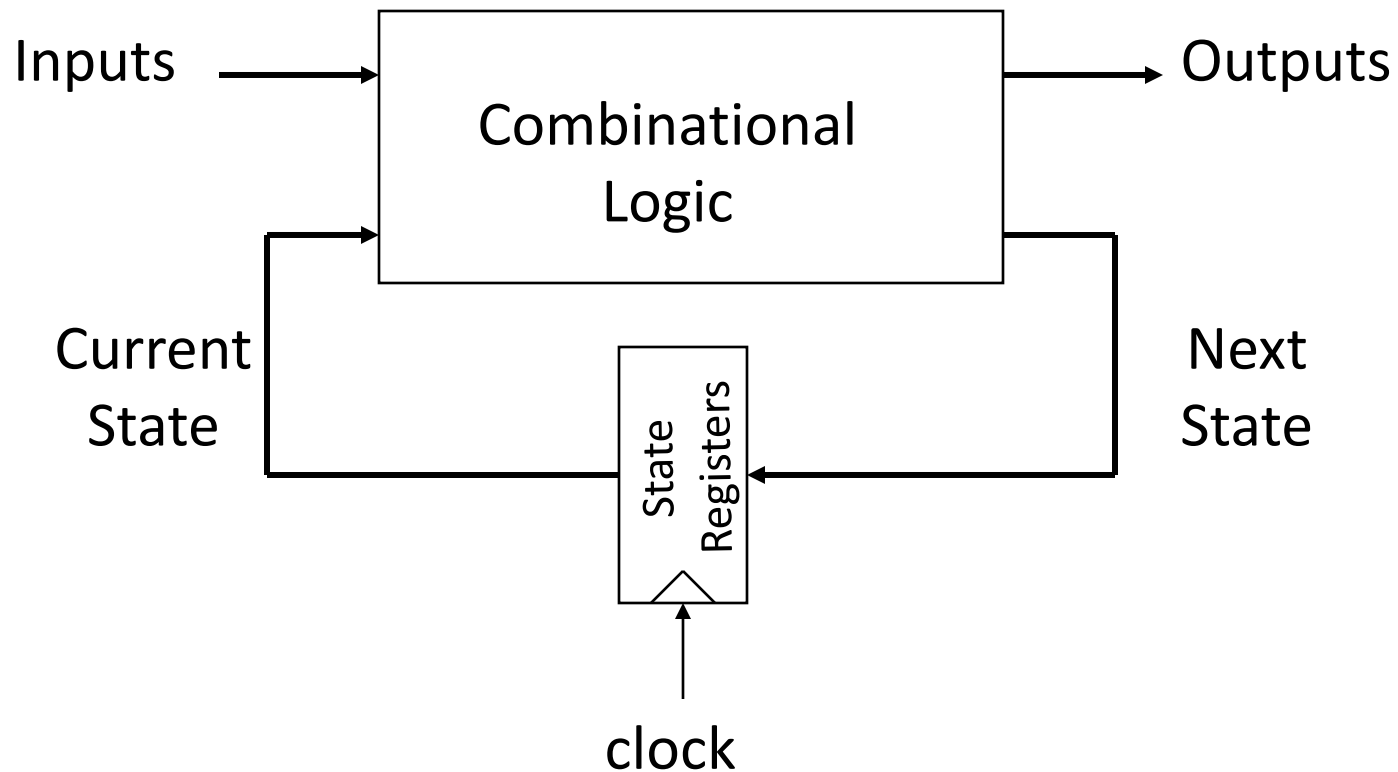


# Timing Metrics

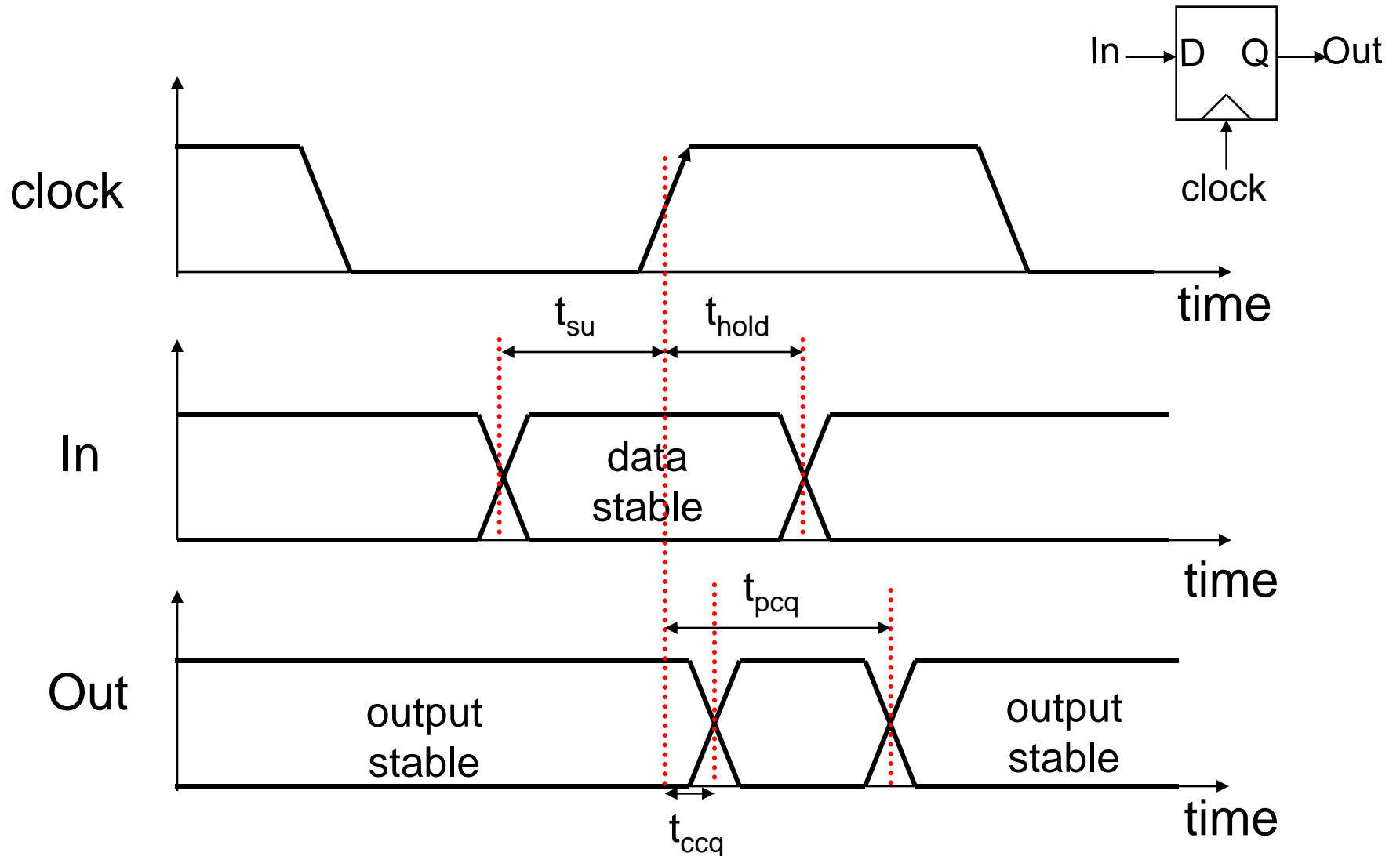

# System Timing Constraints

6- 27

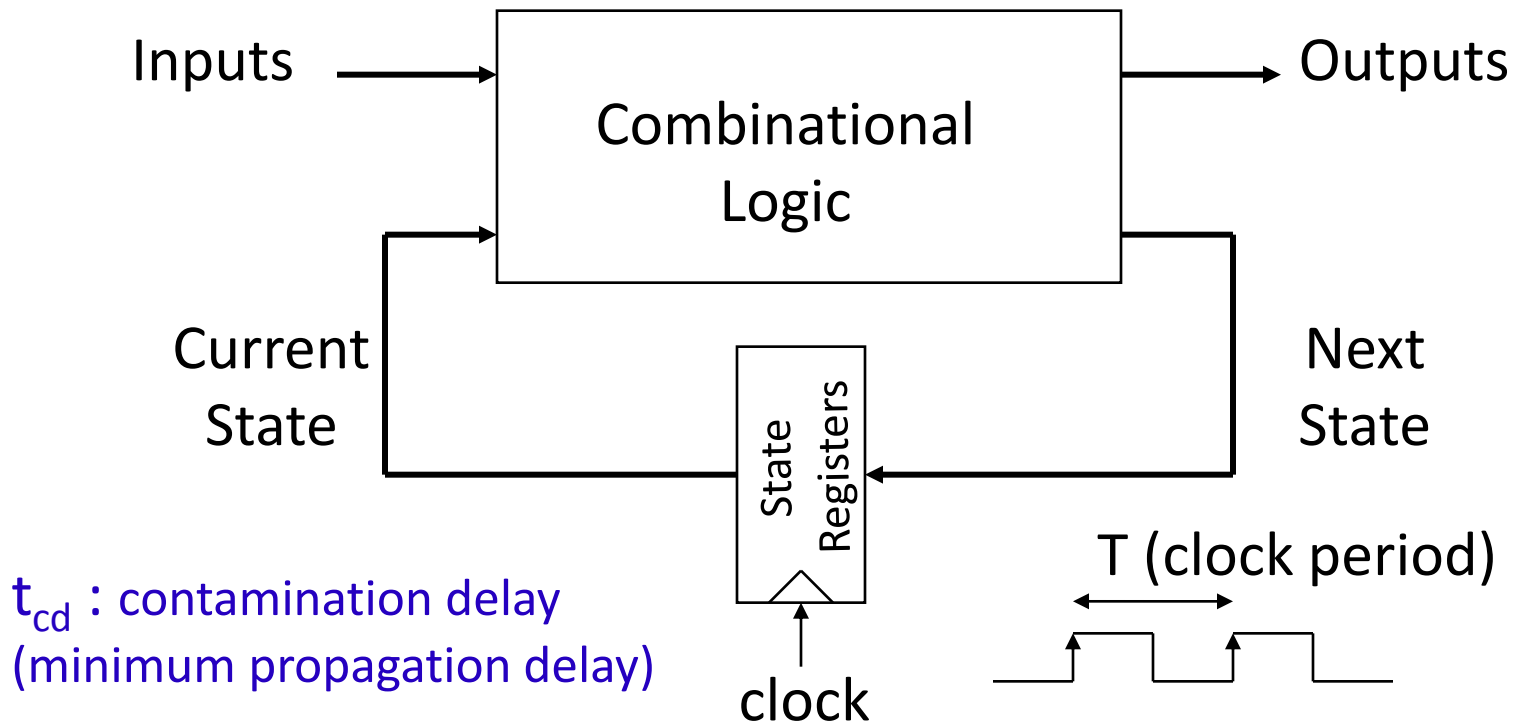


$t_{cd}$  : contamination delay  
(minimum propagation delay)

$$t_{ccq} + t_{cdlogic} \geq t_{hold}$$

$t_{ccq}$  : minimum delay of register

$t_{cdlogic}$  : minimum delay of logic

 

$$T \geq t_{pcq} + t_{plogic} + t_{su}$$

$t_{pcq}$  : maximum delay of register


$t_{plogic}$  : maximum delay of logic

# Max/Min Delay Constraints

- Max-Delay Constraints
  - Combinational logic delay is too great, the receiving element will miss its setup time and sample the wrong value : **setup time failure** (*max-delay failure*)
  - It can be solved by redesign faster logic or by increasing the clock period.
- Min-Delay Constraints
  - If the hold time is large and the contamination delay is small, data can incorrectly propagate through on one clock edge and corrupt the state : **race condition**, **hold time failure**, or *min-delay failure*.
  - Redesign slower logic.
 
# Max-Delay: Flip-Flops


$$t_{pd} \leq T_c - \underbrace{(t_{setup} + t_{pcq})}_{\text{sequencing overhead}}$$


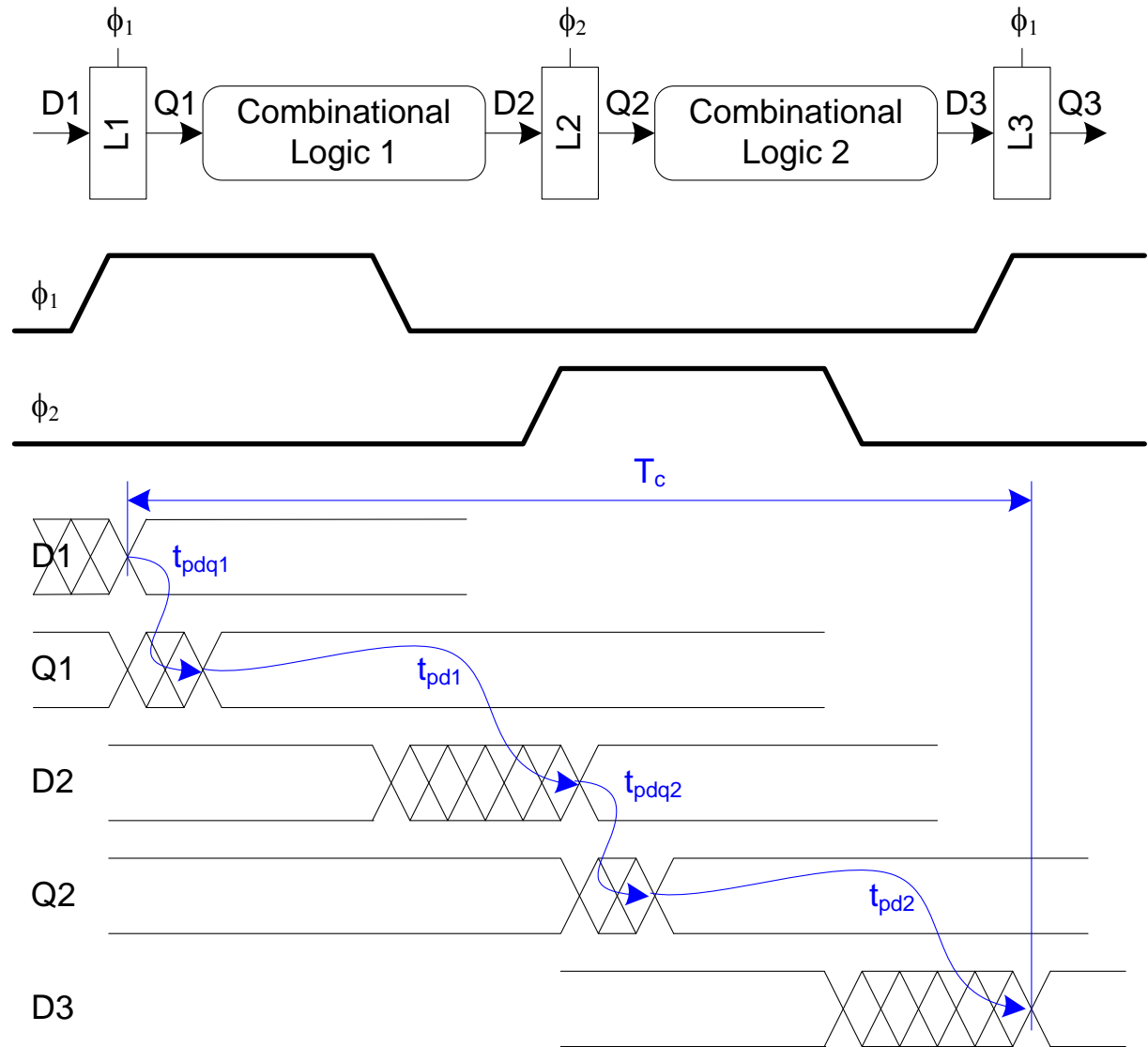
# Max Delay: 2-Phase Latches



$$t_{pd} = t_{pd1} + t_{pd2}$$

$$\leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$




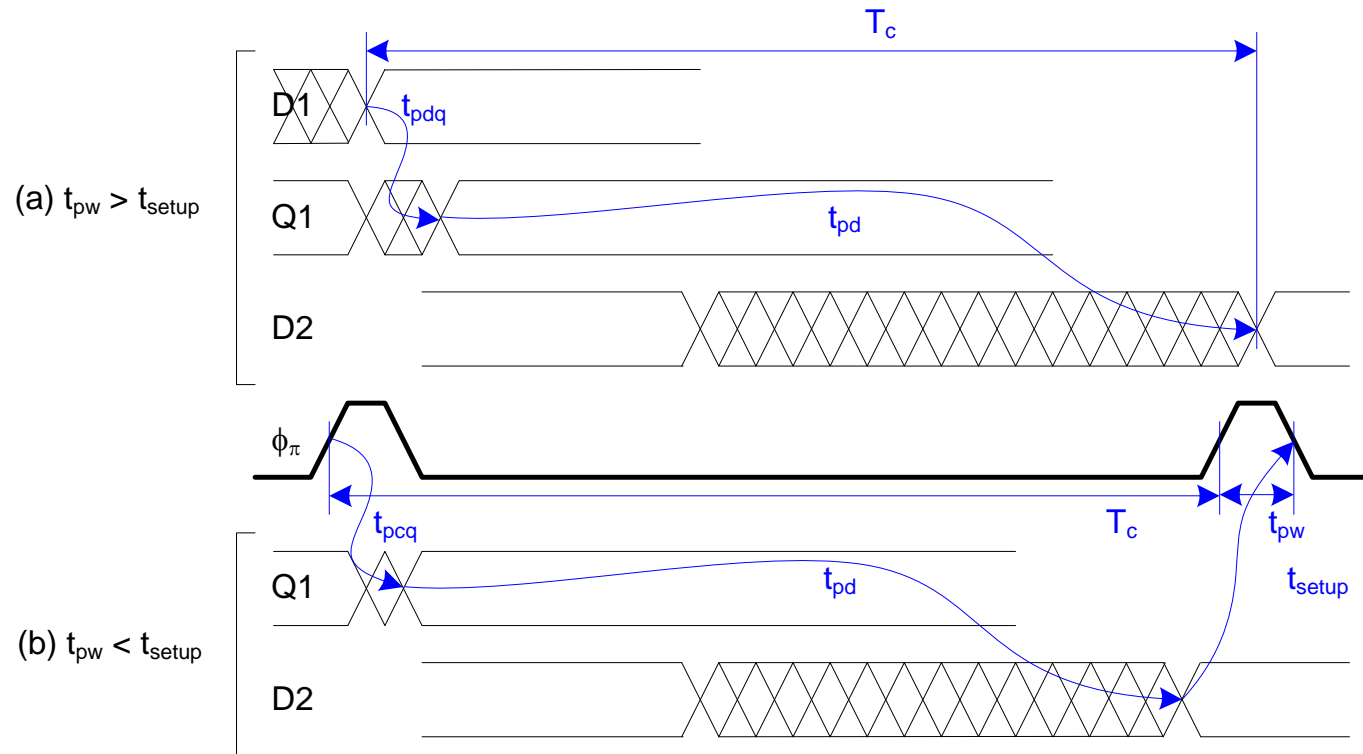
 
# Max Delay: Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}}$$



# Min-Delay: Flip-Flops


$$t_{cd} \geq t_{hold} - t_{ccq}$$

 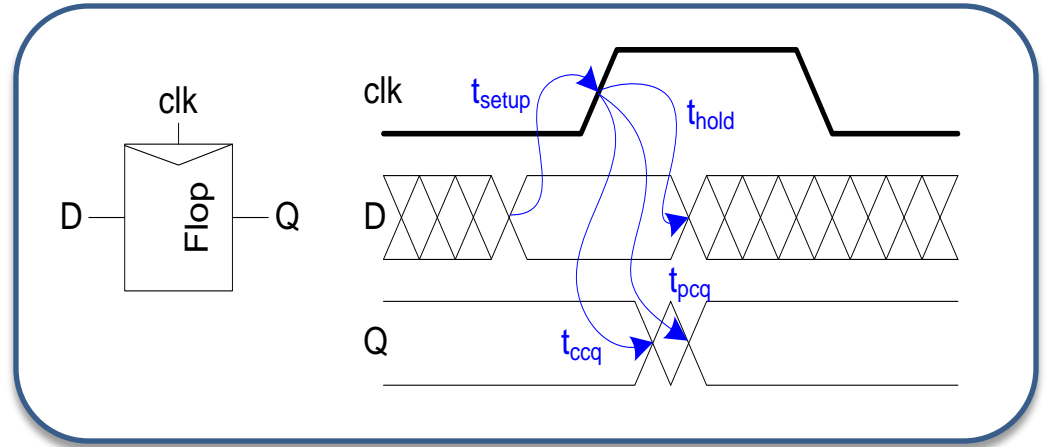 


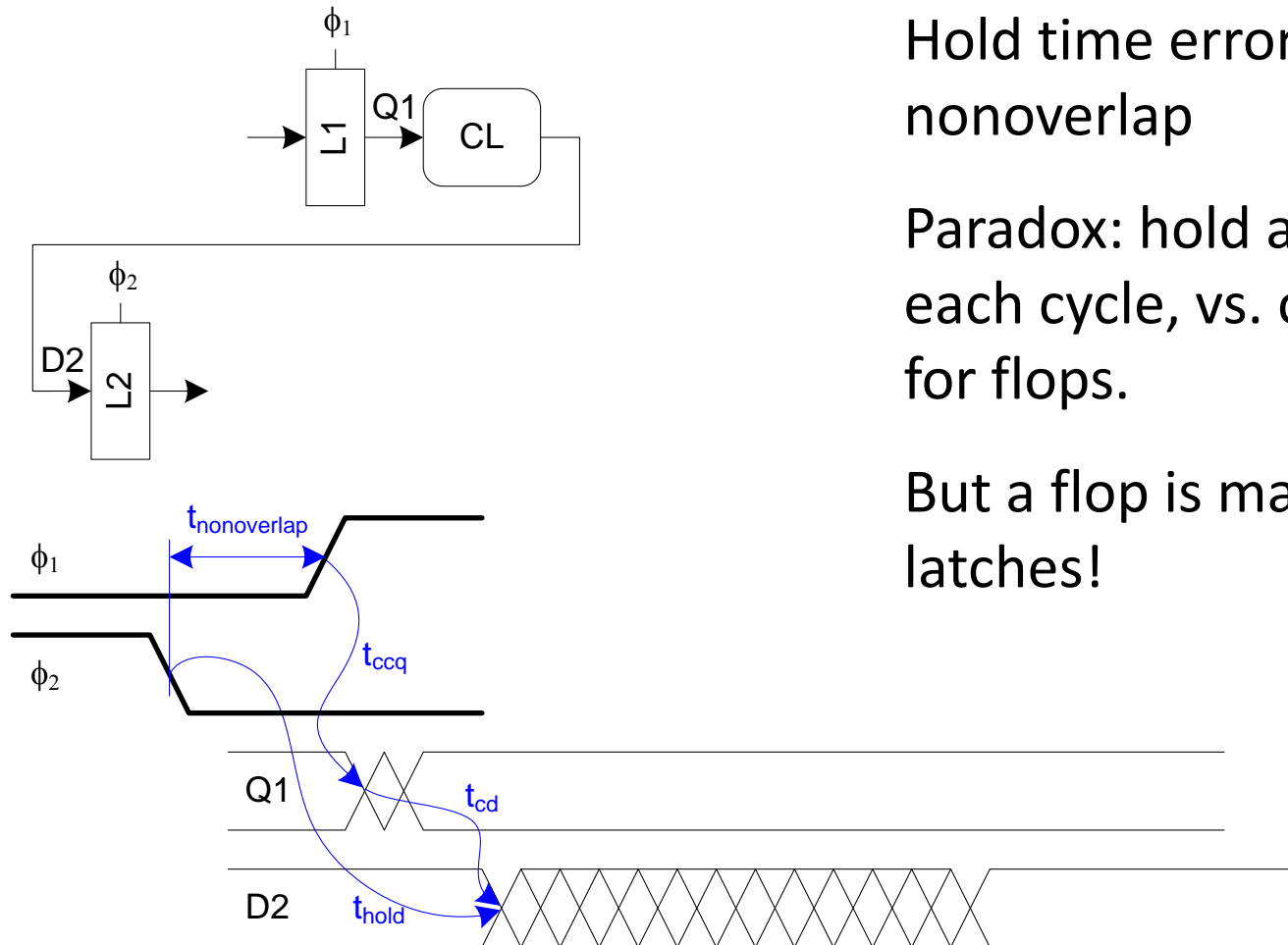
# Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$




Hold time error **reduced** by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.

But a flop is made of two latches!
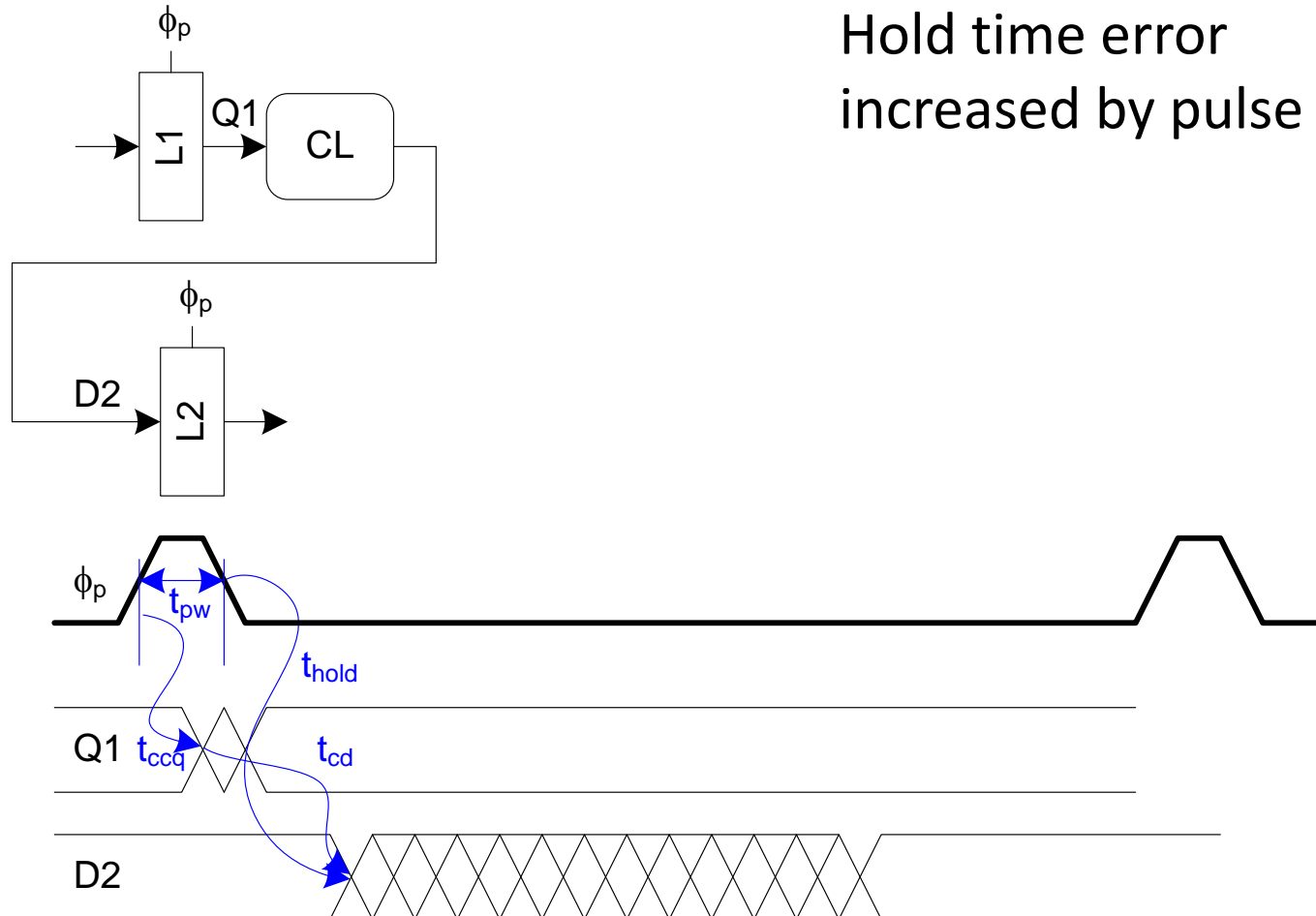
# Min-Delay: Pulsed Latches

$$t_{cd} \geq t_{hold} - t_{ccq} + t_{pw}$$




# Outline

1. Sequencing
2. Sequencing Element Design
3. Max and Min-Delay
- 4. Time Borrowing**
5. Clock Skew
6. Two-Phase Clocking

# Time Borrowing

- In a flop-based system:
  - Data launches on one rising edge
  - Must setup before next rising edge
  - If it arrives late, system fails
  - If it arrives early, time is wasted
  - Flops have hard edges
- In a latch-based system
  - Data can pass through latch while transparent
  - Long cycle of logic can borrow time into next
  - As long as each loop completes in one cycle

# Time Borrowing Example

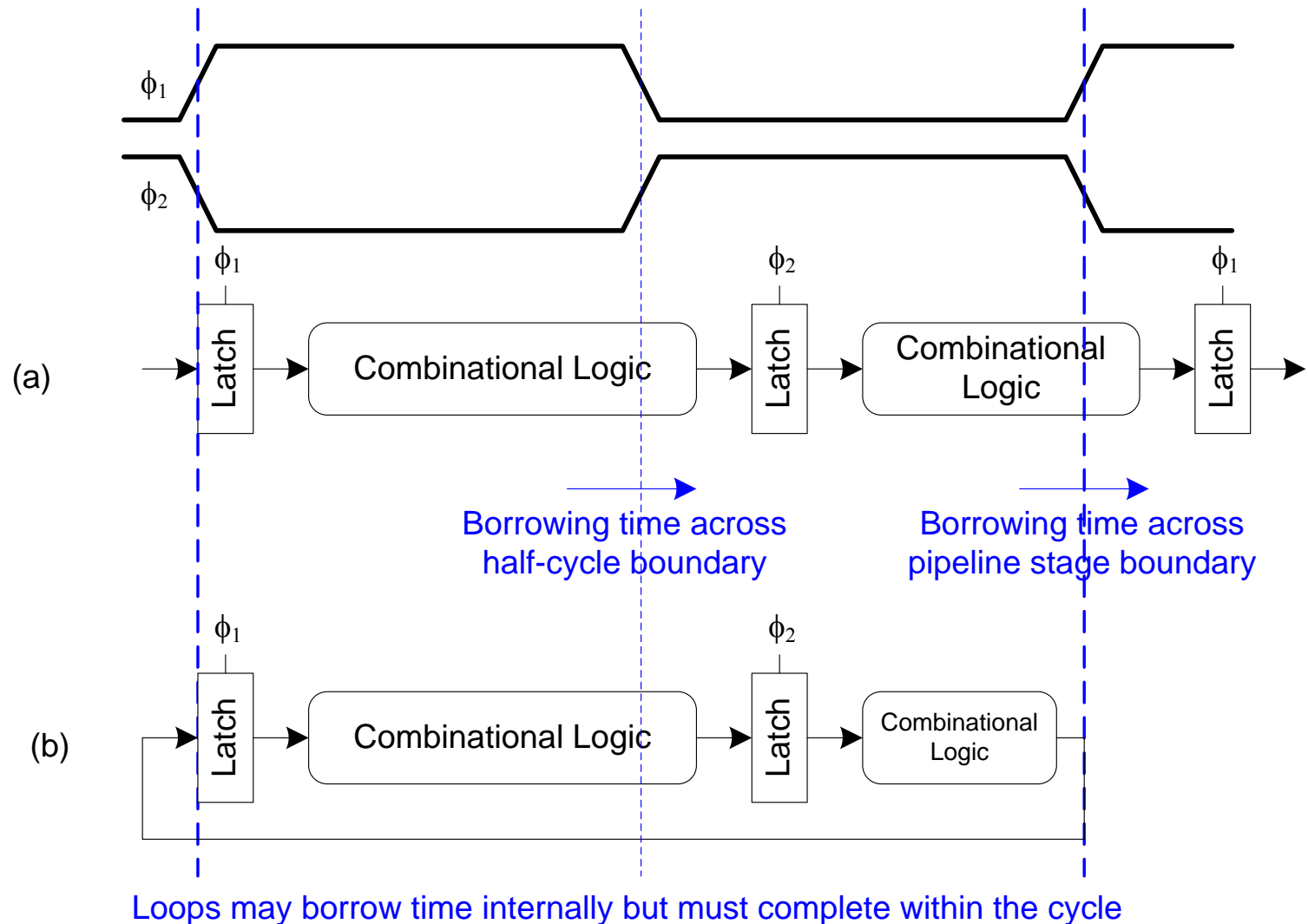


# How Much Borrowing?

## 2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$
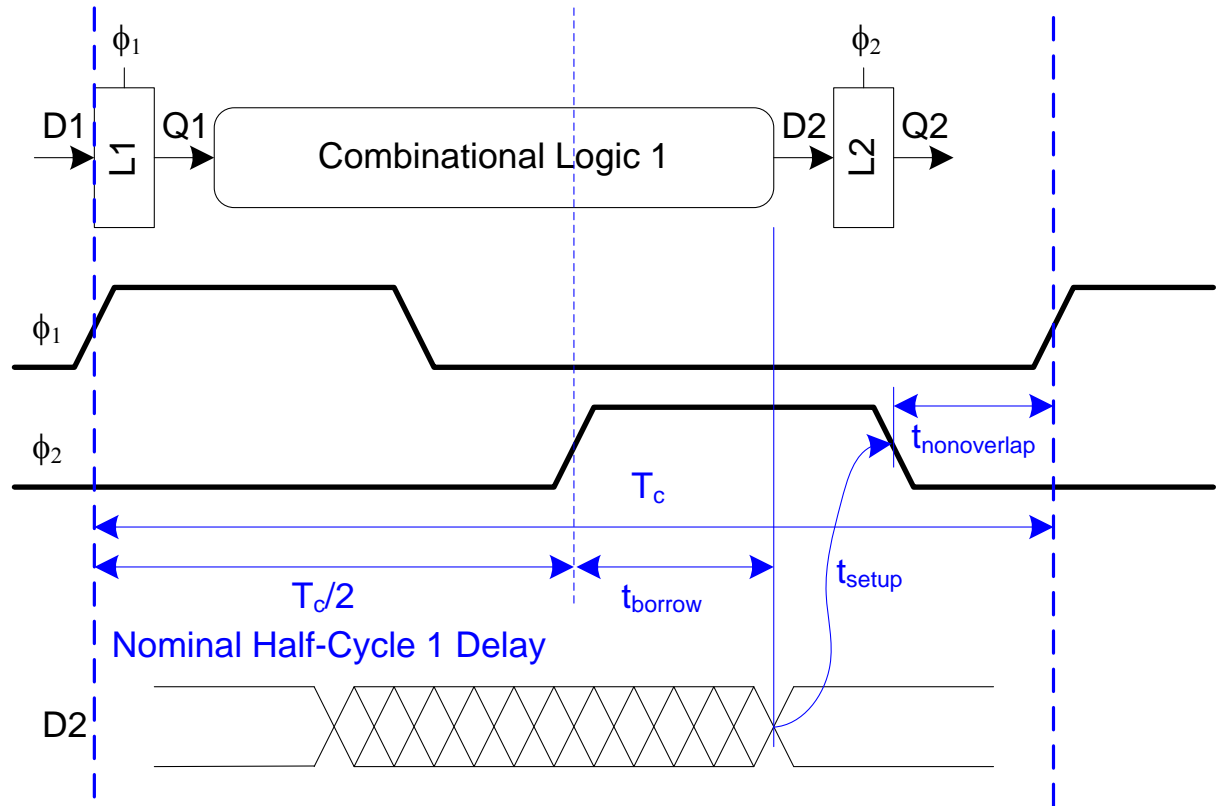
## Pulsed Latches

$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$



# Outline

1. Sequencing
2. Sequencing Element Design
3. Max and Min-Delay
4. Time Borrowing
- 5. Clock Skew**
6. Two-Phase Clocking


# Clock Skew

- We have assumed zero clock skew
- Clocks really have uncertainty in arrival time
  - Decreases maximum propagation delay
  - Increases minimum contamination delay
  - Decreases time borrowing



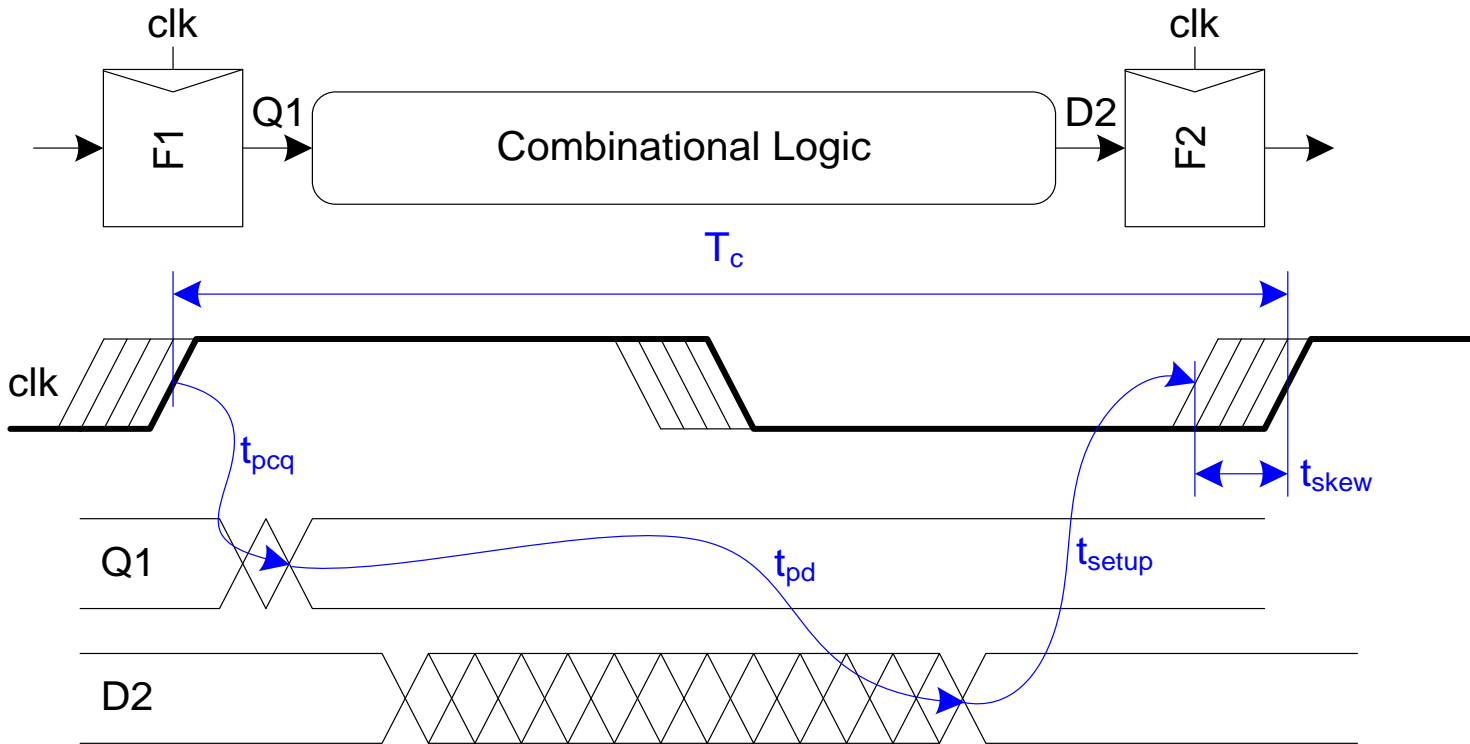
# Skew: Flip-Flops: Max Delay

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$


 
# Skew: Flip-Flops: Min Delay


$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{\text{skew}}$$


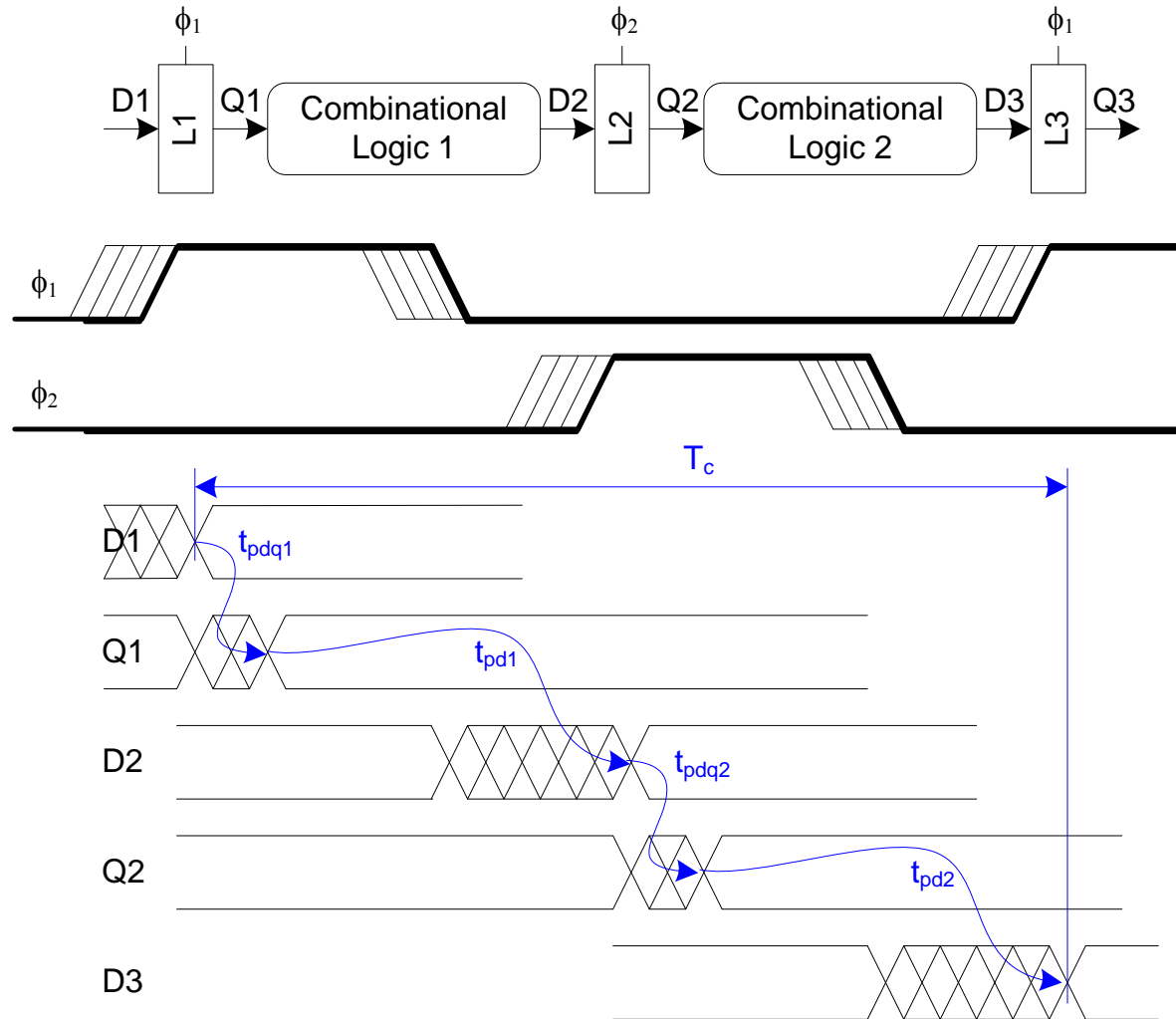
# Skew: 2-Phase Latches: Max Delay

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$


No change → Latch-based systems are **skew-tolerant**


 
# Skew: 2-Phase Latches: Min Delay

6- 44



$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$



# Skew: Pulsed Latches: Max Delay


$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})}_{\text{sequencing overhead}}$$

sequencing overhead

  
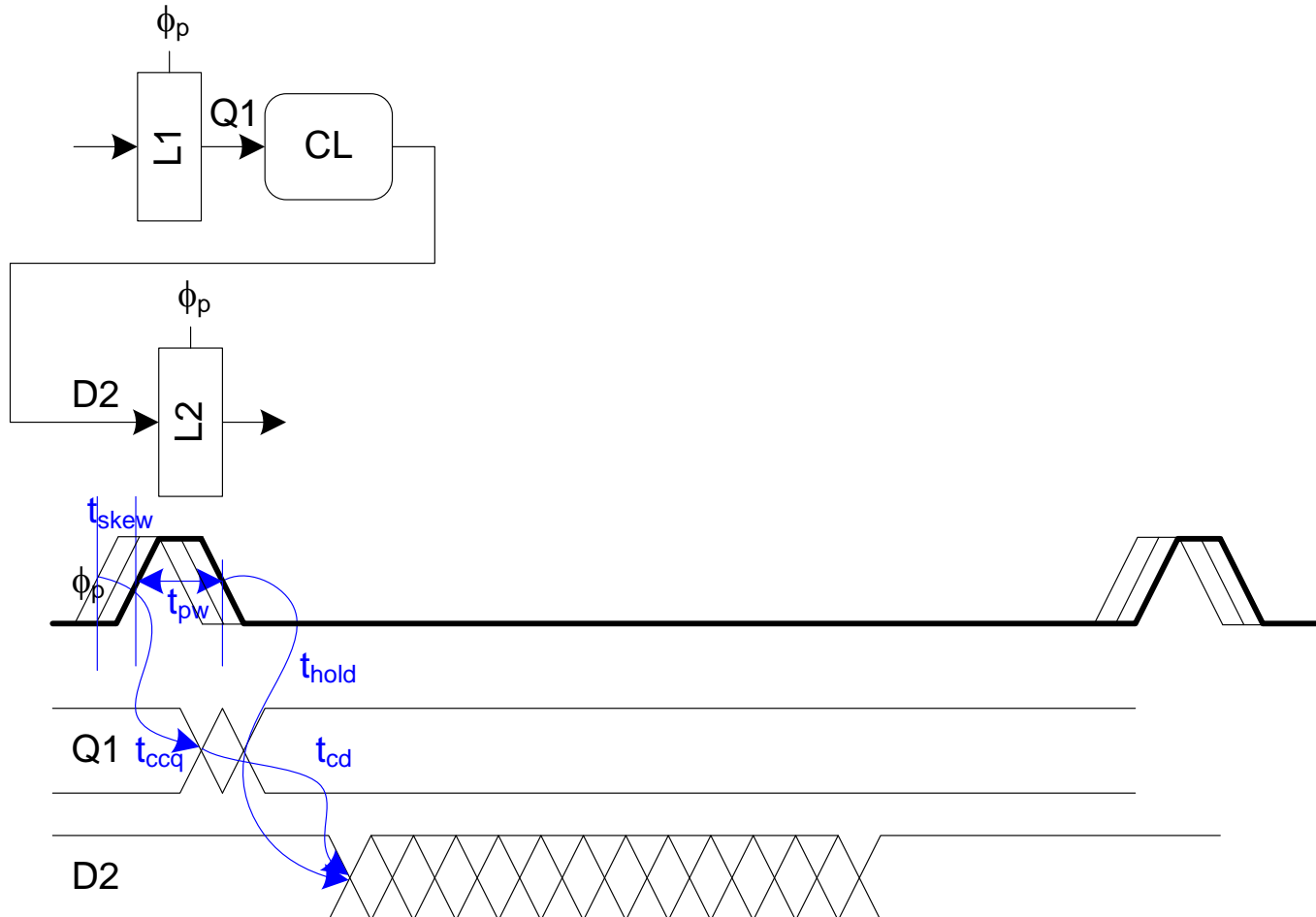
# Skew: Pulsed Latches: Min Delay

$$t_{cd} \geq t_{hold} + t_{pw} - t_{ccq} + t_{skew}$$




# Skew: How Much Borrowing ?

## 2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$
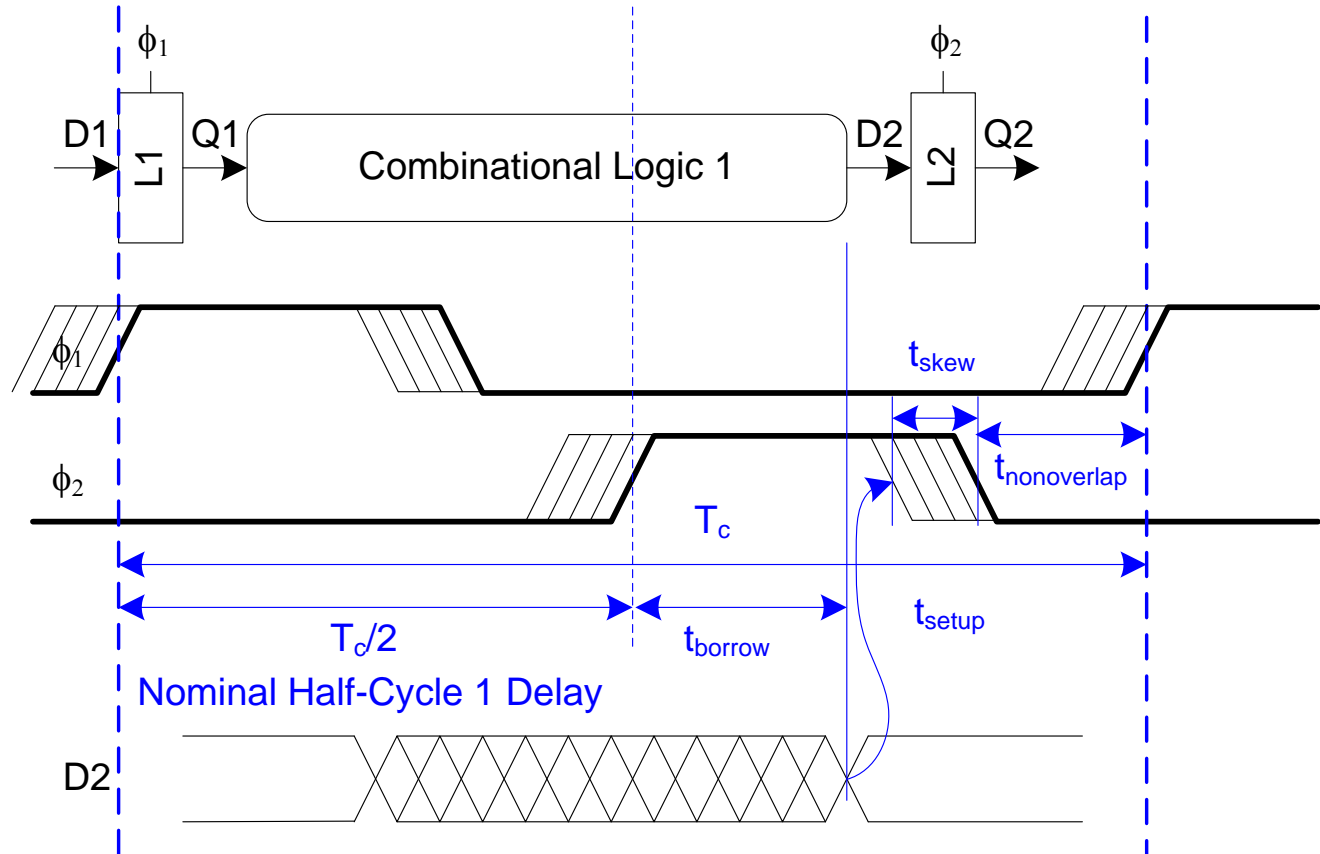
## Pulsed Latches

$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$






# Outline

1. Sequencing
2. Sequencing Element Design
3. Max and Min-Delay
4. Time Borrowing
5. Clock Skew
- 6. Two-Phase Clocking**



# Master Slave Based ET Flipflop

  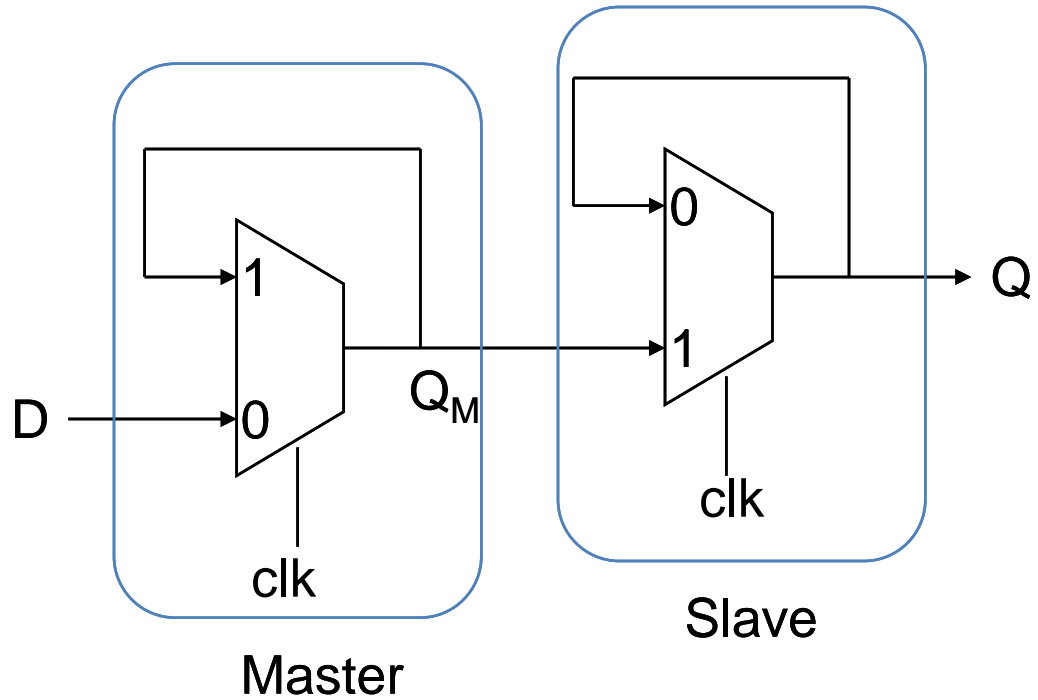



clk = 0 transparent

hold

clk = 0 → 1 hold

transparent

# MS ET Implementation

 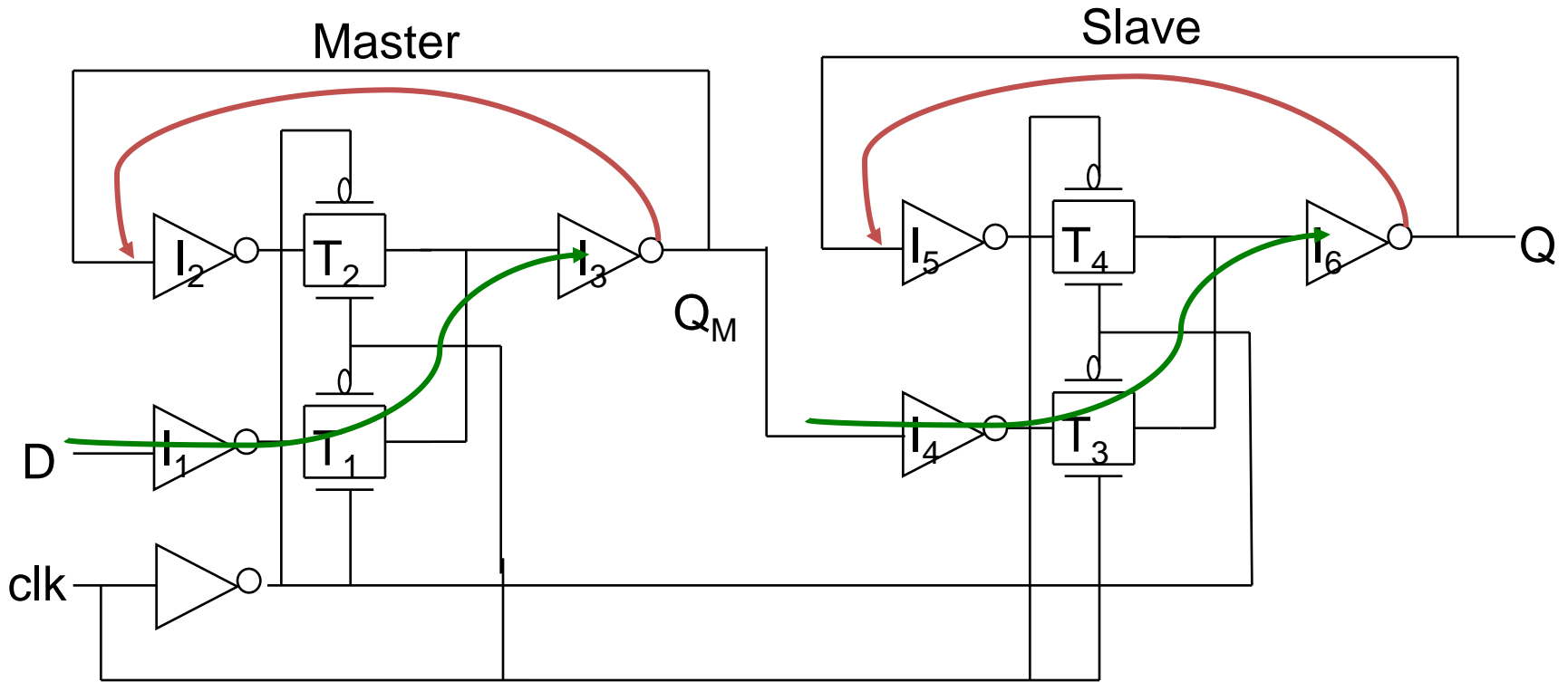

# MS ET Timing Properties

- Assume propagation delays are  $t_{pd\_inv}$  and  $t_{pd\_tx}$ , that the contamination delay is 0, and that the inverter delay to derive !clk is 0
- **Set-up time** - time before rising edge of clk that D must be valid

$$t_{su} = 3 * t_{pd\_inv} + t_{pd\_tx}$$


- **Propagation delay** - time for data to reach Q

$$t_{c-q} = t_{pd\_inv} + t_{pd\_tx}$$

- **Hold time** - time D must be stable after rising edge of clk -

$$t_{hold} = \text{zero}$$


# Set-up Time Simulation

 

$t_{\text{setup}} = 0.21 \text{ ns}$

works correctly


# Set-up Time Simulation

 

$t_{\text{setup}} = 0.20 \text{ ns}$

fails

# Propagation Delay Simulation

 


$$t_{c-q(LH)} = 160 \text{ psec}$$

$$t_{c-q(HL)} = 180 \text{ psec}$$

# Example of Clock Skew Problems

6- 55

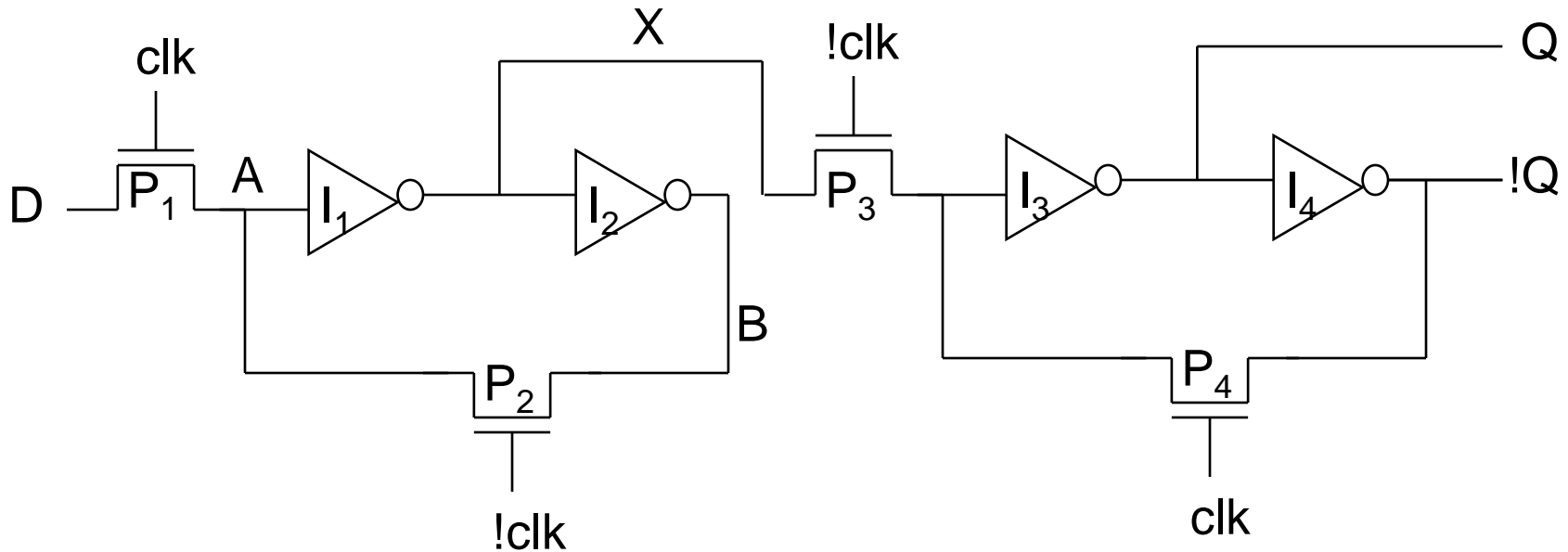

**Race condition** – direct path from D to Q during the short time when both clk and !clk are high (1-1 overlap)

**Undefined state** – both B and D are driving A when clk and !clk are both high

**Dynamic storage** – when clk and !clk are both low (0-0 overlap)


# Two-Phase Clocking

- If setup times are violated, reduce clock speed
- If hold times are violated, chip fails at any speed
- In this class, working chips are most important
  - No tools to analyze clock skew
- An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- Call these clocks  $\phi_1$ ,  $\phi_2$  (ph1, ph2)




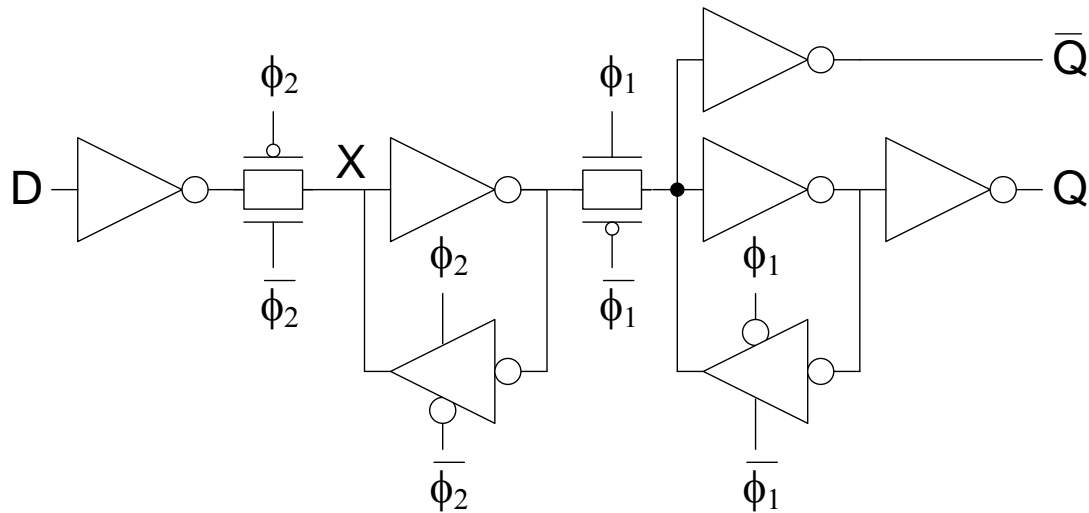
# Safe Flip-Flop



- In class, use flip-flop with nonoverlapping clocks
  - Very slow – nonoverlap adds to setup time
  - But no hold times
- In industry, use a better timing analyzer
  - Add buffers to slow signals if hold time is at risk



# Pseudostatic Two-Phase ET FF

 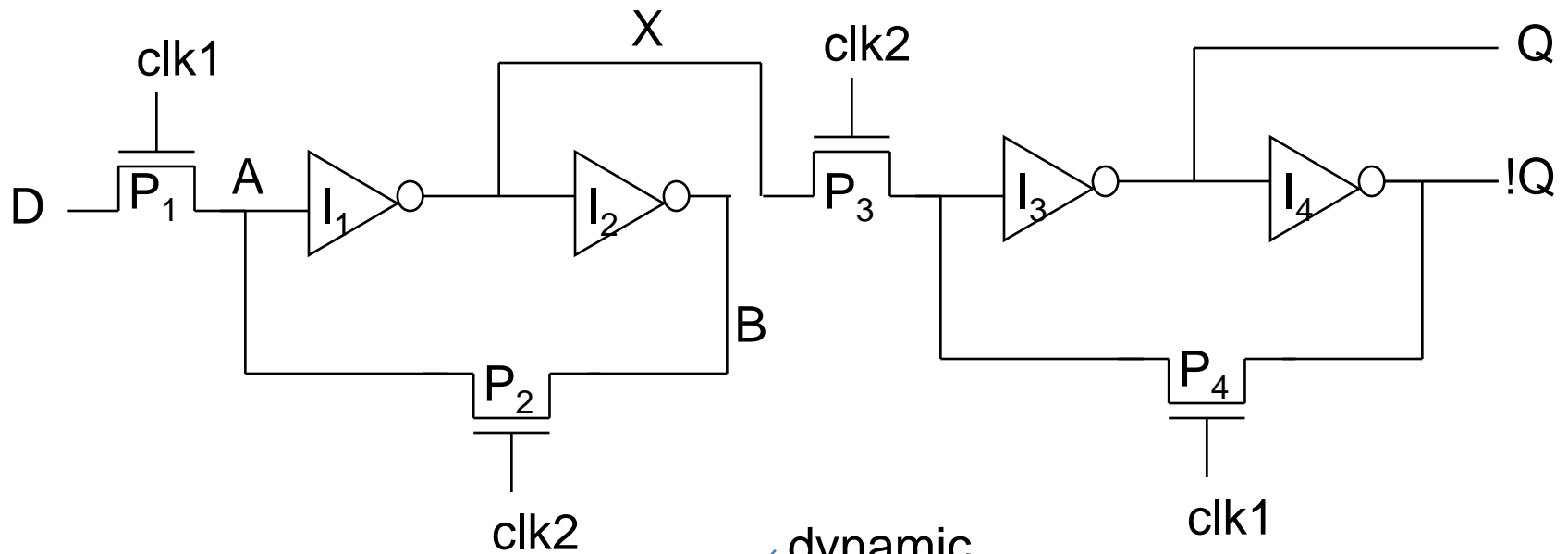

# Two Phase Clock Generator

  

# Summary

- Flip-Flops:
  - Very easy to use, greatest sequencing overhead
- 2-Phase Transparent Latches:
  - Lots of skew tolerance and time borrowing, great design effort to partition logic to half-cycles.
- Pulsed Latches:
  - Fast, some skew tol & borrow, hold time risk

**Table 7.4** Comparison of sequencing elements

	Sequencing overhead ( $T_c - t_{pd}$ )	Minimum logic delay $t_{cd}$	Time borrowing $t_{borrow}$
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{prw} + t_{skew})$	$t_{hold} - t_{ccq} + t_{prw} + t_{skew}$	

# Static Sequencing Element Methodology

6- 61

- Choice of elements
  - Flip-flops have fairly high sequencing overheads but are popular because they are so simple.
  - Transparent latches have lower sequencing overheads and are attractive because of time borrowing (nearly half cycle)
- Low power sequential design
  - Keep device sizes small inside the core latch and minimize the number of clocked transistors
  - Clock gating



# Outline

1. Sequencing
2. Sequencing Element Design
3. Max and Min-Delay
4. Time Borrowing
5. Clock Skew
6. Two-Phase Clocking
- 7. Synchronizers**


# Synchronizers

- Data input should change **outside** the **aperture** between the **setup** time and **hold** time.
- What if cannot?
- Synchronizer
  - Accepts an input that can **change at arbitrary times** and produces an output **aligned** to the synchronizer's clock

# Metastability

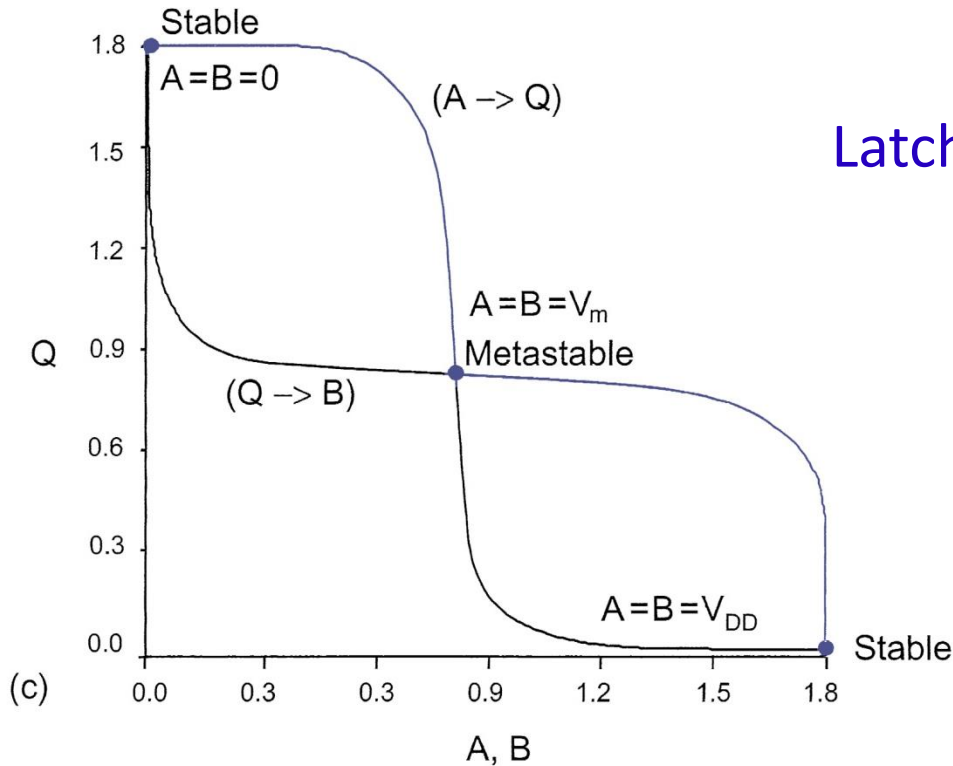 


Latch is a bistable device

 


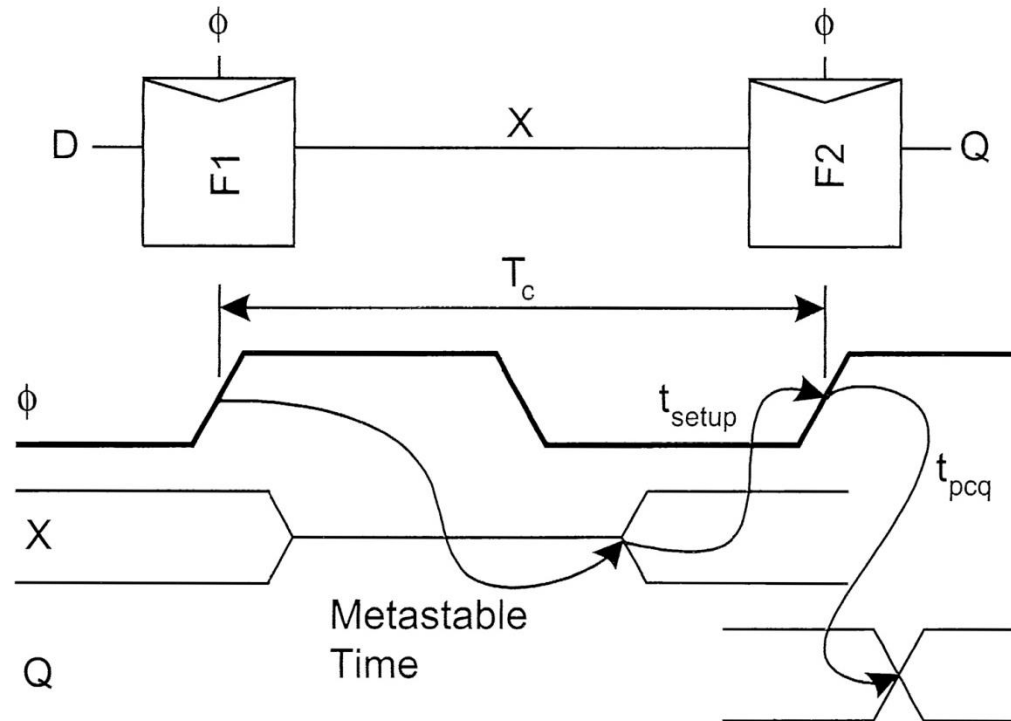
# A Simple Synchronizer


- Synchronizer
  - Data should be stable during the aperture =  $t_{\text{setup}} + t_{\text{hold}}$  around clock rising edge.
  - One clock cycle latency



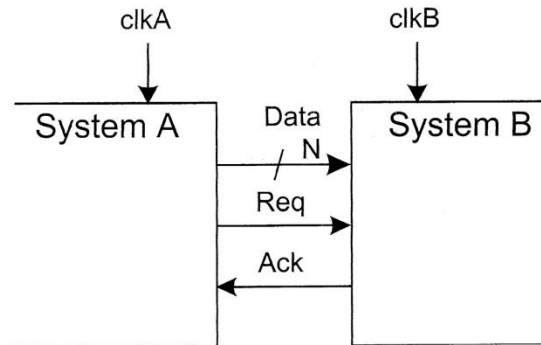
# Communication of Async. Clock Domains

6- 66


- Communication between asynchronous systems
  - Not share a common clock



 - 4-phase and 2-phase handshake protocols
  - Request and acknowledge




(a) Four-phase **Level sensitive**

 


(b) Two-phase **Edge trigger**
 
# Arbiters


- The arbiter is used to determine which of two inputs arrived first
  - If the time spacing exceeds aperture, first input will be acknowledged
  - If time spacing is too small, the choice is arbitrary



(a)

 

(b)

 

(c)