

An aerial photograph of a city grid with various colored overlays. The colors include purple, green, red, and blue, highlighting different areas or zones within the urban layout.

# CHAPTER 7


# Datapath Subsystems

# Outline

- 1. Addition/Subtraction**
2. One/Zero Detectors
3. Comparators
4. Counters
5. Shifters
6. Multiplication
 
# Digital Device Components

- A simple processor illustrates many of the basic components used in any digital system:



- Datapath: The core -- all other components are support units that store either the results of the datapath or determine what happens in the next cycle.

# Digital Device Components


7- 4

- Memory:
  - A broad range of classes exist determined by the way data is accessed:
    - Read-Only vs. Read-Write
    - Sequential vs. Random access
    - Single-ported vs. Multi-ported access
  - Or by their data retention characteristics:
    - Dynamic vs. Static
  - Stay tuned for a more extensive treatment of memories.
- Control:
  - A FSM (sequential circuit) implemented using random logic, PLAs or memories.
- Interconnect and Input-Output:
  - Parasitic resistance, capacitance and inductance affects performance of wires both on and off the chip.
  - Growing die size increases the length of the on-chip interconnect, increasing the value of the parasitic.
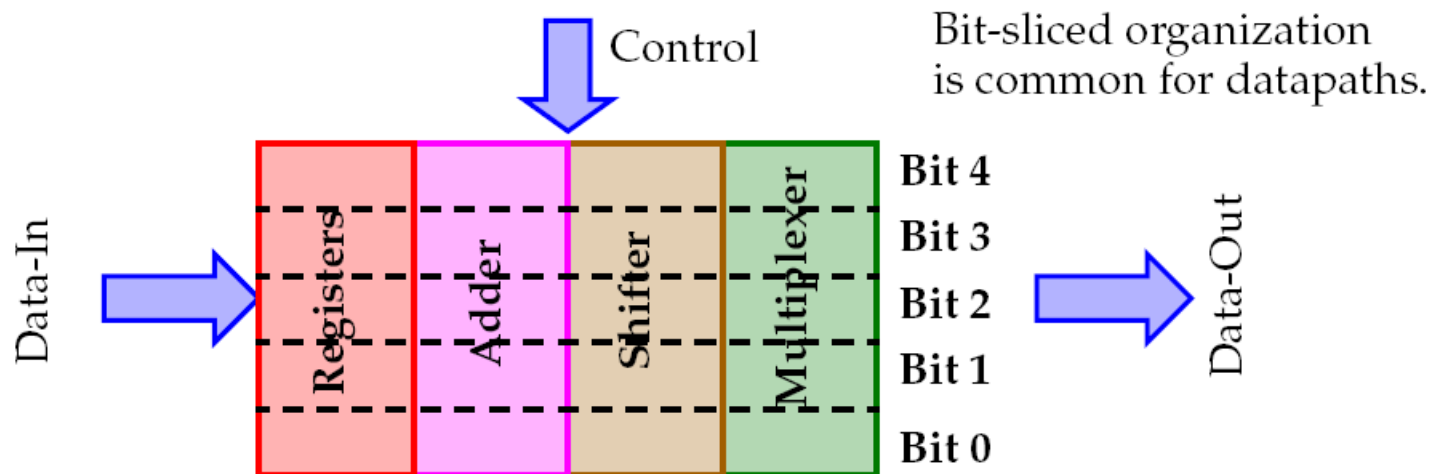
# Digital Device Components

7- 5

- Datapath elements include adder, multiplier, shifter, etc.
  - The speed of these elements often dominates the overall system performance so optimization techniques are important.
  - However, as we will see, the task is non-trivial since there are multiple equivalent logic and circuit topologies to choose from, each with adv./disadv. in terms of speed, power and area.
  - Also, optimizations focused at one design level, e.g., sizing transistors, leads to inferior designs.




# Single-Bit Addition

## Half Adder

$$S = A \oplus B$$

$$C_{out} = A \bullet B$$

 


A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

## Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

$$= AB + BC + AC$$

 

A	B	C	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# PGK

- For a full adder, define what happens to carries
  - Generate:  $C_{out} = 1$  independent of  $C$ 
    - $G = A \cdot B$
  - Propagate:  $C_{out} = C$ 
    - $P = A \oplus B$
  - Kill:  $C_{out} = 0$  independent of  $C$ 
    - $K = \sim A \cdot \sim B$

$A$	$B$	$C$	$G$	$P$	$K$	$C_{out}$	$S$
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1


# Full Adder Design I

- Brute force implementation from eqns

$$S = A \oplus B \oplus C \quad (16 \text{ transistors})$$

$$C_{\text{out}} = \text{MAJ}(A, B, C) \quad (10 \text{ transistors})$$
 
$$\text{INV} \quad (6 \text{ transistors})$$







# Full Adder Design II

- Factor S in terms of  $C_{out}$  :  $S = ABC + (A + B + C)(\sim C_{out})$
- Critical path is usually C to  $C_{out}$  in ripple adder


– 28 transistors

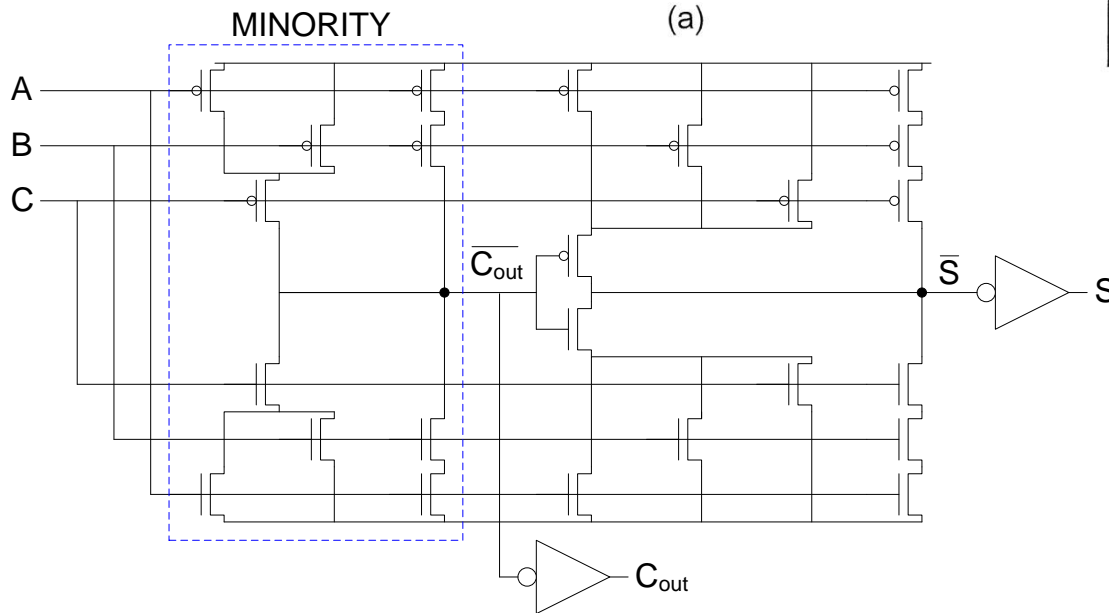 
 
# Full Adder Design II




7- 10

- Feed carry-in (C) to the inner inputs.
- Use minimum size at summing (S) logic for minimizing branching effort on the critical path.
- Asymmetric gate to reduce the logical effort from  $C \rightarrow \sim C_{out}$
- Eliminate output inverter: 24 transistors


 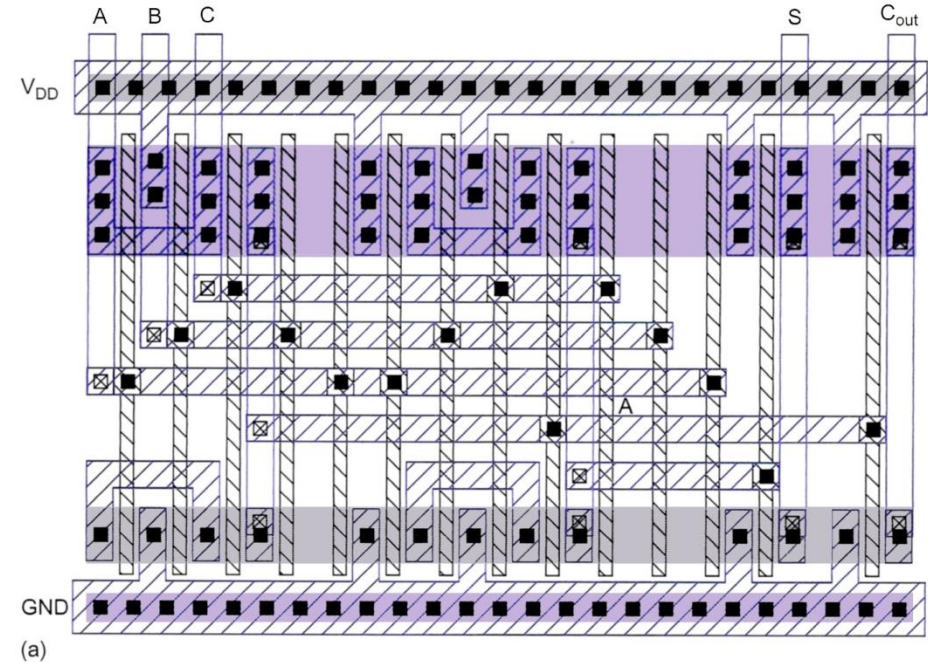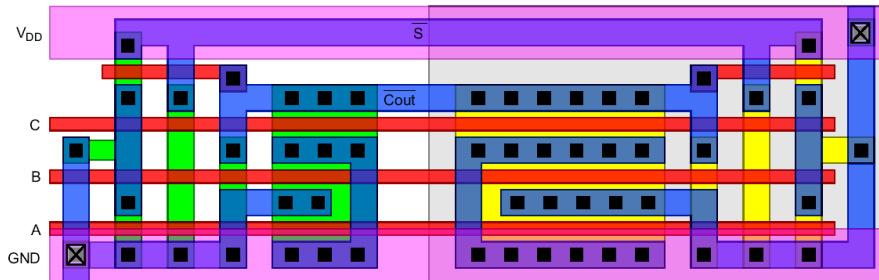
# Layout



- Standard cell layout
  - Fixed pMOS (nMOS) location & pitch
- Datapath layout
  - Smaller bit-pitch (height) with wider MOS size


 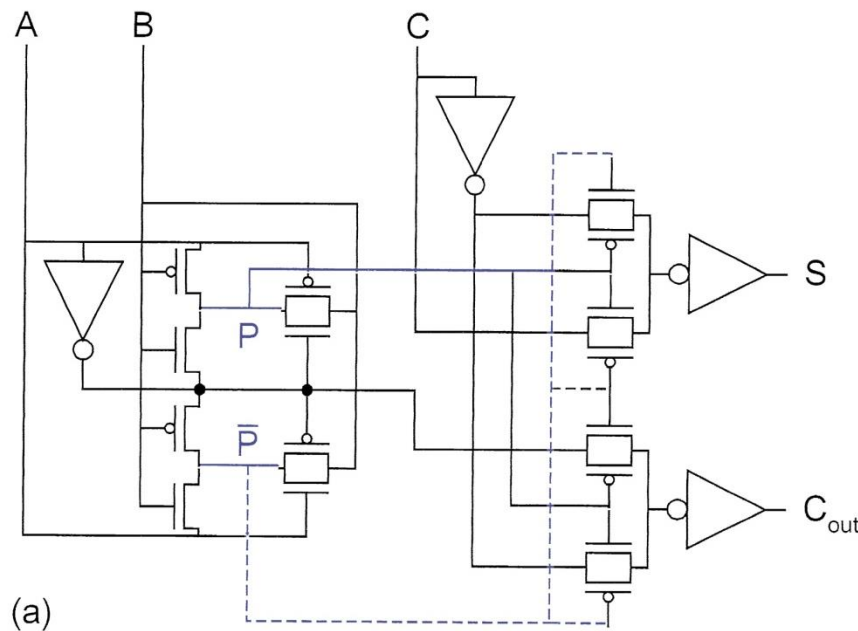
# Full Adder Design III

7- 12



- Transmission gate full adder
  - 24 Transistors, providing buffered outputs of proper polarity with equal delay.


 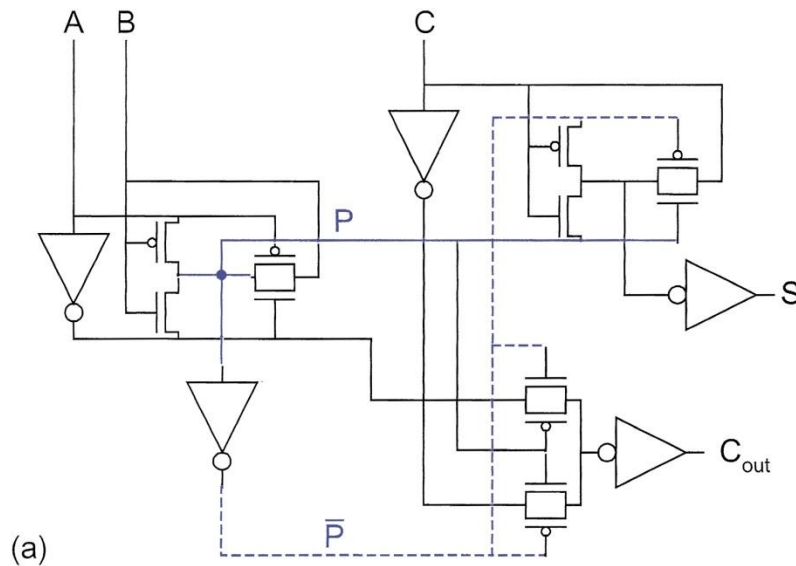
# Full Adder Design IV


7- 13

- Zhuang full adder
  - 22 Transistors, extra inverter delay by computing  $\sim P$  from  $P$ .



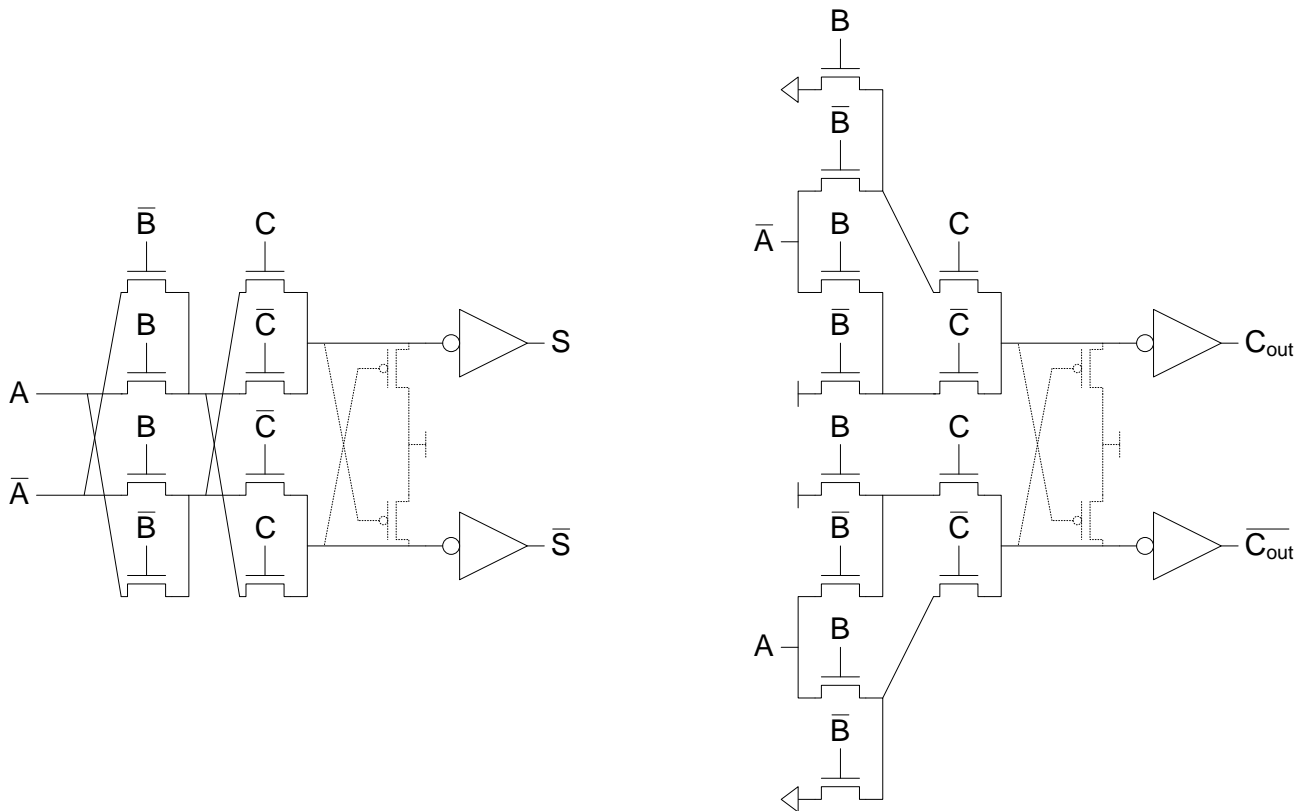
# Full Adder Design V

- Complementary Pass Transistor Logic (CPL)
  - Compared to I : x2 faster, 30% lower power.
  - Compared to II: Slightly faster, but more area





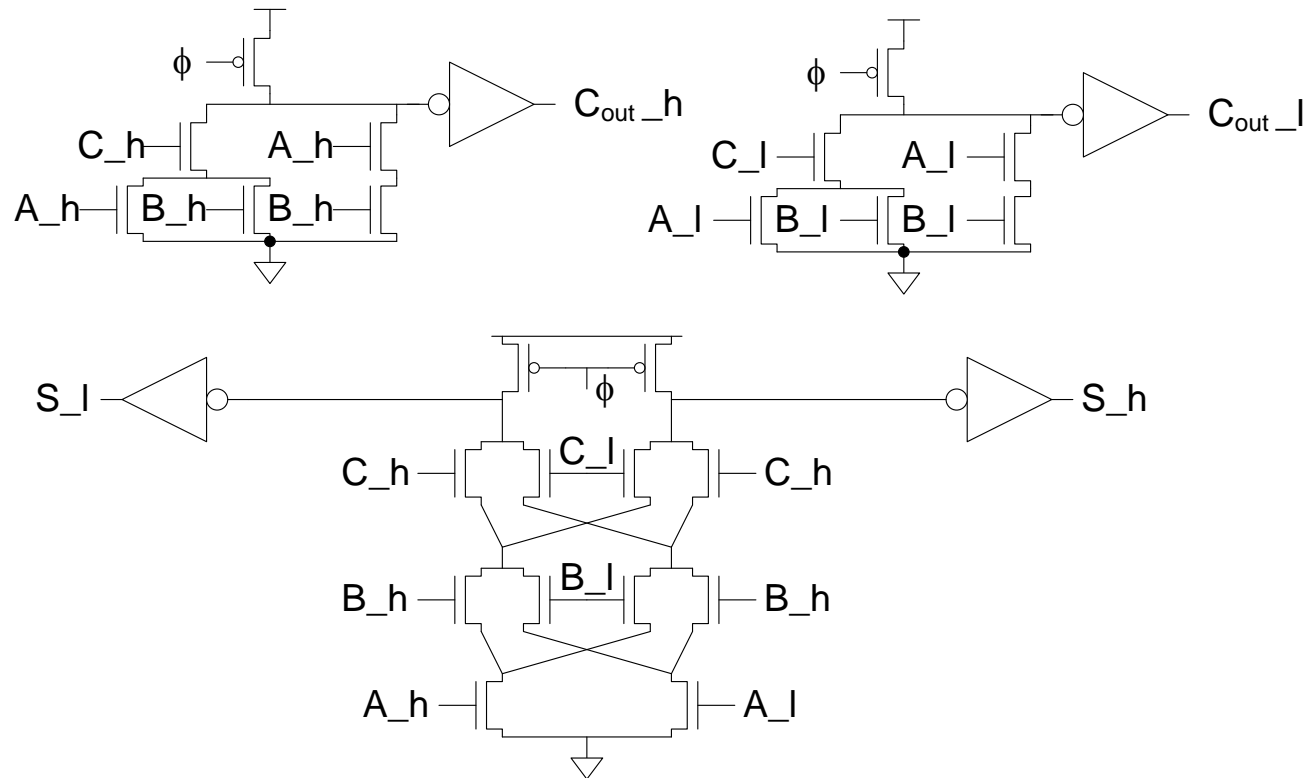
# Full Adder Design VI

- Footless dual-rail domino
- Very fast, but large and power hungry
- Used in very fast multipliers


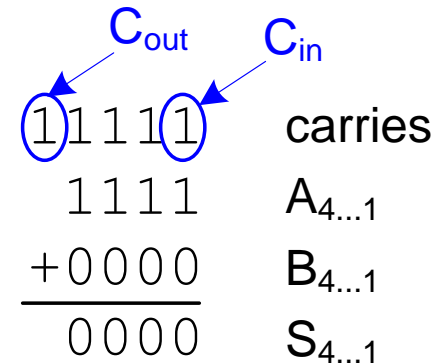  
# Carry Propagate Adders


- N-bit adder called *carry-propagate adder* (CPA)
  - Each sum bit depends on all previous carries
  - How do we compute all these carries quickly?





 
# Carry-Ripple Adder

- Simplest design: cascade full adders
  - Critical path goes from  $C_{in}$  to  $C_{out}$  (minimize  $t_{C \rightarrow C_{out}}$ )
  - Design full adder to have fast carry delay


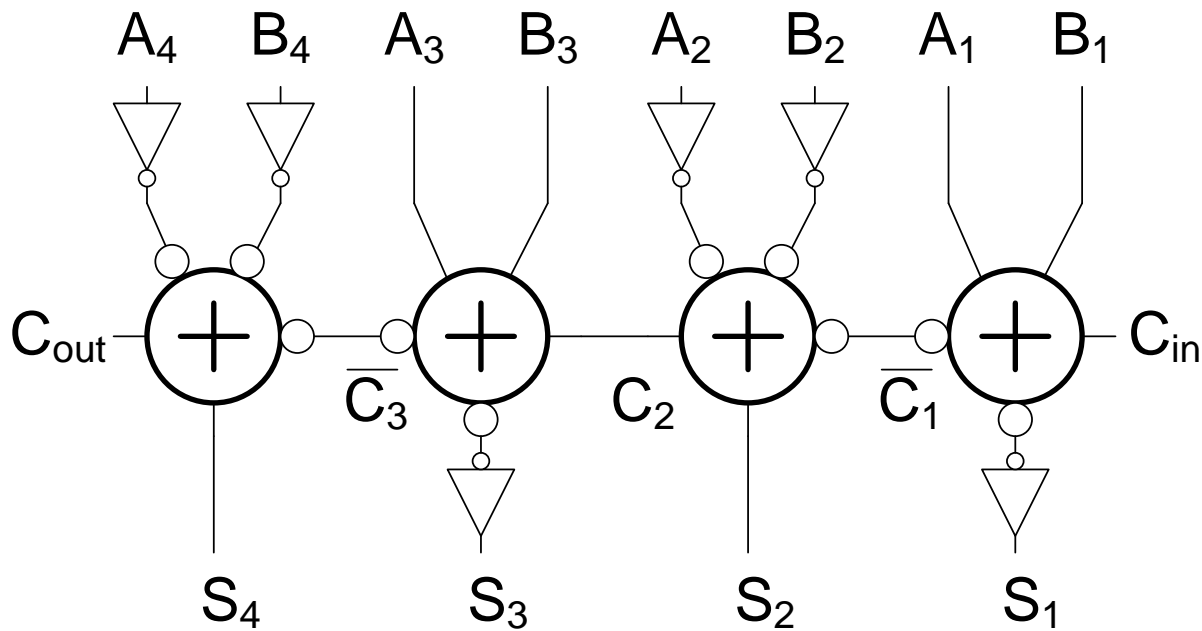
# Inversions

- Critical path passes through majority gate
  - Built from minority + inverter
  - Eliminate inverter and use inverting full adder



# Generate / Propagate

- Equations often factored into G and P
- Generate and propagate for groups spanning i:j

$$G_{i:j} = G_{i:k} + P_{i:k} \bullet G_{k-1:j}$$

$$P_{i:j} = P_{i:k} \bullet P_{k-1:j}$$

Valency-2 group PG Logic

- Base case

$$G_{i:i} \equiv G_i = A_i \bullet B_i$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$


$$G_{0:0} \equiv G_0 = C_{in}$$

$$P_{0:0} \equiv P_0 = 0$$

- Sum:

$$C_{i-1} = G_{i-1:0}, \quad S = P \oplus C, \quad S_i = P_i \oplus G_{i-1:0}$$

# PG Logic

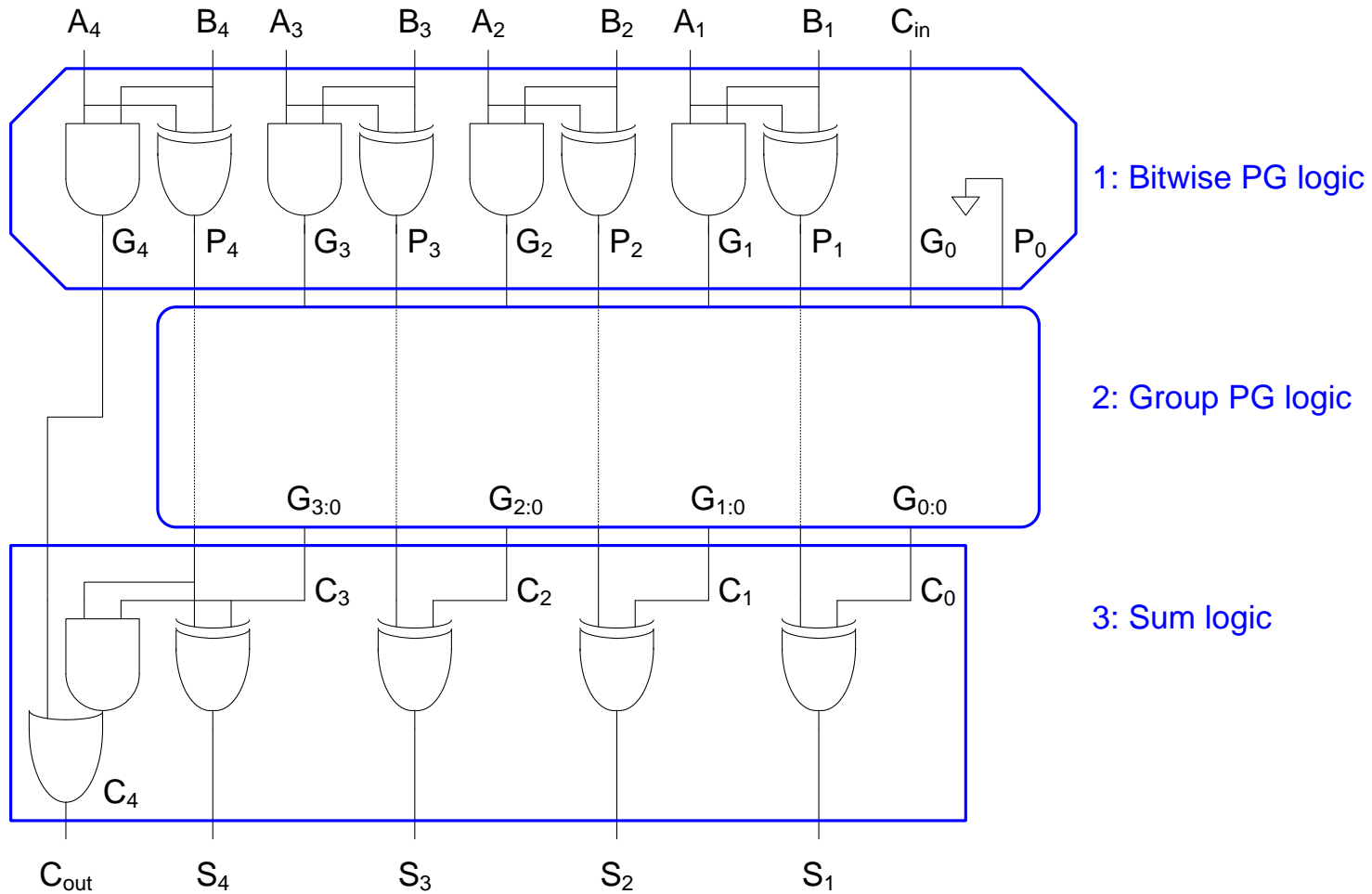


# Carry-Ripple Revisited

$$\begin{aligned}
 C_i &= A_i B_i + (A_i + B_i) C_{i-1} \\
 &= A_i B_i + (A_i \oplus B_i) C_{i-1} \\
 &= G_i + P_i C_{i-1}
 \end{aligned}$$

$$G_{i:0} = G_i + P_i \bullet G_{i-1:0}$$

$$C_{out} = G_{i:0}$$

$$S_i = P_i \oplus G_{i-1:0}$$

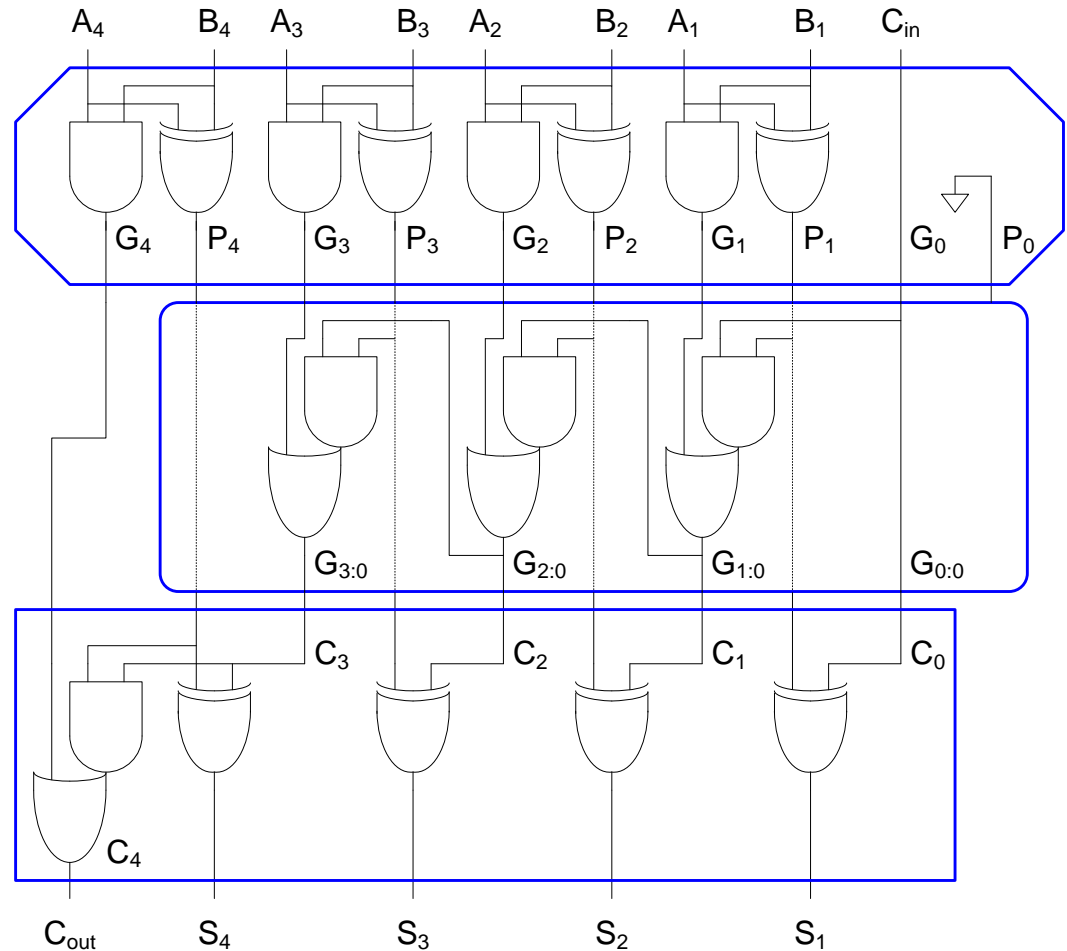

# Carry-Ripple PG Diagram


For N-bit adder

$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{xor}$$

$t_{pg}$  : delay of 1-bit propagate  
/generate gate

$t_{AO}$  : delay of AND-OR gate  
in grey cell



$t_{xor}$  : delay of final sum XOR

 

# PG Diagram Notation



Group generate  
& propagate  
(AND-OR & AND)

Black cell

  



Group generate  
only  
(AND-OR)

Gray cell

  


Minimize the  
load on critical  
path

Buffer

  


# Manchester Carry Chain Adder



## Majority gate

 

## Pass Transistor Logic

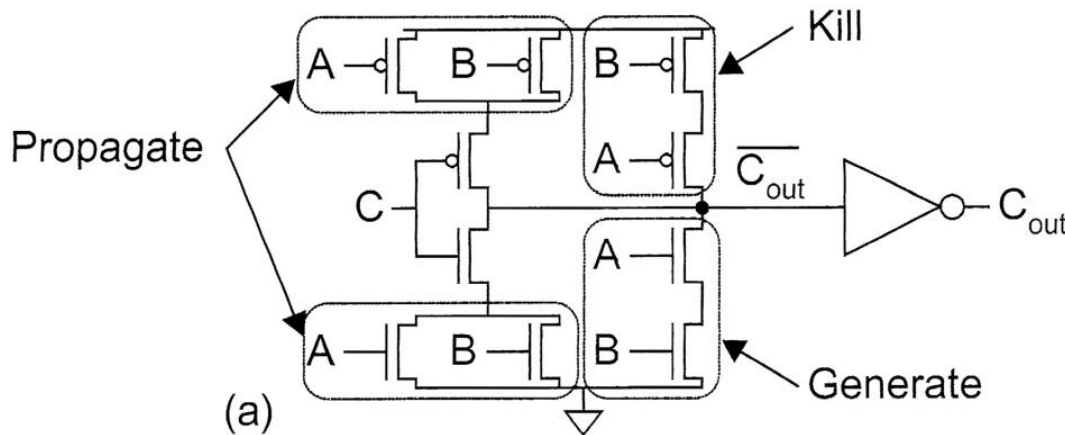

Static

  

Dynamic



# Manchester Carry Chain




- Valency-4 group generate

$$C_0 = G_{0:0} = C_0$$

$$C_1 = G_{1:0} = G_1 + P_1 C_0$$

$$C_2 = G_{2:0} = G_2 + P_2 (G_1 + P_1 C_0)$$

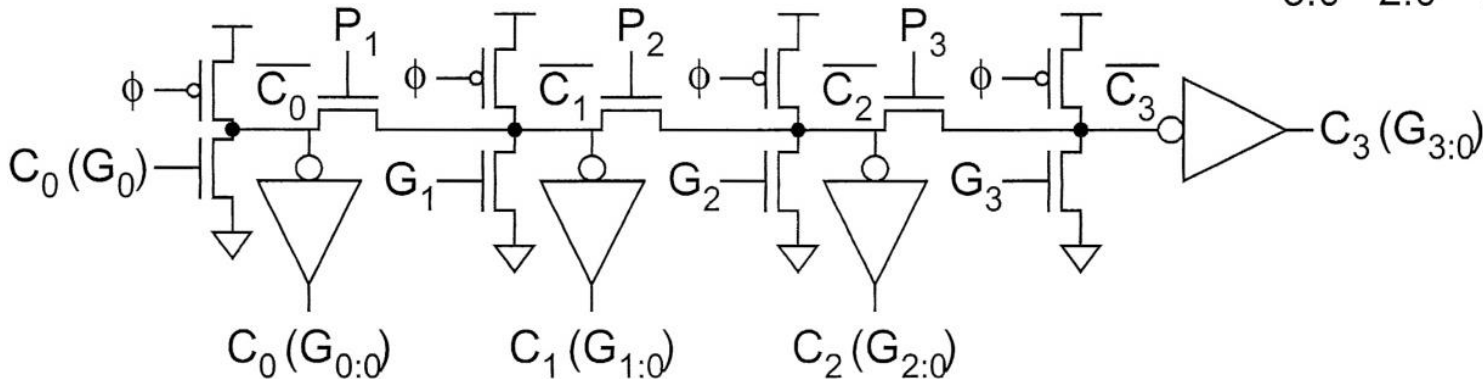 
 
$$C_3 = G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0))$$


 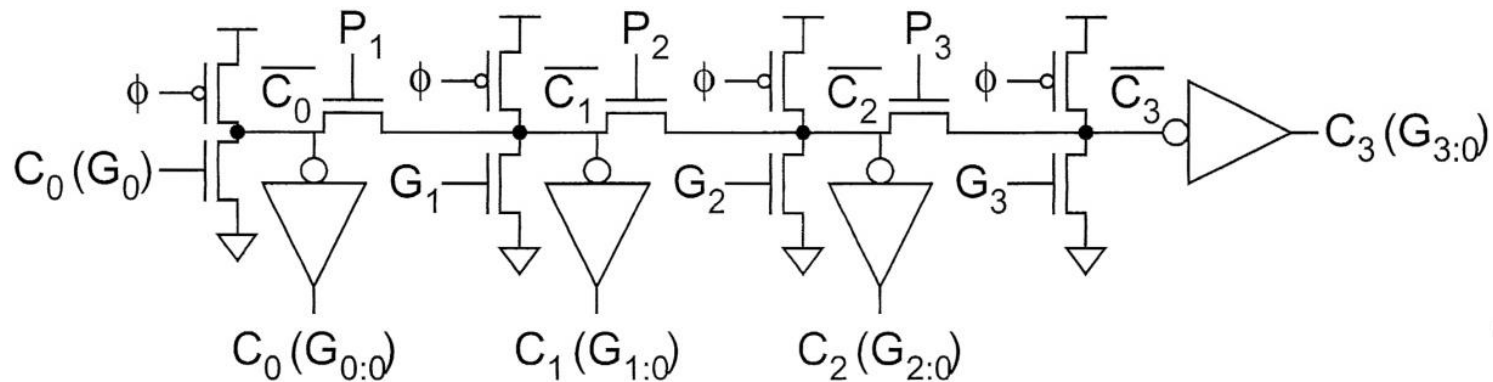
# Manchester Carry Chain - Domino

7- 26


- Equivalence of Manchester carry chain and multiple-output domino gate


 
# Manchester Carry Chain Adder

7- 27

- Valency-4 stages. Similar to carry-ripple adder with  $N/3$  stages




# Carry-Skip Adder

- Carry-ripple is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
  - Decision based on n-bit propagate signal

$$G_{16:0} = G_{16:13} + P_{16:13} \cdot G_{12:0}$$
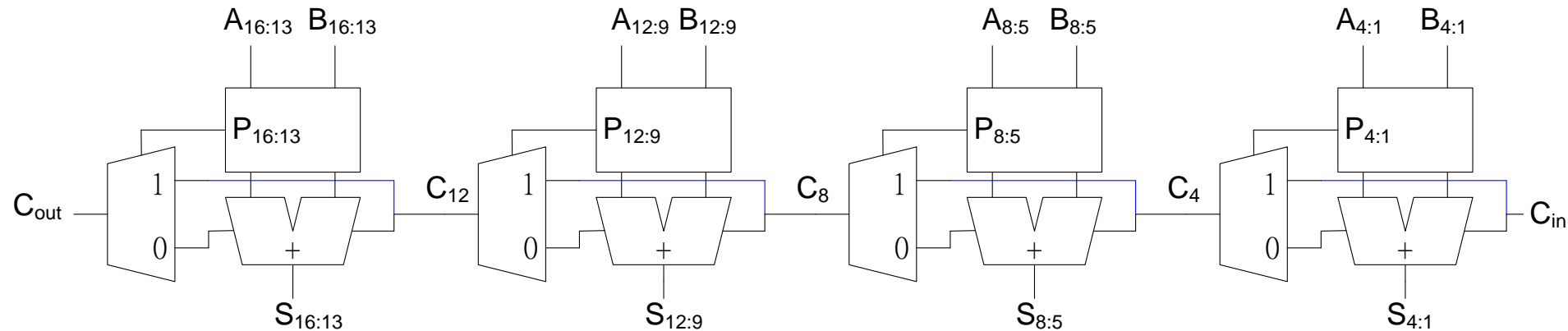
$$G_{8:0} = G_{8:5} + P_{8:5} \cdot G_{4:0}$$




$$G_{12:0} = G_{12:9} + P_{12:9} \cdot G_{8:0}$$

$$G_{4:0} = G_{4:1} + P_{4:1} \cdot G_{0:0}$$

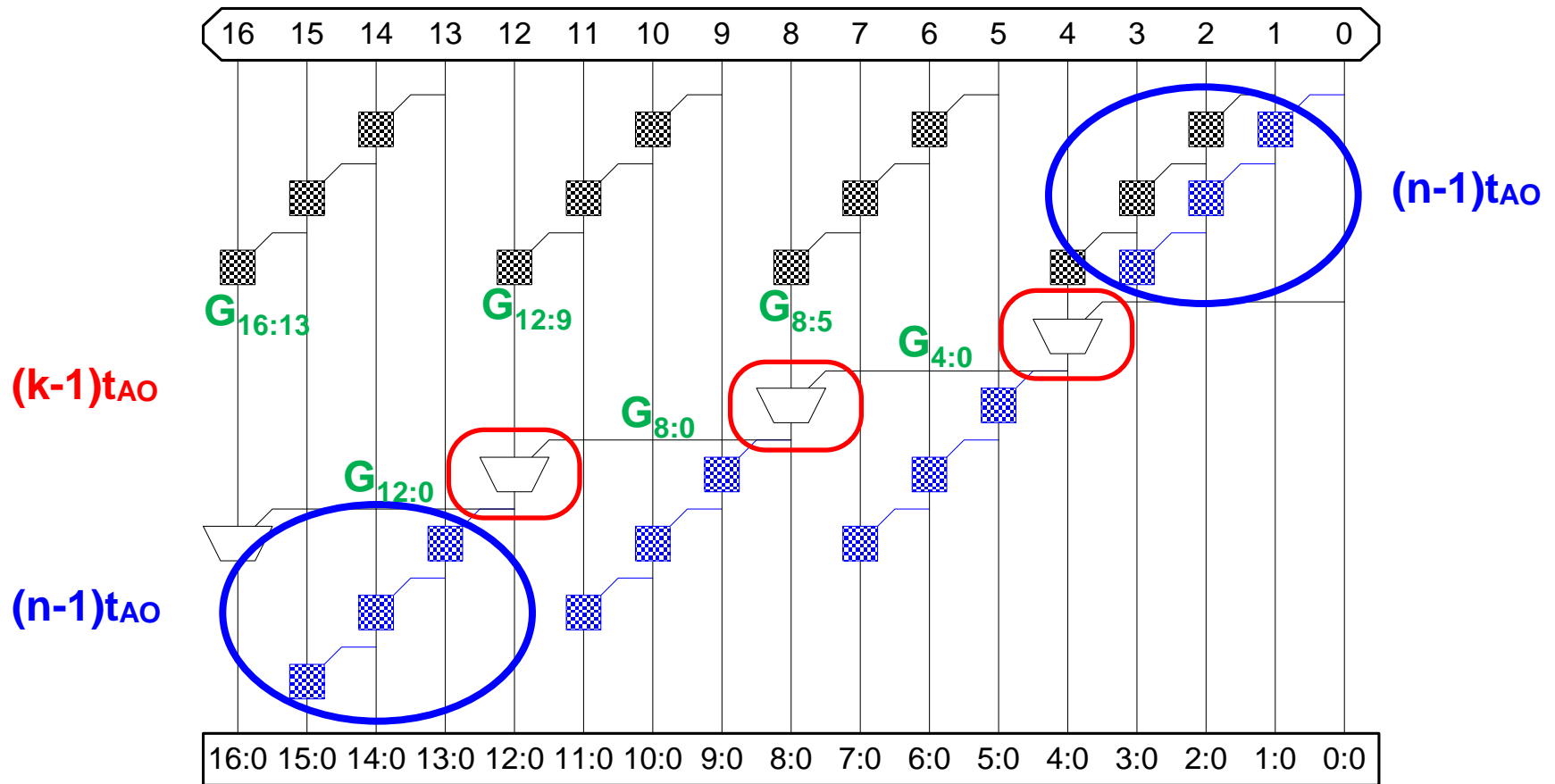
# Carry-Skip PG Diagram

For  $k$   $n$ -bit groups ( $N = nk$ )  $t_{\text{skip}} = t_{pg} + [2(n-1) + (k-1)]t_{AO} + t_{\text{xor}}$



 
# Variable Group Size

Delay grows as  $O(\sqrt{N})$  : [2,3,4,4,3] saves 2 levels of logic compared to [4,4,4,4], shorter group at B/E, longer group at middle.



# Carry-Skip Adder Manchester Stage

7- 31

 


# Carry-Lookahead Adder

- Carry-lookahead adder computes  $G_{i:0}$  for many bits in parallel.
- Uses higher-valency cells with more than two inputs.

$$G_{16:0} = G_{16:13} + P_{16:13} \cdot G_{12:0}$$
 
$$G_{8:0} = G_{8:5} + P_{8:5} \cdot G_{4:0}$$




$$G_{12:0} = G_{12:9} + P_{12:9} \cdot G_{8:0}$$

$$G_{4:0} = G_{4:1} + P_{4:1} \cdot G_{0:0}$$




 
# CLA PG Diagram

For k n-bit groups ( $N = nk$ )  $t_{cla} = t_{pg} + t_{pg(n)} + [(n-1) + (k-1)]t_{AO} + t_{xor}$




# Higher-Valency Cells

*Delay :  $t_{pg(n)}$*

  


# CLA PG Diagram: Manchester

 
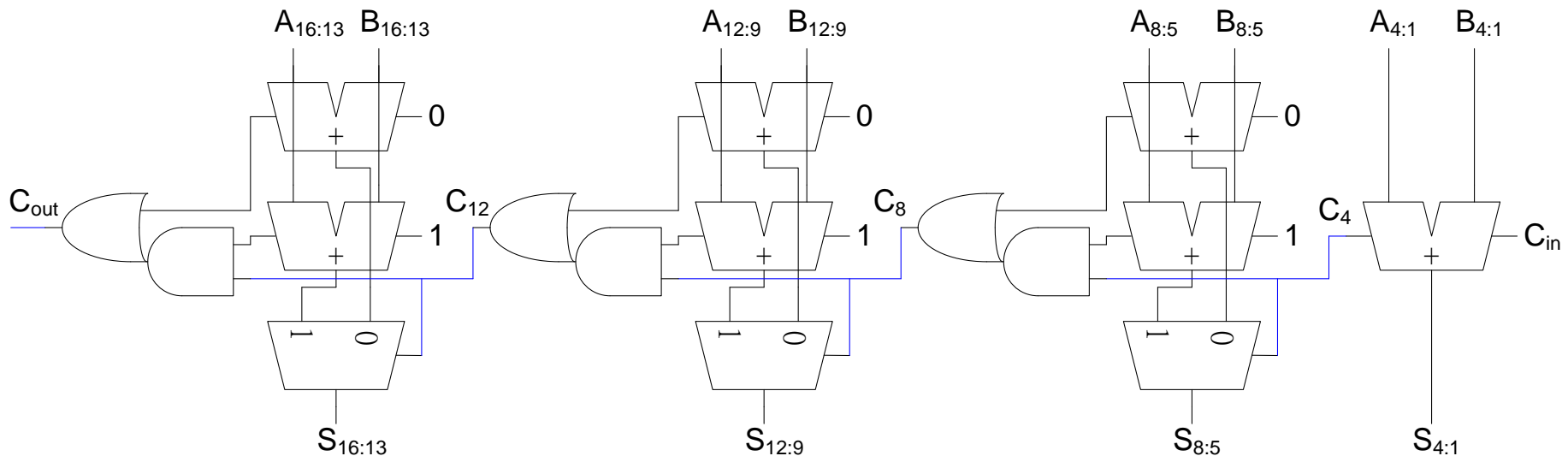
# Carry-Select Adder

- Trick for critical paths dependent on late input X
  - Precompute two possible outputs for  $X = 0, 1$
  - Select proper output when  $X$  arrives
- Carry-select adder precomputes n-bit sum


$$t_{\text{select}} = t_{pg} + [n + (k - 2)]t_{AO} + t_{\text{mux}}$$


 
# Carry-Increment Adder


- Factor initial PG and final XOR out of carry-select

$$t_{\text{increment}} = t_{pg} + \left[ (n-1) + (k-1) \right] t_{AO} + t_{xor}$$


 
# Variable Group Size

- Also buffer noncritical signals
- Reduce branch effort




# Tree Adder

- If lookahead is good, lookahead across lookahead!
  - Recursive lookahead gives  $O(\log N)$  delay
- Many variations on tree adders






# Sklansky

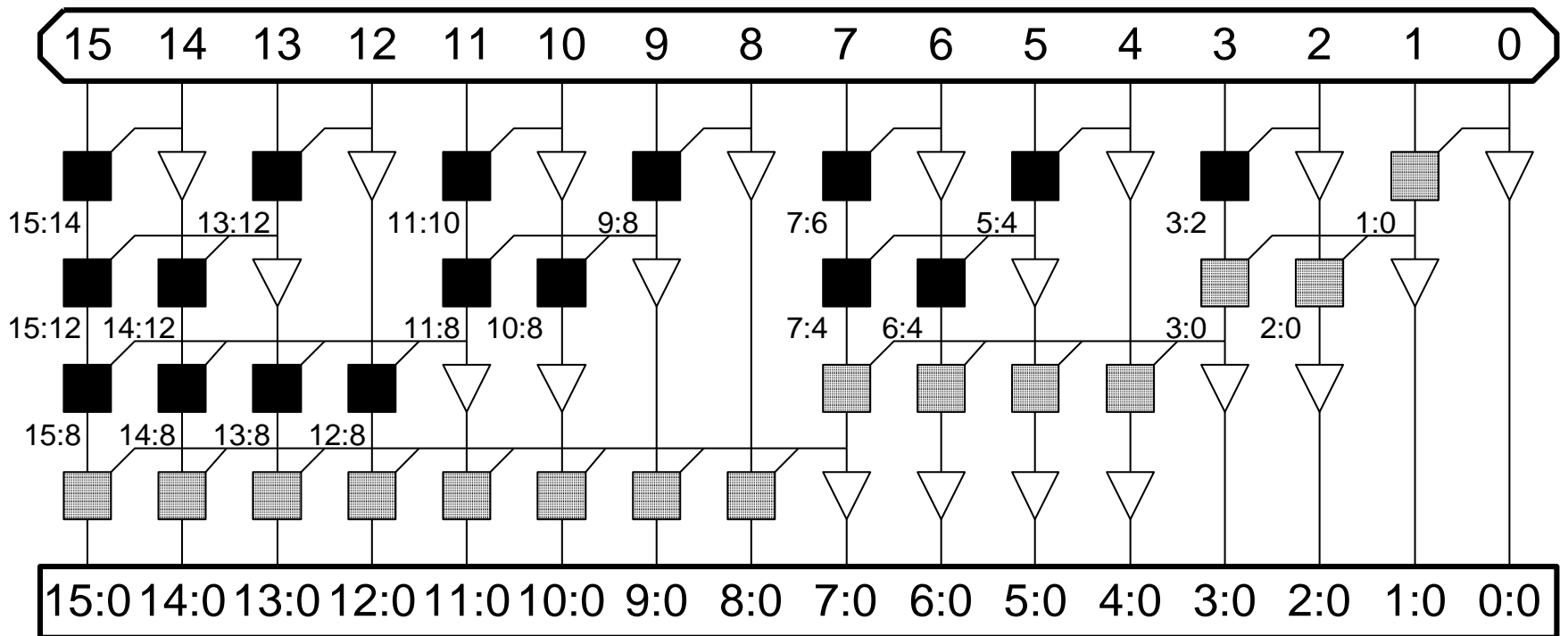


# Kogge-Stone

 


# Tree Adder Taxonomy

- Ideal N-bit tree adder would have
  - $L = \log_2 N$  logic levels
  - Fanout never exceeding 2
  - No more than one wiring track between levels
- Describe adder with 3-D taxonomy ( $l, f, t$ )
  - Logic levels:  $L + l$
  - Fanout:  $2^f + 1$
  - Wiring tracks:  $2^t$
- Known tree adders sit on plane defined by
$$l + f + t = L - 1$$


# Tree Adder Taxonomy

 


# Han-Carlson

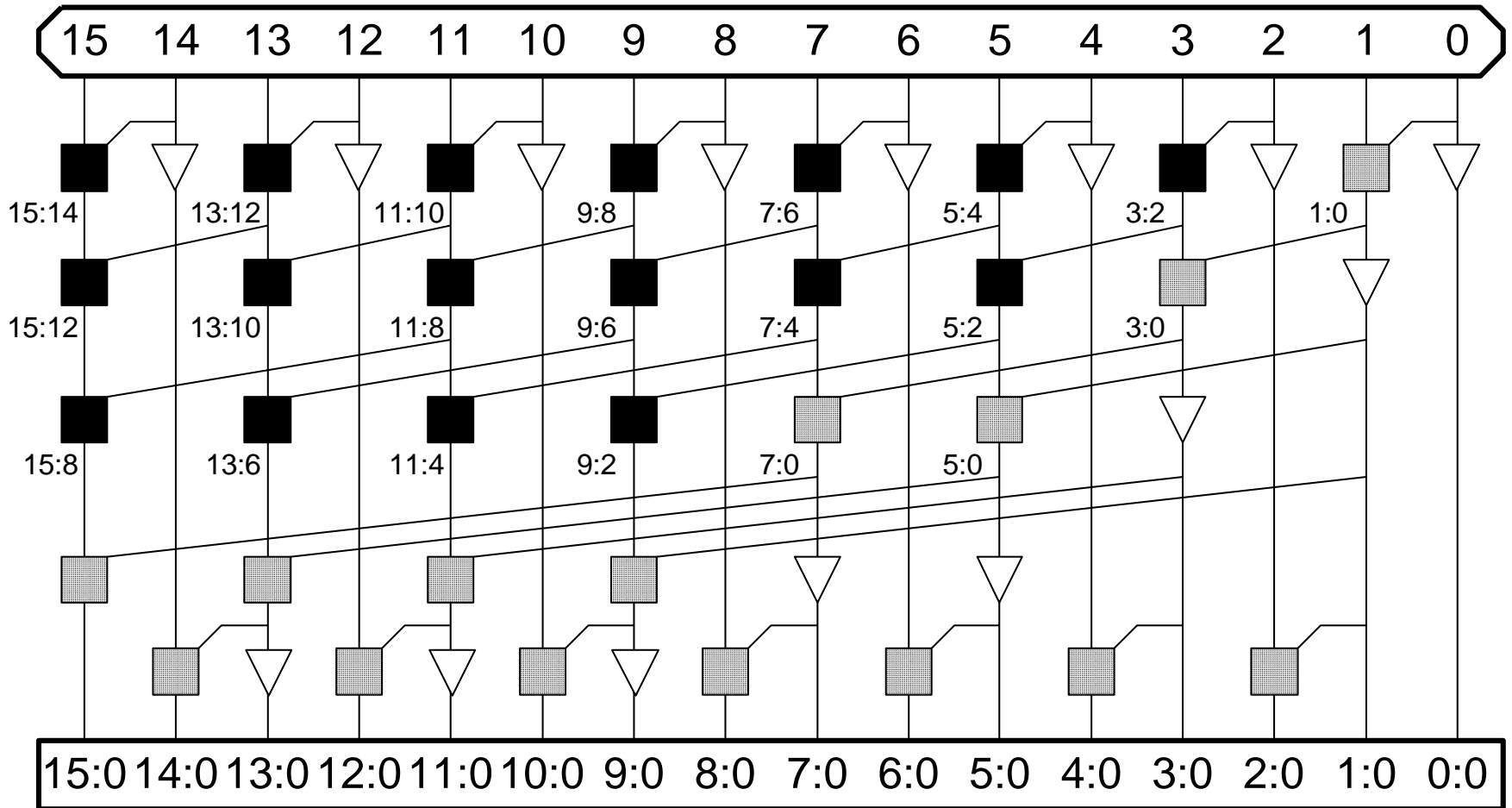


# Knowles [2, 1, 1, 1]

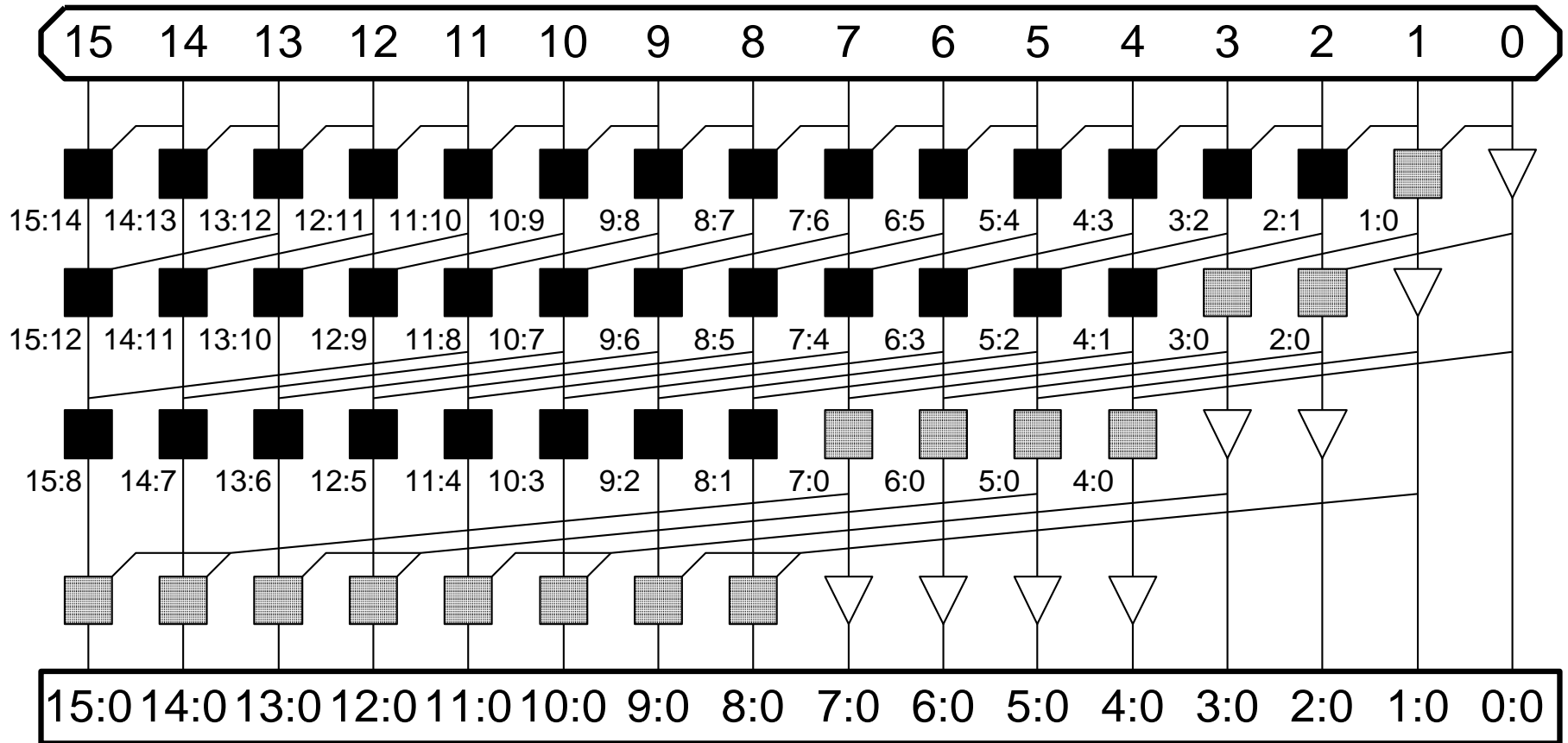

# Ladner-Fischer

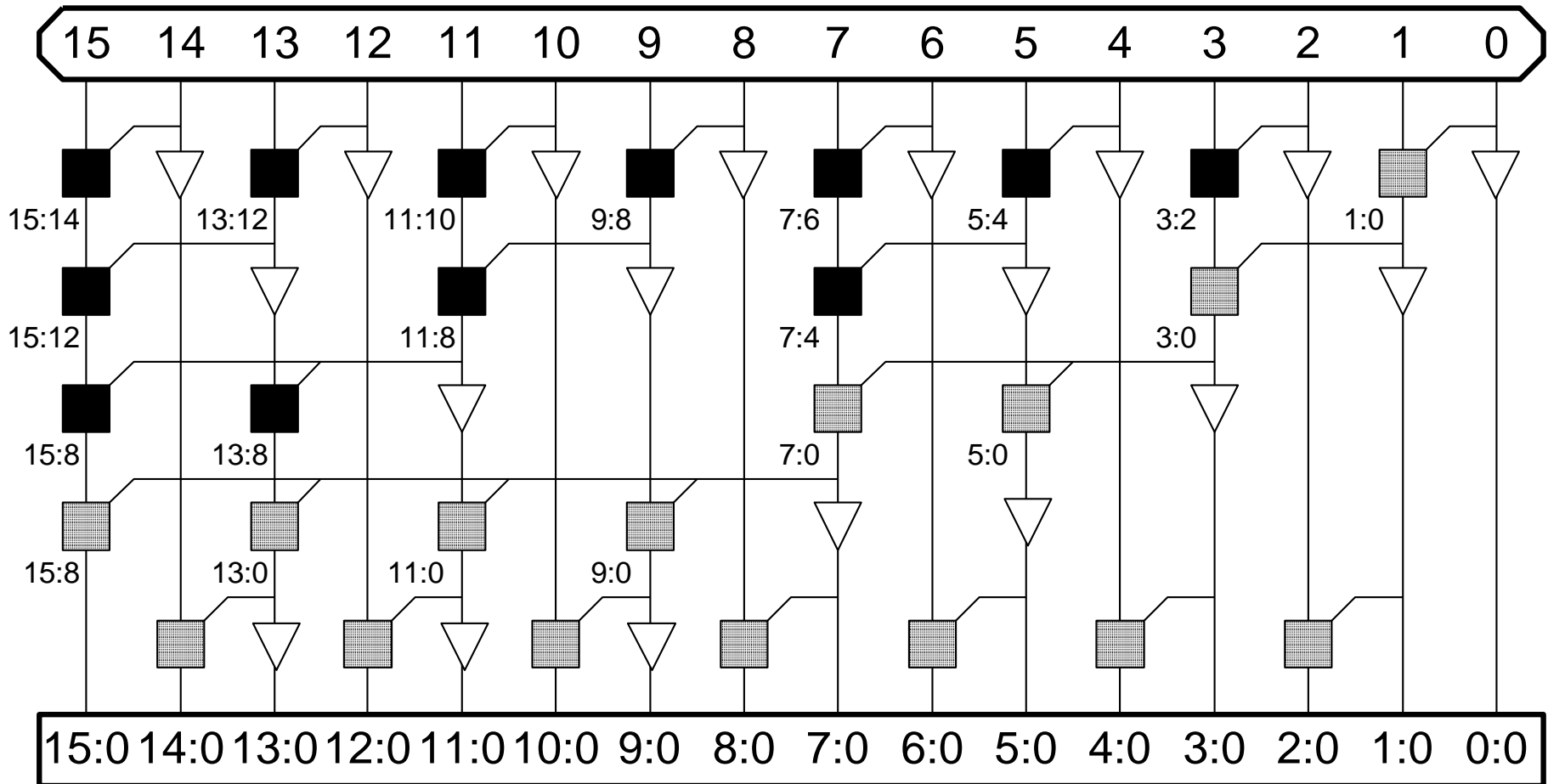

# Taxonomy Revisited

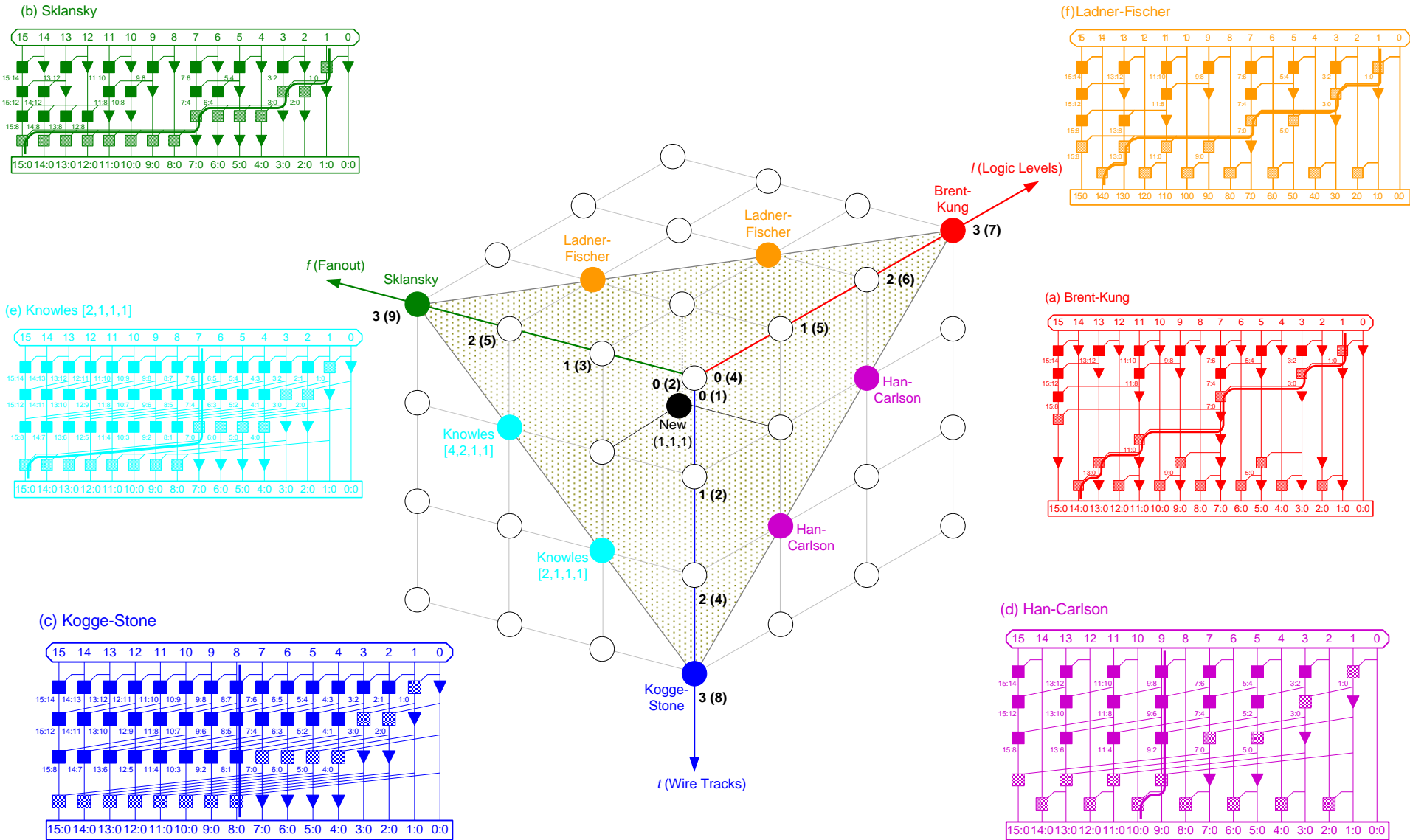




# Summary

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application.



Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N-1$	1	1	$N$
Carry-Skip $n=4$		$N/4 + 5$	2	1	$1.25N$
Carry-Inc. $n=4$		$N/4 + 2$	4	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L-1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$

# Summary

 




# Subtraction

$$A - B = A + \overline{B} + 1$$

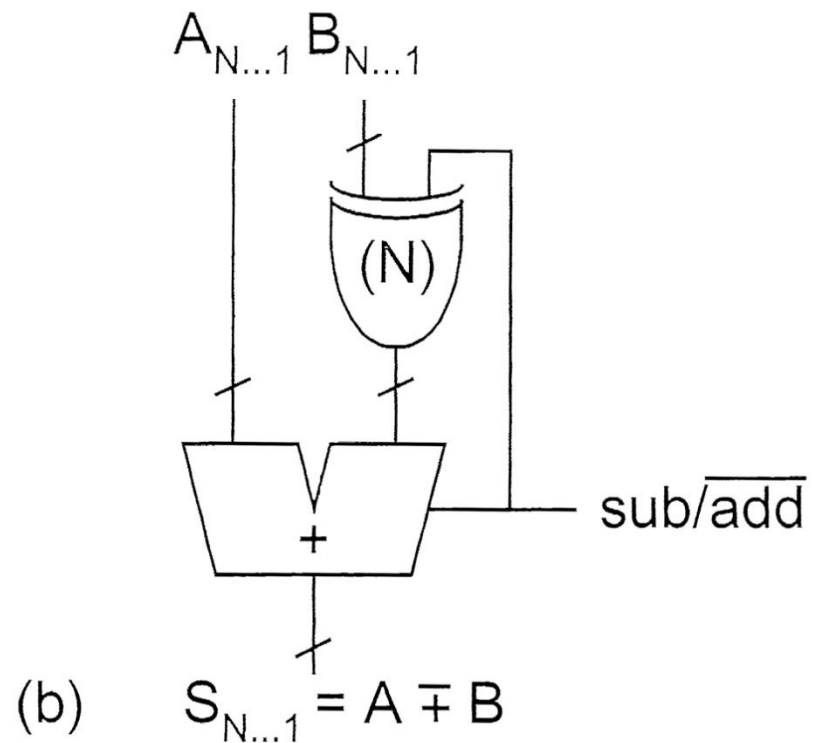 
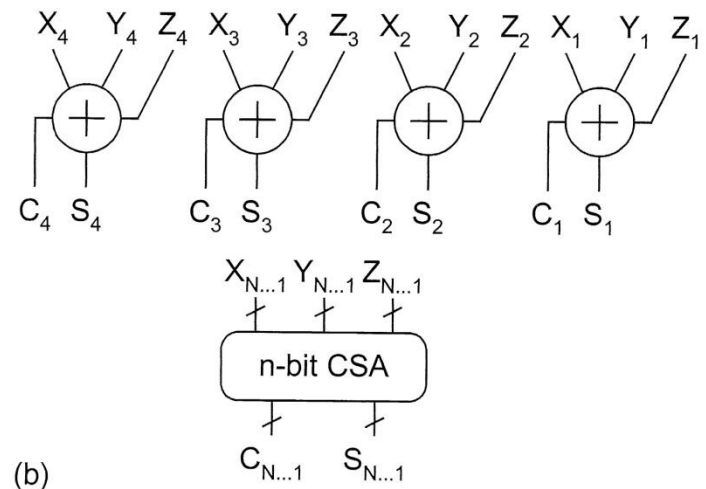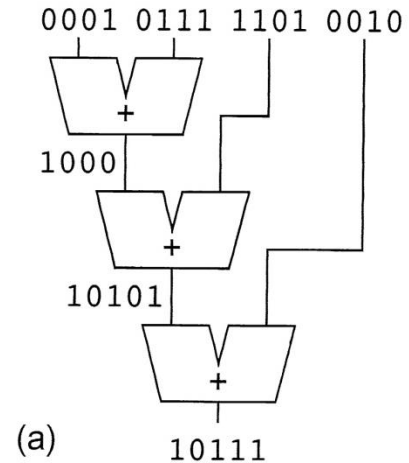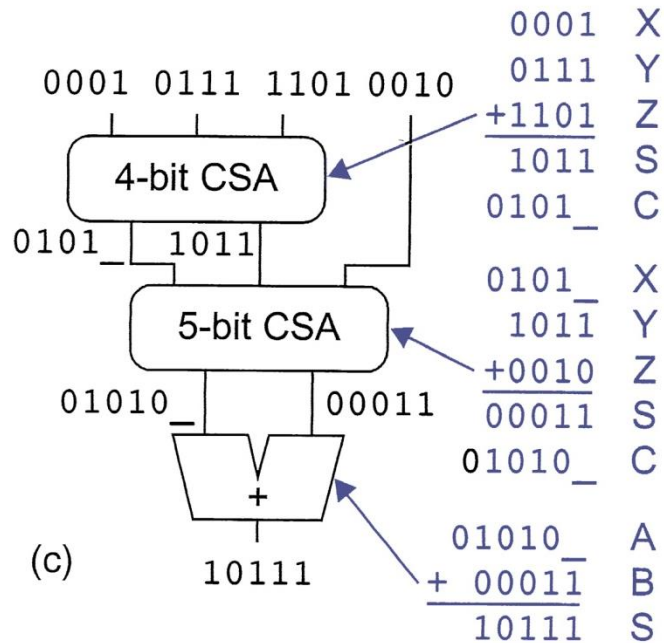
# Multiple-Input Addition

- Carry-Save Adder (CSA)
  - $k$   $N$ -bit words can be summed with  $k-2$  CSA and 1 CPA.






# Outline


1. Addition/Subtraction
- 2. One/Zero Detectors**
3. Comparators
4. Counters
5. Shifters
6. Multiplication
   
# 1's & 0's Detectors

- 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)



Mimic the adder delay

 

"wired-OR"

# Outline

1. Addition/Subtraction
2. One/Zero Detectors
- 3. Comparators**
4. Counters
5. Shifters
6. Multiplication


# Comparators

- 0's detector:  $A = 00\dots000$
- 1's detector:  $A = 11\dots111$
- Equality comparator:  $A = B$
- Magnitude comparator:  $A < B$



 
# Equality Comparator

- Check if each bit is equal (XNOR, aka equality gate)
- 1's detect on bitwise equality


 
# Magnitude Comparator

- Compute  $B-A$  and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



# Signed vs. Unsigned

- For signed numbers, comparison is harder
  - C: carry out
  - Z: zero (all bits of A-B are 0)
  - N: negative (MSB of result)
  - V: overflow (inputs had different signs, output sign  $\neq$  B)


<b>Table 10.4</b> Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	$Z$	$Z$
$A \neq B$	$\bar{Z}$	$\bar{Z}$
$A < B$	$\overline{C + Z}$	$\overline{(N \oplus V) + Z}$
$A > B$	$\bar{C}$	$(N \oplus V)$
$A \leq B$	$C$	$\overline{(N \oplus V)}$
$A \geq B$	$\bar{C} + Z$	$(N \oplus V) + Z$

# Outline


1. Addition/Subtraction
2. One/Zero Detectors
3. Comparators
- 4. Counters**
5. Shifters
6. Multiplication

# Binary Counters


Asynchronous counter

 

Synchronous up/down counter

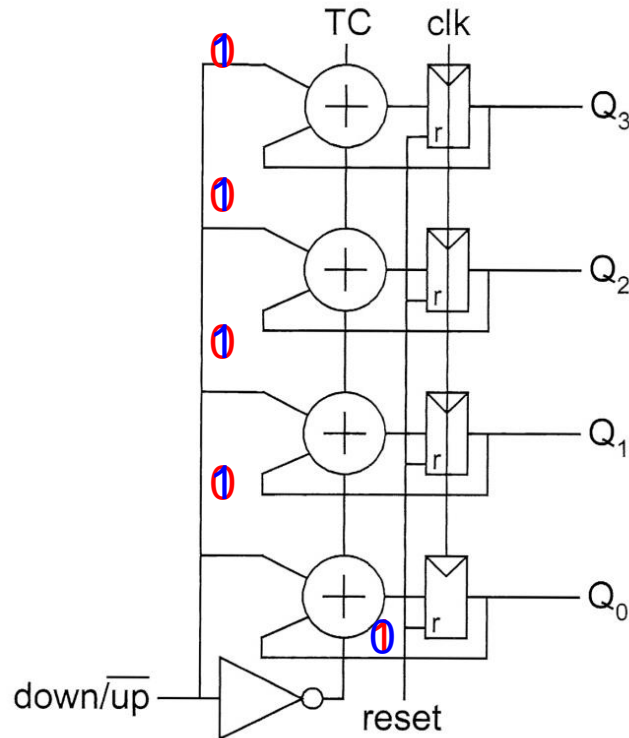


Synchronous incrementer

 

Half adder only

# Linear Feedback Shift Register

- The input to the LFSR register comes from the XOR of particular bits of the register : pseudo-random-bit-sequence (PRBS) generator

 

**Table 10.6** LFSR sequence

Cycle	Q [1]	Q [2]	Q [3] / Y
0	1	1	1
1	0	1	1
2	0	0	1
3	1	0	0
4	0	1	0
5	1	0	1
6	1	1	0
7	1	1	1
repeats forever			

**Table 10.7** Characteristic polynomials

N	Polynomial
3	$1 + x^2 + x^3$
4	$1 + x^3 + x^4$
5	$1 + x^3 + x^5$
6	$1 + x^5 + x^6$
7	$1 + x^6 + x^7$
8	$1 + x^1 + x^6 + x^7 + x^8$
9	$1 + x^5 + x^9$
15	$1 + x^{14} + x^{15}$
16	$1 + x^4 + x^{13} + x^{15} + x^{16}$
23	$1 + x^{18} + x^{23}$
24	$1 + x^{17} + x^{22} + x^{23} + x^{24}$
31	$1 + x^{28} + x^{31}$
32	$1 + x^{10} + x^{30} + x^{31} + x^{32}$


# Linear Feedback Shift Register

7- 63

## Example

Sketch an 8-bit linear-feedback shift register. How long is the pseudo-random bit sequence that it produces?

**Solution:** Figure 10.57 shows an 8-bit LFSR using the four taps after the first, sixth, seventh, and eighth bits, as given in Table 10.7. It produces a sequence of  $2^8 - 1 = 255$  bits before repeating.

 

**FIG 10.57** 8-bit LFSR

# Coding


- Error-detecting and error-correcting codes (ECC) by adding extra bits to the data

- Parity: check number of 1's is even  
single-bit error detecting

$$A_n = PARITY = A_0 \oplus A_1 \oplus A_2 \oplus \dots \oplus A_{n-1}$$

- ECC : single error correcting & double error detecting (SECDED)


 
4 data bits  $D_{0\sim3}$  and 3 check bits  $C_{0\sim2}$



$$C_0 = D_3 \oplus D_1 \oplus D_0$$

$$C_1 = D_3 \oplus D_2 \oplus D_0$$

$$C_2 = D_3 \oplus D_2 \oplus D_1$$

  



# Gray Code

- Consecutive numbers differ in only one bit
  - No glitch when applying to decoder
  - Power saving by reducing transition

## Binary $\rightarrow$ Gray

$$G_{N-1} = B_{N-1}$$

$$G_i = B_{i+1} \oplus B_i$$

## Gray $\rightarrow$ Binary

$$B_{N-1} = G_{N-1}$$

$$B_i = B_{i+1} \oplus G_i \quad N-1 > i \geq 0$$

Number	Binary	Gray Code
0	000	000
1	001	001
2	010	011
3	011	010
4	100	110
5	101	111
6	110	101
7	111	100

# Outline

1. Addition/Subtraction
2. One/Zero Detectors
3. Comparators
4. Counters
- 5. Shifters**
6. Multiplication


# Shifters

- Logical Shifter:
  - Shifts number left or right and fills with 0's
    - $1011 \text{ LSR } 1 = 0101$     $1011 \text{ LSL } 1 = 0110$
- Arithmetic Shifter:
  - Shifts number left or right. Rt shift sign extends, Lf shift fills with 0's
    - $1011 \text{ ASR } 1 = 1101$     $1011 \text{ ASL } 1 = 0110$
- Barrel Shifter (Rotator):
  - Shifts number left or right and fills with lost bits
    - $1011 \text{ ROR } 1 = 1101$     $1011 \text{ ROL } 1 = 0111$

# Combinational shifters

- Useful for arithmetic operations, bit field extraction, etc.
- Latch-based shift register can shift only one bit per clock cycle.
- A multiple-shift shifter requires additional connectivity.

# The Binary Shifter

 


# Barrel shifter

- Can perform n-bit shifts in a single cycle.
- Efficient layout.
- Does require transmission gates and long wires.
 
# Barrel shifter structure

Accepts  $2n$  data inputs and  $n$  control signals, producing  $n$  data outputs.




# Barrel shifter operation


- Selects arbitrary contiguous  $n$  bits out of  $2n$  input bits.
- Examples:
  - right shift: data into top, 0 into bottom;
  - left shift: 0 into top, data into bottom;
  - rotate: data into top and bottom.




# Barrel shifter cell

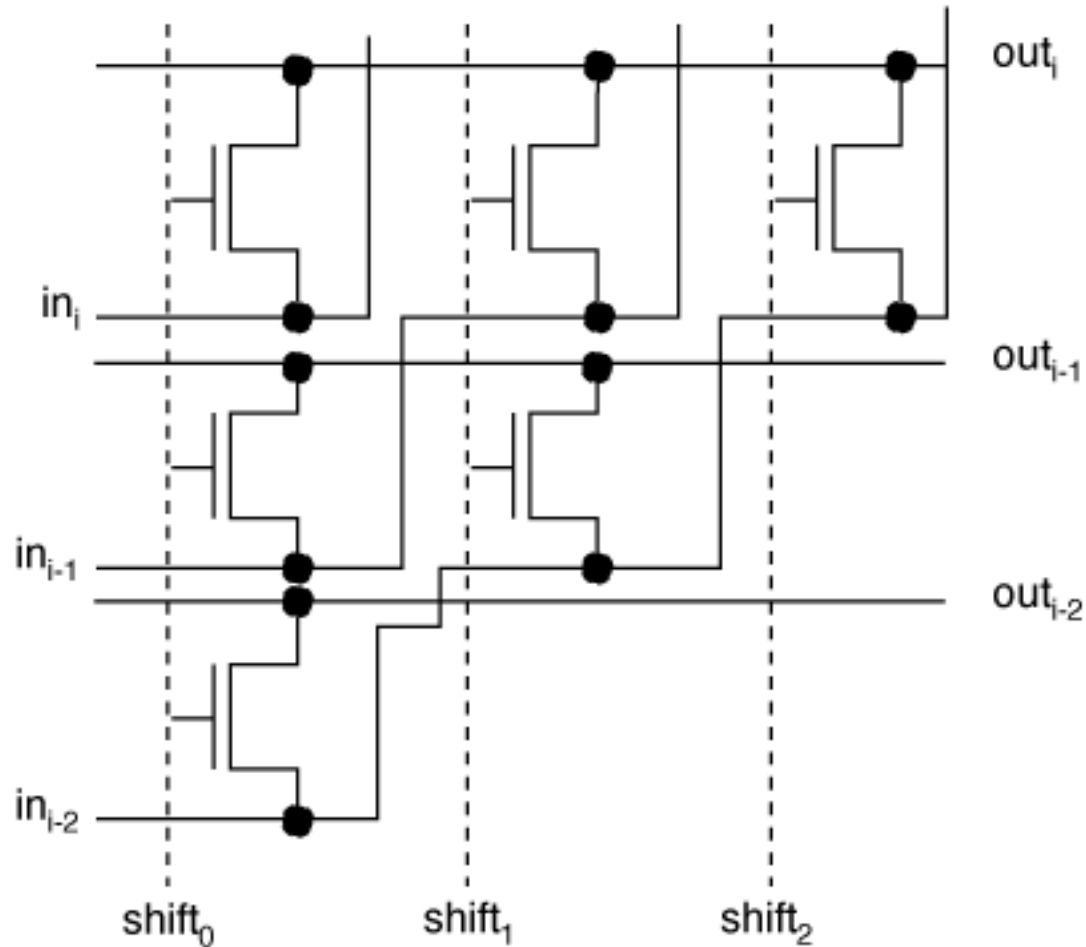

# Barrel shifter in action

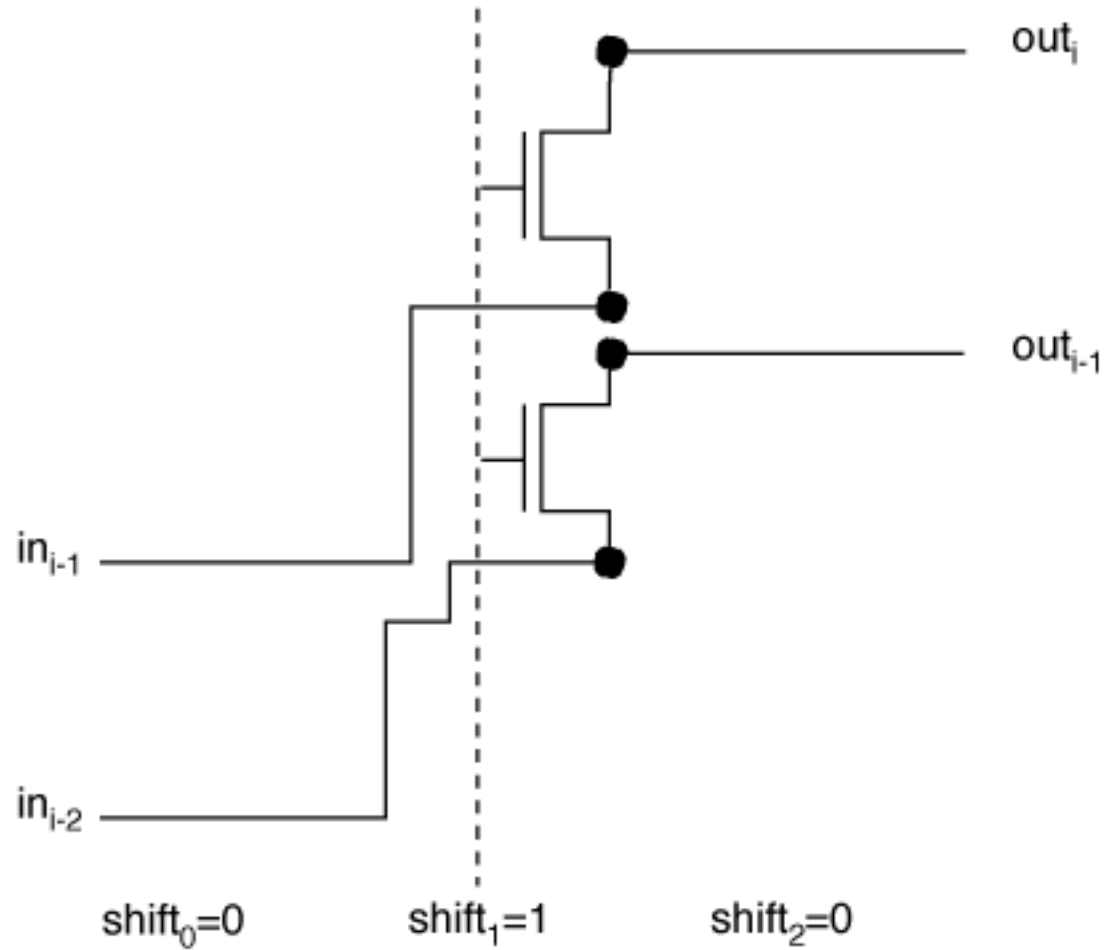

# The Barrel Shifter

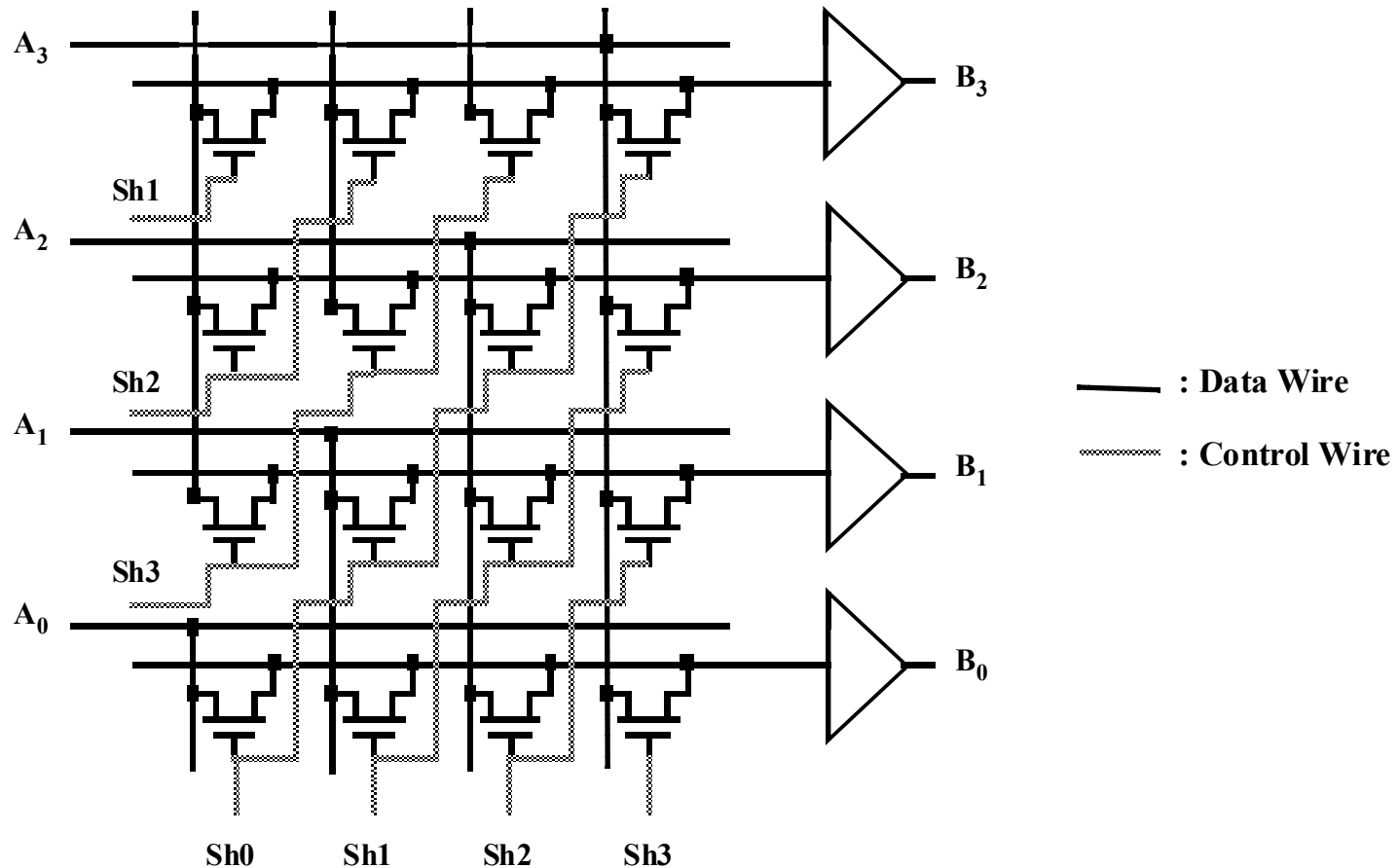


Area Dominated by Wiring

# Barrel shifter layout

- Two-dimensional array of  $2n$  vertical  $\times$   $n$  horizontal cells.
- Input data travels diagonally upward. Output wires travel horizontally.
- Control signals run vertically. Exactly one control signal is set to 1, turning on all transmission gates in that column.

# 4x4 barrel shifter

 


$$\text{Width}_{\text{barrel}} \sim 2 p_m M$$

# Analysis

- Large number of cells, but each one is small.
- Delay is large, considering long wires and transmission gates.
 
# Funnel Shifter

- A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
  - Shift by k bits ( $0 \leq k < N$ )



# Funnel Shifter Operation

- Computing  $N-k$  requires an adder

**Table 10.10** Funnel shifter operation

Shift Type	$B$	$C$	Offset
Logical Right	$0\dots 0$	$A_{N-1}\dots A_0$	$k$
Logical Left	$A_{N-1}\dots A_0$	$0\dots 0$	$N-k$
Arithmetic Right	$A_{N-1}\dots A_{N-1}$ (sign extension)	$A_{N-1}\dots A_0$	$k$
Arithmetic Left	$A_{N-1}\dots A_0$	$0$	$N-k$
Rotate Right	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	$k$
Rotate Left	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	$N-k$



# Simplified Funnel Shifter


- Optimize down to  $2N-1$  bit input

**Table 10.11** Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}..A_0$	$k$
Logical Left	$A_{N-1}..A_0, 0..0$	$\bar{k}$
Arithmetic Right	$A_{N-1}..A_{N-1}, A_{N-1}..A_0$	$k$
Arithmetic Left	$A_{N-1}..A_0, 0..0$	$\bar{k}$
Rotate Right	$A_{N-2}..A_0, A_{N-1}..A_0$	$k$
Rotate Left	$A_{N-1}..A_0, A_{N-1}..A_1$	$\bar{k}$

 
# Funnel Shifter Design 1

- N N-input multiplexers
  - Use 1-of-N hot select signals for shift amount
  - nMOS pass transistor design ( $V_t$  drops!)


 
# Funnel Shifter Design 2

- Log N stages of 2-input muxes
  - No select decoding needed



# Outline

1. Addition/Subtraction
2. One/Zero Detectors
3. Comparators
4. Counters
5. Shifters
- 6. Multiplication**

# Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ \underline{0101} : 5_{10} \end{array}$$

---

# Multiplication

- Example:

$$\begin{array}{r} 1100 \\ \underline{0101} \\ 1100 \end{array} \quad : \quad \begin{array}{l} 12_{10} \\ 5_{10} \end{array}$$



# Multiplication

- Example:

$$\begin{array}{r} 1100 \\ \underline{0101} \\ 1100 \\ 0000 \end{array}$$

—————

# Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ \hline \end{array}$$



# Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline \end{array}$$

# Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 : 60_{10} \end{array}$$

# Multiplication

- Example:

1100	:	$12_{10}$	multiplicand
0101	:	$5_{10}$	multiplier
<u>1100</u>			
0000			partial products
1100			
0000			
<u>00111100</u>	:	$60_{10}$	product


- M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product
 
# General Form


- Multiplicand:  $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier:  $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- Product: 
$$P = \left( \sum_{j=0}^{M-1} y_j 2^j \right) \left( \sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$



# Dot Diagram



- Each dot represents a bit

 

# Unsigned Array Multiplication


- Fast multipliers use carry-save adders (CSA) to sum the partial products.
  - A CSA typically has a delay of 1.5-2 FO4 inverters independent of the width of the partial product,
  - A carry-propagate adder (CPA) tends to have a delay of 4-15 FO4 inverters depending on the width, architecture, and circuit family.

# Array Multiplier

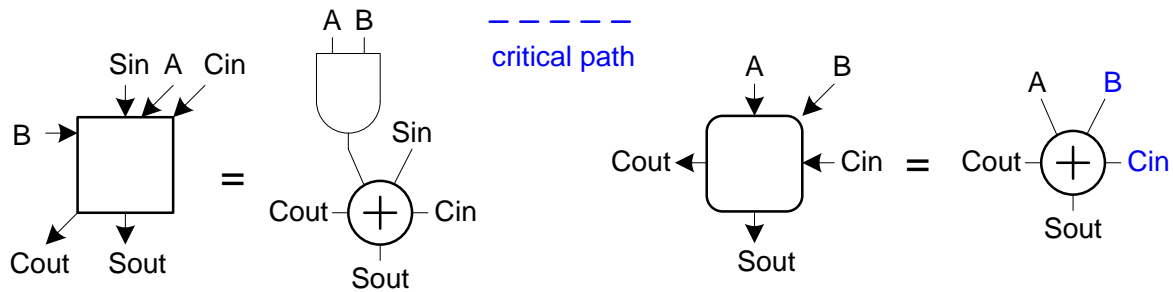 
 
# Rectangular Array

- Squash array to fit rectangular floorplan







# 2's Complement Array Multiplication

7- 98


- Modified Baugh-Wooly multiplier

						$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$						
						$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$						
						<hr/>											
					1	$\overline{x_5 y_0}$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$						
					$\overline{x_5 y_1}$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$							
					$\overline{x_5 y_2}$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$							
					$\overline{x_5 y_3}$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$							
					$\overline{x_5 y_4}$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$							
					$\overline{x_4 y_5}$	$x_3 y_5$	$x_2 y_5$	$x_1 y_5$	$x_0 y_5$								
					$\overline{x_3 y_5}$	$x_2 y_5$	$x_1 y_5$	$x_0 y_5$									
					$\overline{x_2 y_5}$	$x_1 y_5$	$x_0 y_5$										
					$\overline{x_1 y_5}$	$x_0 y_5$											
					$\overline{x_0 y_5}$												
						<hr/>											
						$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$
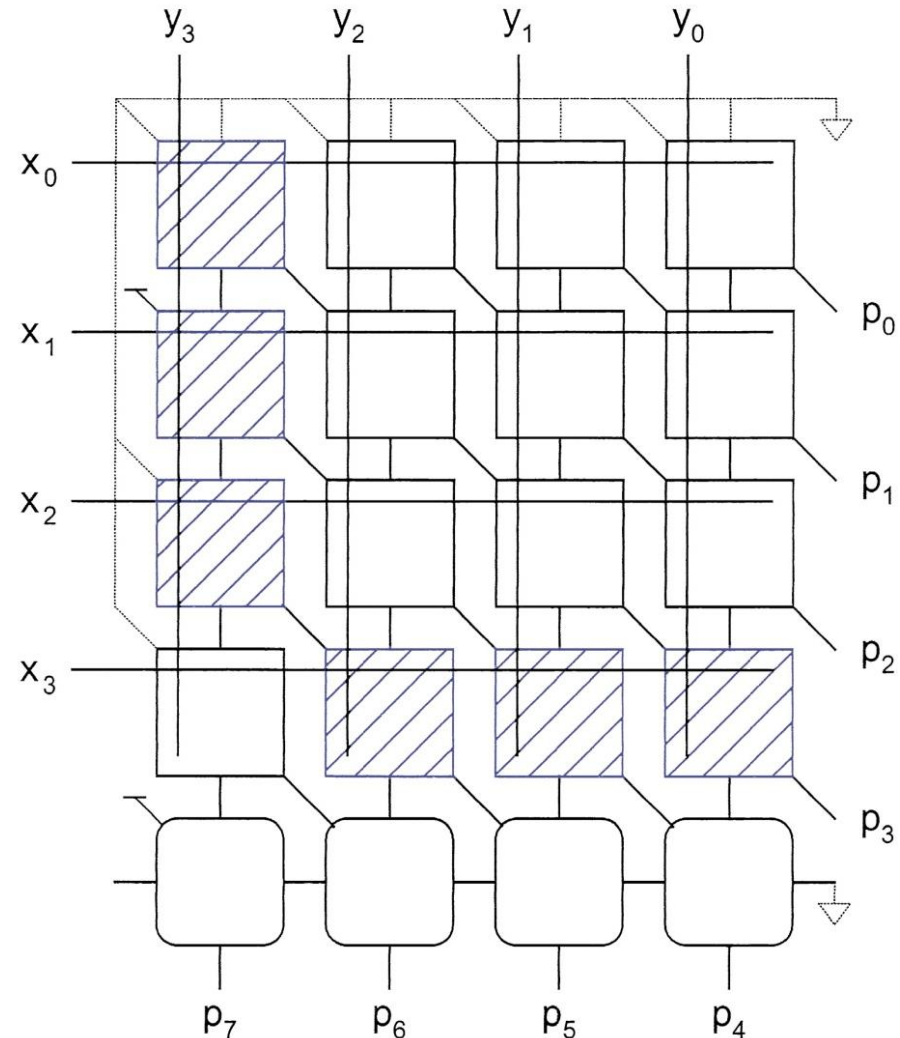
# Modified Baugh-Wooly multiplier

7- 99

- It is almost identical to the unsigned array multiplier except
  - the AND gates are replaced by NAND gates in the hatched cells
  - 1's are added in place of 0's at a few of the unused inputs.



# Fewer Partial Products

- Array multiplier requires  $N$  partial products
- If we looked at groups of  $r$  bits, we could form  $N/r$  partial products.
  - Faster and smaller?
  - Called radix- $2^r$  encoding
- Ex:  $r = 2$ : look at pairs of bits
  - Form partial products of  $0, Y, 2Y, 3Y$
  - First three are easy, but  $3Y$  requires adder ☹️

# Booth Encoding


- Modified Booth encoding
  - Avoid generating 3Y by using negative partial products

**Table 10.12** Radix-4 modified Booth encoding values

Inputs			Partial Product	Booth Selects		
$x_{2i+1}$	$x_{2i}$	$x_{2i-1}$	$PP_i$	$X_i$	$2X_i$	$M_i$
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	2Y	0	1	0
1	0	0	-2Y	0	1	1
1	0	1	-Y	1	0	1
1	1	0	-Y	1	0	1
1	1	1	-0 (= 0)	0	0	1

 
# Booth Hardware

- Booth encoder generates control lines for each PP
  - Booth selectors choose PP bits


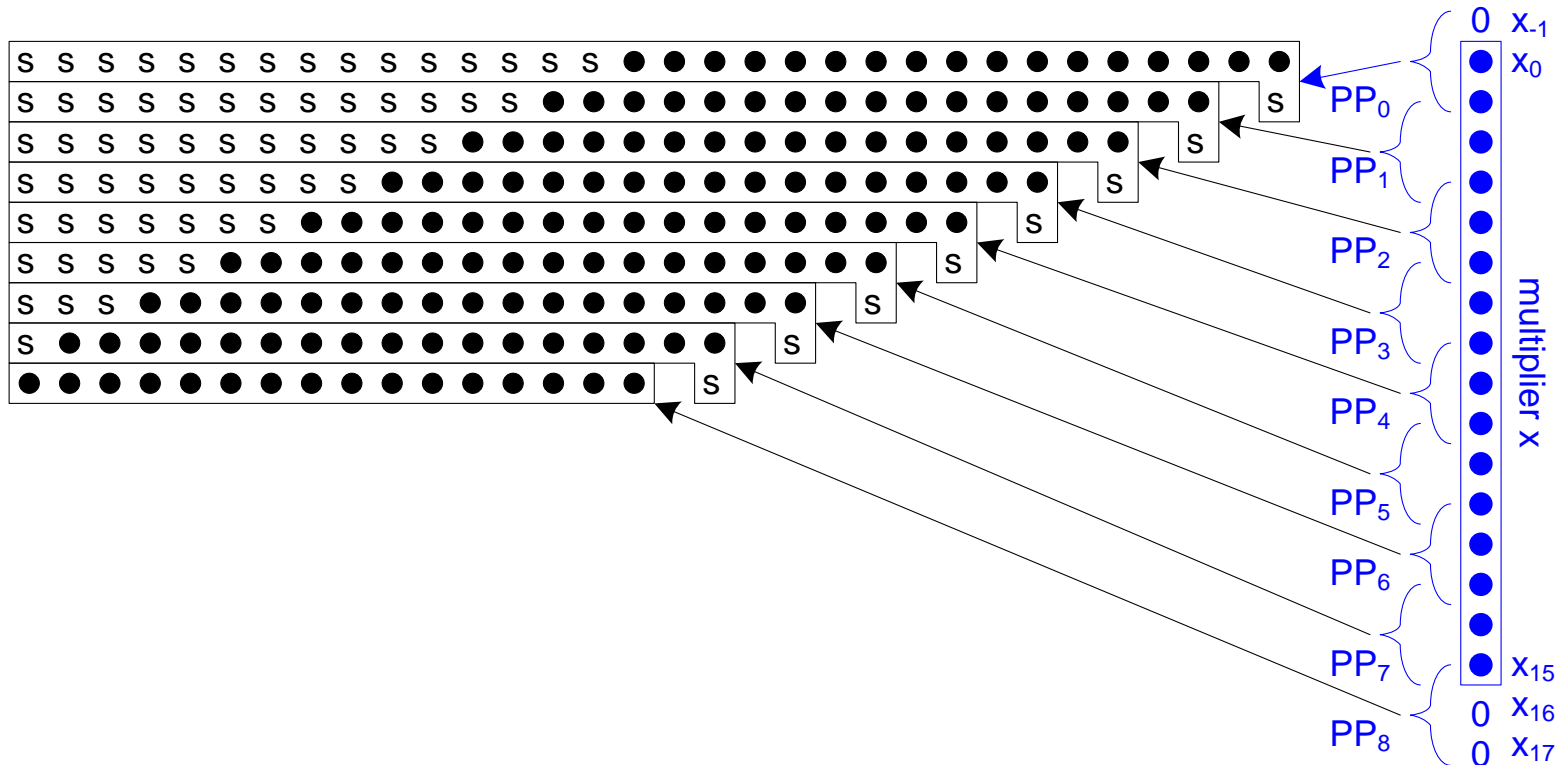
# Sign Extension

- Partial products can be negative
  - Require sign extension, which is cumbersome
  - High fanout on most significant bit










 
# Booth Encoding

- Sketch the partial products used by a radix-4 Booth-encoded multiplier to compute  $01110_2 \times 01101_2$



$X_{2i+1}$	$X_{2i}$	$X_{2i-1}$	$P_i$
1	0	n/a	$-2Y = 100101 + 1$
1	1	1	$-0Y = 111111 + 1$
n/a	0	1	$Y = 001101 + 0$

 

$PP_0$   
 $PP_1$   
 $PP_2$   
 $PP_3$


$PP_3$  is necessary in case  
 $PP_2$  is negative

# Wallace Tree Multiplication

- CSA is effective a “1’s counter”, known as (3,2) counter

**Table 10.14** An adder as a 1’s counter


A	B	C	Carry	Sum	Number of 1's
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	1	0	2
1	0	0	0	1	1
1	0	1	1	0	2
1	1	0	1	0	2
1	1	1	1	1	3

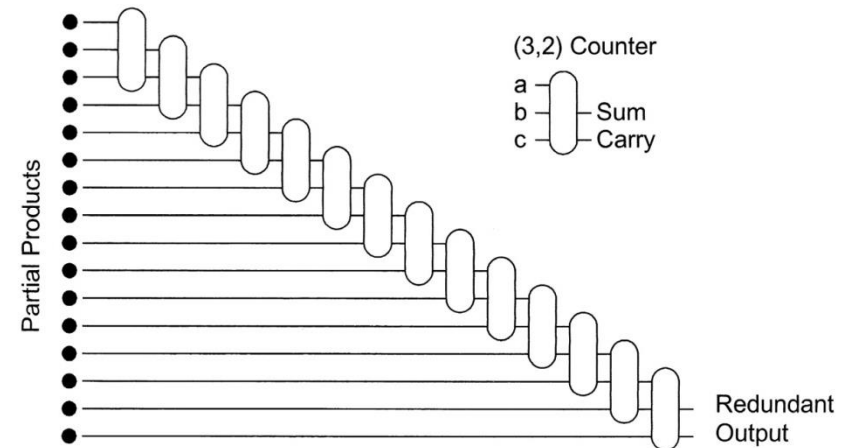
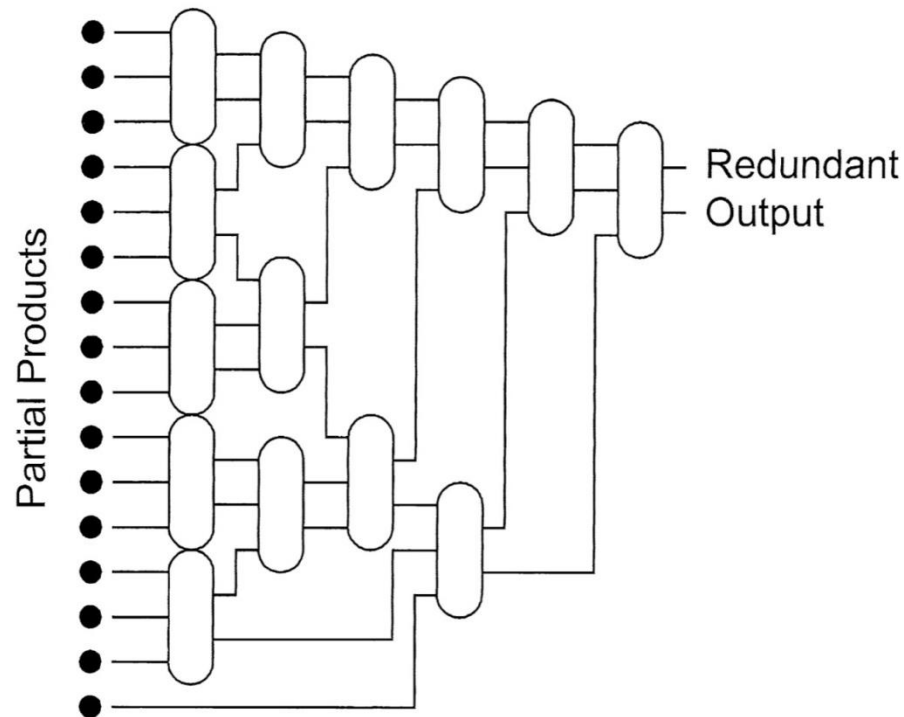
# Wallace Tree Multiplication


7- 108

- Wallace tree architecture can speed the column addition, requires  $\lceil \log_{3/2}(N/2) \rceil$  levels of (3,2) counters.




# Wallace Tree Multiplication

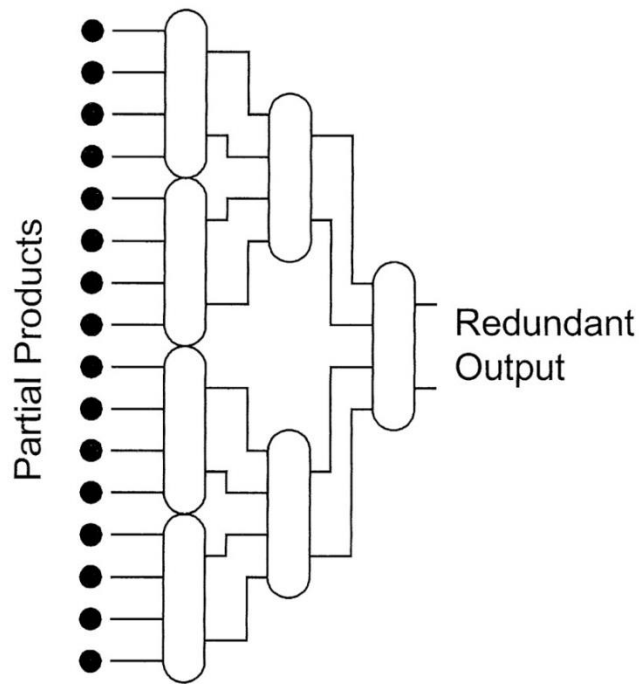- [4:2] compressors are used to produce a more regular layout, requires  $\lceil \log_2(N/2) \rceil$  levels of (5,3) counters.




## [4:2] compressor

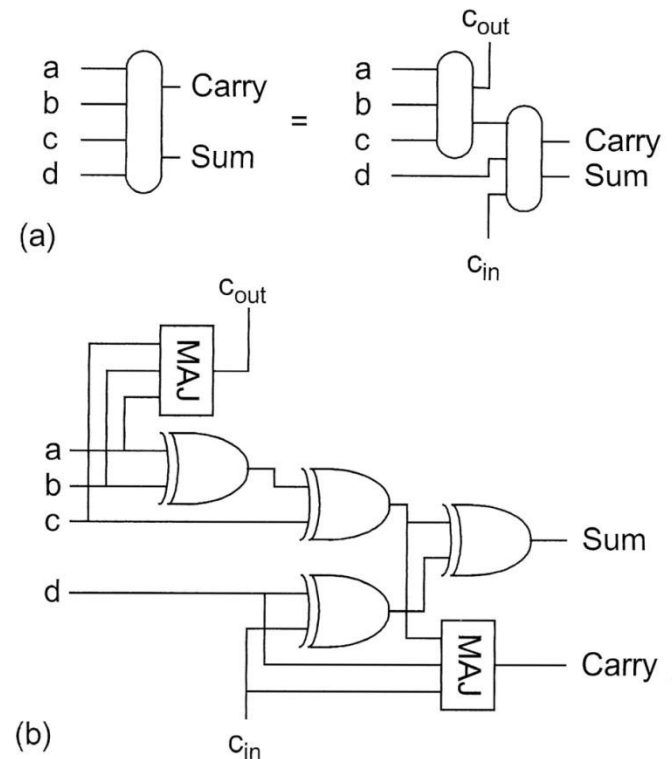
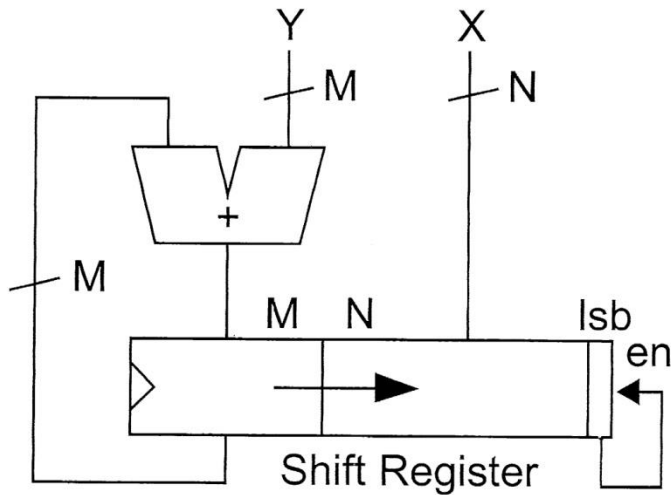
# Serial Unsigned Multiplication

- Serial multiplication need far less hardware, but requires multiple clock cycles to operate.



Step	Shift	Reg	Notes
	0000	0101	initialize
0a	1100	0101	add 1*Y
0b	01100	010	shift right
1a	01100	010	add 0*Y
1b	001100	01	shift right
2a	111100	01	add 1*Y
2b	0111100	0	shift right
3a	0111100	0	add 0*Y
3b	00111100		shift right

# Summary

- For synthesis/APR design flow: choose proper adder/multiplier with various area/speed tradeoff based on applications.
- Custom design at schematic level provide most optimization of performance.
- The wiring capacitance need to be concerned in multiplier design, compact cell and short wires can be fast as well as small and low in power.