
EE3230 Lecture 5: Circuit Characterization and Performance Estimation II

Ping-Hsuan Hsieh (謝秉璇)

Delta Building R908

EXT 42590

phsieh@ee.nthu.edu.tw

Outline

- Delay estimation
- Logical effort and transistor sizing
- **Power dissipation**
- Interconnect
- Wire engineering
- Design margin
- Reliability
- Scaling

Power and Energy


- Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip
- Instantaneous Power:
- Energy:
- Average Power:

Static and Dynamic Power Dissipation


- Static power dissipation
 - Sub-threshold conduction through OFF transistors
 - Tunneling current through gate oxide
 - Leakage through reverse-biased diodes
 - Contention current in ratioed circuits
- Dynamic power dissipation
 - Charging and discharging of load capacitance
 - “Short-circuit” current while both PMOS and NMOS networks are partially ON

Dynamic Power (I)

 - Dynamic power is required to charge and discharge load capacitances when transistors switch
- One cycle involves a rising and falling output.
- On rising output, charge $Q = CV_{DD}$ is required
- On falling output, charge is dumped to GND
- This repeats f_{sw} times per second



Dynamic Power (II)

 

Activity Factor

- Suppose the system clock frequency = f
- Let $f_{sw} = \alpha f$, where **α = activity factor**
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = \frac{1}{2}$
 - **Dynamic gates:** Switch either 0 or 1 times per cycle, $\alpha = \frac{1}{2}$
 - **Static gates:** Depends on design, typically $\alpha = 0.1$
- Dynamic power:

Short-Circuit Current

- When transistors switch, both NMOS and PMOS networks may be momentarily ON at once
- Leads to a blip of **short-circuit current**
- $< 10\%$ of dynamic power if rise/fall times are comparable for input and output (well-controlled)

Example

- 200M transistor chip
 - 20M logic transistors
 - Average width: 12λ
 - 180M memory transistors
 - Average width: 4λ
 - 1.2-V 100-nm process ($\lambda = 0.5 \times \text{feature size} = 50\text{nm}$)
 - $C_g = 2 \text{ fF}/\mu\text{m}$

Dynamic Power Consumption

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks and partially activated at a time!)
- Estimate dynamic power consumption per MHz.
 - Neglect wire capacitance and short-circuit current

Static Power Consumption

- Static power is consumed even when chip is quiescent.
 - Ratioed circuits burn power in fight with ON transistors
 - Leakage draws power from nominally OFF devices

Ratioed Example

- The chip contains a 32 word x 48 bit ROM
 - Uses 1:32 pseudo-nMOS decoder and bit-line pull-ups
 - In average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
 - $\beta = 75 \mu\text{A}/\text{V}^2$, $V_{DD} = 1.8 \text{ V}$
 - $V_{tp} = -0.4\text{V}$

Leakage Example (I)

- The process has two threshold voltages and two oxide thicknesses.
- Subthreshold leakage:
 - 20 nA/ μm for low V_{th} devices
 - 0.02 nA/ μm for high V_{th} devices
- Gate leakage:
 - 3 nA/ μm for thin oxide
 - 0.002 nA/ μm for thick oxide
- Memories use low-leakage transistors everywhere
- Gates use low-leakage transistors on 80% of logic

Leakage Example (II)

- Estimate static power:
 - High leakage:
 - Low leakage:


- Withow leakage devices, $P_{\text{static}} = 749 \text{ mW}$ (!)

Low Power Design


- To reduce dynamic power
 - α : clock gating, sleep mode
 - C: small transistors (esp. on clock), short wires
 - V_{DD} : lowest suitable voltage
 - f: lowest suitable frequency
- To reduce static power
 - Selectively use ratioed circuits
 - Selectively use low V_{th} devices
 - Leakage reduction:
stacked devices, body bias, low temperature

Reduce Static Power



- Leakage stack effect

 

- MTCMOS: multiple threshold CMOS

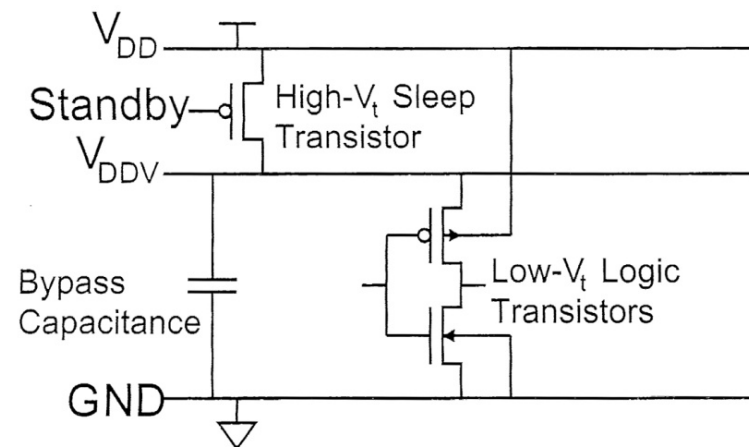

- Body bias

  

Outline


- Delay estimation
- Logical effort and transistor sizing
- Power dissipation
- **Interconnect**
- Wire engineering
- Design margin
- Reliability
- Scaling

Interconnect

- Chips are mostly made of wires called *interconnect*
 - In stick diagrams, wires determine size
 - Transistors are little things under the wires
 - Many layers of wires
- Wires are as important as transistors
 - Speed
 - Power
 - Noise
- Alternating layers run orthogonally

Wire Geometry

 - Pitch = $w + s$
- Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires



Layer Stack

- AMI 0.6- μm process has 3 metal layers
- Modern processes use 6-10+ metal layers
- Example: Intel 180 nm process

- M1: thin, narrow ($< 3\lambda$)

- High density cells




- M2-M4: thicker

- For longer wires

- M5-M6: thickest

- For V_{DD} , GND, clk


Layer	T (nm)	W (nm)	S (nm)	AR
6	1720	860	860	2.0
	1000			
5	1600	800	800	2.0
	1000			
4	1080	540	540	2.0
	700			
3	700	320	320	2.2
	700			
2	700	320	320	2.2
	700			
1	480	250	250	1.9
	800			

   

Substrate

Wire Resistance

 - $\rho = \text{resistivity } (\Omega \cdot \text{m})$
- $R_{\square} = \text{sheet resistance } (\Omega/\square)$
 - \square is a dimensionless unit(!)
- Count number of squares
 - $R = R_{\square} * (\text{\# of squares})$



Choice of Metals

- Until 180 nm, most wires were aluminum
- Modern processes often use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity ($\mu\Omega\cdot\text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3

Sheet Resistance

- Typical sheet resistances in 180-nm process

Layer	Sheet Resistance (Ω/\square)
Diffusion (silicided)	3-10
Diffusion (no silicide)	50-200
Polysilicon (silicided)	3-10
Polysilicon (no silicide)	50-400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02


Contact Resistance

- Contacts and vias also have 2-20 Ω
- Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Wire Capacitance

 - Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$




Capacitance Trend

- Parallel plate equation: $C = \epsilon A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W, t) increases capacitance
 - Increasing distance (s, h) decreases capacitance
- Dielectric constant
 - $\epsilon = k\epsilon_0$
 - $\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$
 - $k = 3.9$ for SiO_2
- Processes are starting to use low-k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

M2 Capacitance Data

 - Typical wires have $\sim 0.2 \text{ fF}/\mu\text{m}$
 - Compare to $2 \text{ fF}/\mu\text{m}$ for gate capacitance




Diffusion and Polysilicon

- Diffusion capacitance is very high (about $2 \text{ fF}/\mu\text{m}$)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Lumped Element Models

 - Wires are a distributed system
 - Approximate with lumped element models



- 3-segment π -model is accurate to 3% in simulation
- L-model needs 100 segments for same accuracy!
- Use single segment π -model for Elmore delay

Example

- M2 wire in 180-nm process
 - 5-mm long
 - 0.32- μm wide
- Construct a 3-segment π -model
 - $R_{\square} = 0.05 \Omega/\square \quad \rightarrow R =$
 - $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m} \quad \rightarrow C =$

Wire RC Delay

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5-mm wire from previous example
 - Effective $R = 2.5 \text{ k}\Omega/\mu\text{m}$ for gates, $C = 2 \text{ fF}/\mu\text{m}$
 - Unit inverter: $4\lambda = 0.36 \mu\text{m}$ nMOS, $8\lambda = 0.72 \mu\text{m}$ pMOS


Crosstalk

- Capacitor do not change voltage instantaneously
- A wire has high capacitance to its neighbor
 - When the neighbor (**aggressor**) switches from $1 \rightarrow 0$ or $0 \rightarrow 1$, the wire (**victim**) tends to switch as well
 - Called *capacitive coupling* or *crosstalk*
- Impacts
 - Cause noise on non-switching wires
 - Increase delay on switching wires

Crosstalk Delay


- Assume layers above and below in average are quiet
 - Second terminal of capacitor can be ignored
 - Modeled as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- Effective C_{adj} depends on behavior of neighbors
 - *Miller Coupling Factor (MCF)*

B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant	V_{DD}	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2

 


Crosstalk Noise (Floating Victims)

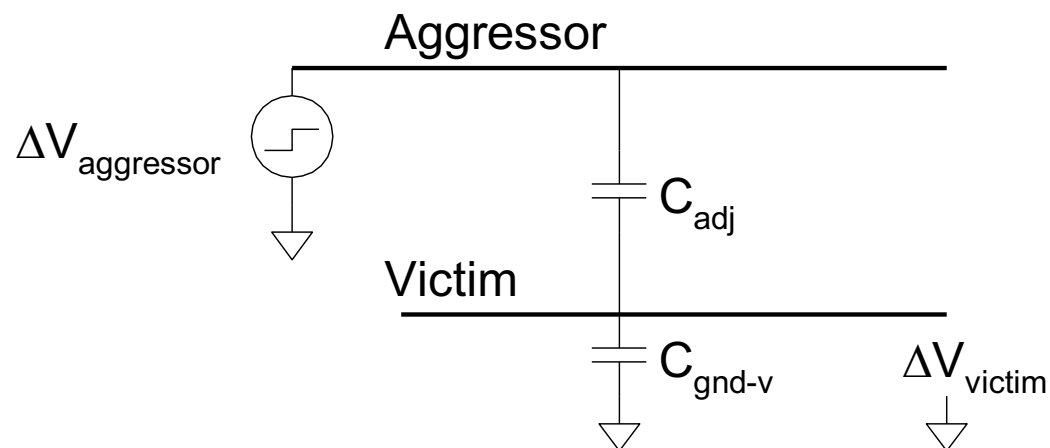- Crosstalk causes noise on non-switching wires
- If victim is **floating**
 - modeled as capacitive voltage divider




Crosstalk Noise (Driven Victims)

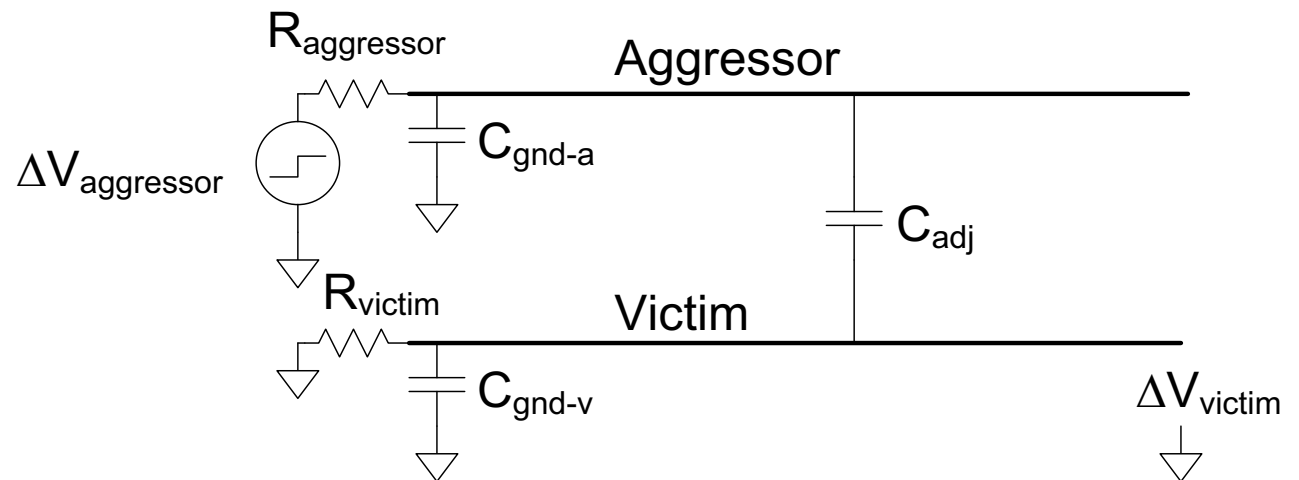- Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Assume victim driver in linear region and aggressor driver in saturation (considering inverter operation)
 - With equal sizes, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$



Coupling Waveforms

 - Simulated coupling for $C_{\text{adj}} = C_{\text{gnd}}$



Noise Implications

- *So what* if we have noise?
- If the noise is less than the noise margin, nothing happens
- Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- Dynamic logic never recovers from glitches
- Memories and other sensitive circuits also can produce wrong outputs

Outline



- Delay estimation
- Logical effort and transistor sizing
- Power dissipation
- Interconnect
- **Wire engineering**
- Design margin
- Reliability
- Scaling

Wire Engineering

- Goal: to achieve delay, area, and power goals with acceptable noise
- Degrees of freedom:

Wire Engineering




 
 
- Goal: to achieve delay, area, and power goals with acceptable noise
- Degrees of freedom:
 - Width
 - Spacing



Wire Engineering



- Goal: to achieve delay, area, and power goals with acceptable noise
- Degrees of freedom:

- Width
- Spacing
- Layer
- Shielding

     

Repeaters

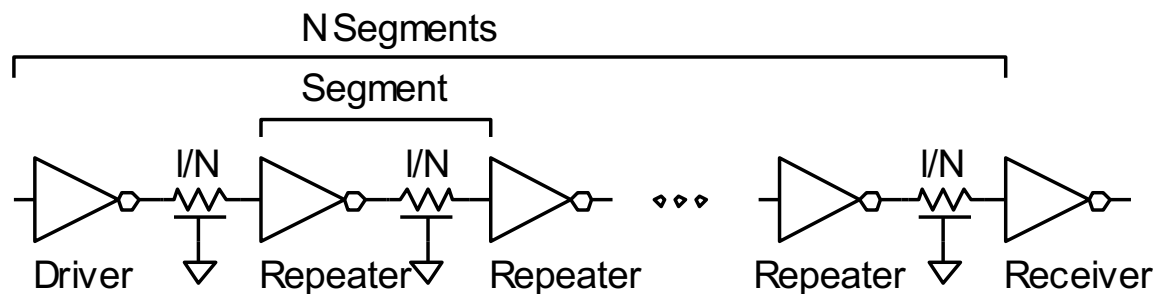 - R and C are proportional to l (length)
- RC delay is proportional to l^2
 - Unacceptably long delays for long wires
- Break long wires into N shorter segments
 - Drive each one with an inverter or buffer



Repeater Design

- How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit
 - Wire length l
 - Wire Capacitance $C_w * l$, Resistance $R_w * l$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W

Repeater Design

- How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit
 - Wire length l/N
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W