
EE3230 Lecture 3: MOS Transistor Theory

Ping-Hsuan Hsieh (謝秉璇)

Delta Building R908


EXT 42590

p hsieh@ee.nthu.edu.tw



Outline

- **Introduction**
- Ideal I-V characteristics
- Nonideal Effects
- DC transfer characteristics
- C-V characteristics
- Switch-level RC delay models



MOS Transistor Symbols

 

NMOS

  


PMOS

  


MOS Structure

NMOS

 

$$V_{gb} > 0$$


- Depletion mode

 

- Inversion mode

形成 channel (inversion layer)

 process dependant
 (doping level
 oxide thickness)




MOS Structure

- Accumulation mode

- Depletion mode

- Inversion mode

 


NMOS Operating Regions (I, II)

- Cutoff

$$V_{gs} < V_{th}$$


no channel

 



Cutoff:
No Channel
 $I_{ds} = 0$

- Linear ^{inversion mode} _{triode}

$$V_{gs} > V_{th}$$

 


  Linear:
Channel Formed
 I_{ds} Increases with V_{ds}




NMOS Operating Regions (III)

- Saturation

 

Saturation:
Channel Pinched Off
 I_{ds} Independent of V_{ds}

 
$$\left. \begin{array}{l} V_{gs} > V_{th} \\ V_{gd} < V_{th} \end{array} \right\} \rightarrow V_{as} > \underbrace{(V_{gs} - V_{th})}_{\text{overdrive voltage: } V_{ov}, V_{GT}}$$



Outline


- Introduction
- **Ideal I-V characteristics**
- Nonideal Effects
- DC transfer characteristics
- C-V characteristics
- Switch-level RC delay models

MOS Channel Charge

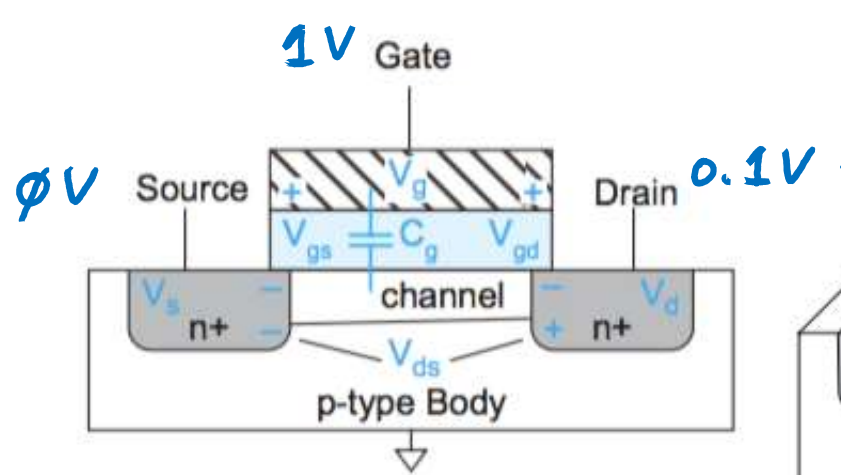

Average gate to channel potential:
 
$$V_{gc} = (V_{gs} + V_{gd})/2 = V_{gs} - V_{ds}/2$$



SiO₂ Gate Oxide
(insulator, $\epsilon_{ox} = 3.9\epsilon_0$)

$$I_{ds} = f(Q_{ch}, \mu, V_{ds})$$

$$(V_{gs} - V_{th}), W$$

$$= \frac{Q_{ch}}{L} \cdot v \quad \left(\text{where } v = \mu \cdot E = \mu \frac{V_{ds}}{L} \right)$$

$$Q_{ch} = C_{ch} \cdot (V_{gs} - \frac{1}{2} V_{ds} - V_{th})$$

$$C_{ch} = \epsilon_{ox} \cdot \frac{W \cdot L}{t_{ox}} = \underbrace{\frac{\epsilon_{ox}}{t_{ox}}}_{\substack{\text{cap/area} \\ \text{fF}/(\mu\text{m})^2}} \cdot WL = C_{ox} \cdot WL$$

Ideal I-V Equations



$$I_{ds} = \frac{C_{ox} \cdot W \cdot L (V_{gs} - \frac{1}{2} V_{ds} - V_{th})}{L} \mu \cdot \frac{V_{ds}}{L}$$



$$= \mu C_{ox} \frac{W}{L} \left(\underbrace{V_{gs} - V_{th}}_{\text{in linear region}} - \frac{1}{2} V_{ds} \right) \cdot \underbrace{V_{ds}}_{\text{(triode)}}$$

At saturation

$$V_{ds} = V_{gs} - V_{th}$$

$$I_{ds_{sat}} = \frac{1}{2} \underbrace{\mu C_{ox} \frac{W}{L}}_{\beta} \left(\underbrace{V_{gs} - V_{th}}_{\text{super-linear relation}} \right)^2$$

Ideal I-V Characteristics

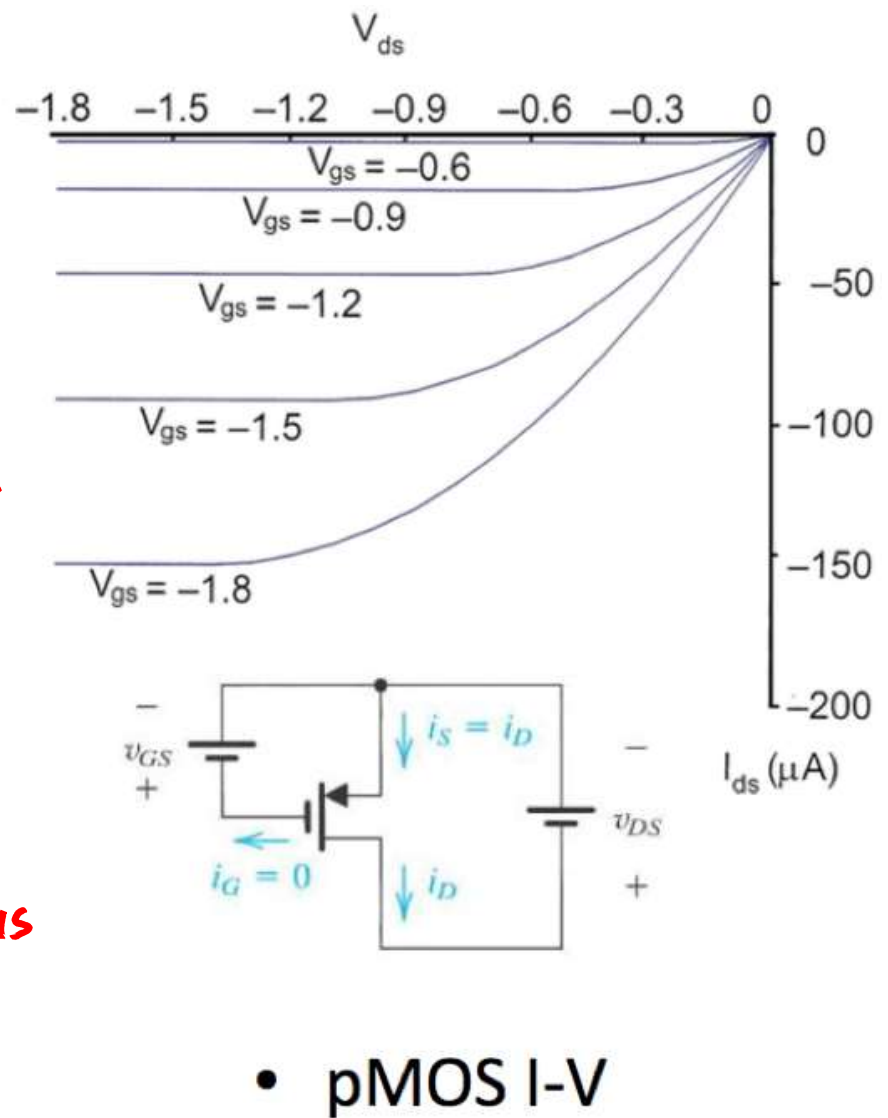 


Outline

- Introduction
- Ideal I-V characteristics
- **Nonideal Effects**
- DC transfer characteristics
- C-V characteristics
- Switch-level RC delay models



Nonideal I-V Effects

- **Channel length modulation** at high V_{ds} \uparrow , depletion of S/D \uparrow , effective L \downarrow , I_{ds} increase \uparrow .
- **Body effect** threshold voltage V_{th} influenced by V_{bs} (body-to-source voltage).
- **Velocity saturation** at high V_{ds} \uparrow , the carrier velocity is no longer proportional to lateral field. I_{ds} decrease \downarrow .
- **Mobility degradation** at high V_{gs} \uparrow , the carrier scatter more and mobility decreases. I_{ds} decrease \downarrow .
- **Subthreshold conduction** $V_{gs} < V_{th}$, I_{ds} is exponentially dropoff instead of abruptly becoming zero
S \rightarrow D @ turn-off
- **Drain/source leakage** reverse diode junction leakage
D/S \rightarrow B
- **Non-zero gate current I_g** carriers tunneling effect

 

Channel Length Modulation

  - Effective channel length reduced due to high V_{ds}



- I-V equation at saturation region:
 - λ' empirical parameter

$$I_{ds} = \beta \frac{(V_{gs} - V_t)^2}{2} (1 + \lambda V_{ds}), \lambda = \lambda' / L$$

- With shorter $L \downarrow$, $\lambda \uparrow$, resulting in output resistance \downarrow , MOSFET intrinsic gain \downarrow

Body Effect

- Threshold voltage V_{th} increased with positive V_{sb}
- V_{sb} < 0 → V_{th} ↓, OFF leakage ↑ (design trade-off)

$$V_t = V_{t0} + \gamma [\sqrt{2\phi_s + V_{sb}} - \sqrt{2\phi_s}]$$

$$\phi_s = 2\psi_T \ln \frac{N_A}{n_i}$$

V_{t0}: threshold voltage for V_{sb} = 0

φ_f: process-dependent parameter


suffered from body effect

$$\gamma = \frac{t_{ox}}{\epsilon_{ox}} \sqrt{2qN_A \epsilon_{si}} = \frac{\sqrt{2qN_A \epsilon_{si}}}{C_{ox}}$$

γ: body-effect coefficient (process-dependent)

N_A: doping concentration of p-substrate

ε_s: permittivity of silicon = 11.7 ε₀

 

PMOS to NWell

可以连接到 source

Velocity Saturation

- Carrier velocity** nonlinearly proportional to lateral electrical field before velocity saturation

$$v = \mu E_{lat} / (1 + E_{lat} / E_{sat})$$


v : carrier velocity

μ : mobility

$E_{lat} = V_{ds} / L$: lateral electrical field

$E_{sat} = v_{sat} / \mu$

 - I_{ds} will saturate to velocity saturation, depending on channel length L and applied V_{ds}



$$\underline{I_{ds}^{sat}} = \frac{Q_{channel}}{t_{channel}} = \frac{Q_{channel}}{L / v_{sat}} = \underline{C_{ox} W (V_{gs} - V_t) v_{sat}}$$

α -power Law Model

- Piecewise linear model to illustrate MOSFET's I-V characteristic with velocity saturation


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ I_{dsat} \frac{V_{ds}}{V_{dsat}} & V_{ds} < V_{dsat} & \text{linear} \\ I_{dsat} & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

$$I_{dsat} = P_c \frac{\beta}{2} (V_{gs} - V_t)^\alpha, \quad V_{dsat} = P_v (V_{gs} - V_t)^{\alpha/2}$$

Empirical parameters: P_c, P_v, α

→ g_m degradation

 - Because $\mu_p < \mu_n$, PMOS experiences less velocity saturation than NMOS → $\alpha_p > \alpha_n$
- Mobility degradation** is modeled by a $\mu_{eff} < \mu$, and it can be included in to the parameter α




Subthreshold Conduction

- Leakage current at subthreshold region
 - $V_{gs} < V_{th}$: weak inversion


$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_t}{nV_T}} \left(1 - e^{\frac{-V_{ds}}{V_T}} \right)$$

$$I_{ds0} = \beta v_T^2 e^{1.8}$$

 - $I_d = 0$ when $V_{ds} = 0$
 - Increase exponentially with V_{gs}
- Drain-induced barrier lowering (DIBL)**
 - V_{th} will reduce with positive V_{ds}
 - Worsens leakage at subthreshold
 - Like channel-length modulation at active mode



Junction Leakage

 


- S/D junction leakage from a reverse-biased diode

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

- Junction leakage used to be the limitation for storage time. In modern processes, subthreshold leakage becomes dominant



Tunneling Effect

 

- Gate leakage: from carriers' tunneling through gate oxide. Exponentially inversely proportional to gate oxide thickness.
- High- k (dielectric constant) gate insulator used



Temperature Dependence

  - $T \uparrow$ $I_{OFF} \uparrow$ $I_{ON} \uparrow$
- Circuit performance improve with $T \downarrow$: subthreshold leakage \downarrow , saturation velocity \uparrow , mobility \uparrow , junction capacitance \downarrow , but breakdown voltage \downarrow .



Geometry Dependence

$\frac{W}{L}$

  

- Effective channel length and width

$$L_{eff} = L_{drawn} + X_L - 2L_D \quad X_L, X_W : \text{Poly over-etch}$$

$$W_{eff} = W_{drawn} + X_W - 2W_D \quad L_D, W_D : \text{Source-drain lateral diffusion}$$

- Use identical and same orientation for MOSFETs for good matching – **EX:** differential pair, current mirror




Outline

- Introduction
- Ideal I-V characteristics
- Nonideal Effects
- **DC transfer characteristics**
- C-V characteristics
- Switch-level RC delay models

CMOS Inverter DC Characteristics (I)

in — V_{DD} — out
CMOS
implementation


KCL

   

	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$


CMOS Inverter DC Characteristics (II)

 - I_{ds} vs. V_{ds} for NMOS and PMOS
- PMOS I-V as load-line for NMOS



CMOS Inverter DC Characteristics (III)

 - I_{ds} vs. V_{ds} for NMOS and PMOS
- PMOS I-V as load-line for NMOS




CMOS Inverter DC Characteristics (IV)

- I_{ds} vs. V_{ds} for NMOS and PMOS KCL
- PMOS I-V as load-line for NMOS


@ \star P, N in saturation
 
$$I_{dsat} \propto \mu C_{ox} \frac{W}{L} (V_{ov})^2$$



CMOS Inverter DC Characteristics (V)

 - V_{in} - V_{out} DC transfer curve
- Rail-to-rail operation
- V_{in} - I_{DD} DC transfer curve
- Dynamic power dissipation




DC Response

- DC response: V_{out} vs. V_{in} for a gate

- **Ex: inverter**


- $V_{in} = 0 \rightarrow V_{out} = V_{DD}$
- $V_{in} = V_{DD} \rightarrow V_{out} = 0$
- In between, V_{out} depends on transistor sizes and currents
- By KCL must settle such that $I_{dsn} = |I_{dsp}|$
- We could solve equations
- Graphical solution gives more insight

 

Transistor Operating Regions

DC characteristics

	NMOS	PMOS
A	cut off	linear
B	sat $\frac{1}{2}$ on	linear
C	sat	sat
D	linear	sat $\frac{1}{2}$ on
E	linear	cut off

 


Beta Ratio Effect

- β ratio and parameters

$$\beta_p = \mu_p C_{ox} (W/L)_p$$

$$\beta_n = \mu_n C_{ox} (W/L)_n$$
 
$$\beta \text{ ratio} = \beta_p / \beta_n$$



- β ratio = 1 \rightarrow largest noise margin
 - $\mu_n > \mu_p$, choose $(W/L)_p > (W/L)_n$ to make β ratio = 1
- β ratio $> 1 \rightarrow$ HI-skewed inverter, switching threshold $> 0.5 V_{DD}$
- β ratio $< 1 \rightarrow$ LO-skewed inverter, switching threshold $< 0.5 V_{DD}$

Noise Margin (I)

- The allowable noise voltage on the input that the output won't be corrupted

$$NM_L = V_{IL} - V_{OL}$$


$$NM_H = V_{OH} - V_{IH}$$

V_{IH} = minimum HIGH input voltage

V_{IL} = maximum LOW input voltage


V_{OH} = minimum HIGH output voltage

V_{OL} = maximum LOW output voltage

 


Noise Margin (II)

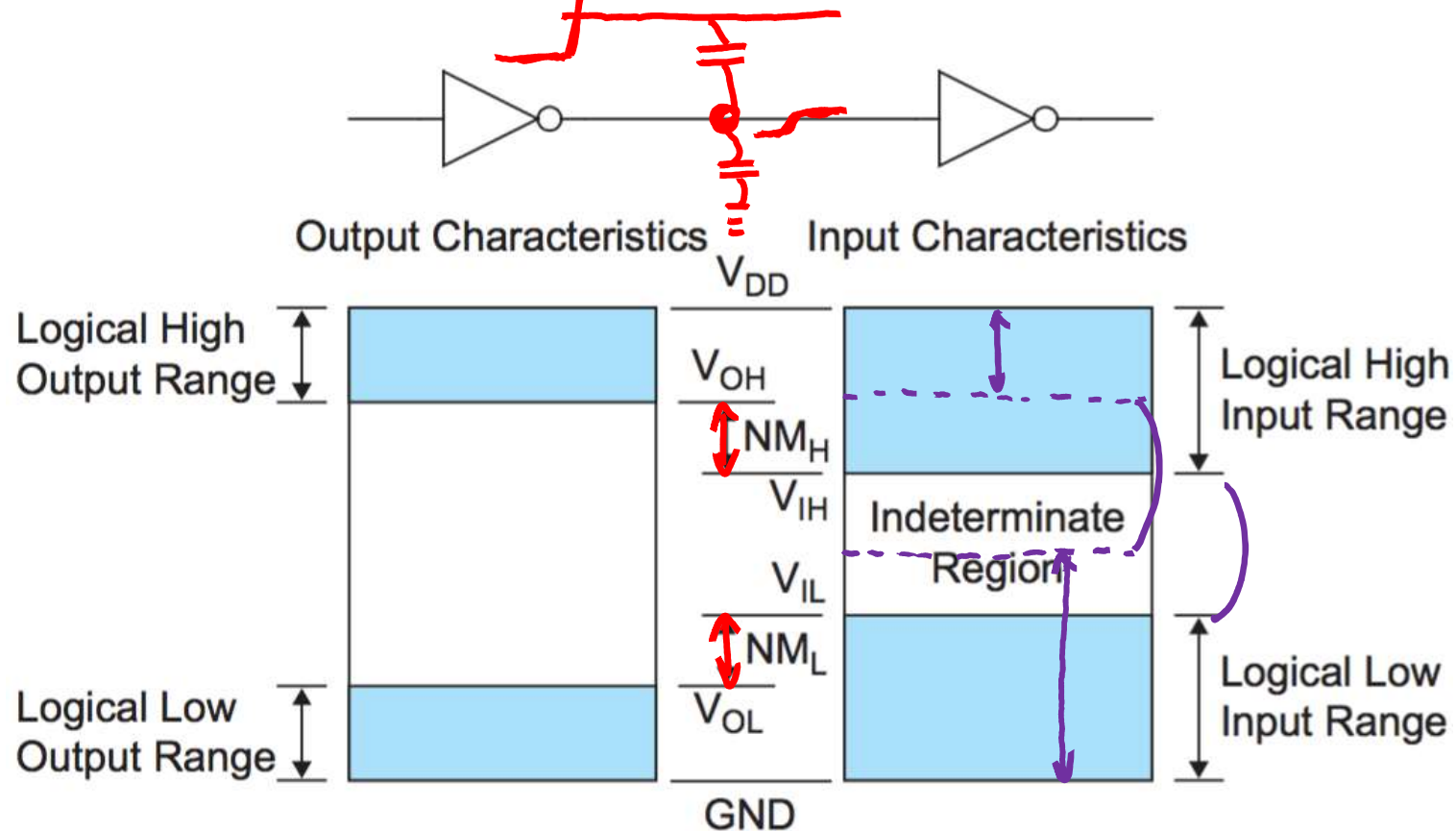- Indeterminate region (*forbidden zone*)
 - $V_{IL} < V_{in} < V_{IH} \rightarrow V_{out} = \text{unknown logic level}$




Beta Ratio and Noise Margin

 - β ratio > 1
 - Switching threshold $> 0.5 V_{DD}$ *curve 往右移*
 - $V_{IH} \uparrow$ $NMH \downarrow$
 - $V_{IL} \uparrow$ $NML \uparrow$
- β ratio < 1
 - Switching threshold $< 0.5 V_{DD}$
 - $V_{IH} \downarrow$ $NMH \uparrow$
 - $V_{IL} \downarrow$ $NML \downarrow$
- Noise tend to scale with V_{DD}
 - As $V_{DD} \downarrow$
smaller NM is acceptable







Ratioed Inverter Transfer Function (I)

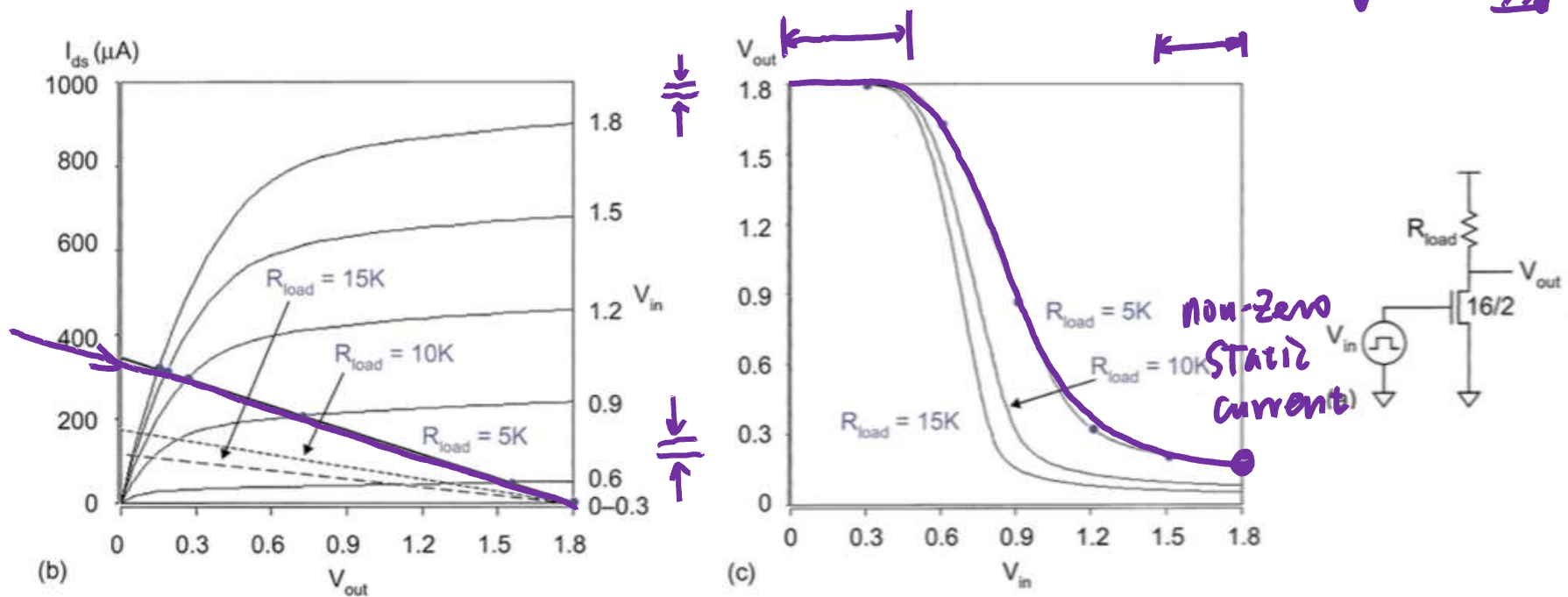- NMOS inverters with resistive or constant current-source load
 - Transfer function depends on the ratio of pull-down to the pull-up transistor (static load)





Ratioed Inverter Transfer Function (II)

    
- NMOS inverters with turn-ON PMOS as load
 - Turn-ON PMOS is made by a depletion mode NMOS in pure NMOS process
 - Dissipating static power when $V_{out} = \text{LOW}$
 - Poor NM but smaller area and input capacitance loading



Pass Transistor DC Characteristics

 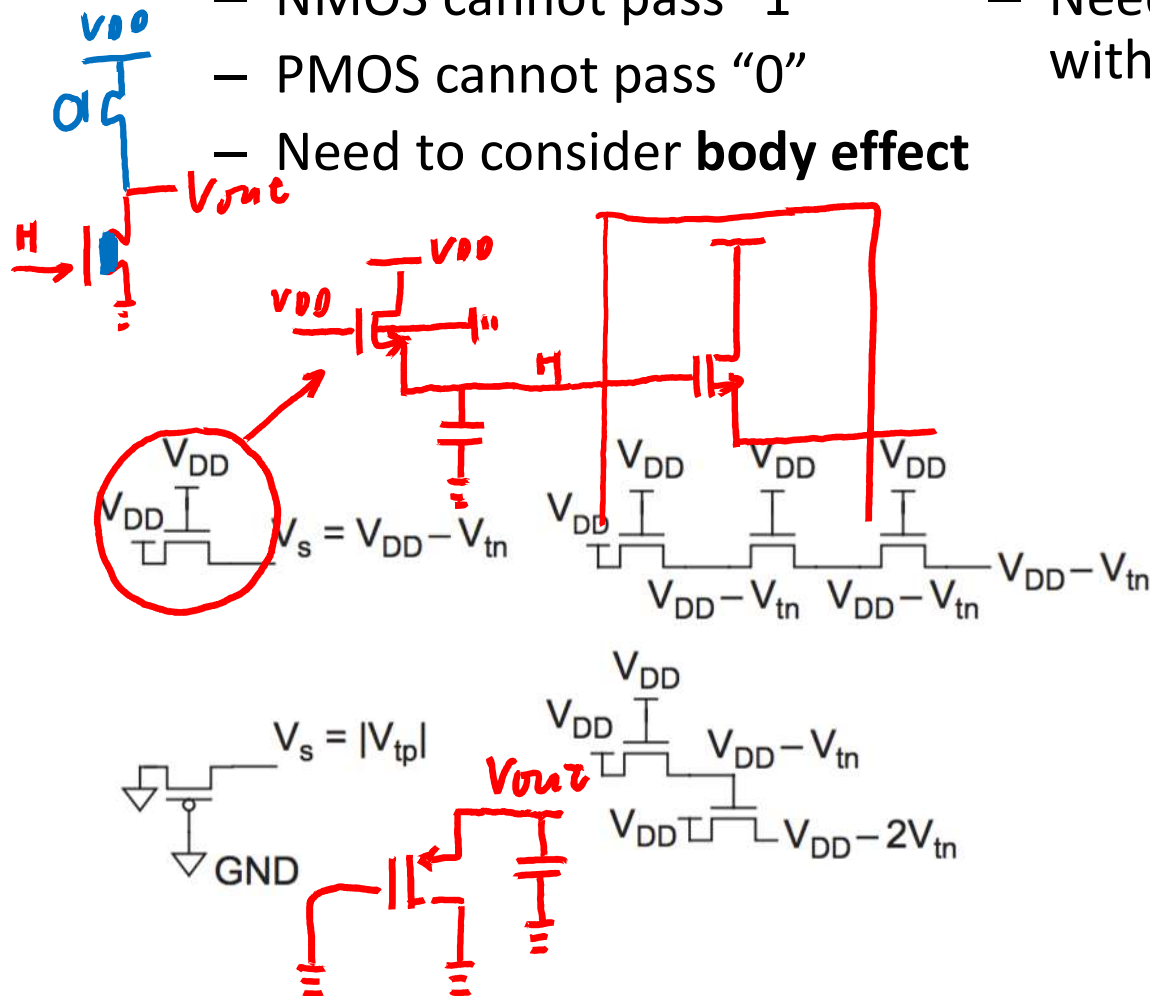- Due to V_{th}
 - NMOS cannot pass “1”
 - PMOS cannot pass “0”
 - Need to consider **body effect**
- ON-resistance depends on V_{in}
 - Need to boost gate voltage with small V_{DD}





 



Tri-state Inverter

- Inverter + transmission gate
 - Approximately half the speed of CMOS inverter for the same n and p device sizes
 - The structure in (d) suffer from A's toggling in tristate
 - Need to consider **body effect**


B → DO —

  


tri-state inverter

  

Outline

 - Introduction
- Ideal I-V characteristics
- • Nonideal Effects
- DC transfer characteristics
- **C-V characteristics**
- Switch-level RC delay models





C-V Characteristics



- Gate capacitance:** with advanced technology, $t_{ox} \downarrow$, $L \downarrow$, $C_{permicron}$ keeps constant

$$C_g = \underline{C_{ox} WL} = C_{permicron} W$$
  
$$C_{permicron} = C_{ox} L = \frac{\epsilon_{ox}}{t_{ox}} L$$



  - Parasitic capacitance:** C_{db} and C_{sb} from reverse-biased p-n junction and proportional to S/D area



MOS Gate Capacitance Model

- Gate capacitance:** vary with channel behavior at different operation regions

old tech: 2 fF/ μm

advanced tech: 1 fF/ μm

$$C_0 = C_{ox} WL$$

width

Parameter	Cutoff	Linear	Saturation
C_{gb}	$\leq C_0$	0	0
C_{gs}	0	$C_0/2$	$(2/3 C_0)$
C_{gd}	0	$C_0/2$	0
$C_g = C_{gs} + C_{gd} + C_{gb}$	C_0	C_0	$2/3 C_0$


- S/D overlap capacitance:** $C_{gs}(\text{overlap})$ and $C_{gd}(\text{overlap})$ from S/D lateral diffusion

單位寬度

$$C_{gs(\text{overlap})} = C_{gsol} W$$


$$C_{gd(\text{overlap})} = C_{gdol} W$$

1 fF/ μm

 


C_{gc} vs. V_{gs} and V_{ds}

- C_{gc} vs. V_{gs}

 



- C_{gc} vs. V_{ds}

 


Gate Capacitance vs V_{ds}

- Long-channel device:
 C_{gd} becomes ~ 0 at saturation

  - Short-channel device:
more $C_{gd(\text{overlap})}$ and $C_{gs(\text{overlap})}$ factor



Data-Dependent Gate Capacitance

 


Outline

- Introduction
- Ideal I-V characteristics
- Nonideal Effects
- DC transfer characteristics
- C-V characteristics
- **Switch-level RC delay models**

Effective Resistance R

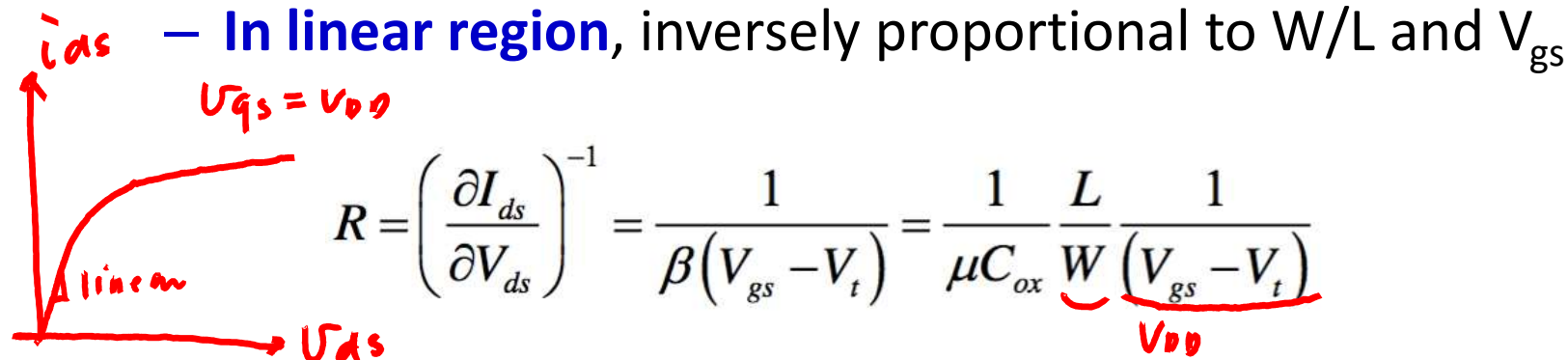
- **R : effective resistance** of unit NMOS (W_{\min} and L_{\min})
 - Unit PMOS has **$2R$** (or **$3R$**) due to lower mobility



- **C : gate capacitance** of unit transistor (NMOS and PMOS)
 - Proportional to gate area $W \cdot L$
- **C : S/D junction capacitance** of unit transistor
 - Proportional to gate width W

RC Circuit Model

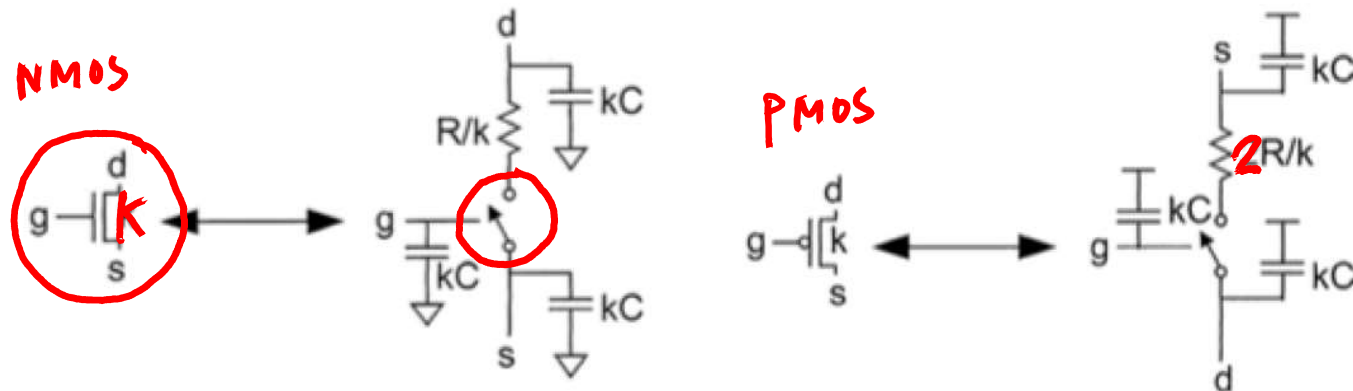- NMOS of k times unit width has resistance of R/k , gate capacitance of kC , and S/D capacitance of kC
 - NMOS parasitic capacitance referenced to GND (p-sub)
- PMOS of k times unit width has resistance of $2R/k$, gate capacitance of kC , and S/D capacitance of kC
 - PMOS parasitic capacitance referenced to V_{DD} (n-well)




Inverter Propagation Delay


- Fanout-of-1 inverter

- Choose PMOS width to be 2x~3x of NMOS width

- $t_{pd} = R(6C) = 6RC$

 

$$V_{out}(0) = V_{DD}$$

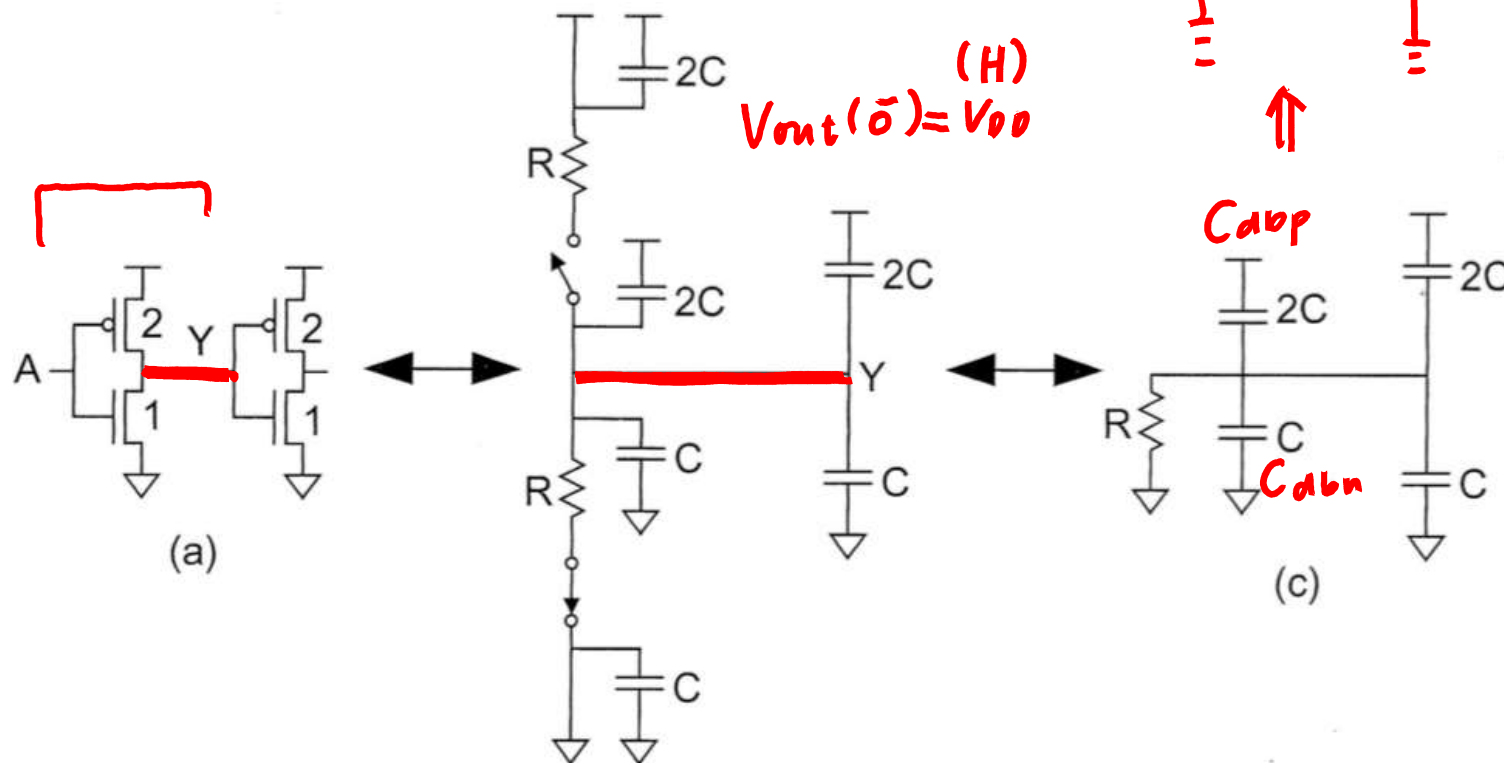

R of Transmission Gate *pass transistor*

- Parallel combination of NMOS and PMOS
 - Depend on signal to pass
 - PMOS pass 0 weakly with larger resistance **$4R$**
 - NMOS pass 1 weakly with larger resistance **$2R$**
 - Usually the same size for NMOS and PMOS
 - Increase size $\rightarrow R \downarrow C \uparrow \rightarrow$ need to check the trade-off

