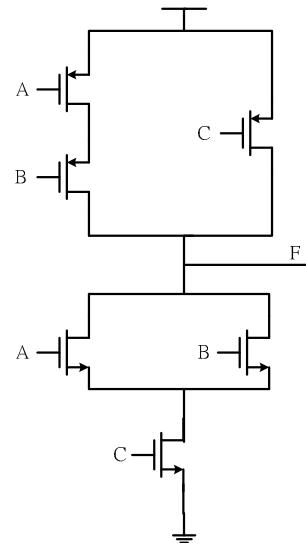



2009 VLSI: Midterm Examination Solution

1.

(a) $F = ((A+B)*C)'$




(b)

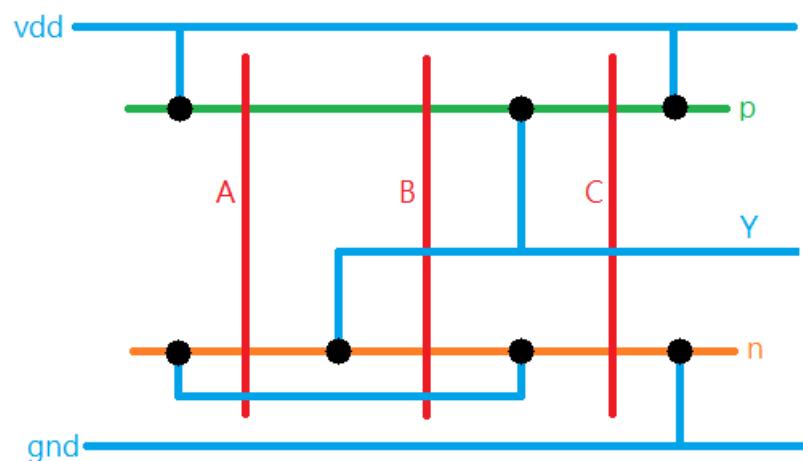


2.

(a) $Y = ((AB + C)^*D)'$

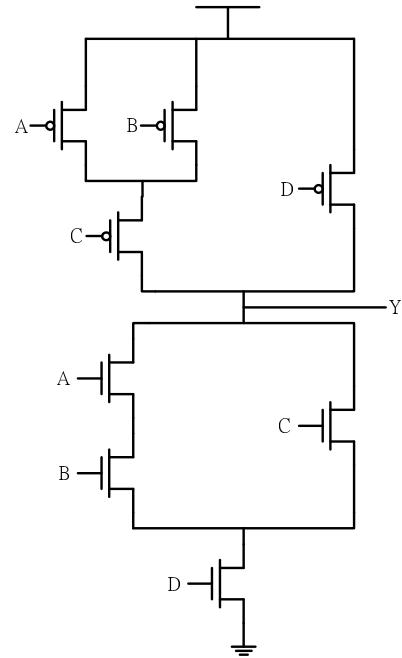

(b) $Y = (AB + C^*(A+B))'$

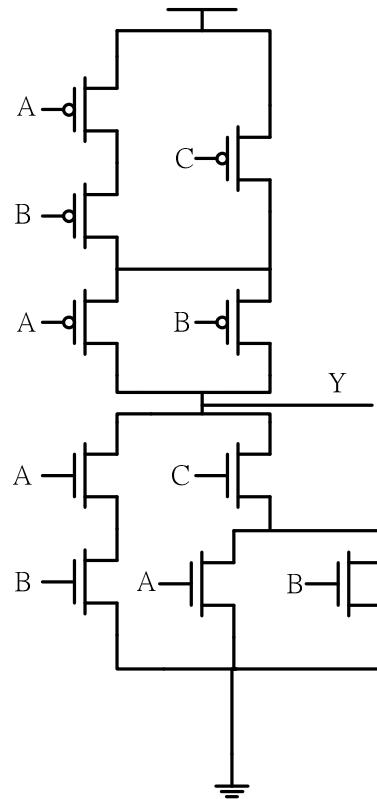

3.

(a) $V_{in}=1.5 \rightarrow 0.3V$; $V_{out}=1 \rightarrow 0.5V$.

(b) $V_{in}=1.5 \rightarrow 0.9V$; $V_{out}=1 \rightarrow 0.9V$.

4.

(a) $\beta=1$.

(b) $\beta_A > \beta_B > \beta_C$.

5.

(a)

$$V_{IL} = 1.0, V_{OL} = 0.2, V_{IH} = 1.3, V_{OH} = 1.6$$

(b)

$$NM_L = V_{IL} - V_{OL} = 1 - 0.2 = 0.8(V)$$

$$NM_H = V_{OH} - V_{IH} = 1.6 - 1.3 = 0.3(V)$$

6.

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t \quad Cutoff \\ \frac{\beta}{2} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{gs} > V_t, V_{ds} < V_{gs} - V_t \quad Linear \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{gs} > V_t, V_{ds} > V_{gs} - V_t \quad Saturation \end{cases}$$

7.

(a)	T	(f)	T
(b)	F	(g)	F
(c)	F	(h)	T
(d)	F	(i)	F
(e)	T	(j)	T

8.


(a)	F	(f)	F
(b)	T	(g)	F
(c)	T	(h)	T
(d)	F	(i)	T
(e)	T	(j)	F

9.

$$C_{gnd} = 0.2 f \frac{F}{\mu m} \times 2000 \mu m = 0.4 pF$$

$$C_{adj} = 0.1 f \frac{F}{\mu m} \times 2000 \mu m = 0.2 pF$$
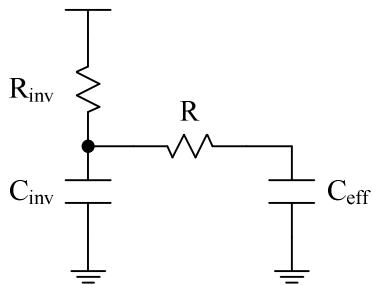
$$R = 0.1 \frac{\Omega}{\mu m} \times 2000 \mu m = 200 \Omega$$



$$t_{cd} \Rightarrow C_{eff} = C_{gnd},$$

$$t_{cd} = R_{inv} C_{inv} + (R_{inv} + R) C_{eff} = 1k \times 5f + 1.2k \times 0.4p = 485ps$$

$$t_{pd} \Rightarrow C_{eff} = C_{gnd} + 2C_{adj},$$

$$t_{pd} = R_{inv} C_{inv} + (R_{inv} + R) C_{eff} = 1k \times 5f + 1.2k \times 0.8p = 965ps$$

10.

$$\text{The path effort} = 14 \times 5 \times 8 = 560$$
$$\hat{f} = \sqrt[4]{560}, D_F = N \times \hat{f} = N \times \sqrt[4]{560}$$

(a)

$$N = 4$$

$$N = 5$$

$$N = 6$$

(b)

$$N = 4, D_F = 4 \times \hat{f} = 4 \times \sqrt[4]{560} = 19.4584$$

$$N = 5, D_F = 5 \times \hat{f} = 5 \times \sqrt[5]{560} = 17.7259$$

$$N = 6, D_F = 6 \times \hat{f} = 6 \times \sqrt[6]{560} = 17.2259$$

11.

(a)

$$F = GBH = 1 \times 1 \times \frac{10p}{20f} = 500$$

$$N = \log_4 F = \log_4 500 = 4.4829$$

let $N = 4$

OR

Find min of $N \sqrt[4]{500}$

$N = 5$ or 6

(b)


$$N = 4, D_F = 4 \sqrt[4]{F} = 4 \sqrt[4]{500} = 18.9148 = 3.78 \times \text{FO4 inverter delay}$$

$$N = 5, D_F = 5 \sqrt[5]{F} = 5 \sqrt[5]{500} = 17.3286 = 3.47 \times \text{FO4 inverter delay}$$

$$N = 6, D_F = 6 \sqrt[6]{F} = 6 \sqrt[6]{500} = 16.9036 = 3.38 \times \text{FO4 inverter delay}$$

12.

(a)

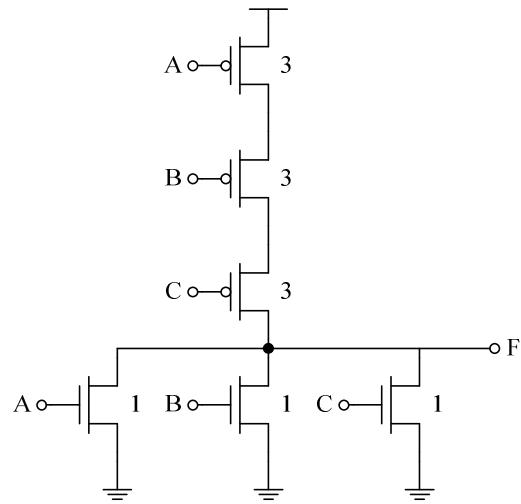

(b)


$$g_u = \frac{3+1}{1+0.5} = \frac{8}{3}$$

$$g_d = \frac{3+1}{2+1} = \frac{4}{3}$$

$$g_{avg} = 2$$

13.

(a)

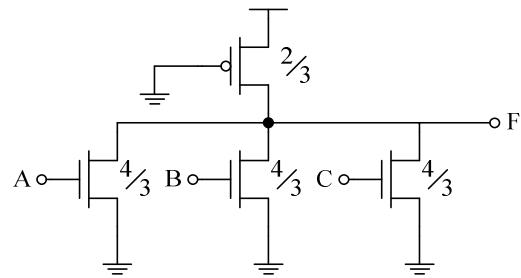


(b)

$$g_u = \frac{\frac{4}{3}}{\frac{2}{3} + \frac{1}{3}} = \frac{4}{3}$$

$$g_d = \frac{\frac{4}{3}}{2+1} = \frac{4}{9}$$

$$g_{avg} = \frac{8}{3}$$

14.

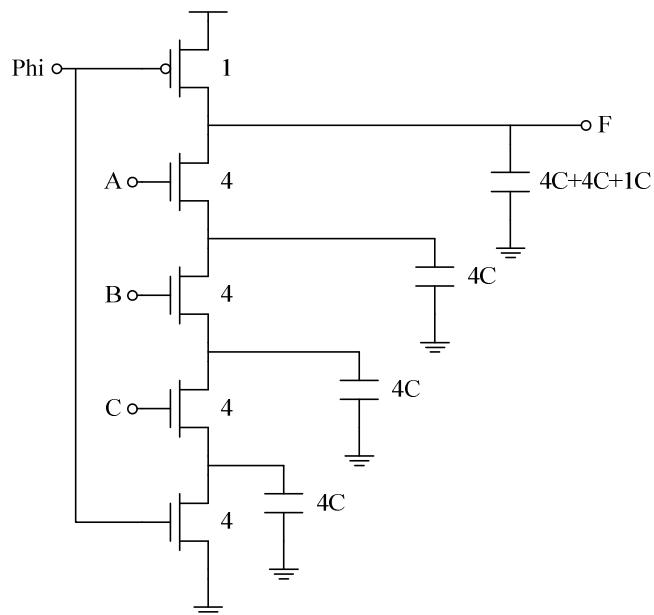

Let V_x be the voltage at node F which is suffered from charge sharing.

The worst charge sharing occurs when:


Pre-charge: $A=B=C=0 \rightarrow$ Evaluation: $A=B=1, C=0$.

$$Q = 9C \times V_{DD} = (9C + 4C + 4C) \times V_x$$

$$\Rightarrow V_x = \frac{9}{17} V_{DD}$$

15.

(a)

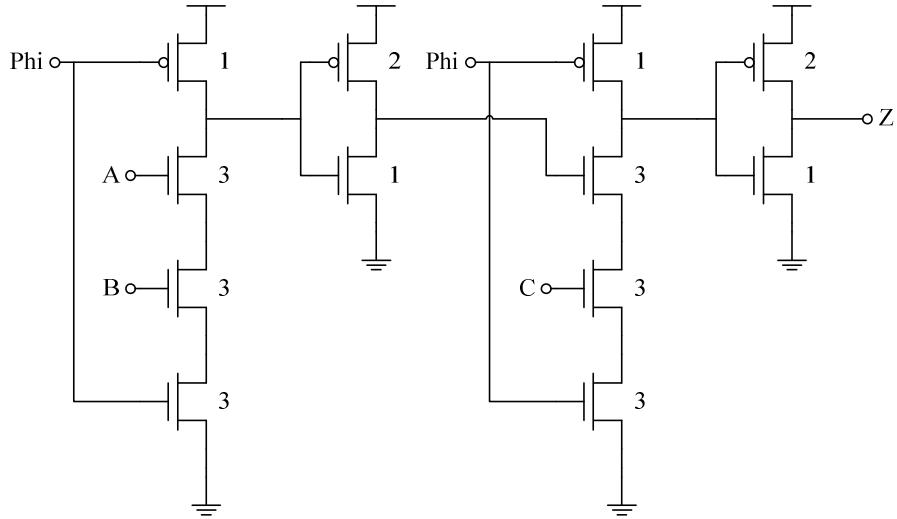

(b)

Loading at Z : $3 \div 10 \times 160 = 48$

$$D_F = \sum f_i = g_1 h_1 + g_2 h_2 + g_3 h_3 + g_4 h_4$$

$$\begin{aligned} D_F &= \frac{3}{3} \times \frac{3}{3} + 1 \times \frac{3}{3} + \frac{3}{3} \times \frac{3}{3} + 1 \times \frac{48}{3} \\ &= 1 + 1 + 1 + 16 = 19 \end{aligned}$$

16.

(a)

$$G = \frac{4}{3} \times \frac{5}{3} \times \frac{5}{3} = \frac{100}{27}$$

$$B = 3 \times 2 = 6$$

$$H = \frac{60}{10} = 6$$

$$F = GBH = \frac{400}{3}$$

$$\hat{f} = \sqrt[3]{F} = 5.1087$$

$$P = 2 + 3 + 2 = 7$$

$$D = 3\hat{f} + P = 22.3262$$

(b)

$$y = \frac{60 \times \frac{5}{3}}{\sqrt[3]{\frac{400}{3}}} = 19.5743$$

$$x = \frac{19.5743 \times 2 \times \frac{5}{3}}{\sqrt[3]{\frac{400}{3}}} = 12.7718$$

$$\text{Size of PMOS of NOR2} : 19.5743 \times \frac{4}{5} = 15.6595$$

$$\text{Size of NMOS of NOR2} : 19.5743 \times \frac{1}{5} = 3.9149$$

$$\text{Size of PMOS of NAND3} : 12.7718 \times \frac{2}{5} = 5.1087$$

$$\text{Size of NMOS of NAND3} : 12.7718 \times \frac{3}{5} = 7.6631$$

17.

(a)	T	(f)	F
(b)	T	(g)	T
(c)	F	(h)	F
(d)	F	(i)	F
(e)	F	(j)	T