

1. Consider the design of a CMOS compound OR-AND-INVERT (OAI21) gate computing $F = \overline{(A+B)} \cdot C$. (5%)

- (a) Sketch the transistor-level schematic. (2.5%)
(b) Sketch the stick diagram. (2.5%)

2. Sketch a transistor-level schematic for a single-stage CMOS logic gate for each of the following functions: (5%)

- (a) $Y = \overline{(AB+C)} \cdot D$ (2.5%)
(b) $Y = \overline{AB+C} \cdot (A+B)$ (2.5%)

3. Suppose $V_{DD} = 1.5V$ and $|V_{tp}| = V_{tn} = 0.5V$. Neglect the body effect, determine V_{out} in Fig. 3 for: (5%)

- (a) $V_{in} = 1.5 \rightarrow 0.3V$. (2.5%)
(b) $V_{in} = 1.5 \rightarrow 0.9V$. (2.5%)

 


Fig. 3

4. Consider the β ratio as β_p/β_n of CMOS inverter transfer characteristics as shown in Fig. 4. (5%)
- (a) Identify the β ratio value of curve B. (2.5%)
(b) Rank the β ratio order of curves A, B, and C. (2.5%)

 


Fig. 4

5. The transfer characteristic of inverter is shown as Fig. 5. (5%)

- (a) Find the V_{IL} , V_{OL} , V_{IH} , and V_{OH} . (3%)
(b) Find the NM_H and NM_L . (2%)

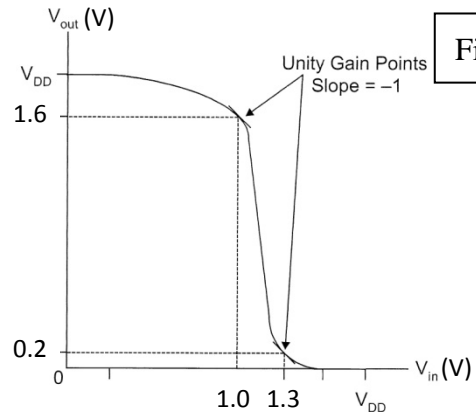


Fig. 5

6. Write down the 3 operation regions of MOS transistor and related ideal I-V equations. (5%)
7. Answer the following questions about MOS characteristics with TRUE or FALSE: (10%)
- (a) C_{gs} is larger than C_{gd} at Saturation. (1%)
(b) C_g (gate capacitance) at Saturation is larger than that at Linear region. (1%)
(c) Source/Drain junction capacitance is proportional to channel area. (1%)
(d) Velocity saturation becomes worse with shorter channel length and lower V_{DD} . (1%)
(e) Mobility degradation is due to the strong vertical electric field from V_{gs} . (1%)
(f) The positive V_{sb} will increase V_t of nMOS. (Body effect) (1%)
(g) Tunneling becomes worse at thinner gate oxide and lower V_{DD} , and it causes gate leakage. (1%)
(h) MOS ON current I_{dsat} is decreased with higher temperature T . (1%)
(i) Junction leakage is worse than subthreshold leakage at modern technology. (1%)
(j) The finite output resistance of MOS at Saturation region is proportional to channel length. (1%)

8. Answer the following questions about MOS process enhancement with TRUE or FALSE: (10%)
- Thinner gate oxide at advanced technology is used to decrease leakage current. (1%)
 - High-K gate dielectric can increase channel charge without thinning gate oxide. (1%)
 - FinFET is used to decrease the subthreshold leakage of advanced transistor. (1%)
 - Silicon-on-Insulator (SOI) can increase device speed, but with higher subthreshold leakage. (1%)
 - SOI is suffered to the floating body voltage (history effect). (1%)
 - Multiple threshold voltage devices need different oxide thickness and are used to provide speed tradeoff. (1%)
 - Copper interconnect development is mainly due to its low parasitic capacitance and thickness. (1%)
 - CMP is used to planarize the inter-layer isolation structure for multi-layer interconnects stacking. (1%)
 - Salicide is used to reduce the S/D and gate resistance. (1%)
 - LDD is used to reduce S/D junction leakage. (1%)
9. Each wire in a pair of 2mm lines has capacitance of $0.2 \text{ fF}/\mu\text{m}$ to ground and $0.1 \text{ fF}/\mu\text{m}$ to its neighbor. The wire resistance is $0.1\Omega/\mu\text{m}$. Each line is driven by an inverter with a $1\text{k}\Omega$ effective resistance and 5fF parasitic capacitance. Find the contamination and propagation delay. (5%)
10. A three-stage logic path is designed so that the effort borne by each stage is 14, 5, 8 delay units, respectively. (5%)
- Find the optimized stage number N . (2.5%)
 - Find the smallest path delay D_F . (2.5%)
11. An output pad contains a chain of successively larger inverters to drive the off-chip 10pF loading capacitance. If the first inverter in the chain has an input capacitance of 20fF , (5%)
- Find the optimized stage number N of inverters. (2.5%)
 - Find the smallest delay $D_F = ?$ FO4 inverter delay (2.5%)
12. Design a 3-input LO-skew NOR gate. Size the devices so that the pull-down is x2 as strong as the pull-up. (5%)
- Sketch and label the transistor widths. (2.5%)
 - Estimate the rising, falling and average logical efforts. (2.5%)
13. Design a pseudo-nMOS 3-input NOR gates. Choose pull-up device size to be $2/3$. (5%)
- Sketch and label the transistor widths. (2.5%)
 - Estimate the rising, falling and average logical efforts. (2.5%)
14. Design a 3-input footed dynamic NAND gate driving an electrical effort of 1. The pull-down transistors' widths are chosen to give unit resistance. Estimate the worst charge sharing noise as a fraction of V_{DD} assuming that diffusion capacitance on uncontacted nodes is about half of gate capacitance and on contacted node it equals gate capacitance. (5%)
15. As shown in Fig. 15, the input loading of A is 10 and output loading of Z is 160 units. (10%)
- Sketch the logic by domino gates and footed dynamic circuits. (5%)
 - Find the path delay (A-Z) D_F . (5%)


 


Fig. 15

16. An example logic path is shown as Fig. 16. The input loading of A is 10 and output loading of B is 60. (10%)

 - (a) Estimate the minimum delay of the path from A to B. (5%)
- (b) Find the transistor sizes (nMOS & pMOS) of each gate. (5%)



17. Answer the following questions about circuit family property with TRUE or FALSE: (10%)

- (a) Pseudo-nMOS can improve the logical effort of static gates. (1%)
- (b) Dynamic circuit is used to decrease static power of pseudo-nMOS. (1%)
- (c) Secondary precharge devices are used to improve speed. (1%)
- (d) HI-skewed gate will favor the pull-down devices. (1%)
- (e) The best P/N ratio for logic gates is 2 to get the lowest average delay. (1%)
- (f) Domino logic is used to provide both true and complementary outputs. (1%)
- (g) Keepers in dynamic logic are used to restore the disturbed output level from leakage. (1%)
- (h) LO-skew inverter is favored in Domino logics. (1%)
- (i) For a multiple input logic, the slower input should be connected to outer node to get smaller delay. (1%)
- (j) Pass transistor logic is suffered from threshold drop and leakage as well. (1%)