
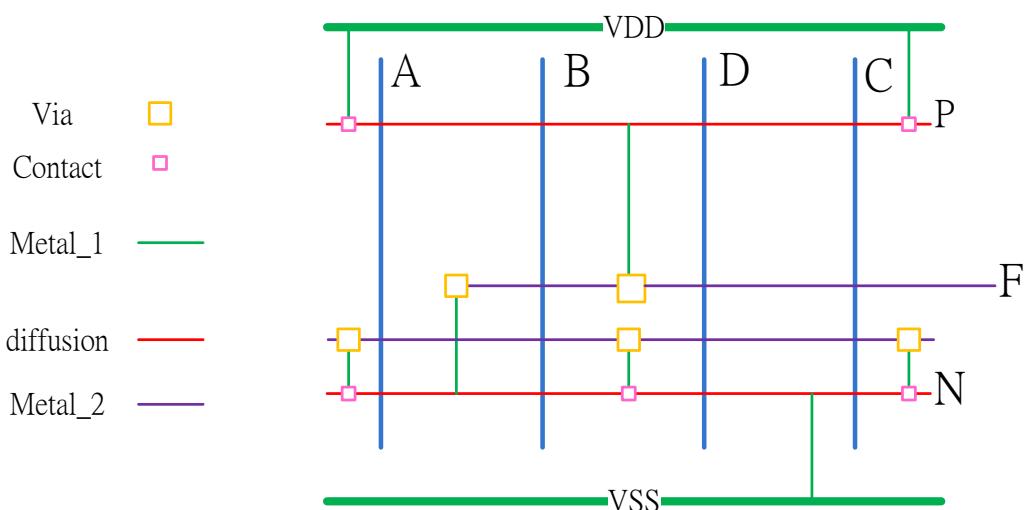


2010 VLSI Solution of Midterm Examination

1.


Ans:

$$F = \overline{(A + B) \cdot (C + D)}$$

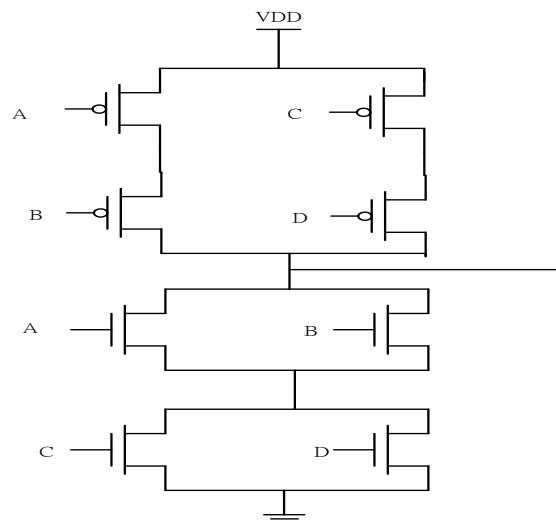

2.


Method(1)

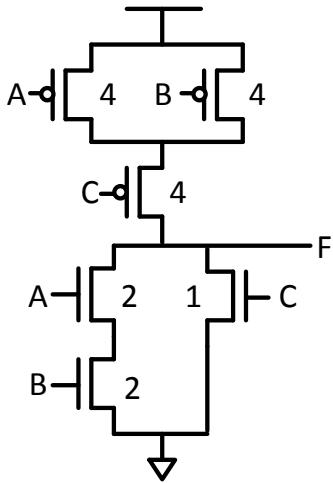

$$(a) g_A = \frac{4+2}{3} = 3, g_B = \frac{4+2}{3} = 3, g_C = \frac{4+1}{3} = \frac{5}{3} \quad (2.5\%, \text{ no partial})$$

$$(b) p = \frac{4+2+1}{3} = \frac{7}{3} \quad (2.5\%, \text{ no partial})$$

Method(2)

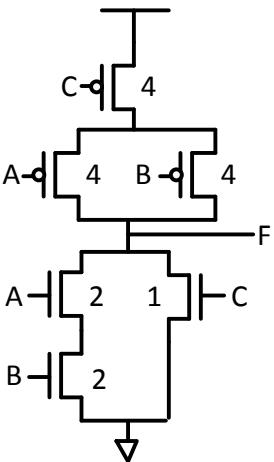

$$(a) g_A = \frac{4+2}{3} = 3, g_B = \frac{4+2}{3} = 3, g_C = \frac{4+1}{3} = \frac{5}{3} \quad (2.5\%, \text{ no partial})$$


$$(b) p = \frac{4+4+2+1}{3} = \frac{11}{3} \quad (2.5\%, \text{ no partial})$$

3.

(a) 2.5%

Ans: $(W/L)p = 6\mu m/0.18\mu m$

(b) 2.5% (one correct: 1.5%)

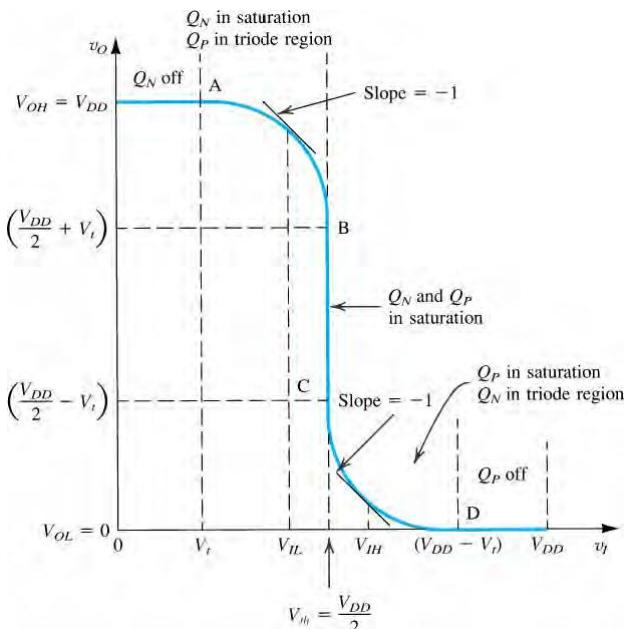

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

$$(V_{OH})A = (V_{OH})B = (V_{OH})C$$

$$(V_{OL})A = (V_{OL})B = (V_{OL})C$$

and

$$(V_{IH})A < (V_{IH})B < (V_{IH})C$$

$$(V_{IL})A > (V_{IL})B > (V_{IL})C$$

Therefore


Ans:

$$NM_H: A < B < C$$

$$NM_L: A > B > C$$

4.

Ans:

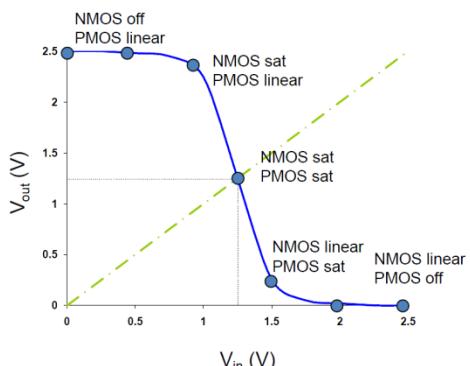

Region	nMOS	pMOS
A	cutoff	linear
B	Sat.	linear
C	Sat.	Sat.
D	linear	Sat.
E	linear	cutoff

5.


Ans:

i,d,j,b,c,f,a,l,g,h,k,m

6.

Ans:

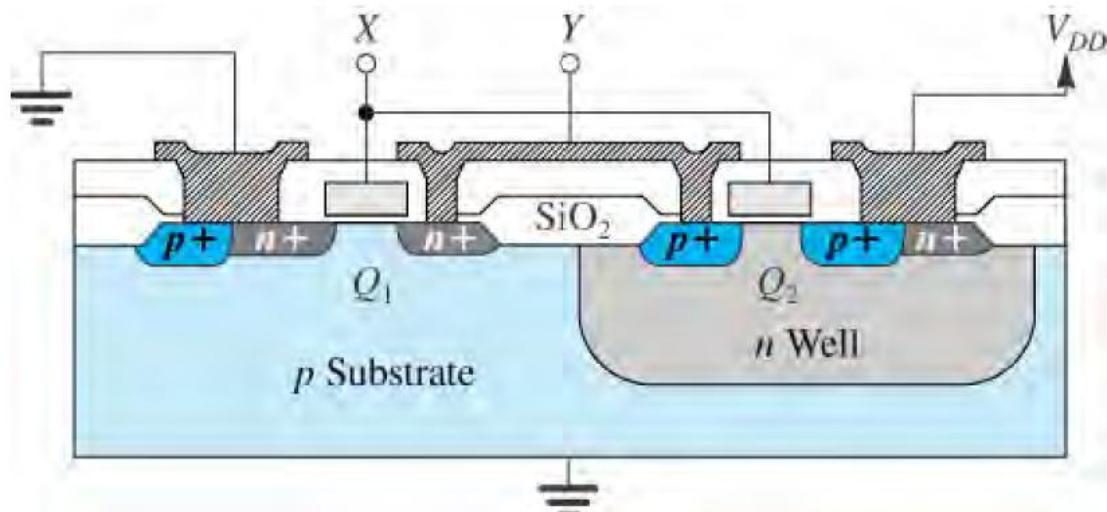(a) (v) \rightarrow (i) \rightarrow (ii) \rightarrow (iii) $=$ (iv) \rightarrow (vii) \rightarrow (vi) (2.5% , no partial)



(b)

(2.5% , no partial)

7.

Initial value: $V_{out1}=V_{out2}=0V$

Ans:

(a) 2.5% v

$$V_{out1} = 0 \rightarrow 1V$$

$$V_{out2} = 0 \rightarrow 0.5V$$


(b) 2.5% (one correct: 1.5%)

$$V_{out1} = 0 \rightarrow 0.9V$$

$$V_{out2} = 0 \rightarrow 0.4V$$

8.

Ans:

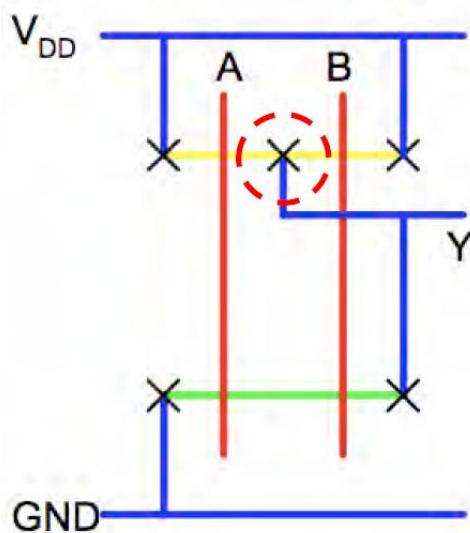

9.

Ans:

(a)

$$d = gh + p = 2$$

$$f_{osc} = \frac{1}{2Nd'} = \frac{1}{2 \times 9 \times 2 \times 1k \times 10f} = 2.778G \text{ (Hz)}$$

(b)


Unit inverter $g_{avg}=1$

Skewed inverter $g_{avg}=\frac{5}{4}$

$$f_{osc} = \frac{1}{2Nd} = \frac{1}{2 \times 9 \times 2 \times 1k \times 10f \times \frac{5}{4}} = 2.22G \text{ (Hz)}$$

10.

Ans:

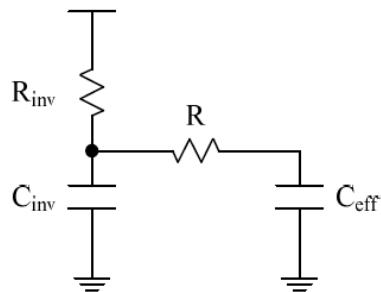

$$R_{inv} = 1k, \quad C_{inv} = 10f$$

$$R = \frac{0.1}{um} * 1mm = 100ohm$$

$$C_{gd} = \frac{0.3f}{um} * 1mm = 0.3pF,$$

$$C_{adj} = \frac{0.2f}{um} * 1mm = 0.2pF$$

a) For X=0->1, Y=0->1, $C_{eff} = C_{gnd}$


$$Tpd = R_{inv} * C_{inv} + (R + R_{inv}) * C_{eff} = 340ps$$

b) For X=1->0, Y=0->1, $C_{eff} = C_{gnd} + 2C_{adj}$

$$Tpd = R_{inv} * C_{inv} + (R + R_{inv}) * C_{eff} = 780ps$$


11.

(a)

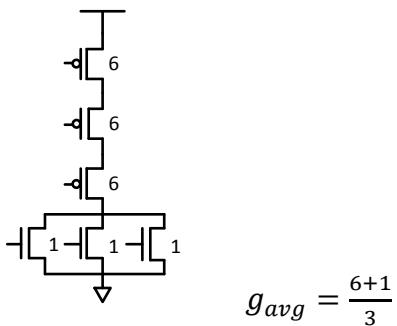


(b)


Method(1)

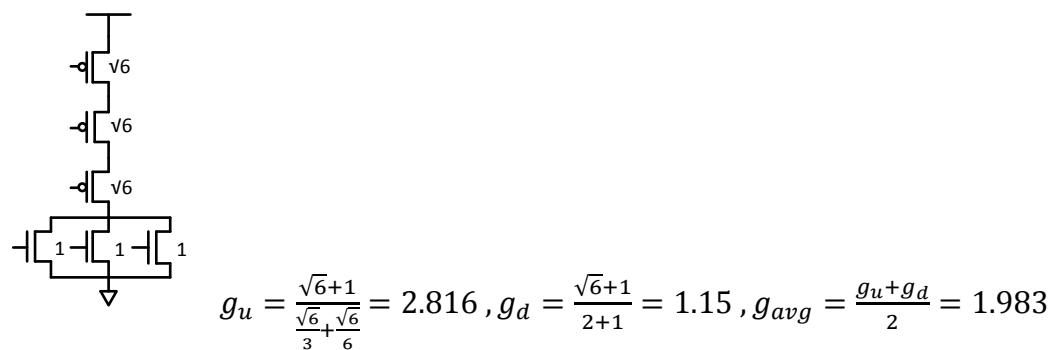

Method(2)

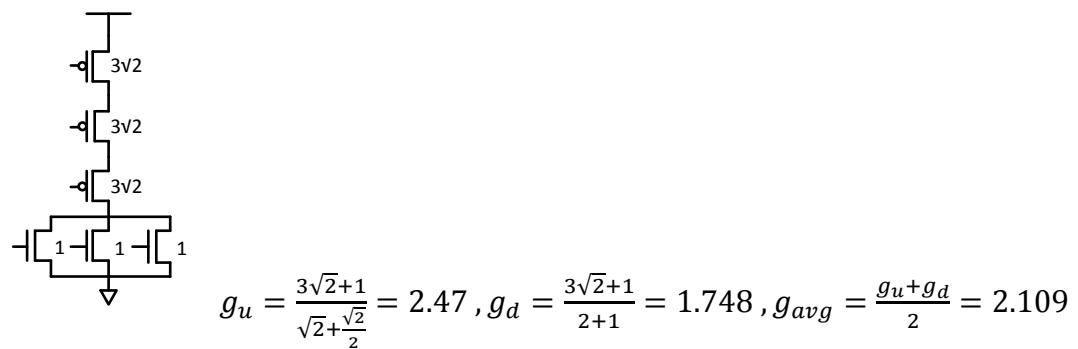

Method(3)

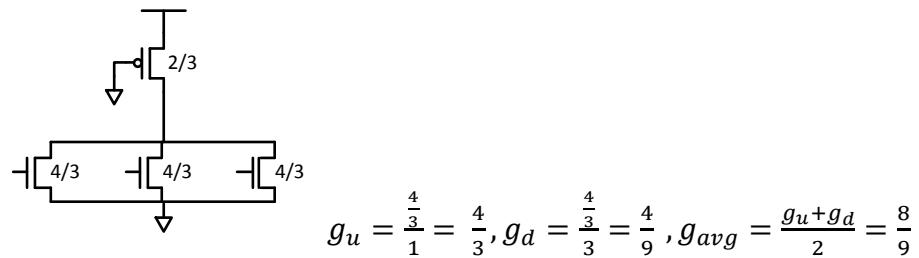


12.

Due to the defect of the question, you can get the score for following computation:

Method 1.

(a) 2.5%

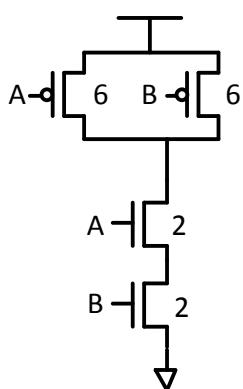

Ans: (gu: 1%, gd: 1%, gavg: 0.5%)

$$gu = \frac{6+2}{6+3} = \frac{8}{9}$$

$$gd = \frac{6+2}{2+1} = \frac{8}{3}$$

$$gavg = \frac{\frac{8}{9} + \frac{8}{3}}{2} = \frac{16}{9}$$

(b) 2.5%

Ans. 1:

Because of resizing A to $\frac{5}{6}$, then resistance of A is $\frac{6}{5}R$, which is larger than the original R

∴ we can't get the correct size of B for keeping the resistance as the same as original.


Ans. 2:

Under the condition of keeping the pull-down resistance the same, we need to minimize the effect of B. Therefore we have to resize B as big as possible for over large size of A, which is resized to bigger than the effective pull-down resistance R from the request of (b).

You can get the score for similar answers above.

Method 2.

(a)

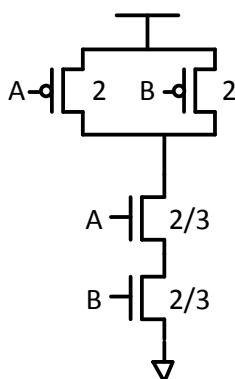

Ans: (gu: 1%, gd: 1%, gavg: 0.5%)

$$gu = \frac{2 + \frac{2}{3}}{2 + 1} = \frac{8}{9}$$

$$gd = \frac{2 + \frac{2}{3}}{\frac{1}{3} + \frac{2}{3}} = \frac{8}{3}$$

$$gavg = \frac{\frac{8}{9} + \frac{8}{3}}{2} = \frac{16}{9}$$

(b)

Ans: (WB: 1.5%)

$$\frac{1}{\frac{6}{5} + \frac{1}{WB}} = \frac{1}{3}$$

$$\rightarrow WB = \frac{5}{9}$$

∴ Ans: (guA & gdA: 1% OR guB & gdB: 1%)

$$guA = \frac{2 + \frac{5}{6}}{2 + 1} = \frac{17}{18}$$

$$guB = \frac{2 + \frac{5}{9}}{2 + 1} = \frac{23}{27}$$

$$gdA = \frac{2 + \frac{5}{6}}{\frac{1}{3} + \frac{2}{3}} = \frac{17}{6}$$

$$gdB = \frac{2 + \frac{5}{9}}{\frac{1}{3} + \frac{2}{3}} = \frac{23}{9}$$

You can get the score for either guA & gdA or guB & gdB.

13.

a) $D = NF^{1/N} + \sum_{i=1}^{n1} Pi + (N - n1)Pinv$


b) $\frac{dD}{dN} = -F^{1/N} \ln F^{1/N} + F^{1/N} + Pinv = 0 \quad \text{and } \rho = F^{1/N}, Pinv = 1$

Thus, the above equation can be rewritten to

$Pinv + \rho(1 - \ln \rho) = 0$, and plug in $Pinv = 1$, we can find that $\rho = 3.59$


14.

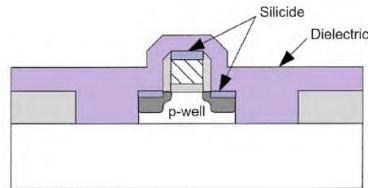(a) Salicide: self-aligned silicide Refractory metal to reduce the interconnection




resistance of gate, source/drain.

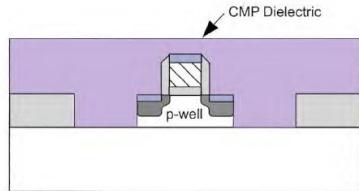(b) CMP : Structure planarization for further stack process.




(c) High-K: Replacing the silicon dioxide gate dielectric with a high- κ material allows increased gate capacitance without the concomitant leakage effects,(thinner EOT)

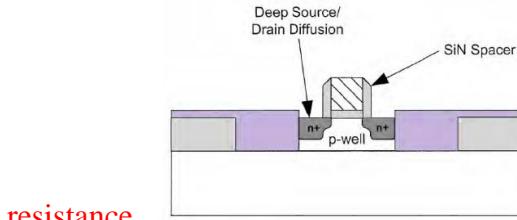(d) LDD: Reduce electrical field of drain junction & hot-electron damage; High sheet



resistance.

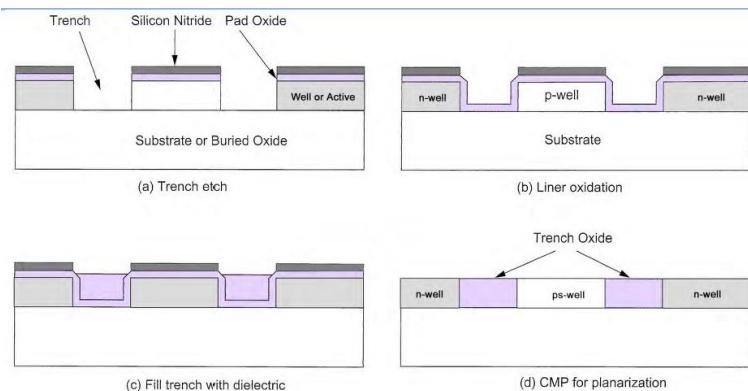(e) STI: Shallow Trench Isolation High density & better isolation, need Chemical Mechanical Polishing (CMP) to planarize the structure.(without bird's beak(LOCOS))



(get 1% when match one red-mark, 2% max)

15.

(a) 5%

Find gavg:

$$gu = \frac{\frac{4}{3}}{\frac{2}{3} + \frac{1}{3}} = \frac{4}{3}$$

$$gd = \frac{\frac{4}{3}}{2+1} = \frac{4}{9}$$

$$gavg = \frac{\frac{4}{3} + \frac{4}{9}}{2} = \frac{8}{9}$$

Find pavg:

$$pu = \frac{8 \times \frac{4}{3} + \frac{2}{3}}{\frac{2}{3} + \frac{1}{3}} = \frac{34}{3}$$

$$pd = \frac{8 \times \frac{4}{3} + \frac{2}{3}}{2+1} = \frac{34}{9}$$

$$pavg = \frac{\frac{34}{3} + \frac{34}{9}}{2} = \frac{68}{9}$$

Find path delay:

$$G = 1 \times \frac{8}{9} = \frac{8}{9}$$

$$F = GBH = \frac{8}{9} \times 1 \times \frac{64}{4}$$

$$P = 1 + \frac{68}{9} = \frac{77}{9}$$


$$N = 2$$

$$D = 2 \times \sqrt{\frac{128}{9}} + \frac{77}{9} = \frac{77 + 48\sqrt{2}}{9} = 16.1$$

Ans: 16.1 (Time Unit)

(b.) 5%

Ans 1:

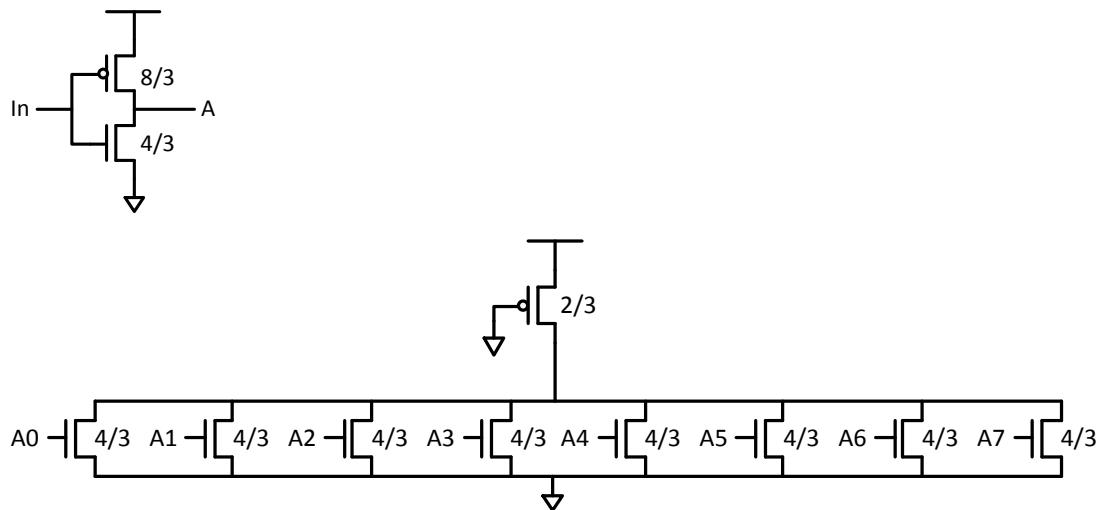


Ans 2:

$$f = \sqrt{F} = \sqrt{\frac{128}{9}} = gh = \frac{8}{9} \times \frac{64}{x}$$

$$\rightarrow x = 15.085$$

$$\text{PMOS: } 15.085 \times \frac{\frac{2}{3}}{\frac{2}{3} + \frac{4}{3}} = 5.028$$
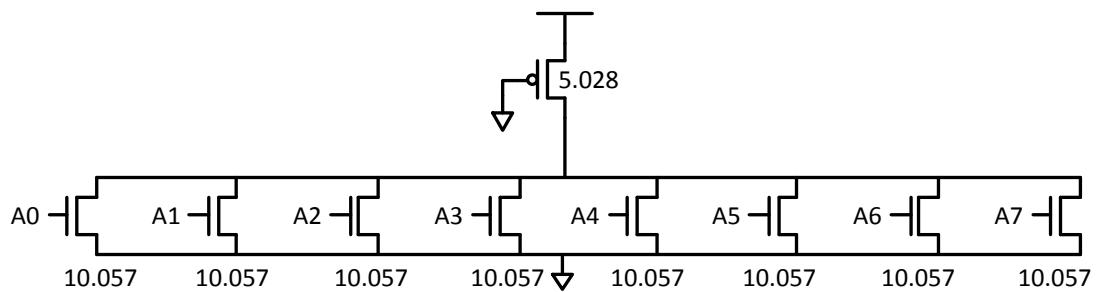
$$\text{NMOS: } 15.085 \times \frac{\frac{4}{3}}{\frac{2}{3} + \frac{4}{3}} = 10.057$$



16.

Ans:

(a)

A → C

$$G = \left(\frac{4}{3}\right) \times \left(\frac{5}{3}\right) \times \left(\frac{7}{3}\right) = \frac{140}{27}$$

$$H = \frac{80}{8} = 10$$

$$B = 3 \times 2 = 6$$

$$F = G \times H \times B = \frac{2800}{9}$$

$$\hat{f} = \sqrt[3]{F} = 6.776$$

$$\therefore y = \frac{80 \times \frac{7}{3}}{6.776} = 27.55, x = \frac{27.55 \times 2 \times \frac{5}{3}}{6.776} = 13.55$$

B→D

$$G = 1 \times 1 \times \left(\frac{5}{3}\right) \times \left(\frac{5}{3}\right) = \frac{25}{9}$$

$$H = \frac{80}{3}$$

$$B = 2 \times 2 = 4$$

$$F = G \times H \times B = \frac{8000}{27}$$

$$\hat{f} = \sqrt[4]{F} = 4.149$$

$$\therefore z = \frac{80 \times \frac{5}{3}}{4.149} = 32.14, x = \frac{32.14 \times 2 \times \frac{5}{3}}{4.149} = 25.82, w = \frac{25.82 \times 2 \times 1}{4.149} = 12.45$$

Ps: 此題題意有瑕疵，若先算 A→C 者，只要 x、y 答對就全對；反之，若先算 B→D 者，z、x、w 答對亦可。

(b)

A→D

$$G = \left(\frac{4}{3}\right) \times \left(\frac{5}{3}\right) \times \left(\frac{5}{3}\right) = \frac{100}{27}$$

$$H = 10, B = 6$$

$$F = \frac{2000}{9}$$

$$\hat{f} = 6.06$$

$$P = 2 + 3 + 2 = 7$$

$$D = 3 \times 6.06 + 7 = 25.18$$

PS: 若利用 A 小題的 X 值帶入此題求出 D，亦可。

17.

Ans:

- (a) F (b) F (c) T (d) T (e) T (f) T (g) F (h) F (i) T (j) T