

1. Consider a dynamic logic (NADN2) as shown in Fig. 1. Assume the  $C_a = C_b = 10\text{fF}$ ,  $C_L = 20\text{fF}$ ,  $C_{gs}(C_{gd})$  of  $M_p = 5\text{fF}$ , and  $V_{DD} = 1.8\text{V}$ . (8%)

- Identify nodes and explain the leakage issue in this circuit and provide the solution add-on circuit. (2%)
- When  $\text{CLK} = 0$ ,  $A = B = 0$ , assume all the charge on  $C_a$  and  $C_b$  are 0. Then,  $\text{CLK} = 0 \rightarrow 1$ , find the voltage  $V_{\text{out}}$ . (2%)
- Continue with (b), then  $B = 0$ ,  $A = 0 \rightarrow 1$ . Find the voltage  $V_{\text{out}}$ . (2%)
- When cascading two identical dynamic NAND2 as shown in Fig. 1 together, explain the possible error issue and solution. (2%) (Hint: monotonic issue)

 


Fig. 1

2. Assign the correct relative timing definition of  $t_A \sim t_L$  in Fig. 2 based on table 1. (12%)

1	$t_{pd}$	Logic Prop. Delay
2	$t_{cd}$	Logic Cont. Delay
3	$t_{pcq}$	Latch/Flop Clk-Q Prop Delay
4	$t_{ccq}$	Latch/Flop Clk-Q Cont. Delay
5	$t_{pdq}$	Latch D-Q Prop Delay
6	$t_{pcdq}$	Latch D-Q Cont. Delay
7	$t_{\text{setup}}$	Latch/Flop Setup Time
8	$t_{\text{hold}}$	Latch/Flop Hold Time

Table. 1

 


Fig. 2

3. A sequential circuit as shown in Fig. 3. Assume the period of  $\text{clk} = T$ , max clk-to-q delay of  $F1 = T_{\text{preg}}$ , min clk-to-q delay of  $F1 = T_{\text{cdreg}}$ , the maximum-delay of combinational logic =  $t_{\text{plogic}}$  and the minimum delay =  $t_{\text{cdlogic}}$ . (5%)

- Write the setup time equation. (2.5%)
- Write the hold time equation. (2.5%)

 


Fig. 3

4. Consider the sequential circuit as shown in Fig. 4. Assume period of  $\phi_1 = \phi_2 = 100\text{ns}$ ,  $t_{pdq1} = t_{pdq2} = 10\text{ns}$ ,  $t_{ccq1} = t_{ccq2} = 6\text{ns}$ ,  $t_{\text{nonoverlap}} = 5\text{ns}$  and the clock skew =  $2\text{ns}$ . (5%)

- Find the maximum delay  $t_{pd} = t_{pd1} + t_{pd2}$  with and without clock skew. (2.5%)
- Find the minimum delay  $t_{cd} = \min(t_{cd1}, t_{cd2})$  with and without clock skew. (2.5%)


 



Fig. 4

 



5. Design a 2-phase clock generator. (5%)

(a) Sketch the schematic. (3%)

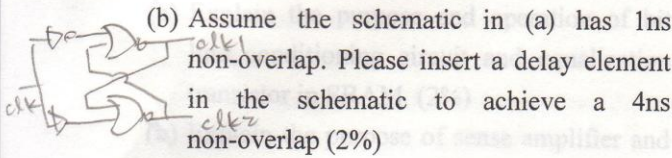


6. Consider a full adder with inputs A and B; carry-in  $C_{in}$ , sum S, and carry-out  $C_{out}$ . (10%)

(a) Write the Boolean expressions of sum S and carry-out  $C_{out}$ . (4%)

(b) Write the Boolean expression of Generate (G) and Propagate (P) signals. (4%)

 (c) Factor S in terms of A, B,  $C_{in}$  and  $C_{out}$ . Write the Boolean expressions of S. (2%)



7. Consider the implementation of four 4-bit words summation. (5%)

(a) Use 4-bit carry-ripple adders (CRA) only to implement the summation, how many CRA is needed. (2%)

(b) Use carry-save adder (CSA) and CRA to implement the summation, sketch the block diagram. (3%)

8. A pass transistor logic is implemented as shown in Fig. 8 with  $V_{DD} = 1.2V$  and  $|V_{tp}| = |V_{tn}| = 0.5V$ . The inverter ( $M_1$  &  $M_2$ ) has  $V_{IL} = 0.2V$  and  $V_{IH} = 1.0V$ . Ignore the body effect. (5%)

(a)  $A = 0 \rightarrow 1.2V$ , find  $V_x = ?$ ,  $V_{out} = ?$ . (2%)

(b) Adding a restorer to recover the level  $V_x$  to full swing, and assume  $R_{on}(M_n) = 100\Omega$ , design the minimum  $R_{on}$  of restorer to avoid logic 1 fail at  $V_{out}$ . (3%)

 


Fig. 8

9. Consider the 6T SRAM cell in Fig. 10. (5%)

(a) Explain the read-disturb behavior (in read operation) and index the cell ratio design concern to overcome it. (2.5%)

(b) Based on the design concern in (a), explain the pull-up ratio design concern to get a correct write operation. (2.5%)

 


Fig. 10

10. Answer the following questions about Clock Distribution & Testing with TRUE or FALSE: (10%)

(a) Jitter is due to process variation and can be solved by one-time calibration. (1%)

(b) Clock skew can be reduced by careful clock distribution, skew tolerant design and calibration. (1%)

(c) Grid type clock distribution is suffered at delay mismatch of local near points from different tree. (1%)

(d) Skew-tolerant domino logic is proposed by replacing flip-flops with latches. (1%)

(e) Design for test = design circuit to increase fault observability and controllability. (1%)

(f) Boundary Scan test can be used to reduce the probe contacts at board-level test. (1%)

(g) Design for manufacturability is the design concern try to increase chip yield. (1%)

(h) JTAG is a protocol for chip level test. (1%)

(i) PRSG is usually used to implement the BIST function of IC. (1%)

(j) Fault coverage is the index of yield information of IC manufacturing. (1%)



11. Answer the following questions about Memory: (10%)

- (a) Explain the purpose and operation of bit line conditioning circuit and equalization transistor in SRAM. (2%)
- (b) Explain the purpose of sense amplifier and isolation transistor. (2%)
- (c) For a 1T1R1C DRAM cell, assume the bit line is precharged to  $V_{DD}/2$ , the cell capacitance is 100fF, and the bit line capacitance is 1pF. Find the data 0 and 1 voltage level on bit line during readout with  $V_{DD} = 3.3V$ . (2%)
- (d) Write down two common methods to improve the yield of memory. (2%)
- (e) What's the 4x4 code in the ROM as shown in Fig. 9. (2%)

 


Fig. 9

12. Answer the following questions about Datapath Subsystems (10%)

- (a) Logic levels, fan-in and wiring track are the 3 design-tradeoff corner parameters of tree adder. (T or F) (1%)
- (b) Order the speed of the following adders: [1] Carry-lookahead [2] Carry-select [3] Carry-ripple [4] Carry-skip. (1%)
- (c) Group P & G signals in adder are used to reduce the delay of carry propagation. (T or F) (1%)
- (d) The critical path of an multi-bit adder is usually the summation propagation. (T or F) (1%)

- (e) Booth encoding is used to solve the glitch problem in decoder. (T or F) (1%)
- (f) Subtraction can be implemented by 2's complement as the following equation:  $A - B = A + \bar{B} + 1$  (T or F) (1%)
- (g) Gray code is a common skill for error correction. (T or F) (1%)
- (h) If we shift "Right" a word 1011 to get 0101, what kind of shifter is implemented? [1] Arithmetic [2] Logic [3] Rotate. (1%)
- (i) MxN-bit multiplication will produce N-1 M-bit partial products. (T or F) (1%)
- (j) If carry generation is the slowest path in the CSA cell in Fig. 12. Identify the critical path of this multiplier. (1%)

 



Fig. 12

13. An output pad contains a chain of successively larger inverters to drive the off-chip 40pF loading capacitance. If the first inverter in the chain has an input capacitance of 10fF, (5%)
- (a) Find the optimized stage number  $N$  of inverters. (2.5%)
- (b) Find the smallest delay  $D_F = ?$  FO4 inverter delay (2.5%)




14. A ring oscillator composed of  $N$ -stages identical inverter is as shown in Fig. 9. Assume the effective resistance of an unit inverter (P:2, N:1) is  $200\Omega$  and parasitic capacitance is  $5\text{fF}$ . (5%)

 - (a)  $N = 5$ , find the oscillated frequency. (2.5%)  
 (b) Use skewed inverter and find the oscillated frequency. (2.5%)



Unit inverter

 

Skewed inverter

 


Fig. 9

15. Sketch the transistor-level schematic of the gate computing  $F = (A + B) \cdot C$ : (5%)

- (a) Find logical effort  $g_A$ ,  $g_B$ , and  $g_C$ . (2.5%)  
 (b) Find parasitic delay  $p$ . (2.5%)

16. There are 2 adjacent wires X and Y. Each wire in a pair of  $2\text{mm}$ -lines has capacitance of  $0.4\text{fF}/\mu\text{m}$  to ground and  $0.6\text{fF}/\mu\text{m}$  to its neighbor. The wire resistance is  $0.2\Omega/\mu\text{m}$ . Each line is driven by an inverter with a  $1\text{k}\Omega$  effective resistance and  $20\text{fF}$  parasitic capacitance. Use L-model to find the propagation delay of X line with the following conditions. (5%)

- (a)  $X=0 \rightarrow 1$ ,  $Y=0$ . (2.5%)  
 (b)  $X=0 \rightarrow 1$ ,  $Y=1 \rightarrow 0$ . (2.5%)

$t_{\text{ccq}}$	Latch/Flop Clk-Q Cont Delay
$t_{\text{pdq}}$	Latch D-Q Prop Delay
$t_{\text{cdq}}$	Latch D-Q Cont. Delay
$t_{\text{setup}}$	Latch/Flop Setup Time
$t_{\text{hold}}$	Latch/Flop Hold Time

Table 1

17. Design a 6-input ( $k=6$ ) AND gate using inverter and pseudo-nMOS NOR gates as shown in Fig. 17. Choose pull-up device size to be  $2/3$  and the output loading  $H = 60$ . (10%)

- (a) Find the path delay. (5%)  
 (b) Sketch and label the transistor widths. (5%)

 


Fig. 17

Fig. 2

A sequential circuit as shown in Fig. 3. Assume the period of  $\text{clk} = T$ , max clk-to-q delay of  $F1 = T_{\text{prop}}$ , min clk-to-q delay of  $F1 = T_{\text{setup}}$ , the maximum delay of combinational logic =  $t_{\text{max}}$ , and the minimum delay =  $t_{\text{min}}$ . (5%)

- (a) Write the setup time equation. (2.5%)  
 (b) Write the hold time equation. (2.5%)

Consider the sequential circuit as shown in Fig. 4. Assume period of  $\phi_1 = \phi_2 = 100\text{ns}$ ,  $t_{\text{setup}} = t_{\text{hold}} = 10\text{ns}$ ,  $t_{\text{ccq}} = t_{\text{cdq}} = 0\text{ns}$ ,  $t_{\text{pdq}} = 5\text{ns}$  and the clock skew =  $2\text{ns}$ . (5%)

- (a) Find the maximum delay  $t_{\text{pd}} = t_{\text{pd1}} + t_{\text{pd2}}$  with and without clock skew. (2.5%)  
 (b) Find the minimum delay  $t_{\text{pd}} = \min(t_{\text{pd1}}, t_{\text{pd2}})$  with and without clock skew. (2.5%)



Fig. 4