

2011 VLSI Final Exam Solution

2012/1/12

1.

(a)

$$t_{su} = 10\text{ns}$$

(b)

$$t_{pcq} = 6\text{ns}$$

2.

(a.) 2.5%


Race condition – direct path from D to Q during the short time when both clk and !clk are high (1-1 overlap)

(b.) 2.5%

Dynamic storage – when clk and !clk are both low (0-0 overlap)

3.

(a.) 3%

 

(b.) 2% Delay chain 為 buffer (2N 個 inverter)

4.

(a)

$$\begin{aligned} t_{pd} &\leq T_c - \max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw}) \\ &= 10n - \max(4n, 2n + 0.5n - 4n) \\ &= 10n - 4n \\ &= 6n \text{ (s)} \end{aligned}$$

(b)

$$\begin{aligned} t_{pd} &\leq T_c - \max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw}) \\ &= 10n - \max(4n, 2n + 0.5n - 2n) \\ &= 10n - 4n \\ &= 6n \text{ (s)} \end{aligned}$$

5.

(a)

$$T_{\text{nonoverlap}} \geq 4\text{ns}$$

(b)

$$T_{\text{pd}} \leq 8\text{ns}$$

(skew tolerance)

6.

(a)

$$t_{\text{pw}} = 2\text{ns}$$

$$t_{\text{nonoverlap}} = \frac{T_c}{2} - t_{\text{pw}} = 10\text{ns} - 2\text{ns} = 8\text{ns}$$

$$t_{\text{cd1}}, t_{\text{cd2}} \geq t_{\text{hold}} - t_{\text{ccq}} - t_{\text{nonoverlap}} + t_{\text{skew}}$$

$$t_{\text{hold}} \geq t_{\text{ccq}} + t_{\text{nonoverlap}} - t_{\text{skew}} + t_{\text{cd1}}, t_{\text{cd2}}$$

$$t_{\text{hold}} \leq 1.5\text{ns} + 8\text{ns} - 2\text{ns} + 4\text{ns} = 11.5\text{ns}$$

(b)

$$t_{\text{cd1}}, t_{\text{cd2}} \geq t_{\text{hold}} - t_{\text{ccq}} - t_{\text{nonoverlap}} + t_{\text{skew}}$$

$$t_{\text{skew}} \leq t_{\text{cd1}}, t_{\text{cd2}} - t_{\text{hold}} + t_{\text{ccq}} + t_{\text{nonoverlap}} \\ = 4\text{ns} - 1\text{ns} + 1.5\text{ns} + 8\text{ns} = 12.5\text{ns}$$

7.

(a)

$$S = A \oplus B \oplus C_{\text{in}}$$

$$C_{\text{out}} = AB + BC_{\text{in}} + C_{\text{in}}A$$

(b)

$$S = P \oplus C_{\text{in}}$$

$$C_{\text{out}} = G + PC_{\text{in}}$$

8.

(a) 參見講義 Chapter 7-32 頁

(b) 參見講義 Chapter 7-36 頁


(c) 參見講義 Chapter 7-28 頁

(d) Speed: (b) > (a) > (c)


(e) 參見講義 Chapter 7-28、32、36 頁，畫出任一即給分

9.

(a) 5%

 


(b) 5%

 

10.

(a)(b)

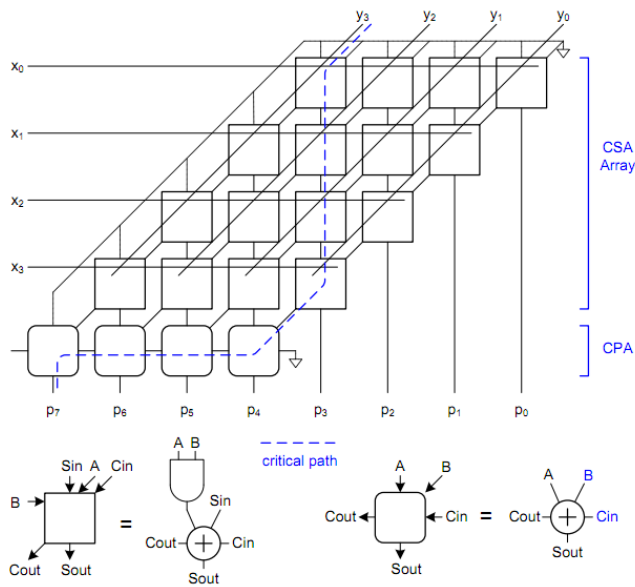

1.5%

2.5%

$$\text{Delay} = 4(C_{in} - C_{out}) + 4(S_{in} - S_{out}) = 36\text{ns} (1\%)$$

11.

(a) 01100 (2.5%)

(b) 11100 (2.5%)

12.

(a)

Assuming $\bar{Q}=0$ and $Q=1$. During read operation, there will be a voltage divider at \bar{Q} , which causes the \bar{Q} voltage increasing. Therefore, the ratio of $M1/M5$ and $M3/M6$ should be much larger than 1.

(b)

During write operation, $M4(M2)$ and $M6(M5)$ are fighting. To make sure of correct write operation, $M6(M5) \gg M4(M2)$.

13.

(a)

precharge bitline to V_{DD}

(b)

sense small voltage difference between two bitlines

14.

(a) $V_0=0.8571 \approx 0.86$

$V_1=0.9429 \approx 0.94$ (1.5% \rightarrow 2.5%)

(b)

1. Double the C_{cell} . (use trench)
2. Halve the $C_{bitline}$. (reduce the cell number in one line)
3. Double the V_{DD} . (any two get 2.5%)

15.

(a)

Try to couple noise equally onto bit and bit_b, and hence reduce the noise effect.

(b)

Equalize bitlines to minimize voltage difference between bit and bit_b when using sense amplifier.

(c)

To cut off large bitline capacitance.

(d)

(1)redundancy cell.

(2)ECC.

(3)built in self test (BIST).

(e)

010101

011001

100101

101010

16.

(a)

N=4

(b)

fi=4

D=20

17.

(a)

$$g_u = \frac{4/3}{1} = \frac{4}{3}$$

$$g_d = \frac{4/3}{3} = \frac{4}{9}$$

$$g_{avg} = \frac{4/3 + 4/9}{2} = \frac{8}{9}$$


(b)

$$p_u = \frac{4 \times 5/3 + 2/3}{1} = \frac{22}{3}$$

$$p_g = \frac{4 \times 5/3 + 2/3}{3} = \frac{22}{9}$$

$$p_{avg} = \frac{22/3 + 22/9}{2} = \frac{44}{9}$$

18.

 

(a) 2.5% (no partial)

$$g_A = \frac{4 + 2}{3} = 2$$

$$g_C = \frac{4 + 2}{3} = 2$$

(b) 2.5% (no partial)

$$p = \frac{4 + 4 + 2 + 2}{3} = 4$$

19.

$$R_{inv} = 1k\Omega$$

$$C_{inv} = 20fF$$

$$R = 0.2(\Omega/\mu m) \times 1mm = 200\Omega$$

$$C_{adj} = 0.6(fF/\mu m) \times 1mm = 600fF$$

$$C_{gnd} = 0.3(fF/\mu m) \times 1mm = 300fF$$

(a)


$$\mathbf{X=0 \rightarrow 1, Y=0}$$

$$C_{eff} = C_{adj} + C_{gnd} = 900fF$$

$$T_{pd} = R_{inv} \times C_{inv} + (R + R_{inv}) \times C_{eff} = \mathbf{1.1ns}$$

(b)

Y is floating, X=1→0

 

$$\Delta Y = \Delta X \times \left(\frac{C_{adj}}{C_{adj} + C_{gnd}} \right) = 1 \times \frac{2}{3} = \frac{2}{3}$$

20.

FFFTFFTFTF (1%per1)

21.

TTFFTTTFTF (1%per1)