

- Consider the dynamic logics as shown in Fig. 1 (10%)
 - Write down the Boolean equations. (4%)
 - Find the logical efforts g_d and p_d for each (6%)

 


Fig. 1

- Explain the following terminology and solution of dynamic logic. (10%)
 - Leakage. (2.5%)
 - Backgate coupling. (2.5%)
 - Clock feedthrough. (2.5%)
 - Charge sharing. (2.5%)

- A sequential circuit using flip-flop is shown in Fig. 3. Assume the period of $clk = 20ns$, max clock-to-q delay $t_{pcq} = 2ns$, min clock-to-q delay $t_{ccq} = 0.5ns$, max data-to-q delay $t_{dcq} = 2ns$, min data-to-q delay $t_{ccq} = 1.5ns$, setup time = $1.2ns$, and hold time = $2.8ns$. (10%)
 - Find the max delay of combination logic t_{pd} . (2%)
 - Sketch the timing diagram of “clk”, “Q1”, and “D2” to illustrate the max delay. (2%)
 - Find the min delay of combination logic t_{cd} . (2%)
 - Sketch the timing diagram of “clk”, “Q1”, and “D2” to illustrate the min delay. (2%)
 - Add clock skew on (d) and find the min delay. (2%)

 


Fig. 3

- Consider the ET FF as shown in Fig. 4. Explain the relative clock conditions (clk and $!clk$) to cause the problems (a)~(c). (10%)
 - Race. (2.5%)
 - Undefined state. (2.5%)
 - Dynamic storage. (2.5%)
 - How to modify the design to guarantee it is hold time issue free? (2.5%)

 


Fig. 4

- Write down the Boolean equation of carry behaviors in full adder. (5%)
 - Generate (G). (2.5%)
 - Propagate (P). (2.5%)
- Explain the design concept of the following 3 types of adder. (10%)
 - Carry-Lookahead. (2%)
 - Carry-Select. (2%)
 - Carry-Skip. (2%)
 - Order in speed of these 3 adders. (2%)
 - Pick one type of adder and sketch the block diagram. (2%)
- Sketch the block diagram of the following design with flip-flop and MUX. (5%)
 - 4-bits serial-in-parallel-out shift register. (2.5%)
 - 4-bits parallel-in-serial-out shift register. (2.5%)
- Explain the implementation, pros, and cons of the following bitlines design of DRAM. (5%)
 - Open bitlines. (2.5%)
 - Folded bitlines (2.5%)

9. Sketch the block diagram and Boolean equation of addition of four 3-bit words (111, 001, 100, 101) with the following 2 types of adder. (10%)
- (a) Carry-Save Adder (CSA). (5%)
 - (b) Carry-Propagation Adder (CPA). (5%)

10. Consider the 4-bits array multiplier as shown in in Fig. 10. For CSA block, the C_{in} -to- C_{out} delay = 2ns. For CPA block, C_{in} -to- C_{out} delay = 6ns. (5%)
- (a) With S_{in} -to- S_{out} delay = 3ns, find the total delay of the critical path. (2.5%)
 - (b) With S_{in} -to- S_{out} delay = 1.5ns, find the total delay of the critical path. (2.5%)

 


Fig. 10

11. Assume the bit line of a 1T DRAM cell is pre-charged to $V_{DD}/2$, the cell capacitance is 200fF, and the bit line capacitance is 0.6pF. (5%)
- (a) Find the data 0 and 1 voltage level on bit line during readout with $V_{DD} = 1V$. (2.5%)
 - (b) List two approaches to double the signal swing. (2.5%)

12. Consider the 6T SRAM cell in Fig. 12. (5%)
- (a) Explain the read-disturb behavior (in read operation) and index the cell ratio design concern to overcome it. (2.5%)
 - (b) Based on the design concern in (a), explain the pull-up ratio design concern to get a correct write operation. (2.5%)

 


Fig. 12

13. Answer the following about Memory: (10%)
- (a) Explain the purpose of “bitline conditioning” in SRAM. (2%)
 - (b) Explain the purpose of “column multiplexing” in SRAM. (2%)
 - (c) Write down two common methods to improve the yield of memory. (2%)
 - (d) List two types of nonvolatile memory. (2%)
 - (e) Explain the purpose of content address memory (CAM). (2%)

14. Design a tapered buffer to drive a 512-unit loading (relative to C_{in} of unit inverter) as shown in Fig. 14. (5%)
- (a) Design stage number N to get the minimum delay. (2.5%)
 - (b) Find the minimum stage effort delay f_i and the total path delay D . (2.5%)

 


Fig. 14

15. There are 2 adjacent wires X and Y. Each wire in a pair of 2mm lines has capacitance of 0.8 fF/ μm to ground and 0.4 fF/ μm to its neighbor. The wire resistance is 0.2 $\Omega/\mu\text{m}$. Each line is driven by an inverter with a 1k Ω effective resistance and 40fF parasitic capacitance. Use L-model to find the propagation delay of X wire with the following conditions. (5%)

- (a) $X=1 \rightarrow 0, Y=0 \rightarrow 1$. (2.5%)
- (b) If Y is floating, find the cross talk value ΔV_Y when $X = 1 \rightarrow 0$. (2.5%)

16. A logic path as shown in Fig. 16. (5%)

- (a) Find the minimum path delay. (2.5%)
- (b) Find the size of the x, y, z to get the minimum path delay. (2.5%)

 


Fig. 16

17. Consider a NAND2 driving h copies of NAND2 as shown in Fig. 17. (5%)

- (a) Find the propagation delay. (2.5%)
- (b) Find the contamination delay. (2.5%)

 


Fig. 17

18. Answer the following questions with TRUE or FALSE: (10%)

- (a) Flip-flop is edge triggered and Latch is level triggered. (1%)
- (b) Sequential logic using 2-phase latch is skew tolerant. (1%)
- (c) Clock jitter is due to the low frequency environment variation and cannot be calibrated. (1%)
- (d) *Drift* clock skew is due to process variation and can be solved by one-time calibration. (1%)
- (e) Clock skew can be reduced by careful clock distribution, skew tolerant design and plenty of metal wire routing. (1%)
- (f) *Grid* type clock distribution is suffered at systematic skew between points closet and furthest to the driver. (1%)
- (g) *H-Tree* type clock distribution is suffered at delay mismatch of local near points from different tree. (1%)
- (h) *Design for test* = design circuit to increase fault observability and controllability. (1%)
- (i) *Boundary Scan test* can be used to verify solder joints on PCB. (1%)
- (j) The RLC effect of I/O pads and pins should be included in circuit simulation to increase the accuracy. (1%)