 



1. (A) MOS has leakage current when operating in subthreshold. Output settles to an intermediate voltage determined by a resistive divider of the pull-up and pull-down networks.




Leakage sources

Solution:


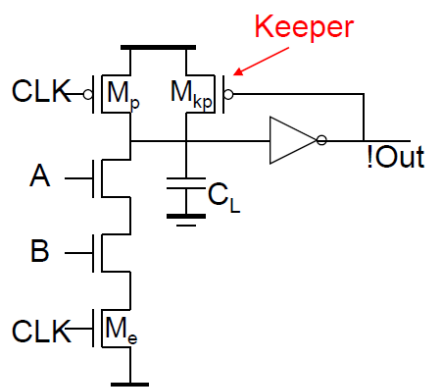
Keeper compensates for the charge lost due to the pull-down leakage paths.



 (B) Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to static power consumption by downstream gates and possible circuit malfunction.



secondary precharge transistor

  

Solution: add loading at CLK

2.

$$(a) S = A \oplus B \oplus C_{in} \quad C_{out} = AB + BC_{in} + AC_{in}$$

$$(b) G = A \cdot B \quad P = A \oplus B$$

3.

$$(a) (I) Y = \overline{A \cdot B} \quad (II) Y = \overline{A + B}$$

$$(b) (I) g_d = 1, p_d = \frac{4}{3} \quad (II) g_d = \frac{2}{3}, p_d = \frac{5}{3}$$

4.

(a) (寫其中一種即可)

$$\text{Without skew: } T_{pd} \leq T_c - (T_{setup} + T_{pcq}) = 10ns - (0.8ns + 2ns) = 7.2ns.$$

With skew: 5.2ns

(b) (兩種都要寫)

$$\text{Without skew: } T_{cd} \geq T_{hold} - T_{ccq} = 1.2ns - 0.5ns = 0.7ns.$$

With skew: 2.7ns

5.

(a)

$$\text{setup time} = 3I_X + 1T_X = 3 \times 1 + 2 = 5ns.$$

(b)

$$T_{pcq} = 1I_X + 1T_X = 1 + 2 = 3ns.$$

6.

(a) (寫其中一種即可)

Without skew:

$$t_{cd} \geq T_{hold} - t_{ccq} - t_{nonoverlap}.$$

$$0.6ns \geq 1.2ns - 0.5ns - t_{nonoverlap} \rightarrow t_{nonoverlap} \geq 0.1ns.$$

With skew:

$$t_{cd} \geq T_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}.$$

$$0.6ns \geq 1.2ns - 0.5ns - t_{nonoverlap} + 1ns \rightarrow t_{nonoverlap} \geq 1.1ns.$$


(b) (兩種都要寫)

With and without skew (skew-tolerant):


$$t_{pd} \leq T_c - (t_{pdq1} + t_{pdq2}) = 12ns - 2 \times 1.5ns = 9ns.$$

7.

(a)

 


(B)

 


8.


(a)

 

(b)

 

9.

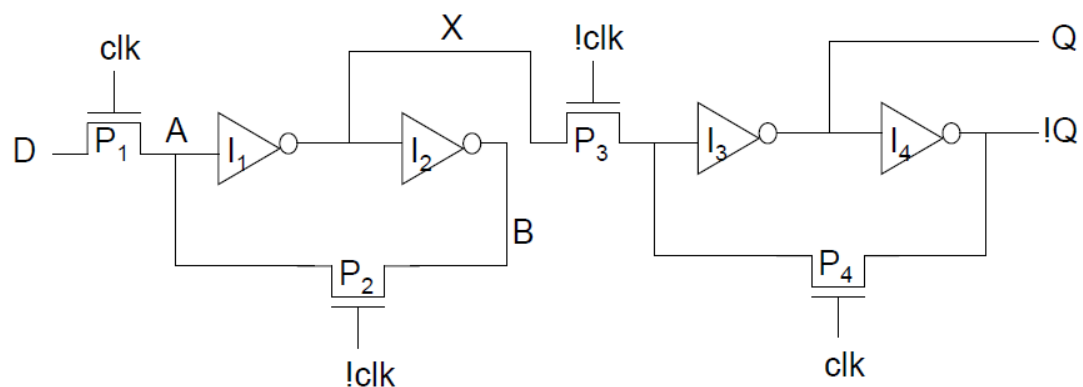


(a) direct path from D to Q during the short time when both clk and !clk are high (1-1 overlap)

(b) both B and D are driving A when clk and !clk are both high

(c) when clk and !clk are both low (0-0 overlap)

 (d) An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times



10.

(a)


Word0=[010101]

Word1=[011001]

Word2=[100101]

Word3=[101010]

(b)

 

11.

(a) Open bitlines: use another subarray as reference

–Higher density

–Noise affect one array more than the other appears as differential noise.

(b) Folded bitlines: take the neighbor cell in the same subarray as reference

–Noise appears as common mode

–Larger layout area

12.

(a)

For read purpose: Precharge both bitlines high

- Then turn on wordline

- One of the two bitlines will be pulled down by the cell


(b) *Sense amplifiers* are triggered on small voltage swing to reduce read time.

(c) *Add dummy lines*: The dummy lines are placed at the edge because photolithography and etch problems occur most often near the edge of large repetitive structure.

ECC: Error-detecting and correcting codes are commonly used to recover from soft errors that spontaneously flip a bit store in one of the cell.

BIST: Built-in self-test that place multiplexers in the address and data paths to take over the memory during test mode.

13.

 

(a)

Read stability

If $I_Q=0$, voltage will bump up by resistive voltage division while word-line open.

$M1 > M5$

(b) in write 1 operation, M6 must overpower M4 pull up MOS.

14.

1. The sense amplifiers are disconnected.
2. The bit-lines are precharged to exactly equal voltages that are in between high and low logic levels (e.g., 0.5 V if the two levels are 0 and 1 V). The bit-lines are physically symmetrical to keep the capacitance equal, and therefore at this time their voltages are equal.
3. The precharge circuit is switched off. Because the bit-lines are relatively long, they have enough **capacitance** to maintain the precharged voltage for a brief time. This is an example of **dynamic logic**.
4. The desired row's word-line is then driven high to connect a cell's storage capacitor to its bit-line. This causes the transistor to conduct, transferring **charge** from the storage cell to the connected bit-line (if the stored value is 1) or from the connected bit-line to the storage cell (if the stored value is 0). Since the capacitance of the bit-line is typically much higher than the capacitance of the storage cell, the voltage on the bit-line increases very slightly if the storage cell's capacitor is discharged and decreases very slightly if the storage cell is charged (e.g., 0.54 V and 0.45 V in the two cases). As the other bit-line holds 0.50 V there is a small voltage difference between the two twisted bit-lines.

$$(b) \Delta V_x = \frac{1.8}{2} \times \frac{50f}{50f+500f} = 0.08V$$

15.

FTFTT

FFTTT

TTFTT

TTFFF

16.

FTFTF

TTTFF