

- Consider the design of a CMOS compound gate computing $F = A + (B \bullet C) + (D \bullet E)$. (10%)
 - Sketch transistor-level schematic. (2.5%)
 - Find g_A , g_C , g_D . (2.5%)
 - Sketch the stick diagram. (2.5%)
 - Find the maximum and minimum p with different layout style. (2.5%)
- For DC characteristic of nMOS with $V_{tn}=0.5V$ (5%)
 - Sketch the I-V curves at $V_{GS} = 0 \sim 2V$ and identify the operation regions. (2.5%)
 - Write down the corresponding ideal I-V equations. (2.5%)
- Assume an nMOS with $V_{tn} = 0.5V$ and $C_0 = C_{ox}WL$. (5%)
 - Sketch the gate capacitance (C_{gd} , C_{gs} , C_{gb}) in terms of C_0 @ $V_{ds} = 1V$ for $V_{gs} = -1V \sim 1V$. (2.5%)
 - Sketch the gate capacitance (C_{gd} , C_{gs}) in terms of C_0 for $V_{ds}/V_{dsat} = 0 \sim 1$. (2.5%)
- A ring oscillator composed of N-stages identical inverters is as shown in Fig. 4. Assume the effective resistance of an unit inverter (P:2, N:1) is $5k\Omega$ and parasitic capacitance is $10fF$. (5%)
 - $N = 5$, find the oscillated frequency. (2.5%)
 - Use skewed inverter and find the oscillated frequency. (2.5%)

 


Fig. 4

- Explain the following terminologies and its root cause: (10%)
 - Channel length modulation effect. (2%)
 - Velocity saturation. (2%)
 - Latchup. (2%)
 - Body effect. (2%)
 - Hot carriers. (2%)
- A transmission gate as shown in Fig. 6 with $V_{DD} = 1.4V$ and $|V_{tp}| = V_{tn} = 0.5V$. (5%)
 - Sketch the transfer curve of R_{on} with $V_{in} = 0 \sim V_{DD}$ (2.5%)
 - Sketch the curve with $V_{DD} = 0.8V$, observe and comments the possible issue. (2.5%)

 


Fig. 6

- Fig.7 shows the transfer curves of CMOS inverter with $\mu_n/\mu_p = 3$ and $V_{tn} = |V_{tp}| = 0.5V$ (10%)
 - For “B” curve, find $(W/L)_p$ with $(W/L)_n = 2\mu m/0.18\mu m$. (2.5%)
 - Based on “B” curve, sketch and identify V_{IL} , V_{IH} , V_{OL} , and V_{OH} . (2.5%)
 - Define NM_H and NM_L . (2.5%)
 - Rank the noise margins (NM_H and NM_L) of A, B, and C. (2.5%)

 


Fig. 7

8. The logic block shown in Fig. 8 has n_1 stages and a path effort of $F = 128$. Consider adding $N - n_1$ inverter to the end. Assume the i -th parasitic of logic block is p_i and the parasitic of inverter $p_{inv} = 1$. (5%)
- (a) Express path delay D in terms of N , F , p_i , n_1 and p_{inv} . (2.5%)
- (b) $N = 10$, $n_1 = 4$, $p_i = 3$, find the best stage effort ρ and the least delay D . (2.5%)

 


Fig. 8

9. Design a tapered buffer to drive a 256-unit loading (relative to C_{in} of unit inverter) as shown in Fig. 9. (5%)
- (a) Design stage number N to get the minimum delay. (2.5%)
- (b) Find the minimum stage effort delay f_i and the total path delay D . (2.5%)

 


Fig. 9

10. Design the asymmetric gate in Fig. 10. (5%)
- (a) Choose the nMOS size of reset_B as 20 units, design and sketch the transistor sizes to get the rising and falling effective resistance equal to unit inverter. (2.5%)
- (b) Find g_A and g_B . (2.5%)

 


Fig. 10

11. Two adjacent wires X and Y are in a pair of 1mm lines with capacitances of $0.5 \text{ fF}/\mu\text{m}$ to ground and $0.2 \text{ fF}/\mu\text{m}$ to its neighbor. The wire width is $0.5 \mu\text{m}$ with a sheet resistance of $0.6 \Omega/\square$. Each line is driven by an inverter with a $0.5 \text{ k}\Omega$ effective resistance and 50 fF parasitic capacitance. Use one-segment pi-model for wire and Elmore delay model to find the propagation delay of X wire with the following conditions. (10%)

- (a) $X=0 \rightarrow 1.8 \text{ V}$, $Y=1.8 \text{ V} \rightarrow 0$. (2.5%)
- (b) $X=1.8 \text{ V} \rightarrow 0$, $Y=0$. (2.5%)
- (c) If Y is floating, find the cross talk value ΔV_Y when $X = 1.8 \text{ V} \rightarrow 0$. (2.5%)
- (d) List 2 ways to reduce the cross talk. (2.5%)

12. A logic path as shown in Fig. 12. (5%)

- (a) Find the minimum path delay. (2.5%)
- (b) Find the size of the x, y, z to get the minimum path delay. (2.5%)

 


Fig. 12

13. Design an 8-input ($k=8$) AND gate using inverter and pseudo-nMOS NOR gates as shown in Fig. 13. Choose pull-up device size to be $1/3$ and the output loading $H = 64$. (5%)
- (a) Find the path delay. (2.5%)
- (b) Sketch and label the transistor widths. (2.5%)

 


Fig. 13

14. Consider a NAND3 driving h copies of NAND3 as shown in Fig. 14. (5%)

- (a) Find the propagation delay. (2.5%)
- (b) Find the contamination delay. (2.5%)

 


Fig. 14

15. Explain the following terminologies and its purpose: (10%)

- (a) High-K dielectric. (2%)
- (b) Low-K dielectric. (2%)
- (c) Copper interconnect. (2%)
- (d) FinFET. (2%)
- (e) SOI. (2%)

16. Answer the following questions with TRUE or FALSE: (10%)

- (a) Metal-insulator-metal capacitor is more popular in advanced technology for its low cost. (1%)
- (b) The delay of logic gate is proportional to product of logical effort and fanout. (1%)
- (c) Electromigration is caused by electron wind of AC current. (1%)
- (d) The dimension precision of source/drain implantation is higher than well. (1%)
- (e) Multiple threshold voltage devices use same oxide thickness for manufacturing concern. (1%)
- (f) The pitch of M1 is smaller than M6. (1%)
- (g) CMP is used to planarize the structure for multi-layer inter- connects stacking. (1%)
- (h) Salicide is used to reduce the S/D and gate resistance. (1%)
- (i) DRC is for design issue and LVS is for manufacturing issue. (1%)
- (j) For a multiple input logic, the slower input should be connected to outer node to get smaller delay. (1%)