

- Consider a NAND2 logic $F = \overline{X \bullet Y}$ with Y as the inner input. (5%)
 - Find the transition-threshold ordering of the following cases: (i) X, Y: $0 \rightarrow 1$, (ii) X = 1, Y: $0 \rightarrow 1$, (iii) Y = 1, X: $0 \rightarrow 1$. (2.5%)
 - Explain the root cause of the data-dependent voltage transfer curve. (2.5%)
- Design a 32-input ($k = 32$) AND gate using inverter and pseudo-nMOS NOR gates as shown in Fig. 2. Choose pull-up device size to be $2/3$ and the output loading $H = 128$. (5%)
 - Find the path delay. (2.5%)
 - Sketch and label the transistor widths. (2.5%)

 


Fig. 2

- Consider a dynamic logic (NADN2) as shown in Fig. 3. Assume the $C_a = C_b = 10\text{fF}$, $C_L = 40\text{fF}$, $C_{gs}(C_{gd})$ of $M_p = 5\text{fF}$, and $V_{DD} = 1\text{V}$. (5%)
 - In precharge, assume all the charge on C_a and C_b are 0. Find the voltage V_{out} in evaluation with $B = 0$, $A = 0 \rightarrow 1$. (2.5%)
 - Provide an add-on circuit to solve the issue in (a). (2.5%)

 


Fig. 3

- Explain the mechanism of the following reliability issues. (10%)
 - Electromigration. (2.5%)
 - Self-heating. (2.5%)
 - Hot carrier. (2.5%)
 - Latchup. (2.5%)
- Explain the following issues and solution of dynamic logic. (10%)
 - Leakage. (2.5%)
 - Cascading gates. (2.5%)
 - Backgate coupling. (2.5%)
 - Clock feedthrough. (2.5%)
- A sequential circuit using pulse latch is shown in Fig. 6. Assume the period of $\text{clk} = 20\text{ns}$, max data-to-q delay $t_{pdq} = 6\text{ns}$, min data-to-q delay $t_{cdq} = 4\text{ns}$, max clk-to-q delay $t_{pcq} = 5\text{ns}$, min clock-to-q delay $t_{ccq} = 3\text{ns}$, setup time = 2.4ns , hold time = 4.2ns , the clock skew = 0.5ns . (5%)
 - With pulse width $t_{pw} = 2\text{ns}$, find the max delay of combination logic t_{pd} . (2.5%)
 - Find the min delay of combination logic t_{cd} with and without clock skew. (2.5%)

 


Fig. 6

- Determine the maximum amount of borrowing time in the following sequencing styles with clock period = 20ns , $t_{\text{setup}} = t_{\text{hold}} = 2\text{ns}$. (10%)
 - Positive-triggered Flip-flops. (2.5%)
 - Two-phase transparent latches with 1ns nonoverlap between phases. (2.5%)
 - Pulsed latched with 5ns pulse width. (2.5%)
 - Repeat (b) and (c) with a clock skew of 0.5ns . (2.5%)

8. Consider the MUX type ET FF in Fig. 8. Assume the propagation delays of $I_{1-6} = 2\text{ns}$ and $T_{1-4} = 3\text{ns}$ respectively. The delay between clk and !clk is 2.5ns . (5%)
- (a) Find the setup time. (2.5%)
 - (b) Find the t_{pcq} . (2.5%)
 - (c) Find the hold time. (2.5%)
 - (d) How to modify the design to guarantee it is hold time issue free? (2.5%)

 


Fig. 8

9. Using two 9-bit words input with a 3-bit grouping as an example, sketch and explain the operation of the following types of adder. (10%)
- (a) Carry-Lookahead. (2.5%)
 - (b) Carry-Select. (2.5%)
 - (c) Carry-Skip. (2.5%)
 - (d) Order these adders in term of speed. (2.5%)
10. Answer the following questions about Datapath Subsystems. (T or F) (10%)
- (a) *One-zero detection* is used to check the magnitude equality of two inputs. (1%)
 - (b) Logic levels, fan-in and grouping are the 3 design-tradeoff corner parameters of tree adder. (1%)
 - (c) *Parity check* is commonly used to do the data error-detection and correction. (1%)
 - (d) *Linear feedback shift register* is used to generate pseudo random code. (1%)
 - (e) The critical path of a multi-bit adder is usually the carry propagation. (1%)

- (f) *Booth encoding* is used to solve the $x3$ operation in multi-bit multiplier. (1%)
- (g) *Gray code* is used to reduce dynamic power and glitch of decoder. (1%)
- (h) If we shift “Right” a word 1011 to get 1101, it is an Arithmetic shifter operation. (1%)
- (i) $M \times N$ -bit multiplication will produce M N -bit partial products. (1%)
- (j) If carry generation is the slowest path in the CSA cell in Fig. 10. Identify the critical path of this multiplier. (1%)

 


Fig. 10

11. Consider the 6T SRAM cell in Fig. 11. (5%)
- (a) Explain the transistor sizing requirement for read stability. (2.5%)
 - (b) Explain the transistor sizing requirement for write stability. (2.5%)

 


Fig. 11

12. Answer the following about Memory: (10%)

- (a) For a 1T1R DRAM cell, assume the bit line is precharged to $V_{DD}/2$, the cell capacitance is 50fF, and the bit line capacitance is 1pF. Find the data 0 and 1 voltage level on bit line during readout with $V_{DD} = 3.3V$. (2%)
- (b) Explain the purpose of “column multiplexing”. (2%)
- (c) Explain the purpose of sense amplifier and isolation transistor. (2%)
- (d) Write down two common methods to improve the yield of memory. (2%)
- (e) Write the Boolean function of x, y in Fig. 12. (2%)

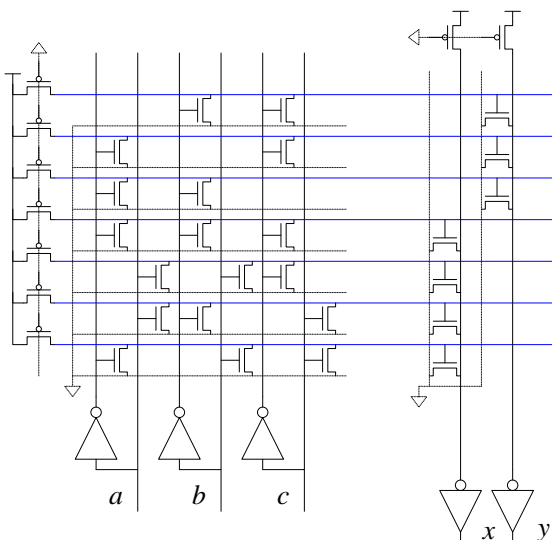


Fig. 12

13. Explain the implementation, pros, and cons of the following bitline design of DRAM. (5%)

- (a) *Open bitline*. (2.5%)
- (b) *Folded bitline* (2.5%)

14. Answer the following questions. (T or F) (10%)

- (a) *Drift* clock skew is due to process variation and can be solved by one-time calibration. (1%)
- (b) *Random* skew is caused by time-dependent environmental variations. (1%)

- (c) H-Tree type clock distribution is suffered at random skew between points closet and furthest to the driver. (1%)
- (d) JTAG is development for components test on PCB to verify solder joints. (1%)
- (e) Electron-beam (ebeam), u-Probe, and Focused Ion Beam (FIB) are all debugging methods without mechanical contacts. (1%)
- (f) DRAM is not compatible to standard CMOS process technology due to special capacitor structure. (1%)
- (g) Fault coverage is a measure of manufacturing yield. (1%)
- (h) The RLC effect of I/O pads will affect the power quality and signal settling behavior as well. (1%)
- (i) Schmitt trigger is used to filter out the noise of output pin. (1%)
- (j) Bypassing capacitors are used to stabilize voltage and normally implemented with identical capacitances in parallel. (1%)

15. Sketch the timing diagrams of ϕ_1 , ϕ_2 , word_q1, birt_v1f, and out_v1r to explain the SRAM operations in Fig. 15. (5%)

- (a) Read operation. (2.5%)
- (b) Write operation. (2.5%)

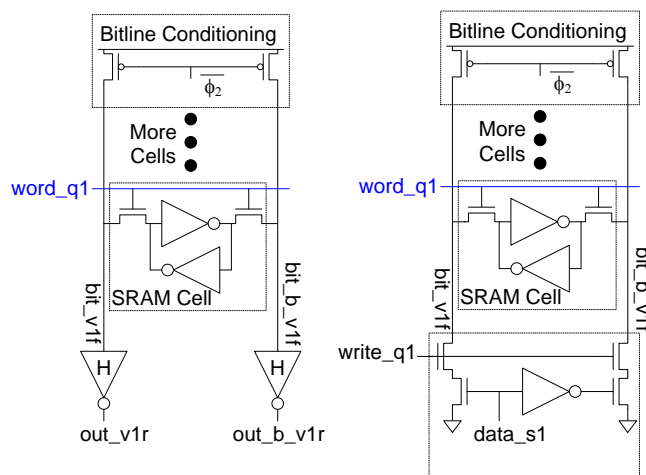


Fig. 15

16. A logic path as shown in Fig. 16. (5%)

- (a) Find the minimum path delay. (2.5%)
- (b) Find the size of the x , y , z to get the minimum path delay. (2.5%)

 


Fig. 16

17. Design a tapered buffer to drive a 512-unit loading (relative to C_{in} of unit inverter) as shown in Fig. 17. (5%)

- (a) Design stage number N to get the minimum delay. (2.5%)
- (b) With the N in (a), find the stage effort delay f_i and the total path delay D . (2.5%)

 


Fig. 17