

2016 VLSI Final Solution

1. (a) 1. A=1 B=0~1 2. B=1 A=0~1 3. AB=0~1

(b) Body effect

(c) 講義 5-17

(d) NMOS tail 5 NMOS out 5/4 $gb = 7/3$


2. (a) $P=3$

(b) $3^{0.5}$

3. Leakage, charge average, back-gate coupling, clock feed-through, cascade

$$4. (a) F = GBH = \frac{1}{2} \times 1 \times \frac{64}{2} = \frac{64}{4} \quad D = NF^{\frac{1}{N}} + P = 2 \left(\frac{64}{4} \right)^{\frac{1}{2}} + \left(\frac{193}{2} + 1 \right) = 105.5$$

(b)

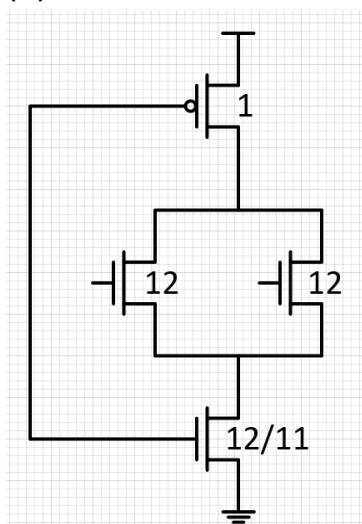

5. (a) 講義 6-12

(b) 講義 6-13

(c) 講義 6-14

(d) 講義 6-15

6. (a) 0ns

$$(b) \frac{10}{2} - (2 + 1) = 2\text{ns}$$

$$(c) 4 - 2 = 2\text{ns}$$

$$(d) \frac{10}{2} - (2 + 1 + 1) = 1\text{ns} \quad 4 - (2 + 1) = 1\text{ns}$$

7. (a) $T_{pd} \leq T_c - (T_{setup} + T_{pcq}) = 20 - (1.5 + 2) = 16.5\text{ns}$ (講義 6-29)

(b) 講義 6-29

(c) $T_{cd} \geq T_{hold} - T_{ccq} = 3 - 0.4 = 2.6$ ns (w/o clock skew)

$T_{cd} \geq T_{hold} - T_{ccq} + T_{skew} = 3 - 0.4 + 0.5 = 3.1$ ns (w/ clock skew)

(d) 講義 6-42

8. (a) 解釋請參照講義 8.p8, M3>M6

(b) 解釋請參照講義 8.p9, M6>M4

(c) 解釋請參照講義 8.p18

(d) 解釋請參照講義 8.p19

9. (a) Race: Direct path from D to Q during the short time when both

CLK and !CLK are high (1-1 overlap) (講義 6-56)

(b) Undefined state: Both B and D are driving A when CLK and !CLK are both high (講義 6-56)

(c) Dynamic storage: when CLK and !CLK are both low (講義 6-56)

(d) Using 2-phase latches with big nonoverlap times (講義 6-56)


10. (a) (講義 8-32)

(b) $\Delta V = V_{DD}/2 * (C_{cell}/C_{cell} + C_{bit}) = 0.078$ V

(c) (講義 8-34)


(d) (講義 8-34)

11. (a)

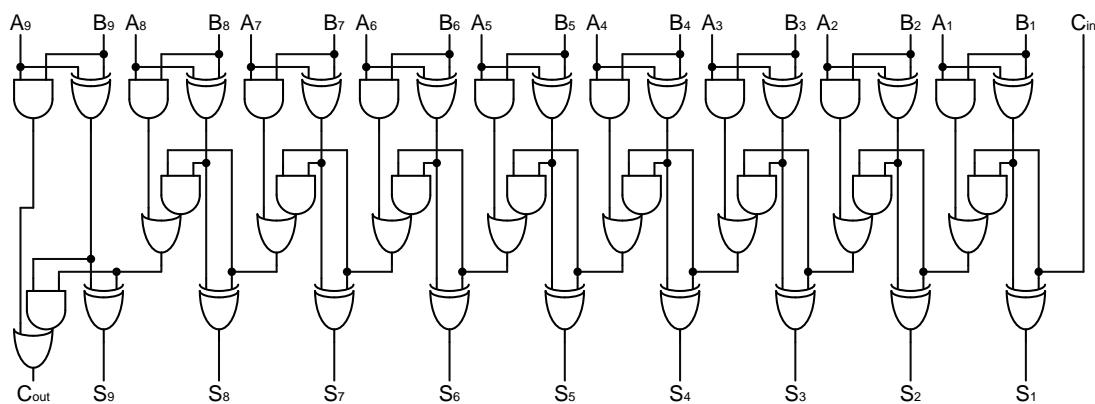


(b) $t_{ripple} = t_{pg} + 8t_{AO} + t_{XOR}$

(c)

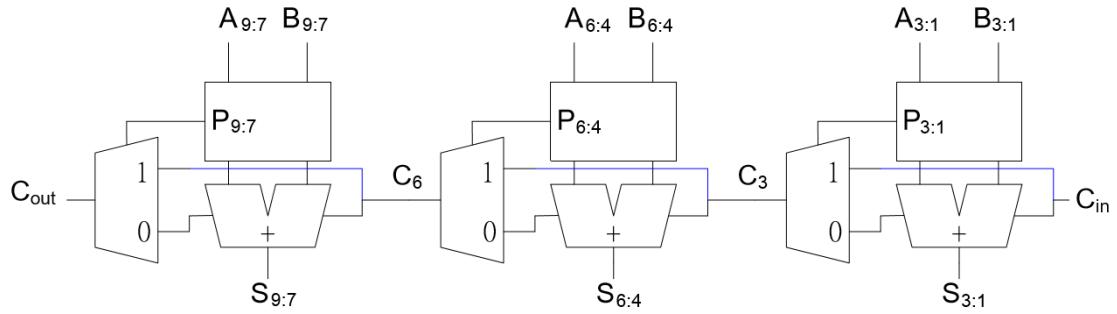


$$(d) \quad t_{skip} = t_{pg} + 6t_{AO} + t_{XOR}$$

12. (a)

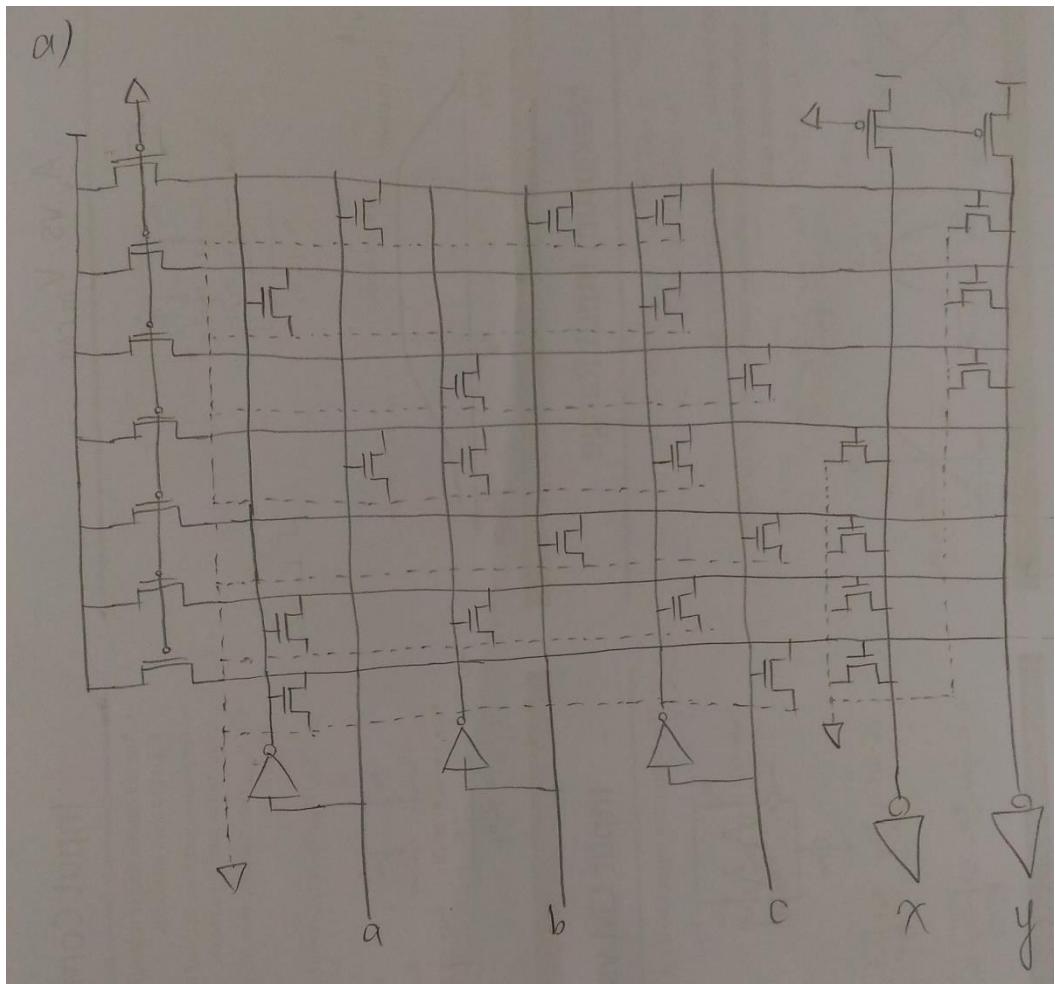

(b)

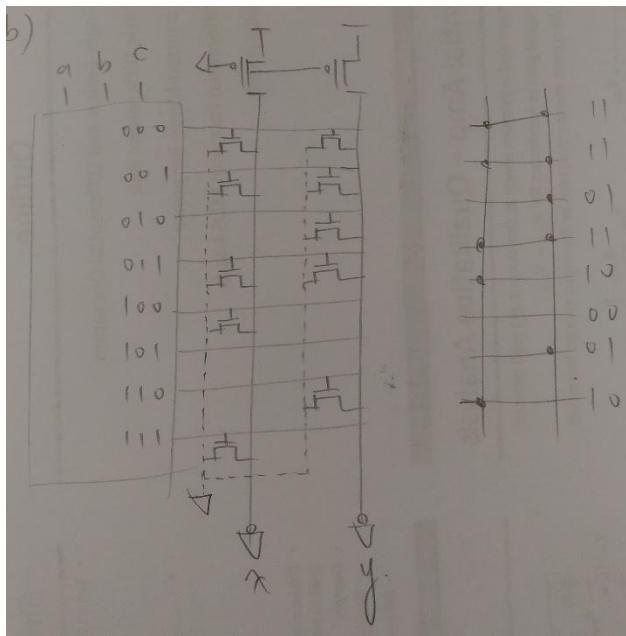

$$13. (a) G = 1 \times \frac{4}{3} \times \frac{4}{3} \times \frac{5}{3} = \frac{80}{27}$$

$$B = 2 \times 2 = 4$$

$$H = \frac{256}{2} = 128$$

$$(b) F = GBH = \frac{40960}{27} \rightarrow f = F^{\frac{1}{4}} = 6.24$$


$$P = 1 + 2 + 2 + 2 = 7$$

$$D = NF^{\frac{1}{N}} + P = 6.24 \times 4 + 7 = 31.96$$

$$(c) C_{in} = \frac{g \times C_{out}}{f}$$


$$\rightarrow \begin{cases} z = \frac{\frac{5}{3} \times 256}{6.24} = 68.3659 \\ y = \frac{\frac{4}{3} \times 68.3659}{6.24} = 14.608 \\ x = \frac{\frac{4}{3} \times 14.608 \times 2}{6.24} = 6.24 \end{cases}$$

14. (a)

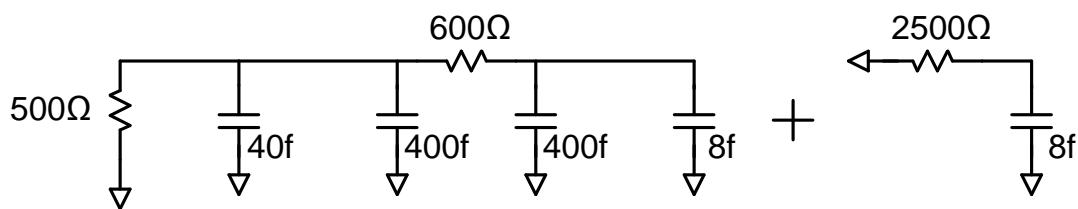

$$t_{pd} = (500 \times 440f) + (600 + 500) \times 408f + 2500 \times 8f = 688.8 \text{ ps}$$

(b)

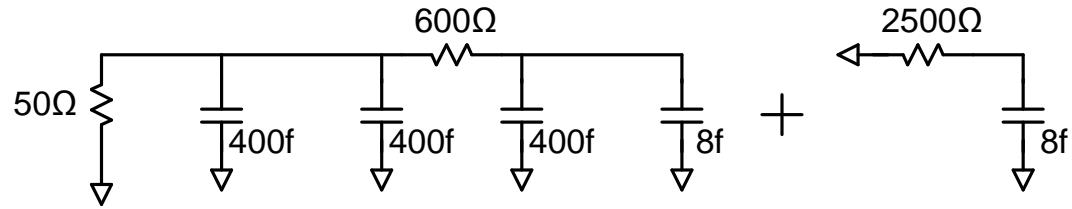

$$t_{pd} = (50 \times 800f) + (600 + 50) \times 408f + 2500 \times 8f = 325.2 \text{ ps}$$

15. TTTFF FFFTT