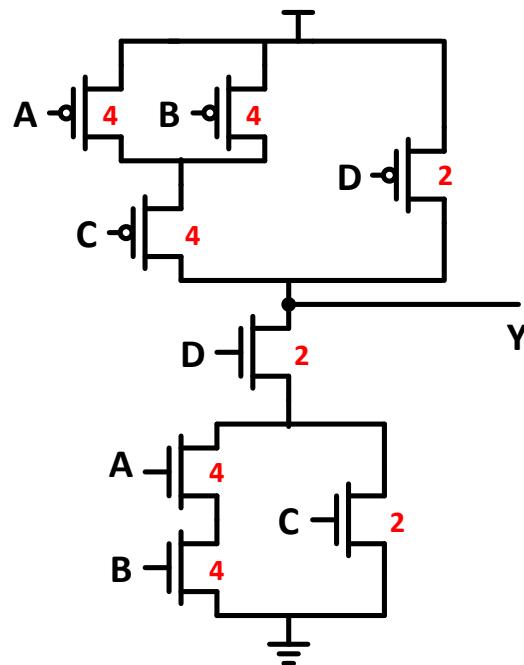


2016 VLSI Midterm Solution

1. (a)




(b) $g_A = 8/3, g_C = 6/3 = 2, g_D = 4/3$


(c) 略

(d) $p_{\max} = (4+4+2+4+2)/3 = 16/3, p_{\min} = (4+2+2)/3 = 8/3$

2. (a) $g_{\text{avg}} = 5/3$

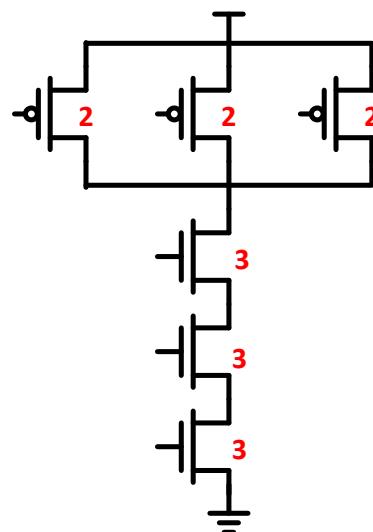

(b)

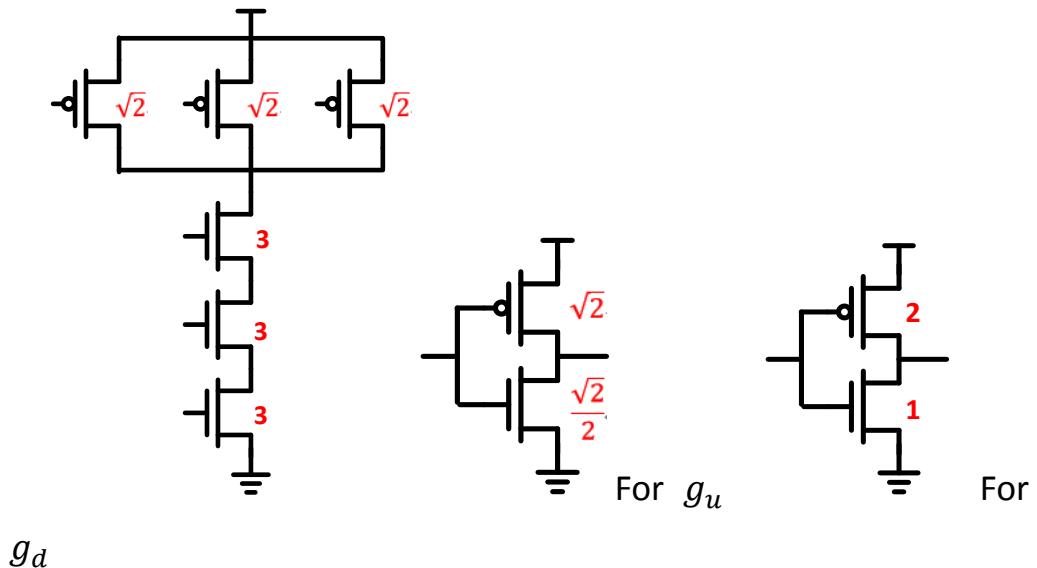

Computing Logical Effort

4- 35


- The ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current

$$g_u = \frac{3+\sqrt{2}}{\sqrt{2}+\sqrt{2}/2} = 2.08, \quad g_d = \frac{3+\sqrt{2}}{2+1} = 1.47, \quad g_{avg} = 1.775$$


3. (a)(b) $F=GBH=1*1*(128/2)=64, \quad f_i = F^{1/N} = 64^{1/N}$

For $N=3, \quad f_i=4, \quad D=N*F^{1/N}+N=15$

4. (a)

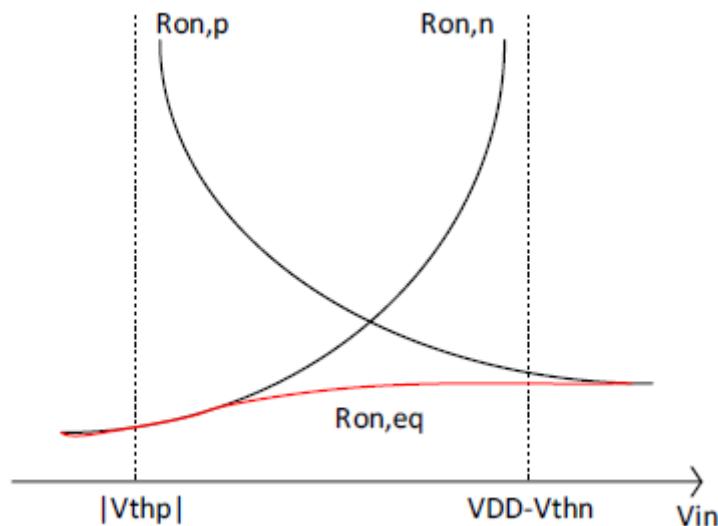


(b)

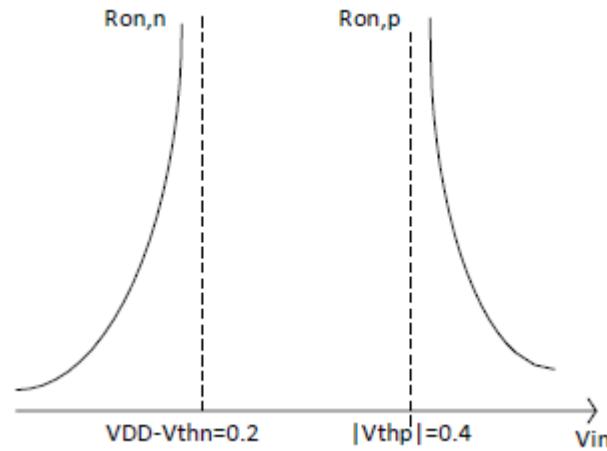

Comment : Both N/PMOS turn off when $0.2 < V_{in} < 0.4$, and $R_{on} \rightarrow \infty$

The transmission gate switch as open circuit.

5. (a)

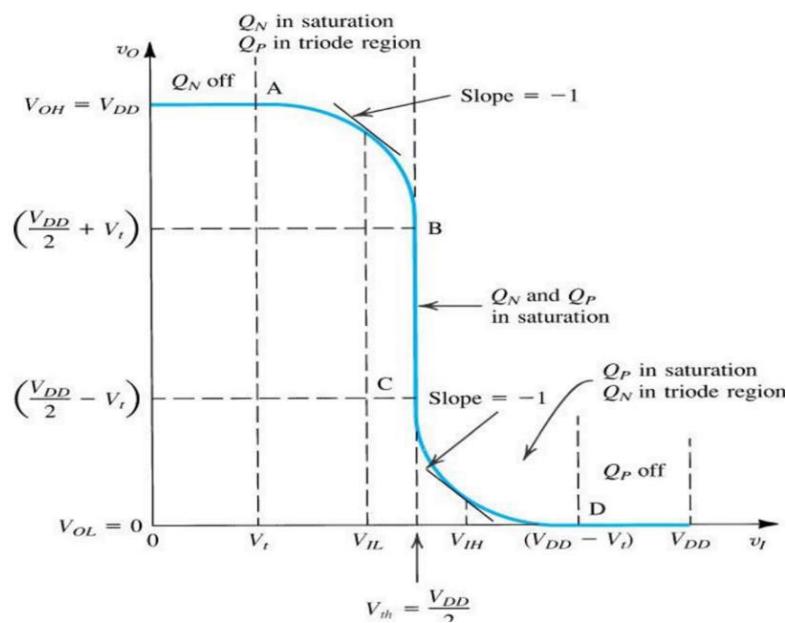


(b) $NM_H = V_{OH} - V_{IH}$, $NM_L = V_{IL} - V_{OL}$

(c) High-skewed : $NM_H \downarrow$, $NM_L \uparrow$; Low-skewed : $NM_H \uparrow$, $NM_L \downarrow$

(d) $W_P/W_N = 3/1$, with the same L

(e) Both in saturation region.

6. (a)

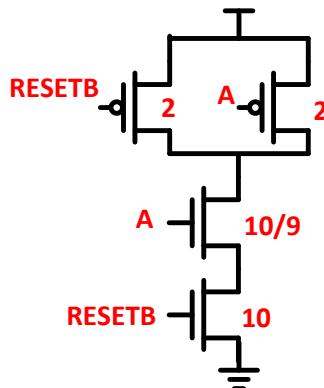

(b) $g_A = 28/27$, $g_{RESETB} = 4$ (RESETB would be non-critical input)

$$7. (a) G = 1 \times \frac{5}{3} \times \frac{4}{3} \times \frac{5}{3} = \frac{100}{27}$$

$$B = 2 \times 2 = 4$$

$$H = \frac{120}{2} = 60$$

$$(b) F = GBH = \frac{8000}{9} \rightarrow f = F^{\frac{1}{4}} = 5.46$$

$$P = 1 + 3 + 2 + 2 = 8$$

$$D = NF^{\frac{1}{N}} + P = 5.46 \times 4 + 8 = 29.84$$

$$(c) C_{in} = \frac{g \times C_{out}}{f}$$

$$\rightarrow \begin{cases} z = \frac{\frac{5}{3} \times 120}{5.46} = 36.63 \\ y = \frac{\frac{4}{3} \times 36.63}{5.46} = 8.945 \\ x = \frac{\frac{5}{3} \times 8.945 \times 2}{5.46} = 5.46 \end{cases}$$

8. (a) $d = gh + p = 2$

$$d' = d \times R \times C = 1k \times 10f$$

$$f_{osc} = \frac{1}{2Nd'} = \frac{1}{2 \times 9 \times 1k \times 10f} = 5.556 \text{ GHz}$$

(b) Down-sized inverter $g_{avg} = 1$

$$f_{osc} = \frac{1}{2Nd'} = \frac{1}{2 \times 9 \times 1k \times 10f} = 5.556 \text{ GHz}$$

$$9. (a) D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1)p_{inv}$$

$$(b) N = 6 \rightarrow D = 6 \times 2048^{\frac{1}{6}} + 6 \times 2 = 33.38$$

$$10. (a) T_{pdr} = (9 + 4h)RC$$

$$T_{pdf} = \left(3C \times \frac{R}{3}\right) + \left(3C \times \frac{2R}{3}\right) + R \times (9 + 4h)C = (12 + 4h)RC$$

$$T_{pd} = (10.5 + 4h)RC$$


$$(b) T_{cdr} = \frac{R}{3} \times (9 + 4h)C$$

$$T_{cdf} = (9 + 4h)RC$$

$$T_{cd} = \frac{2}{3} \times (9 + 4h)RC = (6 + \frac{8}{3}h)RC$$


11. g → l → i → f → k → b → h → c → d → a → j → e

12. (a)

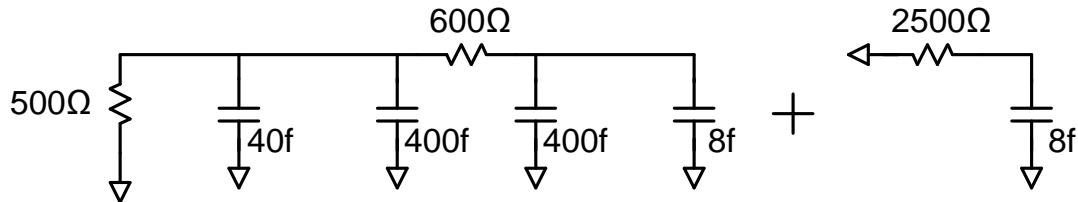

$$t_{pd} = (500 \times 440f) + (600 + 500) \times 408f + 2500 \times 8f = 688.8 \text{ ps}$$

(b)

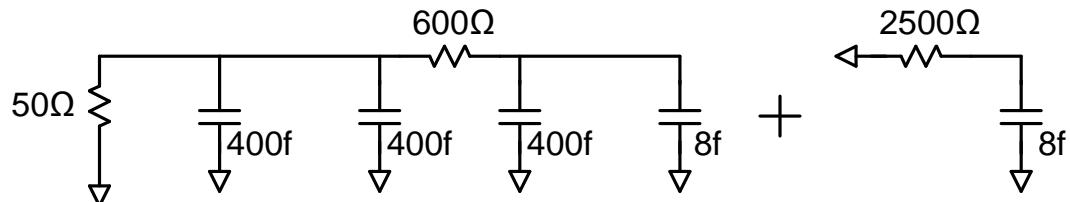

$$t_{pd} = (50 \times 800f) + (600 + 50) \times 408f + 2500 \times 8f = 325.2 \text{ ps}$$

$$13. C_{wire} = 400f$$

$$C_{adj} = 800f$$

$$(a) \Delta V_Y = 1.8 \times \frac{800f}{1200f} = 1.2 \text{ V}$$

(b) Shielding, Increase the loading Cap, Put two wire away

14.

- A. 講義 3-11
- B. 講義 3-11
- C. 講義 2-62
- D. 講義 3-11
- E. 講義 3-11
- F. 講義 4-15
- G. 講義 4-14
- H. 講義 4-12
- i. 講義 4-13
- j. 講義 4-19

15.

- A. 講義 2-27
- B. 講義 2-27
- C. 講義 2-34
- D. 講義 2-30
- E. 講義 2-28

$$16. P = [(0.1 \times 20M \times 0.5) + (0.04 \times 60M \times 0.25)] \times 2f \times 1.8^2 \times 100M = 1.0368W$$

17.

- TFTTT
- FTFTF