 


2017 VLSI midterm solution

1.


(a)

參考答案：



(b)

參考答案：(可分不同 diffusion，畫對就給分)

 

2.

(a)

$$V_{out} = 1 \rightarrow 0.8(V)$$

$$(b) (1) V_{out} = 0.5 \rightarrow 1(V)$$

$$(2) V_{out} = X \rightarrow 0.5 \rightarrow 1(V)$$

(1)、(2)皆可

3.

(a)

$$D = N \left(\frac{256}{10} \right)^{\frac{1}{N}} + N$$

N	2	3	4	5	6
F	5.06	2.95	2.25	1.91	1.72
D	12.12	11.84	13.00	14.56	16.30

$$N = 3$$

(b)

$$f_i = 2.95$$

$$D = 11.84$$

4.

(a)

$$t_{pdf} = (6+4h)RC$$

$$t_{pdr} = 4C*R/2 + (6+4h)RC = (8+4h)RC$$

$$t_{pd} = (t_{pdf} + t_{pdr})/2 = (7+4h)RC$$

(b)


$$t_{cdf} = (3+2h)RC$$

$$t_{cdr} = (6+4h)RC$$

$$t_{cd} = (t_{cdf} + t_{cdr})/2 = (9/2+3h)RC$$

5.

(a)

 

(b)

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

(c)

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = 3$$

(d)

A > B > C

6.

(a)

$$d = gh + p = 2$$

$$f_{osc} = \frac{1}{2Nd'} = \frac{1}{2 \times 5 \times 2 \cdot 500 \cdot 100f} = 1GHz$$

(b)

Multiply the length of PMOS and NMOS by $\sqrt{2}$.

7.

(a)

$$G = 1 \times \frac{4}{3} \times \frac{5}{3} \times \frac{5}{3} = \frac{100}{27}$$

$$B = 2 \times 2 = 4$$

$$H = \frac{480}{4} = 120$$

(b)

$$F = GBH = \frac{48000}{27}$$

$$N = 4$$

$$P = 1 + 2 + 3 + 2 = 8$$

$$D = NF^{\frac{1}{N}} + P = \textcolor{red}{33.97}$$

(c)

$$f = F^{\frac{1}{N}} = 6.49$$

$$C_{in} = \frac{g \times C_{out}}{f}$$

$$z = \frac{\frac{5}{3} \times 480}{6.49} = 123.27$$

$$\rightarrow y = \frac{\frac{5}{3} \times 123.27}{6.49} = 31.66$$

$$x = \frac{\frac{4}{3} \times 31.66 \cdot 2}{6.49} = 13$$

8.

(a)


$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n1} p_i + (N - n1)p_{inv}$$

(b)

$$N = 10 \rightarrow D = 10 \times \sqrt[10]{1024} + 30 = 50$$


9.

(a)

 

$$\begin{aligned} t_{pd} &= 2000 \times (20f + 400f) + (2000 + 400) \times (400f + 40f) + 1000 \times 40f \\ &= 1.936\text{ns} \end{aligned}$$

(b)

 


$$t_{pd} = \frac{4000}{60} \times (600f + 400f) + \left(\frac{4000}{60} + 400 \right) \times (400f + 40f) + 1000 \times 40f \\ = 0.312\text{ns}$$

10.

- (a) Lightly doped drain: Reduce electrical field of drain junction & hot-electron damage, High sheet resistance
- (b) Structure planarization for further stack process.
- (c) 使用 high-K dielectric 可以降低 EOT，並降低 gate leakage
- (d) 可以增加對 Gate 的控制能力，降低 leakage
- (e) Shallow Trench Isolation: High density & better isolation, need Chemical Mechanical Polishing (CMP) to planarize the structure

11.

(a)

 

$$C_{wire} = 2000\mu\text{m} \times 0.1\text{ fF}/\mu\text{m} = 200\text{fF}$$

$$C_{adl} = 2000\mu\text{m} \times 0.5\text{ fF}/\mu\text{m} = 1000\text{fF}$$

$$\Delta V_Y = \frac{1000\text{fF}}{1000\text{fF} + 200\text{fF}} \times 1.5V = 1.25V$$

(b)

Shielding

Increase the loading cap

Put two wire away

12.

(a) Dynamic power (in W/MHz)

$$P = \alpha CV^2f = [(0.1 \times 20 \times 10^6 \times 5 \times 2) + (0.02 \times 80 \times 10^6 \times 2 \times 2)] \times 1.5^2 \times 10^6 = 59.4 \text{ (mW/MHz)}$$

(b) Static power

$$P = I \times V = [(20 \times 10^6 \times 0.05 \times 10^{-9} \times 5) + (80 \times 10^6 \times 1 \times 10^{-9} \times 2)] \times 1.5 = 247.5 \text{ (mW)}$$

13.

I → c → i → f → g → j → a → k → d → h → b → e

14.

- (a) 講義 2-62: wire attracts charge during plasma processing and builds up voltage
- (b) 講義 4-12 : "Electron wind" causes movement of metal atoms along wires
- (c) 講義 3-11: at high V_{ds} ↗, depletion of S/D ↗, effective $L \searrow$. I_{ds} increase ↗
- (d) 講義 3-11: threshold voltage V_t is influence by V_{bs} (body-to-source voltage)
- (e) 講義 3-11: at high V_{gs} ↗, the carrier scatter more and mobility decrease. I_{ds} decrease ↘
- (f) 講義 4-15: paracitic BJT causes positive feedback leading to VDD – GND short
- (g) 講義 4-13: Current through wire resistance generates heat
- (h) 講義 4-19: Collisions with particles create electron-hole pairs in substrate
- (i) 講義 4-14: Electric fields across channel impart high energies to some carriers
- (j) 講義 3-11: at high V_{ds} ↗, the carrier velocity is not proportional to lateral field. I_{ds} decrease ↘

15.

T T T T F

T F T F F