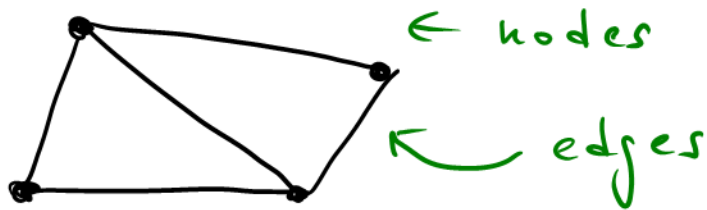


Small world graphs

$$G = \{ \text{nodes, edges} \}$$

= collection of nodes joined by edges

Social network

Each node is a person, two nodes are connected by edges if they are friends

Q: What is the farthest distance between two people in the graph?


Six degrees of separation

⇒ It's a small world! ↓

Other example

WWW: nodes are websites
edges are links

Electrical network

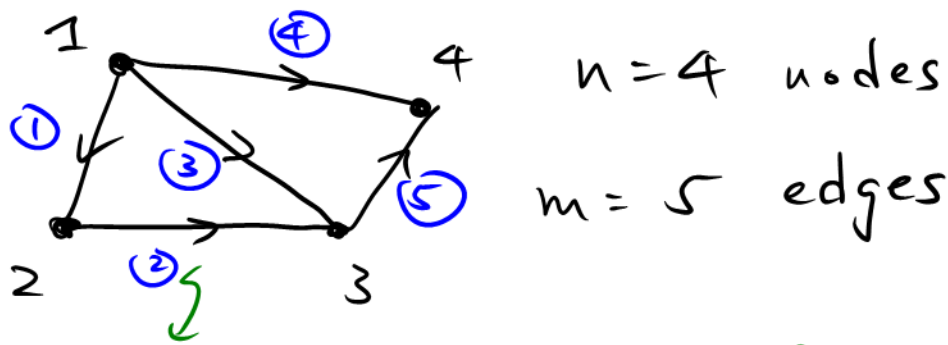

(direction of currents) (Directed graph)

Incidence matrix

one col. for each node, one row for each edge

If edge runs from node 1 \rightarrow node 2
(-1 in col 1) (+1 in col 2)


$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{array}{l} \text{edge 1} \\ 2 \\ 3 \\ 4 \\ 5 \end{array}$$

Node 1 2 3 4 if large

(Incidence matrix A is sparse in general \Rightarrow most entries are zero)

(Each row only has 2 nonzero entries)

Loops:

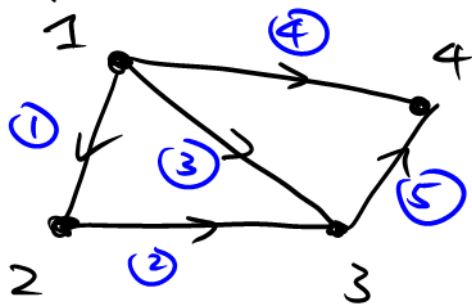

$n = 4$ nodes

$m = 5$ edges

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

Node 1 2 3 4

edge 1 } lin.
 2 } dependent
 3 }
 4 (row 3 = row 1
 5 + row 2)

Null space of A

$\underline{x} = (x_1, x_2, x_3, x_4)$: potentials at nodes

$$A \underline{x} = \underline{0}$$

$$\Rightarrow A \underline{x} = \begin{bmatrix} x_2 - x_1 \\ x_3 - x_2 \\ x_3 - x_1 \\ x_4 - x_1 \\ x_4 - x_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \underline{x} = c \begin{bmatrix} 1 \\ -1 \\ -1 \\ 1 \\ 0 \end{bmatrix}$$

(diff. of potentials)

$\Rightarrow \dim N(A) = 1$ with basis $\begin{bmatrix} 1 \\ -1 \\ -1 \\ 1 \\ 0 \end{bmatrix}$

(Nothing will move if all potentials are the same) (or potential diff. = 0)
 (But potentials can only be determined up to a constant)

(If we ground node 4, $x_4 = 0$
 $\Rightarrow x_1 = x_2 = x_3 = 0$)

Q: What is $\text{rank}(A)$?

$$\text{rank}(A) + \dim N(A) = n = 4$$

$$\Rightarrow \text{rank}(A) = 4 - 1 = 3$$

(We can also see this via Elimination)

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \Rightarrow R = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$


$\uparrow \quad \uparrow \quad \uparrow$
 $\uparrow \quad \uparrow \quad \uparrow$

basis for $C(A)$
pivot col.

(Top 3 rows of R are indep.)

\Rightarrow The graph it forms has no

(loops \Rightarrow It's a tree!)

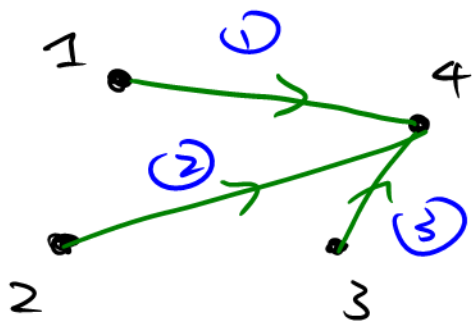

(This is a tree with no loops)

Left nullspace $N(A^T)$

$$A^T \underline{y} = \underline{0}$$

$$\begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\dim N(A^T) = m - r = 5 - 3 = 2$$

($\underline{y} = (y_1, y_2, y_3, y_4, y_5)$ are currents
& $A^T \underline{y} = 0$ is Kirchhoff's current law)

(will come back to this later)


Basis :

$$\text{node 1: } -y_1 - y_3 - y_4 = 0$$

$$\text{node 2: } y_1 - y_2 = 0$$

$$\text{node 3: } y_2 + y_3 - y_5 = 0$$


$$\text{node 4: } y_4 + y_5 = 0$$

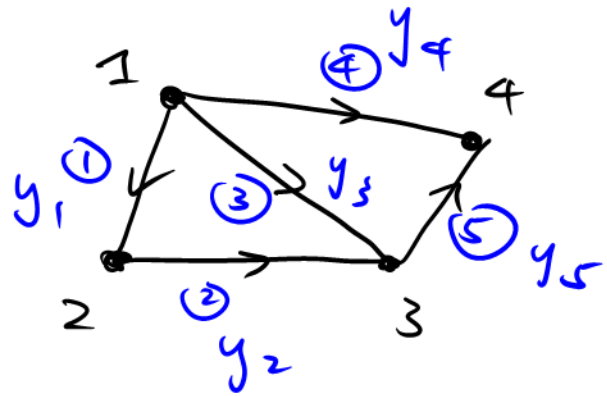

(currents in = currents out)

($-y_1$: current out, $+y_1$: current in)

Basis by inspection:

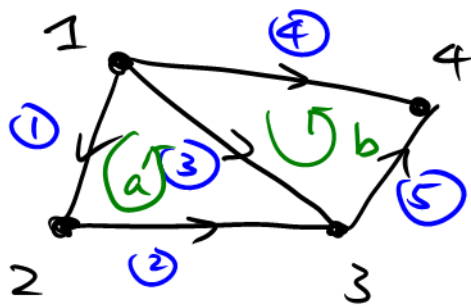

current in loops

$$\text{loop } y = \begin{bmatrix} 1 \\ -1 \\ 0 \\ 0 \end{bmatrix}, \begin{bmatrix} 0 \\ 0 \\ -1 \\ 1 \end{bmatrix}$$

(same as # of loops)

(loop a) (loop b)

($\dim N(A^T) = 2$ so only need these two vectors for a basis)

(Outer loop also gives a special sol. $(1, 1, 0, -1, 1)$)


Row space $C(A^T)$

$$A^T = \begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

↑ ↑ ↑
pivot cols

not a pivot col.
since node 1, 2, 3
forms a loop
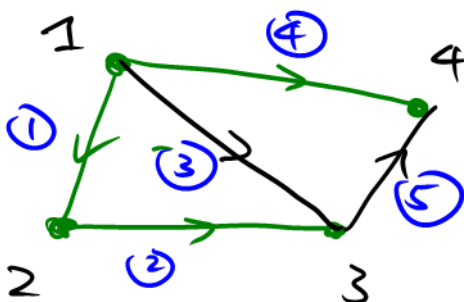
$$\text{rank}(A) = 3 \Rightarrow \dim C(A^T) = 3$$



(lin indep. edges 1, 2, 4
form a tree)

Complete picture

$\underline{x} = (x_1, x_2, x_3, x_4)$
potentials at nodes

$$A^T \underline{y} = \underline{0}$$

Kirchhoff's current law

↓ $A \underline{x} = \underline{e}$ (conductance matrix)

↑ $A^T \underline{y}$

$x_2 - x_1$, etc.

$$\underline{y} = -C \underline{e}$$

y_1, y_2, y_3, y_4, y_5

potential differences

→ Ohm's Law

currents on edges

Euler's formula

$$\dim N(A^T) = m - n$$

$$\# \text{ loops} = \# \text{ edges} - (\# \text{ nodes} - 1)$$


$$(\text{rank} = n - 1) \quad (\dim N(A) \text{ always} = 1)$$

$$\Rightarrow \# \text{ nodes} - \# \text{ edges} + \# \text{ loops} = 1$$

(small loops)

(True for any connected graph)

Ex:

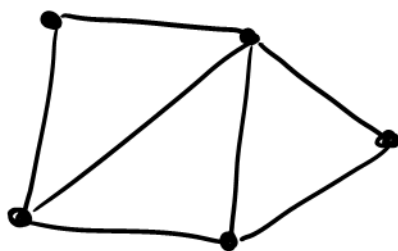

$$5 - 7 + 3 = 1$$

One more thing

Still need an outside source to drive the circuit

Current source \underline{f}

$$\underline{x} = (x_1, x_2, x_3, x_4)$$

potentials at nodes

$$\downarrow A \underline{x} = \underline{e}$$

$x_2 - x_1$, etc.

potential differences

(conductance matrix)

$$\underline{y} = -C \underline{e}$$

Ohm's Law


$$A^T \underline{y} + \underline{f} = \underline{0}$$

Kirchhoff's current law

$$\uparrow A^T \underline{y}$$

y_1, y_2, y_3, y_4, y_5

currents on edges

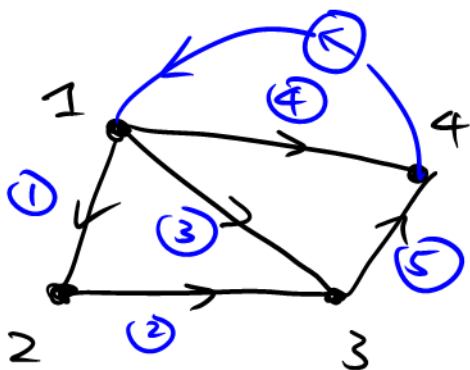

(outside current source

$$\underline{f} = \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix})$$

Combining all 3 eqns

$$A^T C A \underline{x} = \underline{f}$$

Symmetric matrix

Ex 1 in textbook (p. 427)

Ex 1: All conductances are $c=1$
 so $C=I$

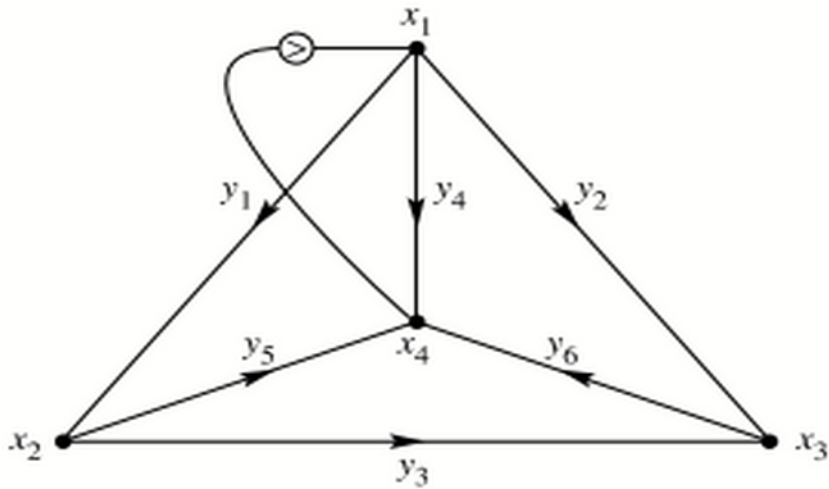


Figure 56: The currents in a network with a source S into node 1.

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$\Rightarrow A^T C A = A^T A$$

$$= \begin{bmatrix} -1 & -1 & 0 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 & -1 & 0 \\ 0 & 1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3 & -1 & -1 & -1 \\ -1 & 3 & -1 & -1 \\ -1 & -1 & 3 & -1 \\ -1 & -1 & -1 & 3 \end{bmatrix}$$

Ground node 4 $\Rightarrow x_4 = 0$

\Rightarrow remove col 4 & row 4 from $A^T C A$

Solve

$$\begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 5/2 \\ 5/4 \\ 5/4 \end{bmatrix}$$

By Ohm's law $y = -C A x$ ($x_4 = 0$)

$$\begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \\ y_6 \end{bmatrix} = - \begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 5/2 \\ 5/4 \\ 5/4 \\ 0 \end{bmatrix} = \begin{bmatrix} 5/4 \\ 5/4 \\ 0 \\ 5/2 \\ 5/4 \\ 5/4 \end{bmatrix}$$

