

Computer Architecture


CH3 Computer Arithmetic (I)

Prof. Ren-Shuo Liu

NTHU EE

Fall 2017



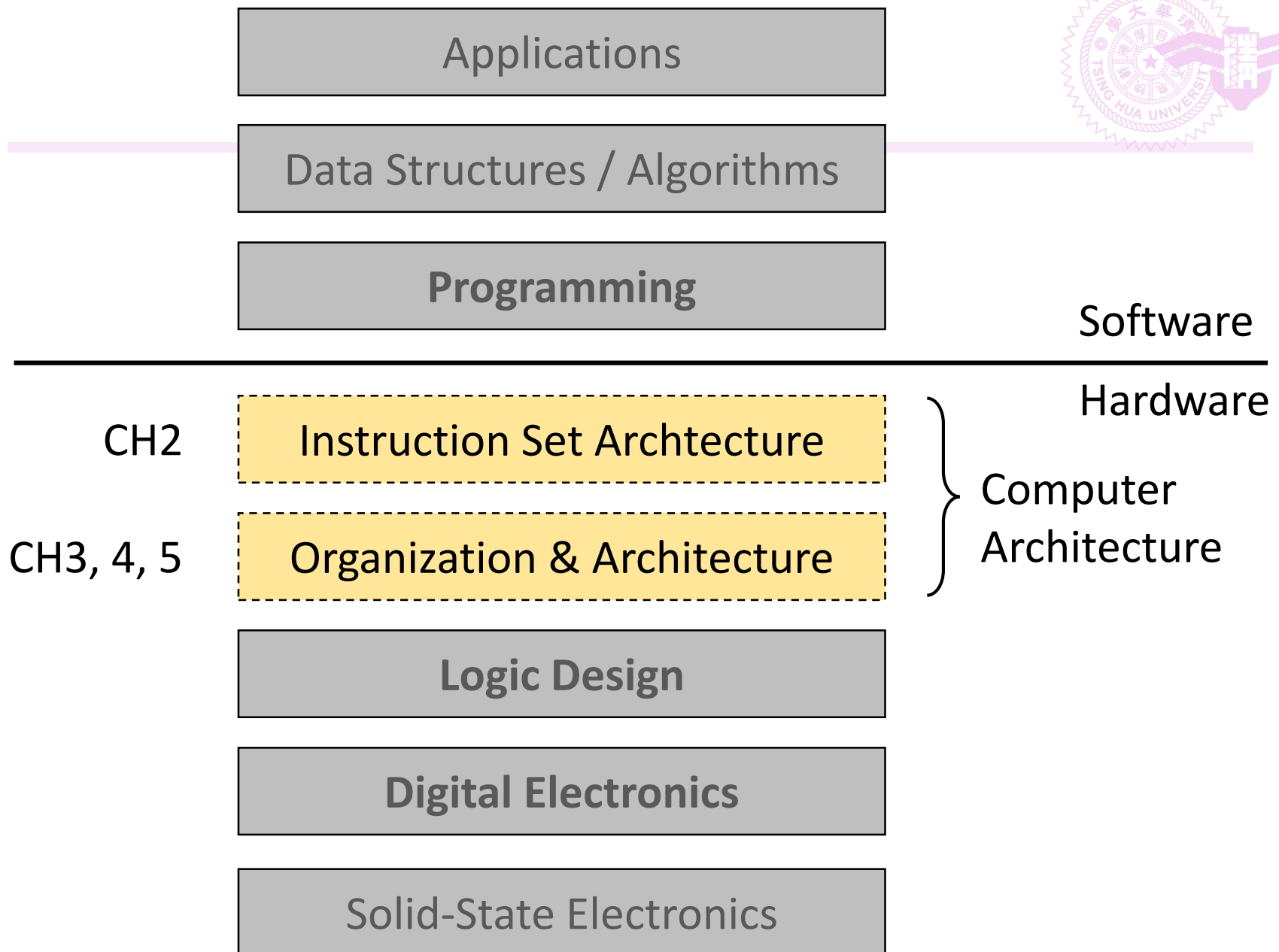



Outline

- Overview
- Integer operations
 - Bit-wise logical operations
 - Additions, subtractions
 - Comparisons
 - Multiplications
 - Divisions
- Floating point operations
 - Additions, subtractions
 - Multiplications



Outline

- **Overview**

- Arithmetic logic unit (ALU)
 - Integer
 - ~~Inter~~ instructions
 - Logic gates
 - Value representation and interpretation
- Integer operations
 - Floating point operations



Common Integer Instructions


- Bit-wise logical

- and, andi
- or, ori
- xor, xori
- nor

and: 做bitwise的AND運算
andi: 做bitwise AND運算，其中一項直接賦值，而不用存到Register
裡面(Ex: a = b & 0xff)

- Arithmetic


- add, addi
- sub
- mult
- div

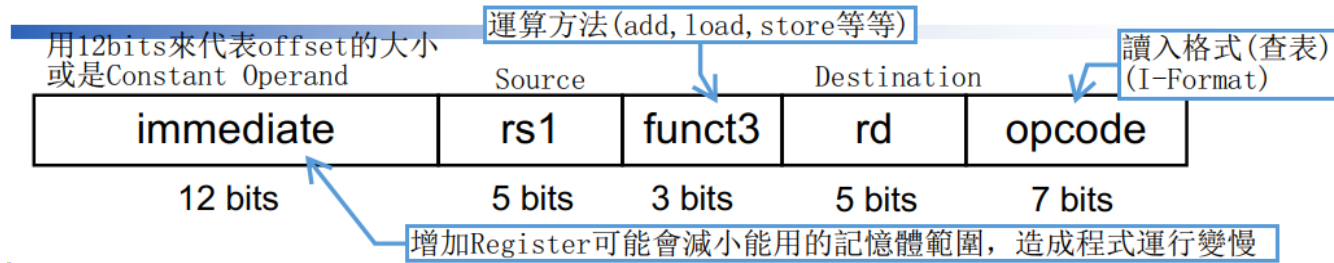

- Comparisons


- slt, slti, sltu, sltiu

兩個unsigned
數字做比較

 


Arithmetic Logic Unit (ALU)

ADDI R1, R2, 100

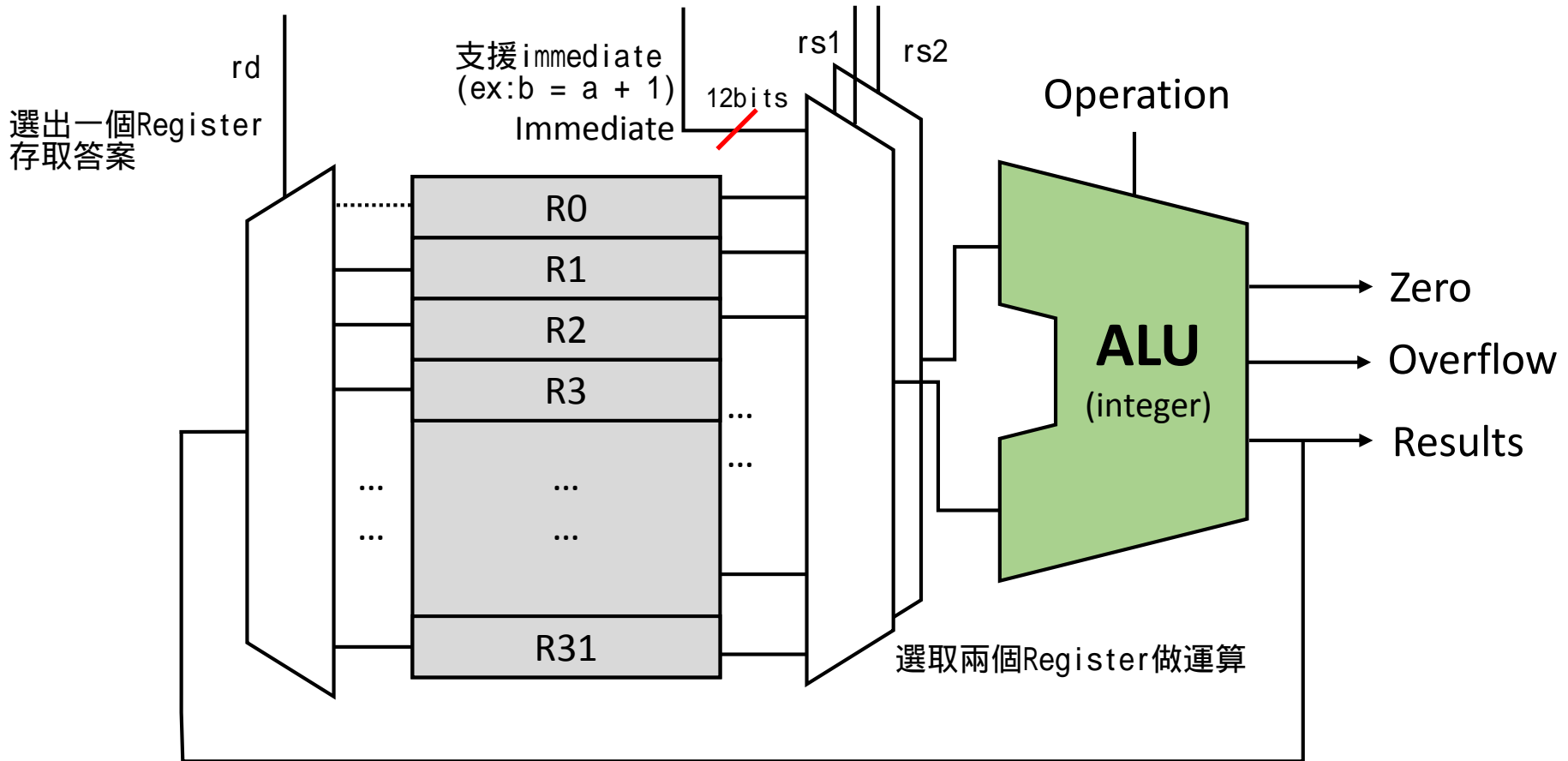




Integer ALU Block Overview

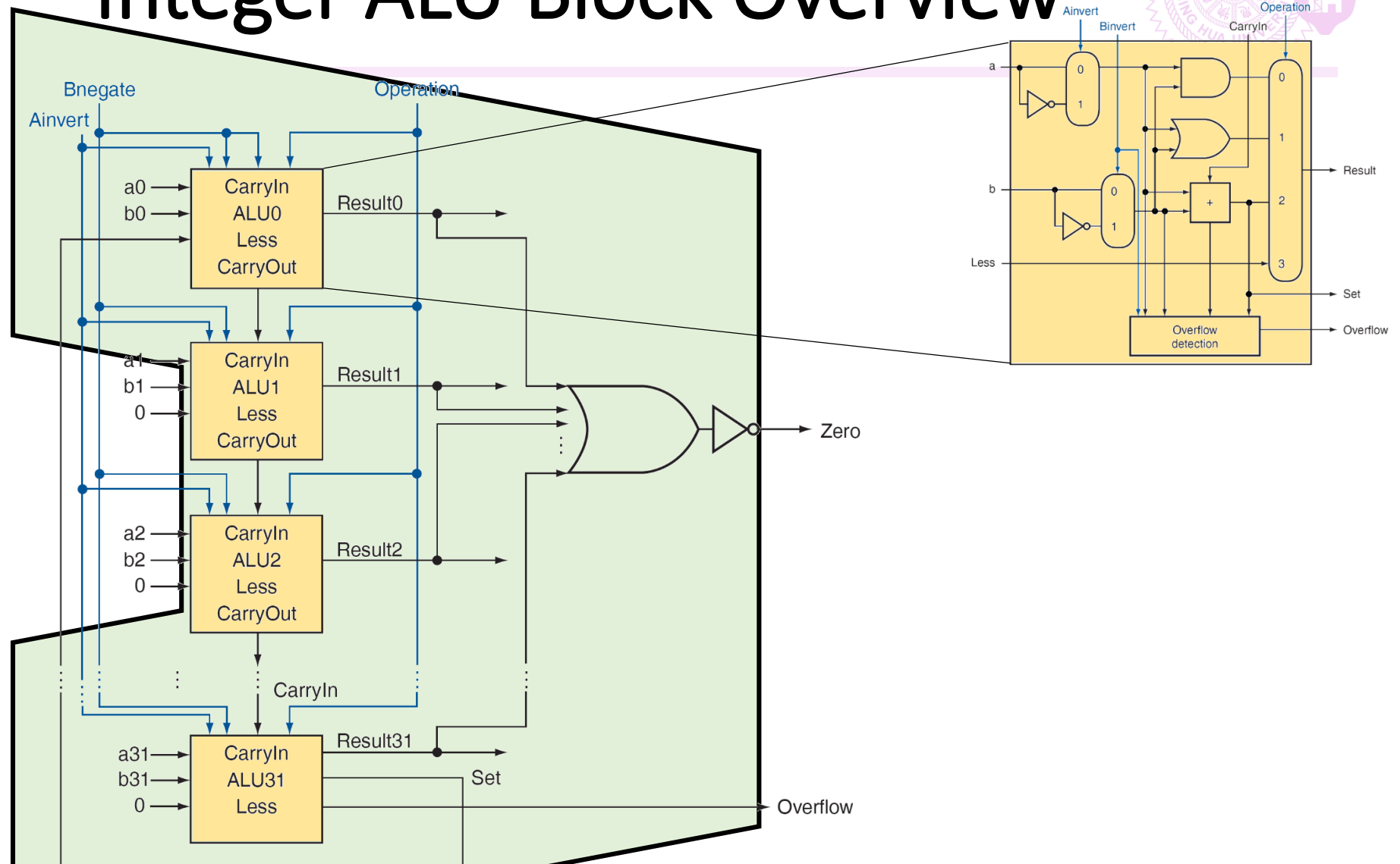





Logic Gates

 

In	Out
all 1's	1
others	0

 

In	Out
all 0's	0
others	1

 


In	Out
0	1
1	0




Logic Gates (Cont'd)

OR Gate + NOR Gate

 


Exclusive OR

 

奇數個1輸出為1

In	Out
all 0's	1
others	0

In	Out
odd num. of 1's	1
others	0

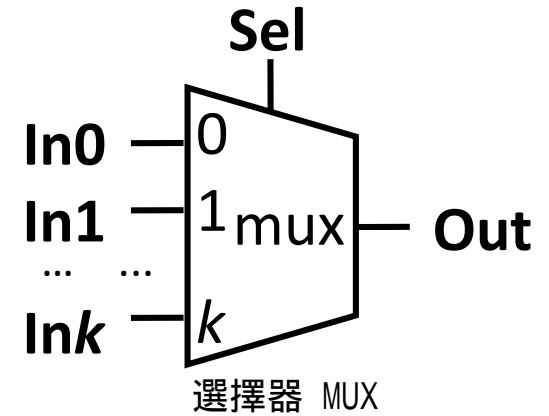


Sel	Out
0	In0
1	In1
...	...
k	Ink




Value Representation and Interpretation

Representation (表示方式)

 


Interpretation (解讀方式)

 



Value Representation and Interpretation

Two representation strategies (兩種表示方式)

 


(Excess-11)



Value Representation and Interpretation


Two interpretation strategies (兩種解讀方式)

 



Binary Unsigned Integers


a 32-bit register

 

- Above is interpreted as $(2^{31}+2^{30}+2^{12}+2^8+2^5+2^3+2^0)$
- Range
 - Min: 0
 - Max: ~~$2^{33}-1$~~
 $2^{32}-1$




Unsigned Integers (Cont'd)

 

N-bit unsigned integers
can have 2^N values



Unsigned Integers (Cont'd)

 



Signed Integers


Signed(有正負)

- Many widely-used **representations**
 - Biased/offset/excess-K
 - Signed magnitude
 - Two's complement




Biased / Offset / Excess-K

a 32-bit register

 


- Above is interpreted as
 - $(2^{30}+2^{12}+2^8+2^5+2^3+2^0) - K$
 - Where K is a predefined value
- Range
 - Most negative: $-K$
 - Most positive: $2^{32} - K - 1$

先減去K

 


Sign Magnitude Representation

a 32-bit register

 


- Above is interpreted as
 - $S \times (2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0)$
 - $(2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0)$ if sign == 0 (i.e., positive)
 - $-(2^{31} - (2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0))$ if sign == 1 (i.e., negative)

 - Range
 - Most negative: $-2^{31} + 1$
 - Most positive: $2^{31} - 1$




2's Compliment Signed Integers


a 32-bit register

 


 - Above is interpreted as
 - $S \times (-2^{31}) + (2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0)$
 - $(2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0)$ if sign == 0 (i.e., positive)
 - $-(2^{31} - (2^{30} + 2^{12} + 2^8 + 2^5 + 2^3 + 2^0))$ if sign == 1 (i.e., negative)
- Range
 - Most negative: $-(2^{31} - 1)$
 - Most positive: $2^{31} - 1$





2's Compliment Signed Integers (Cont'd)

 

 



2's Compliment Signed Integers (Cont'd)

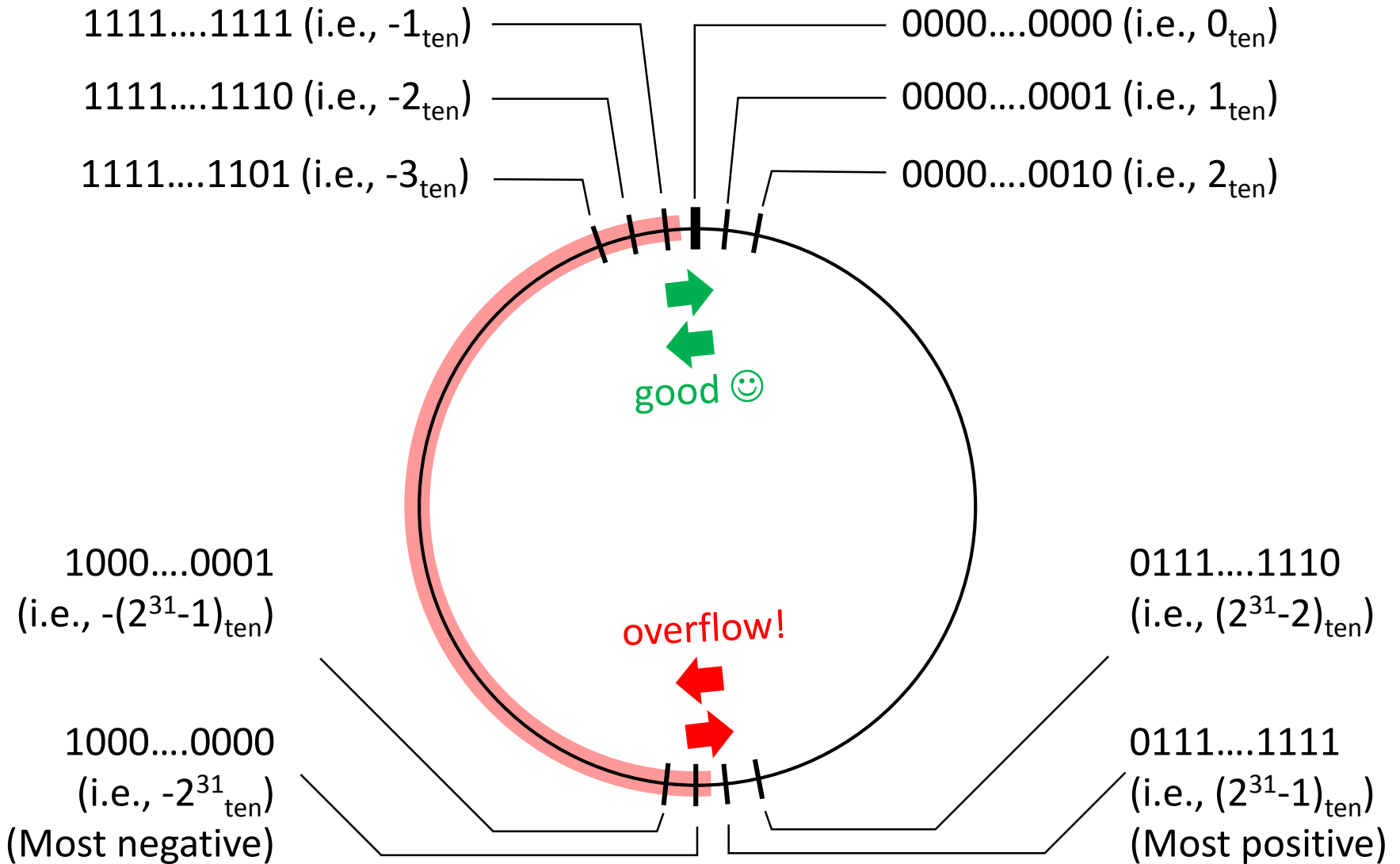

 

2's Compliment Signed Integers (Cont'd)

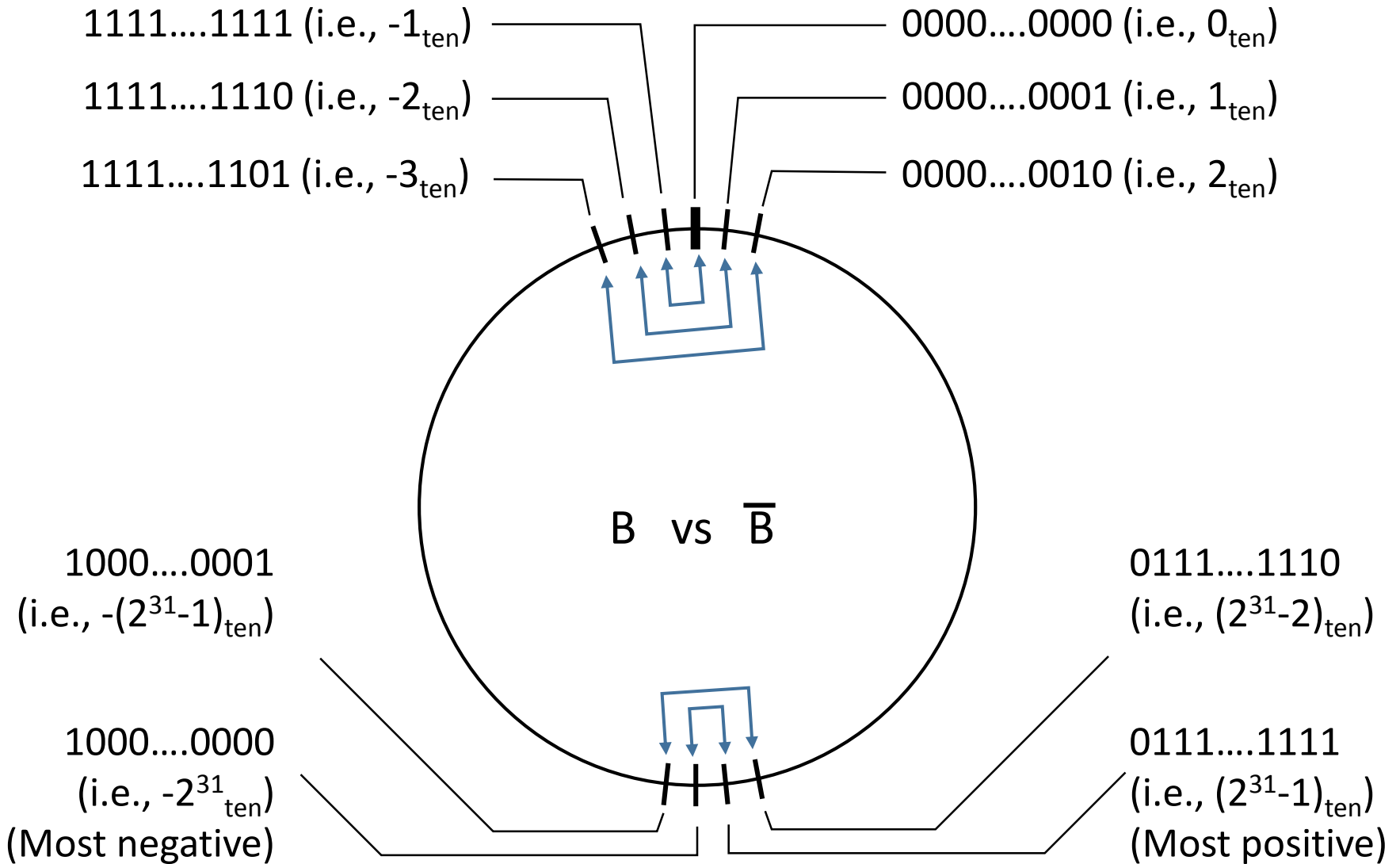

 

2's Compliment Signed Integers (Cont'd)

1111...1111 (i.e., -1_{ten}) \longleftrightarrow 0000...0000 (i.e., 0_{ten})
1111...1110 (i.e., -2_{ten}) \longleftrightarrow 0000...0001 (i.e., 1_{ten})
1111...1101 (i.e., -3_{ten}) \longleftrightarrow 0000...0010 (i.e., 2_{ten})

$$-B = \bar{B} + 1 = 2^N - B$$
$$\bar{B} = -(B + 1) = 2^N - (B + 1)$$

1000...0001 (i.e., $-(2^{31}-1)_{ten}$) \longleftrightarrow 0111...1110 (i.e., $(2^{31}-2)_{ten}$)
1000...0000 (i.e., -2^{31}_{ten}) (Most negative) \longleftrightarrow 0111...1111 (i.e., $(2^{31}-1)_{ten}$) (Most positive)




Outline

- Overview
- Integer operations
 - Bit-wise logical operations
 - Additions, subtractions
 - Comparisons
 - Multiplications
 - Divisions
- Floating point operations
 - Additions, subtractions
 - Multiplications




Bit-Wise Logical Operations

 - Common CPU instructions
 - and, andi, or, ori, nor, xor, xori
- Example
 - and R1, R4, R5 // R1 = (R4 & R5)






Supporting AND is Easy

 




Support AND (Block Diagram)

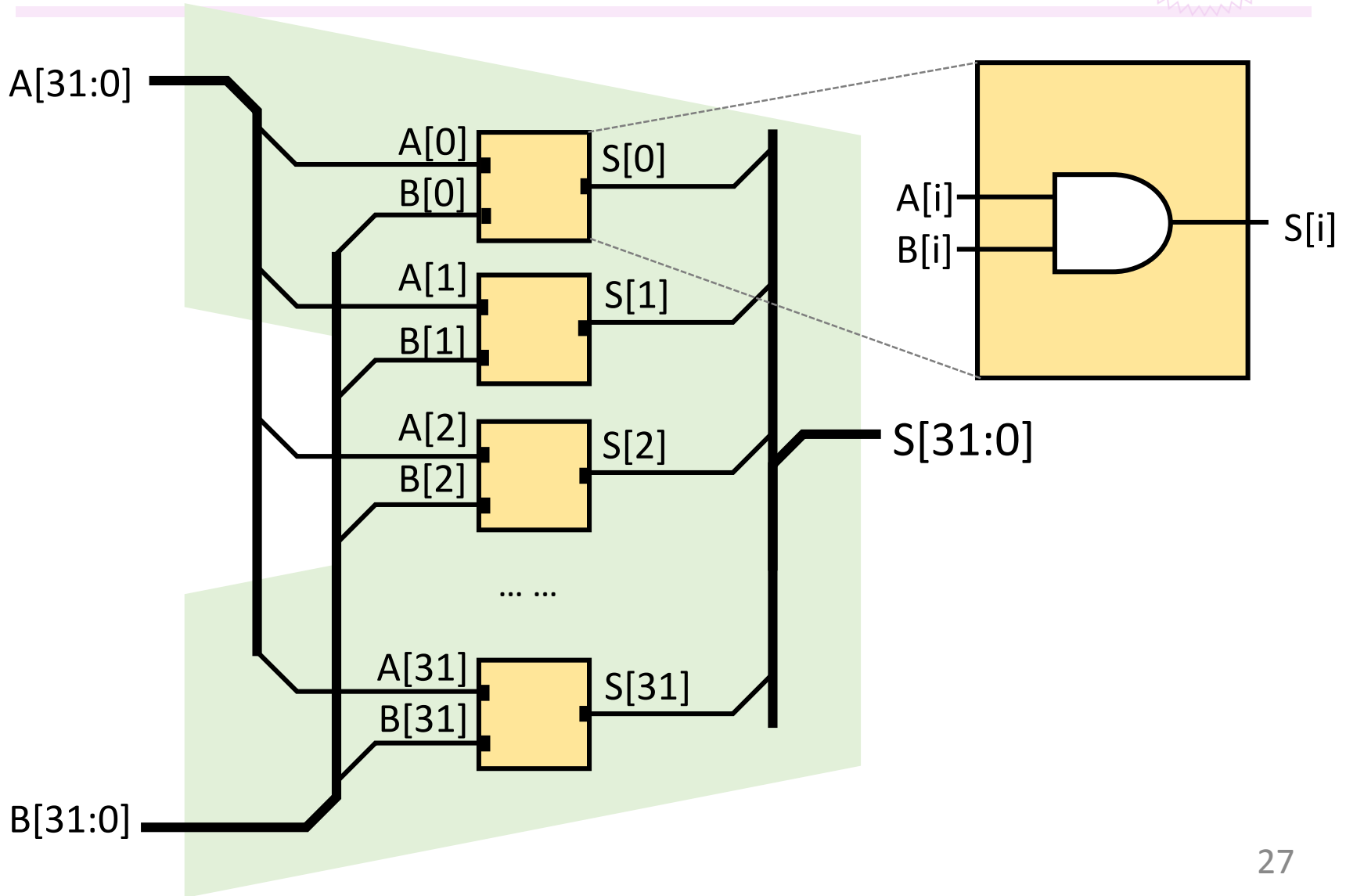




Support OR

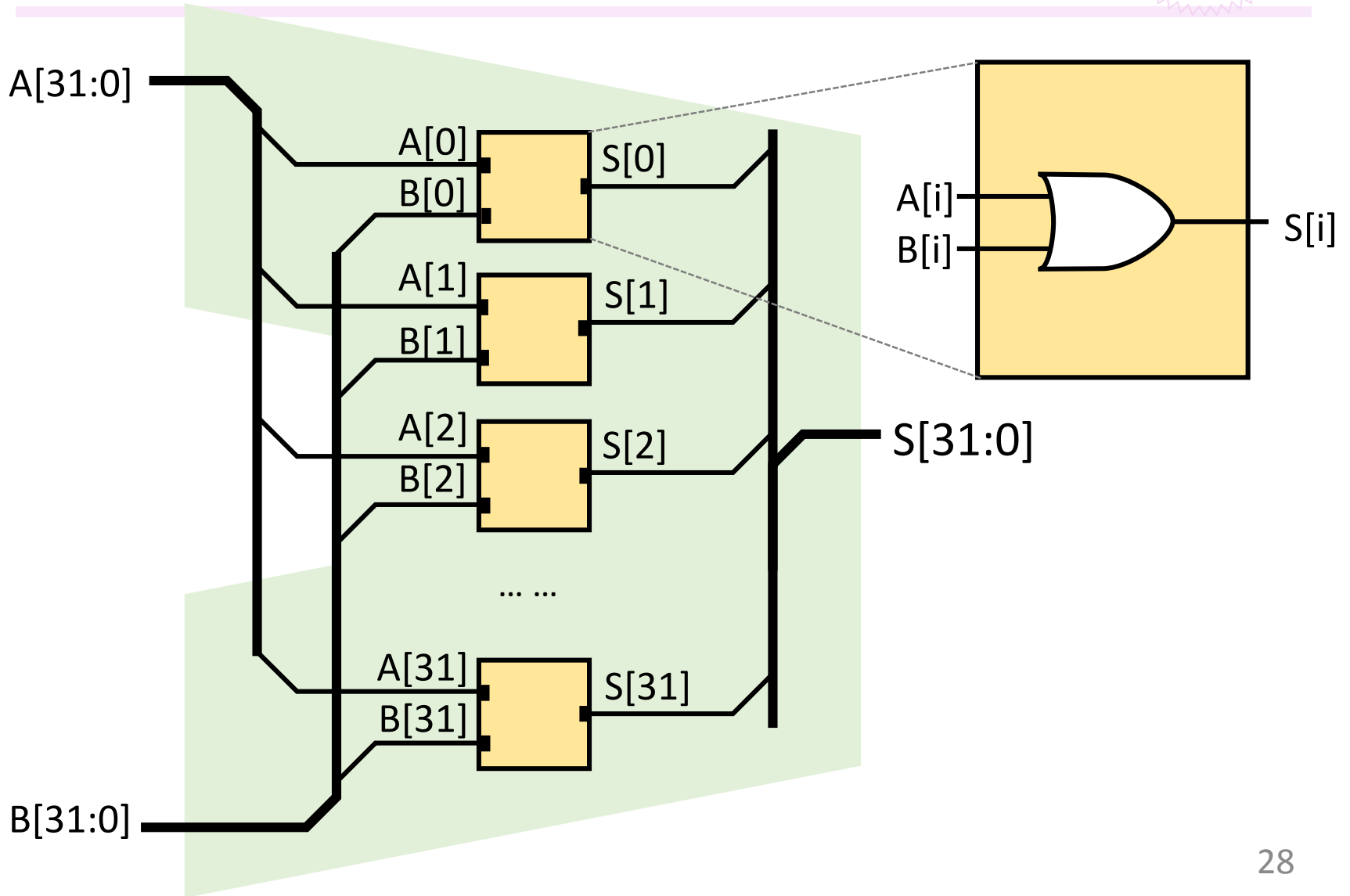



Support Both AND and OR

 




Support All Logical Instructions

- and, andi, or, ori, xor, xori, nor


由machine code存的2個bit去選取要操作的operation

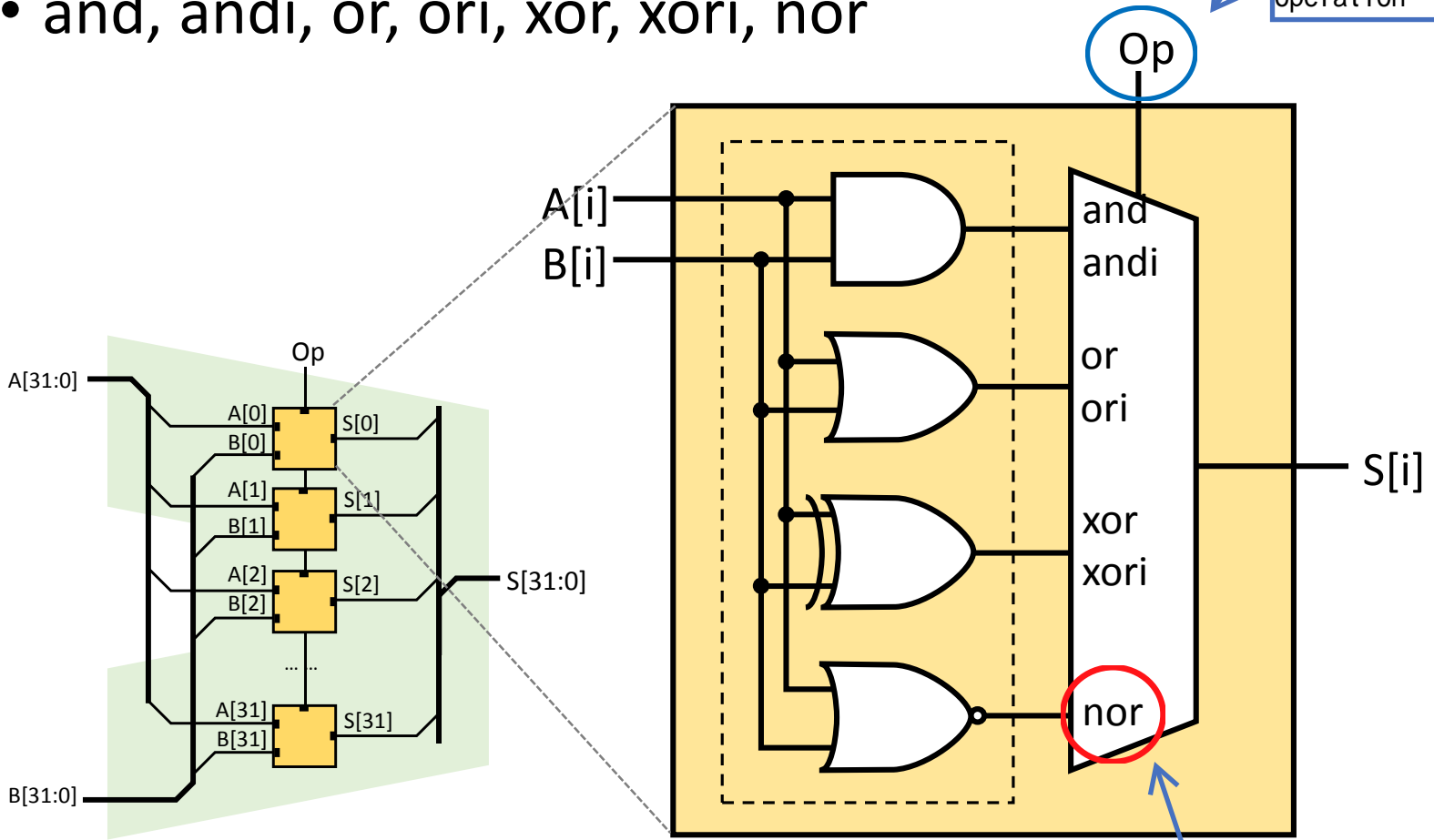


因為nori 較不常用，又指令集空間有限，故不做



Further Support ADD

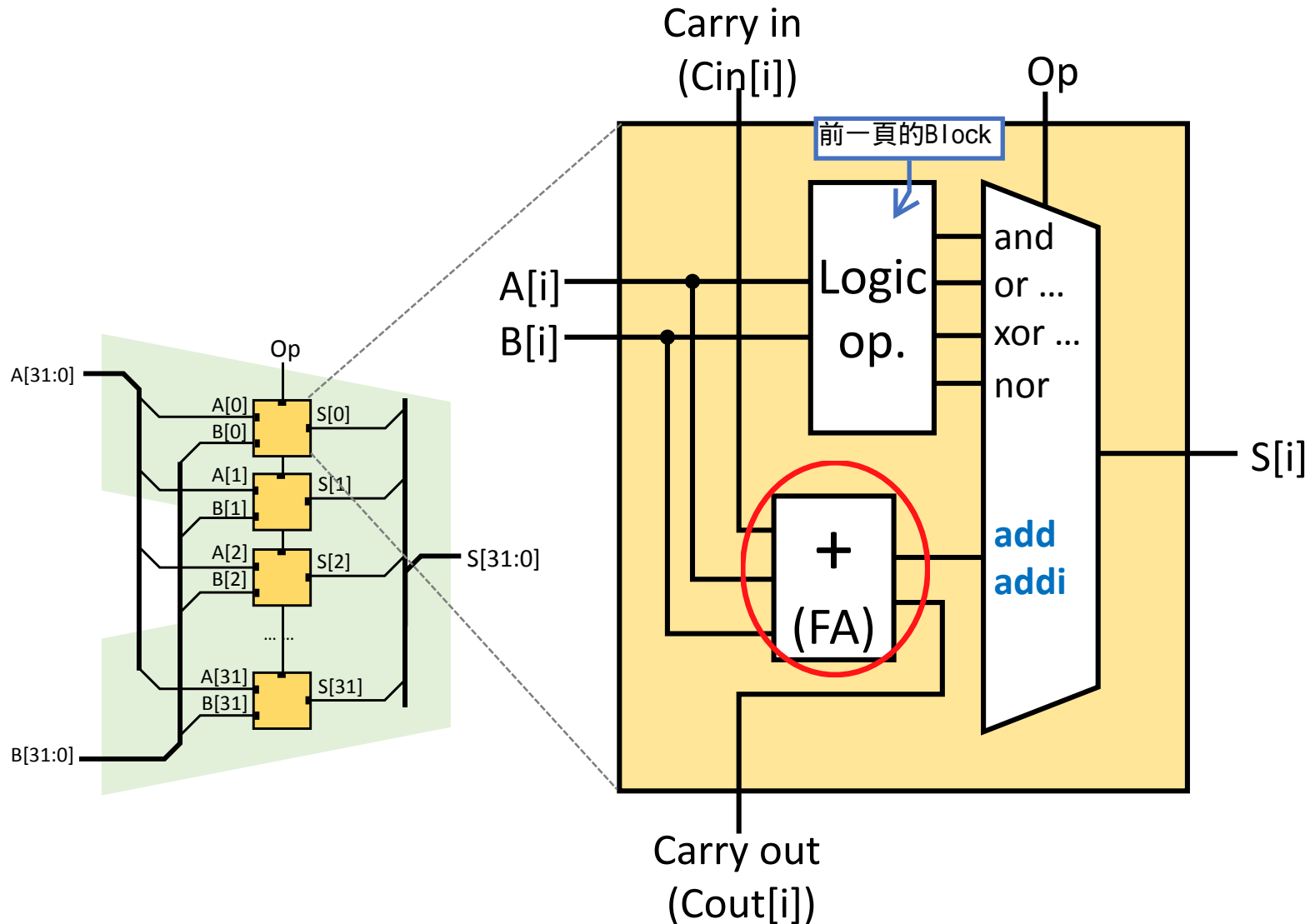


1-Bit Full Adder (FA)

 

- Outputs = the sum of the three input bits

$Cin[0]$	$A[i]$	$B[i]$	$Cout[i]$	$S[i]$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


1-Bit Full Adder (FA)

 

- Some observations
 - Three inputs are interchangeable
 - Outputs = the number of 1's in the inputs
 - S is 1 if the number of 1's is odd (i.e., XOR)
 - Cout (進位) is 1 if the number of 1's ≥ 2

Cin[0]	A[i]	B[i]	Cout[i]	S[i]
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


1-Bit Half Adder (HA)

 

- Outputs = the sum of the two input bits

A[i]	B[i]	Cout[i]	S[i]
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

1-Bit Half Adder (HA)

 


- Some observations
 - Two inputs are interchangeable
 - Outputs = the number of 1's in the inputs
 - S is 1 if the number of 1's is odd (i.e., XOR)
 - Cout (進位) is 1 if both the inputs are 1's (i.e., AND)



$A[i]$	$B[i]$	$Cout[i]$	$S[i]$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



Building a 1-Bit Full Adder

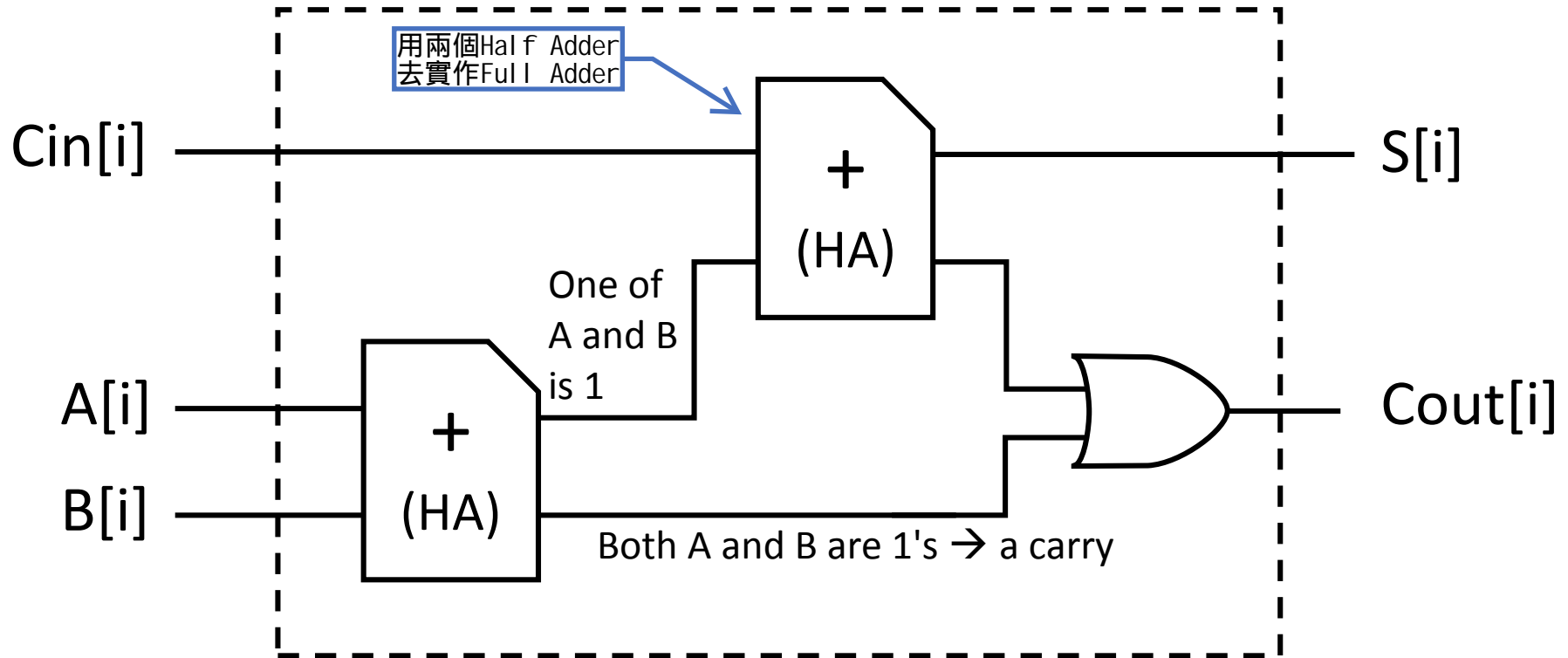


Building a 1-Bit Full Adder (Cont'd)

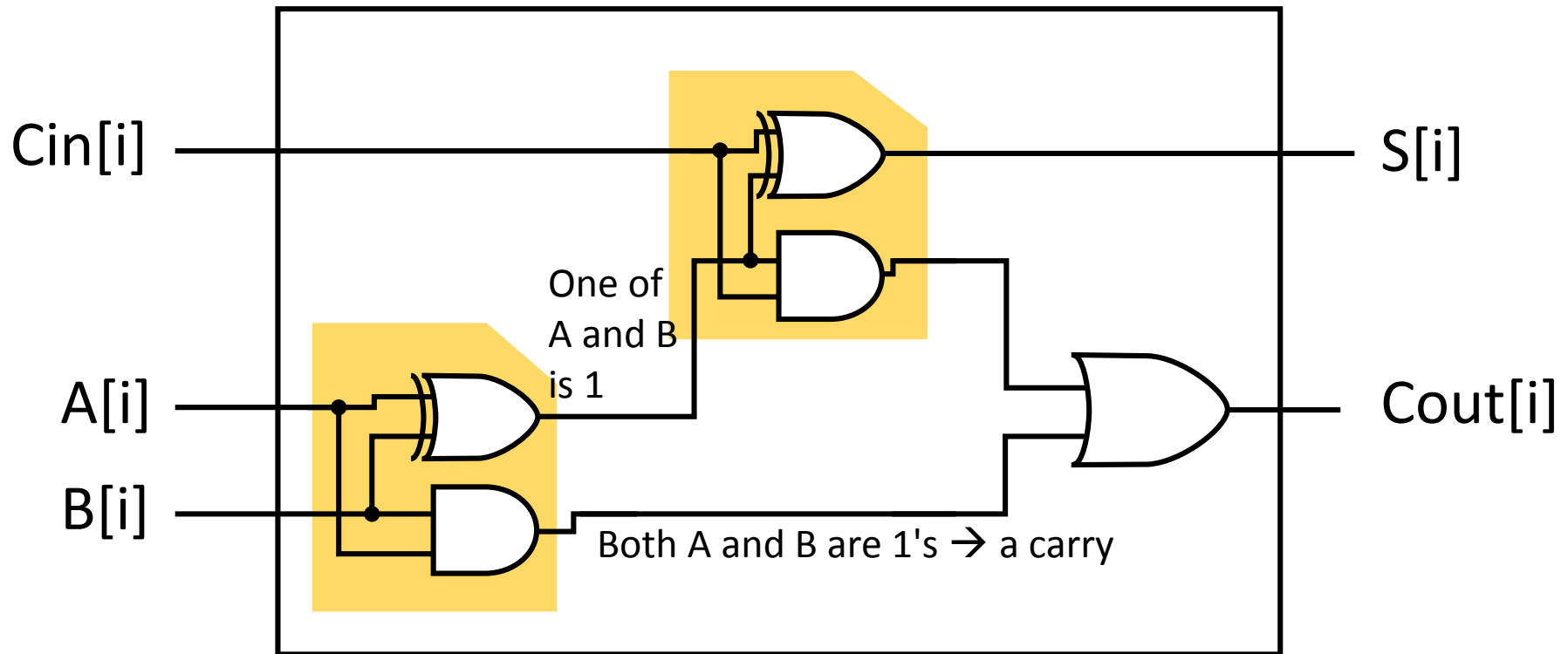 



Addition

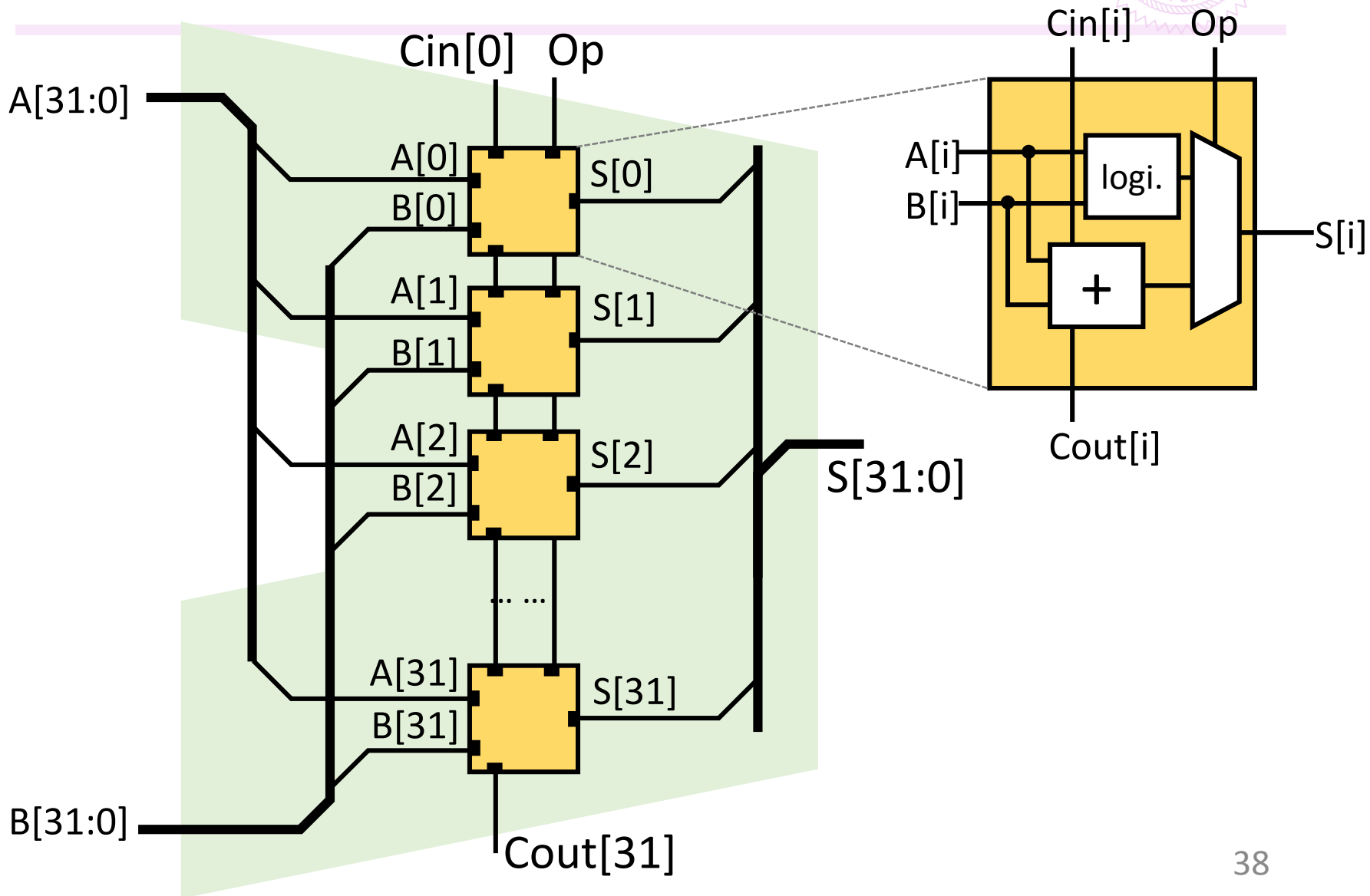




Subtraction

- Subtraction can be done using an addition and an negation(取負)


- $A - B$
 $= A + (-B)$
 $= A + (\overline{B} + 1)$

- E.g., in 5-bit (modulo 32) arithmetic

 - $7 - 11$
 $= 7 + (-11)$
 $= 7 + 21$ // $32 - 11 = 21$; $(\overline{11} + 1) = 21$
 $= -4$ // interpreted as signed




||

 



Subtraction

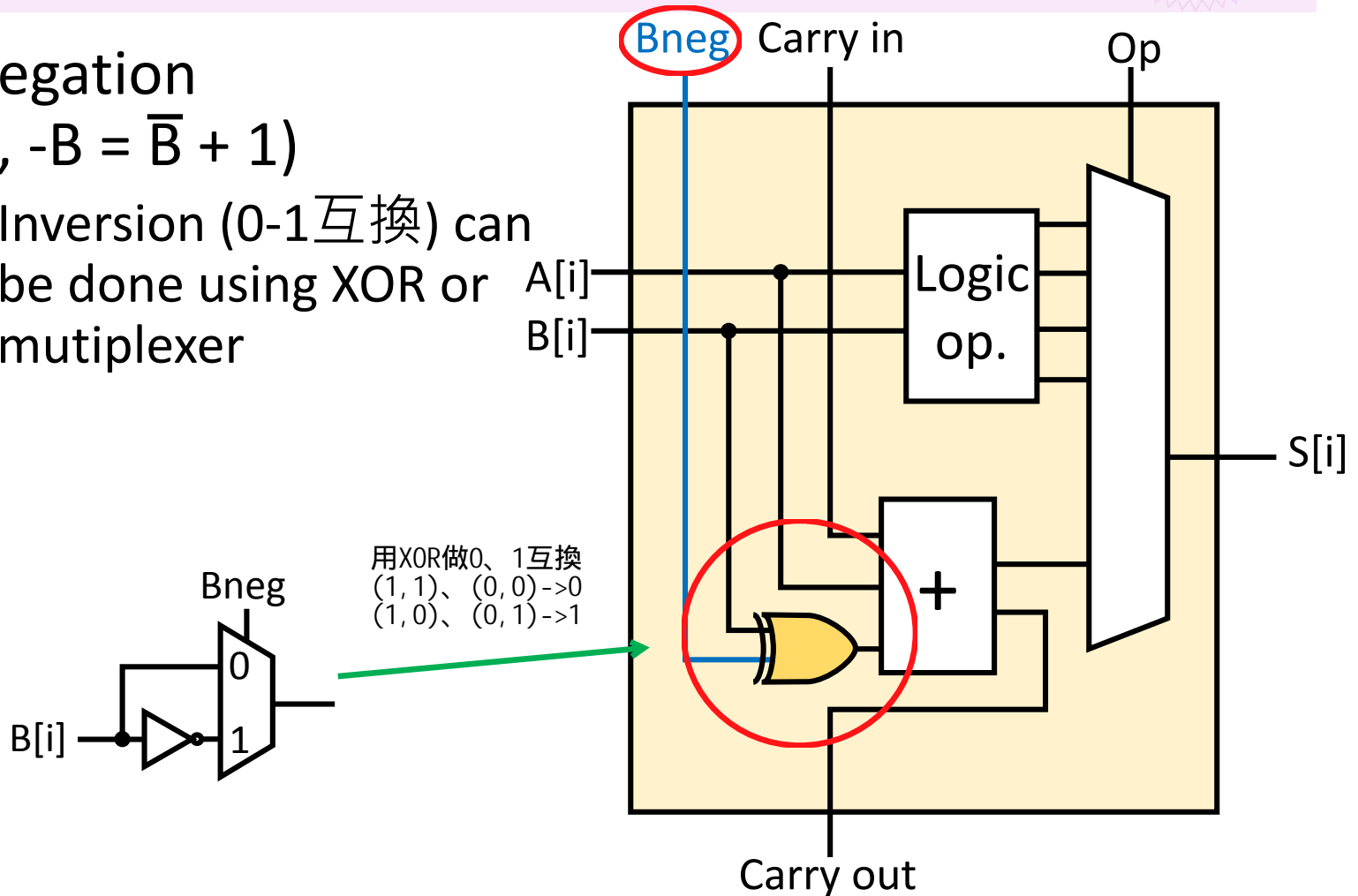- B negation (i.e., $-B = \bar{B} + 1$)
 - Inversion (0-1互換) can be done using XOR or multiplexer







Subtraction

如果是Subtraction, BNeg=1
(1,0互換), 同時Cin[0]=1(+1)
=>所以可以接在一起

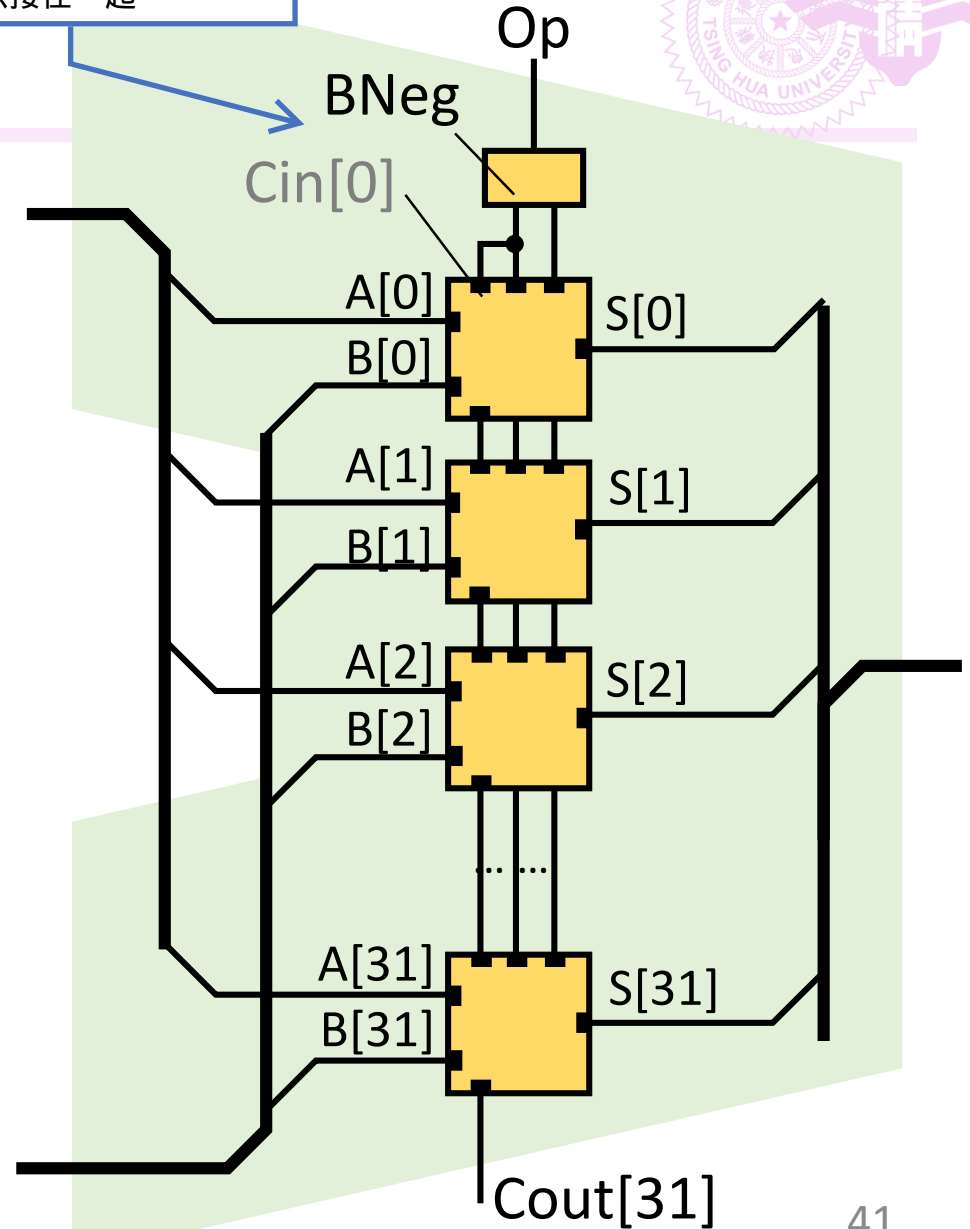
- B negation
(i.e, $-B = \bar{B} + 1$)
 - +1 is done by using Cin[0]



 

Zero Detection

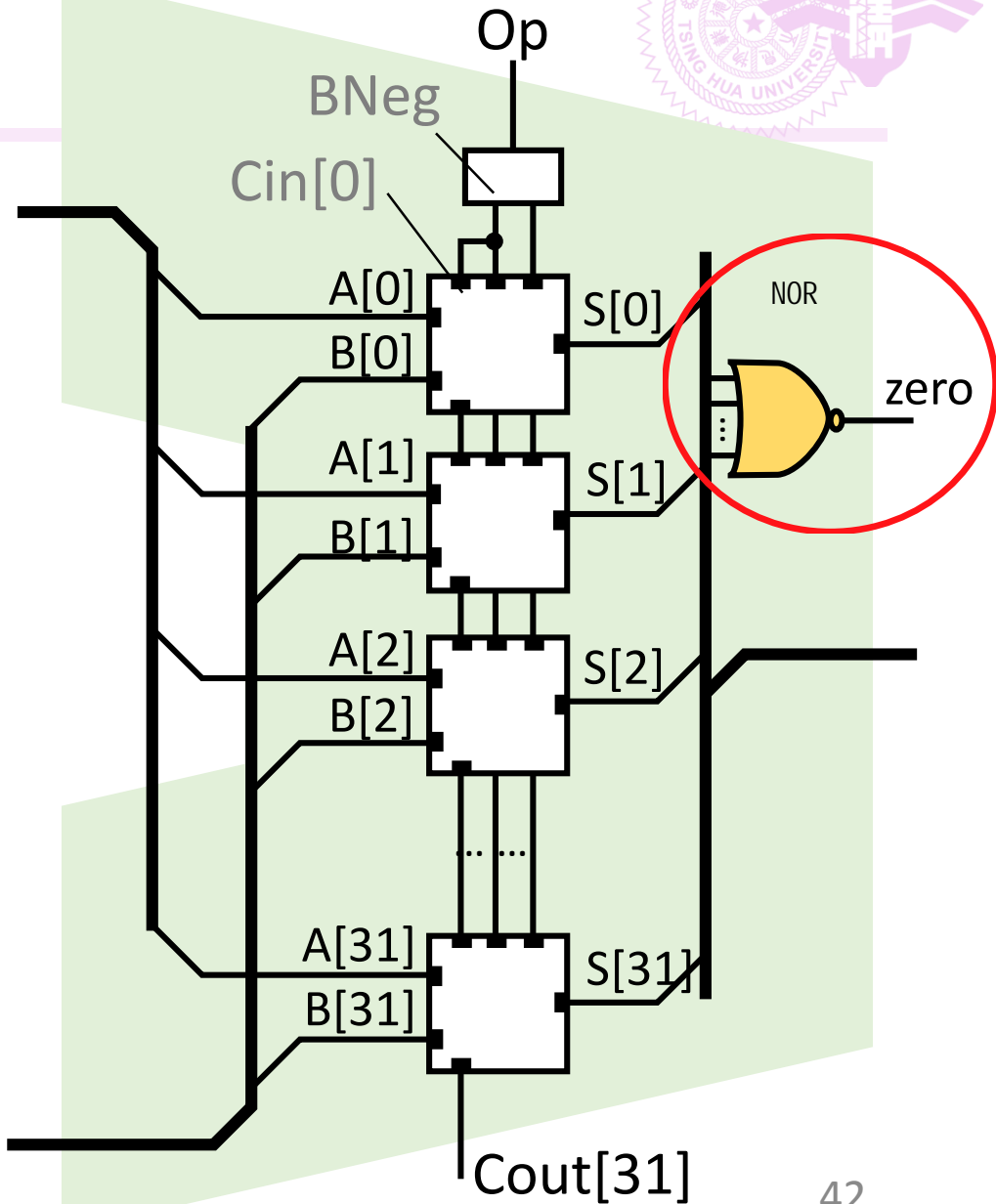- Indicate whether the output 32-bit result is a zero





Overflow Detection


- Before describing overflow detection methods, some things need to be clarified
 - Overflow detection methods are different for signed and unsigned operations
 - Comparisons (SLT and SLTU) are related to overflow detection



Overflow Detection (Signed Add)

A	B	S=A+B	overflow?
+	+	-	Yes
-	-	+	Yes
+	+	+	No
-	-	-	No
+	-	(overflow cannot occur)	
-	+		
0	+		
0	-		
+	0		
-	0		

Overflow Detection (Signed Add)

 


- According to the above descriptions

兩個正數相加後變成負的(Overflow)

A[31]	B[31]	Cin[31]	Cout[31]	S[31]	Overflow
0	0	0	0	0	0
0	0	1	0	1	Yes
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	Yes
1	1	1	1	1	0

傳統作法：將兩個Case做OR Gate去輸出是否Overflow
(先3個做AND Gate)

兩個負數相加後變成正的(Overflow)

 

Overflow Detection (Signed Add)

- Tricky approach

Tricky作法: 觀察Cin和Cout發現兩者不相等就Overflow

A[31]	B[31]	Cin[31]	Cout[31]	S[31]	Overflow
0	0	0	0	0	0
0	0	1	0	1	Yes
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	Yes
1	1	1	1	1	0



Overflow Detection (Unsigned Add)

A	B	A + B overflow?
non-zero	non-zero	If (A+B) produces a carry
0	non-zero	(cannot occur)
non-zero	0	
0	non-zero	

Overflow condition: If (A+B) produces a carry



Overflow Detection (Unsigned Sub)

A	B	A - B = A + (-B) overflow?
non-zero	non-zero	If (A-B) > A (i.e., if A + (-B) does not produce a carry)
0	non-zero	
non-zero	0	(cannot occur)
0	0	

只要A-B<0對於unsigned來說
就是overflow

Overflow condition: If A + (-B) does not produce a carry


Unsigned Integers和2's complement都是用一樣的加法電路，但是在判斷overflow有些不同。



Overflow Detection (Unsigned Operands)

- 7 + 11
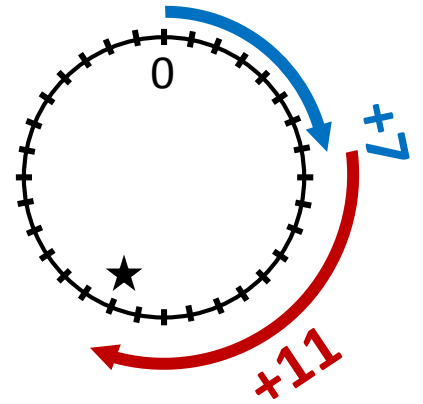
$$\begin{array}{r}
 00111 \\
 + 01011 \\
 \hline
 010010
 \end{array}$$




- 7 + 26 (overflow)

$$\begin{array}{r}
 00111 \\
 + 11010 \\
 \hline
 100001
 \end{array}$$

↖ 1

 carry==1 during unsigned add indicates overflow






Overflow Detection (Unsigned Operands)


- $7 - 11$
 $= 7 + (-11)$
 $= 7 + 21$ (11' +1)
 $= 28$ 😞

carry==0 during unsigned sub indicates overflow
 
$$\begin{array}{r}
 00111 \\
 + 10101 \\
 \hline
 011100
 \end{array}$$






||

 



Overflow Detection

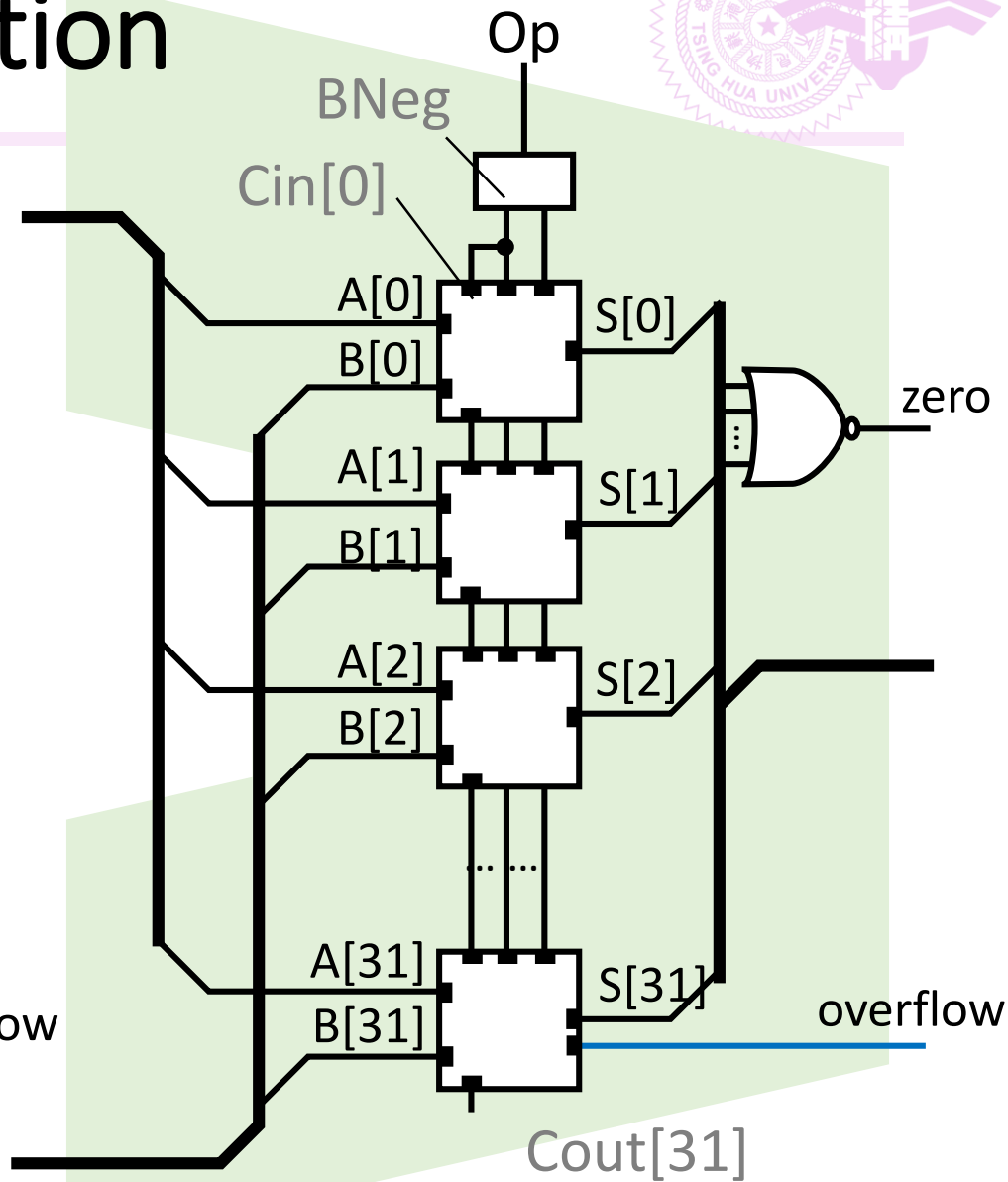 

 


More Discussions on Overflow

- Different languages have different designs

Language	Unsigned integer	Signed integer
Ada	modulo the type's modulus	raise Constraint_Error
C/C++	modulo power of two	undefined behavior
C#	modulo power of 2 in unchecked context; System.OverflowException is raised in checked context	
Java	NA	ignored
Python 2	NA	convert to long
Seed7	NA	raise OVERFLOW_ERROR
Scheme	NA	convert to bigNum
Smalltalk	NA	convert to LargeInteger
Swift	Causes error unless using special overflow operators.	

繞回1(對 2^n 取餘數)

 

wikipedia



SLT and SLTU (Set Less Than)



- Requirements
 - ALU outputs 1 (i.e., 0000...0001) if $A < B$, otherwise outputs 0
- Methods
 - Leverage SUB and SUBU hardware

所以最後set要接回去第一個bit

	Operation	Overflow	Sign(S) (i.e., S[31])	Carry out (i.e., S[32])	Outcome
SLT	$S = A - B = A + \overline{B} + 1$	0	1 $A - B < 0$	Don't Care	1 ($A < B$)
			0		0 ($A \geq B$)
		1	1		0 ($A \geq B$)
			0		1 ($A < B$)
SLTU Unsigned	Don't care	Don't care	No Carry ->Overflow ($A - B < 0$)	1	0 ($A \geq B$)
			0	1 ($A < B$)	



SLT (Set Less Than)

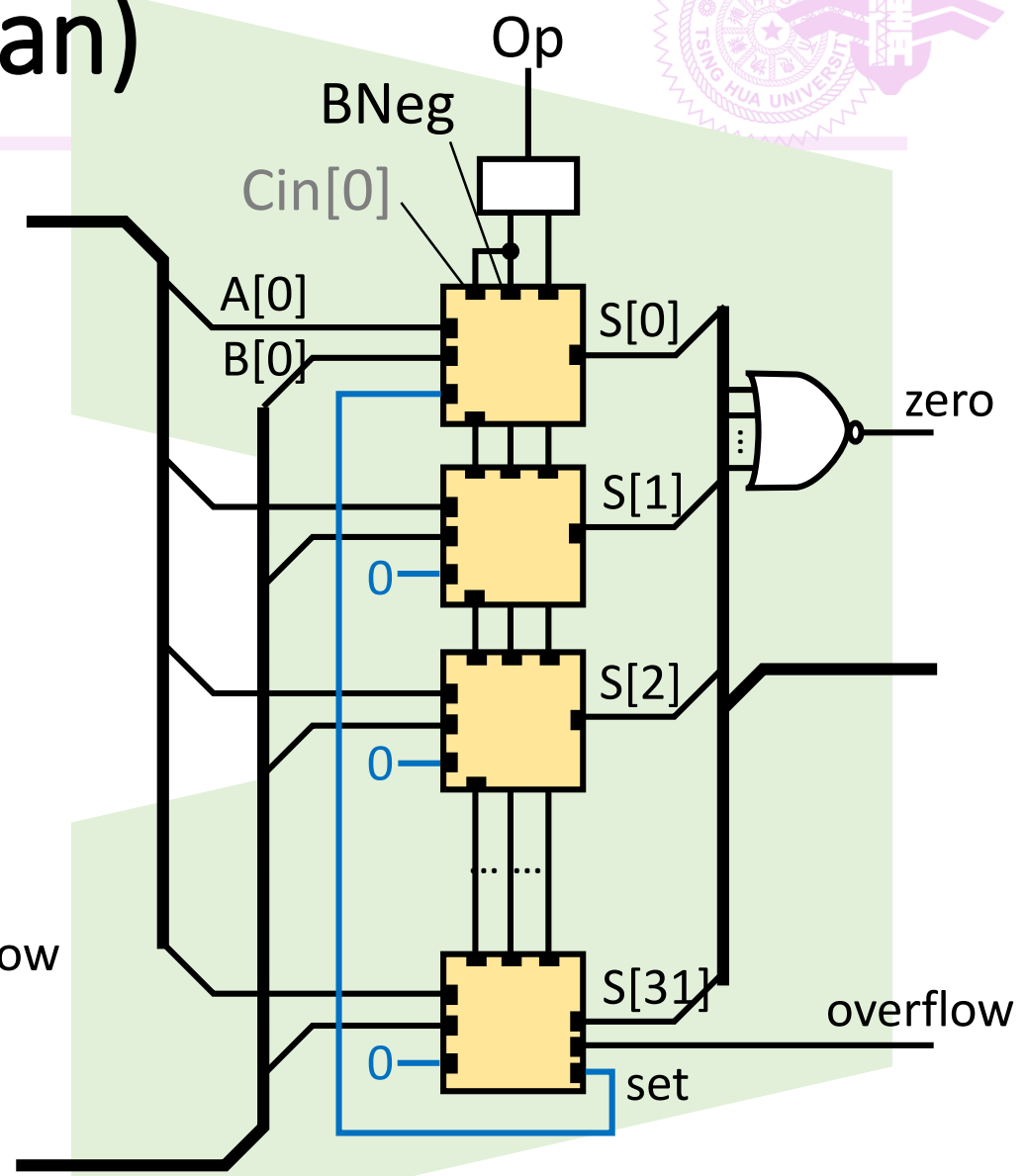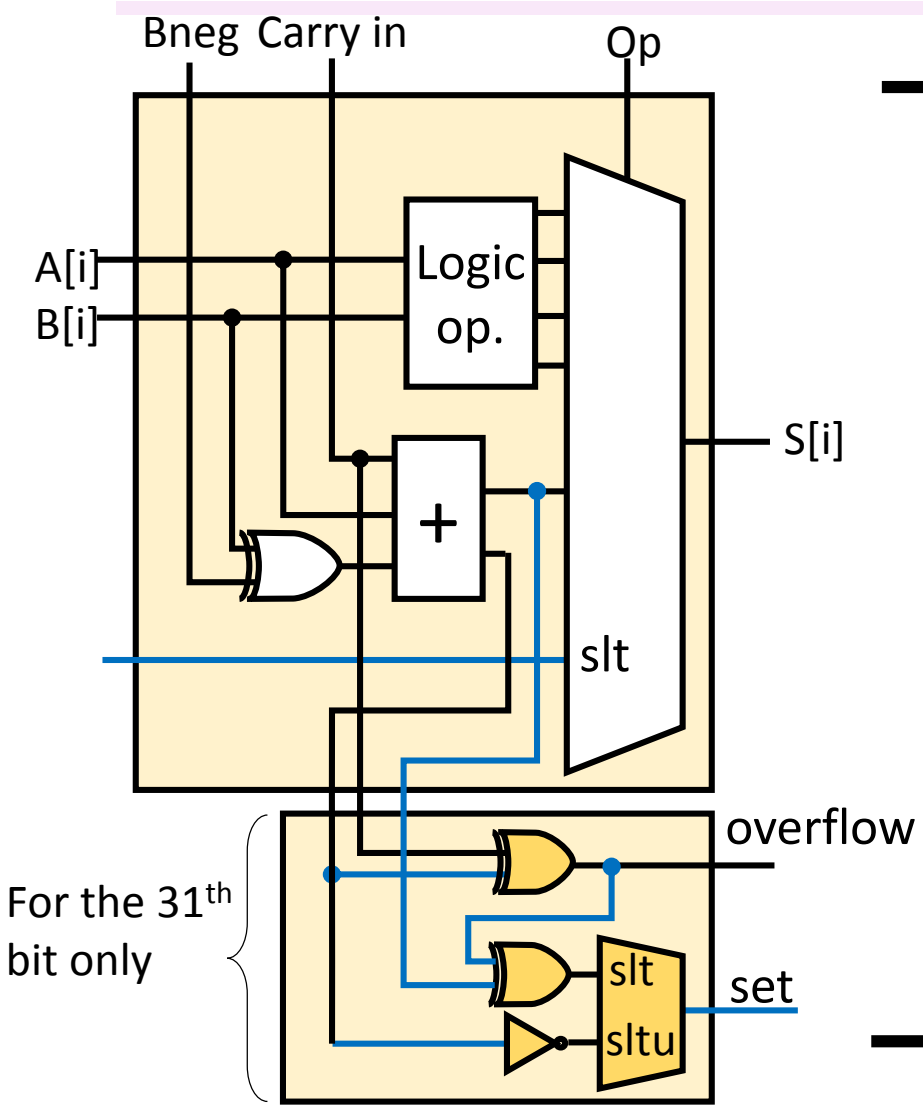



Summary

- Bit-wise logical
 - ✓ and, andi
 - ✓ or, ori
 - ✓ xor, xori
 - ✓ nor
- Arithmetic
 - ✓ add, addi
 - ✓ sub, subu
 - mul
 - div
- Comparisons
 - ✓ slt, slti, sltu, sltiu



Outline

- Overview
- Integer operations
 - Bit-wise logical operations
 - Additions, subtractions
 - Comparisons
 - **Multiplications**
 - **Divisions**
- Floating point operations
 - Additions, subtractions
 - Multiplications