

邏輯設計實驗 Lab01 結報

104060012 邱怡庭

34+10=44

1 Design and implement a full adder. ($s+c_{out}=x+y+c_{in}$)

1.1 Write the logic equation.

1.2 Draw the related logic diagram.


1.3 Verilog RTL representation with verification.

Design Specification 2/2

Input: x, y, c_{in}

Output: s, c_{out}

block diagram:

 

Design Implementation

logic function:


5/5

$$s = (x \oplus y) \oplus c_{in}$$


$$c_{out} = ((x \wedge y) \wedge c_{in}) \vee (x \wedge y)$$

logic diagram

3/3

 

The Final Result:

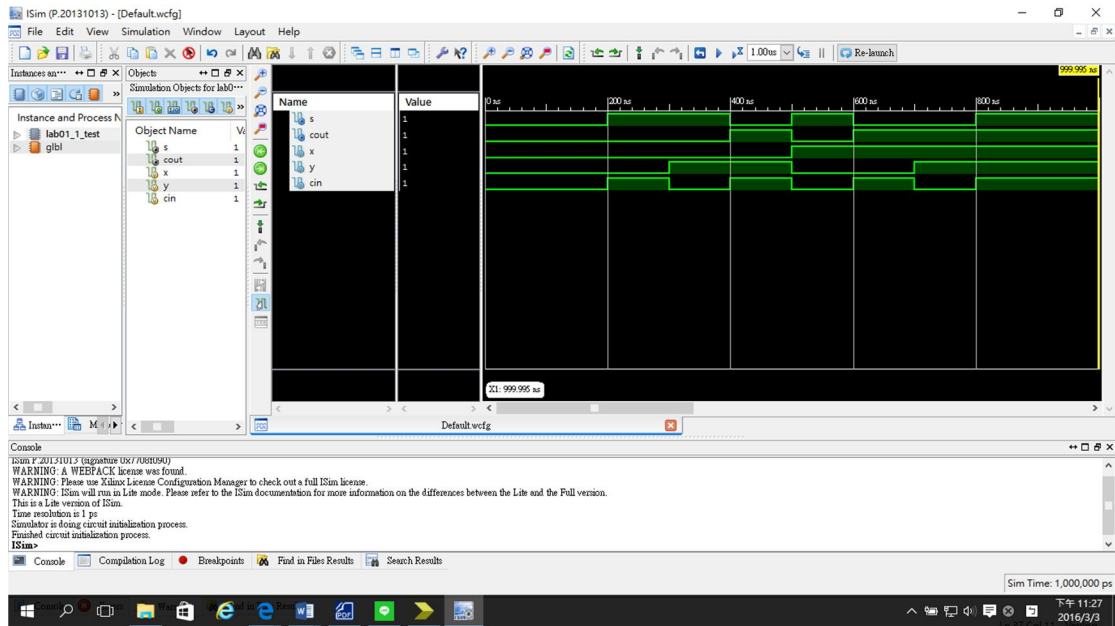

Discussion:

1. 第一次模擬時，Value 欄位出現"x"、"z"錯誤訊息，原來是點錯模擬的檔案，要選擇 Verilog Test Fixture 而不是 Verilog Module。
2. x=0 y=0 cin=0 -> s=0 cout=0,
x=0 y=0 cin=1 -> s=1 cout=0,
x=0 y=1 cin=0 -> s=1 cout=0,
x=0 y=1 cin=1 -> s=0 cout=1,
x=1 y=0 cin=0 -> s=1 cout=0,
x=1 y=0 cin=1 -> s=0 cout=1,
x=1 y=1 cin=0 -> s=0 cout=1,
x=1 y=1 cin=1 -> s=1 cout=1。

5/5

Discussion 不是用來貼輸出的，請簡述自己實作過程。

2 Design a single digit decimal adder with input A(a3a2a1a0), B(b3b2b1b0), Cin(ci), and output S(s3s2s1s0) and Cout(co).

Design Specification 2/2


Input:A[3:0],B[3:0],Cin

Output:Cout[3:0],S[3:0]

Wire:z[3:0],K0

block diagram:

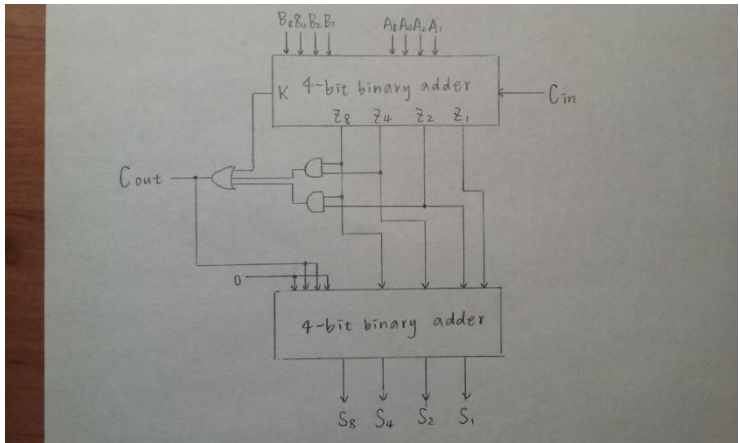你畫的是Logic diagram
block diagram 指4bits
full adder



5/5


Design Implementation

logic function:

5/5

$$Cout[0] = K0 | (z[3] \& z[2]) | (z[3] \& z[1])$$

The Final Result:

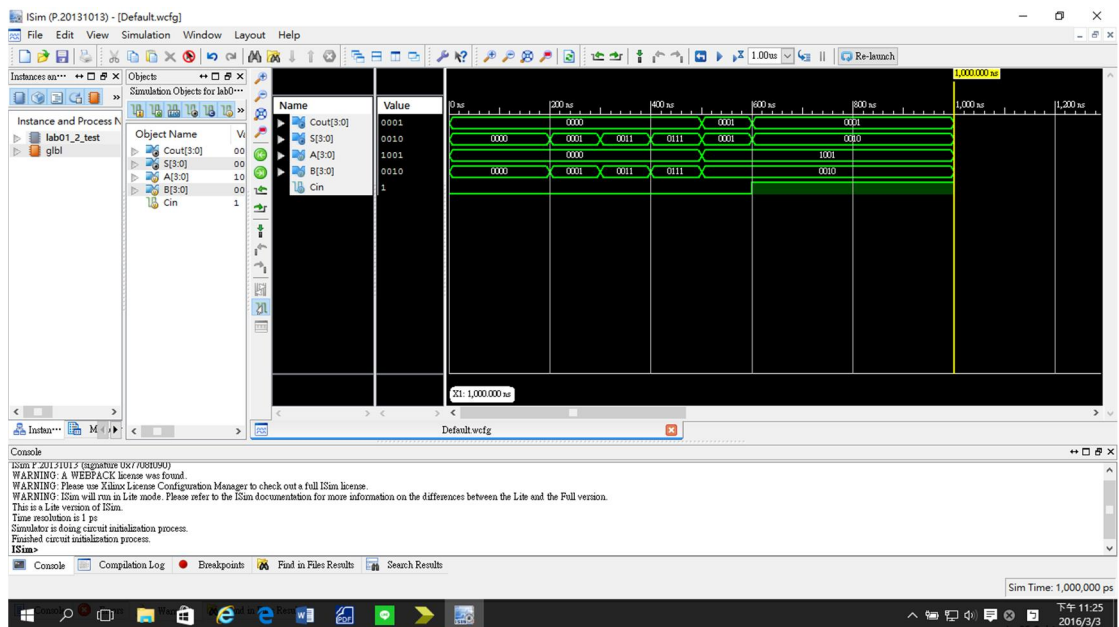

Discussion:

5/5

Discussion 不是用來貼輸出的，請簡述自己實作過程，下次請注意。

- A=0000 B=0000 Cin=0 -> S=0000 Cout=0000,
- A=0000 B=0001 Cin=0 -> S=0001 Cout=0000,
- A=0000 B=0011 Cin=0 -> S=0011 Cout=0000,
- A=0000 B=0111 Cin=0 -> S=0111 Cout=0000,
- A=1001 B=0010 Cin=0 -> S=0001 Cout=0001,
- A=1001 B=0010 Cin=1 -> S=0010 Cout=0001,

3 (Bonus) Design a 2-to-4-line decoder with enable (input in[1:0], enable en and output d[3:0]). 2/2

3.1 Logic equation,

3.2 Logic schematic,


3.3 Verilog RTL representation with verification.

Design Specification

Input: in[1:0], en

Output: d[3:0]

block diagram

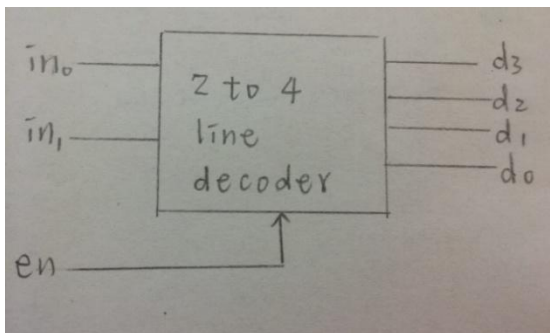

Design Implementation

logic function:


$$d[3]=en\&in[0]\&in[1]$$

$$d[2]=en\&in[0]\&(\sim in[1])$$


$$d[1]=en\&(\sim in[0])\&in[1]$$

$$d[0]=en\&(\sim in[0])\&(\sim in[1])$$

logic diagram:

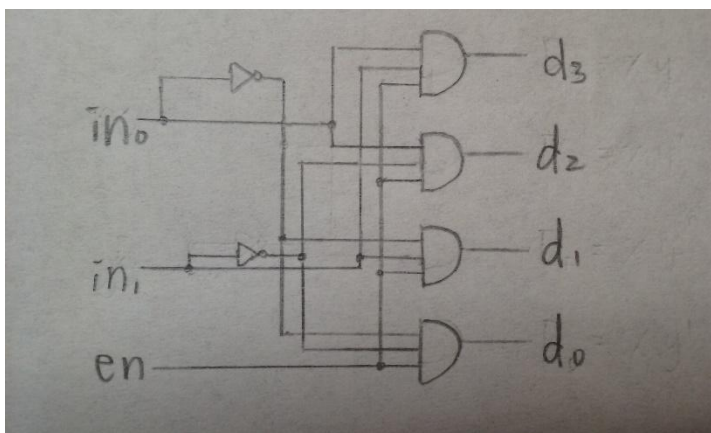

The Final Result:

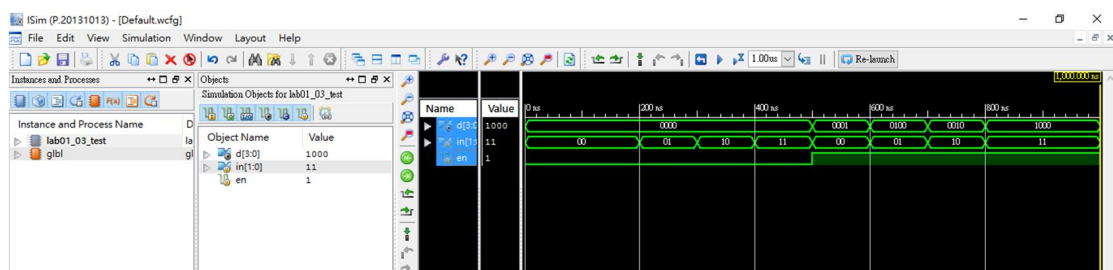

Discussion:

當 enable(en)=0 時，output(d)不受 input(in)影響，其值皆為 1;當 enable(en)=1 時 output(d)受 input(in)影響:in=00 -> d=0001,in=01 -> d=0100,in=10 -> d=0010,in=11 -> d=1000。

Conclusion:

第一次學習 Verilog，對於其與 C 語言的差異有些不習慣，所以花了很長的時間去熟悉，一開始只會一步一步按照講義指示進行，甚至不太清楚自己在做什麼，但慢慢摸索後漸漸找到了方向，最後完成時覺得相當有成就感，期望未來的實驗能更加順利!