

邏輯設計實驗 Lab12 結報


104060012 邱怡庭

1 For the time delay of electronic clock in lab7. Instead using 14-segment displays to show the time, use LCD to present all the functions in lab7.

Design Specification

```
input  clk,  
input  rst_n,  
  
output LCD_rst,  
output wire [1:0] LCD_cs,  
output LCD_rw,  
output LCD_di,  
output wire [7:0] LCD_data,  
output LCD_en  
wire [3:0]second1,second0,minute1,minute0,hour1,hour0,day1,day0,month1,  
month0,year1,year0;  
wire en,out_valid;  
wire [7:0] data_out;  
wire clk_div;  
wire clk_d;
```


block diagram:

 


Design Implementation

logic function / logic diagram:


upcounter

 


freq_div:

 


RAM_ctl

 

 

LCD_ctl

 

counter

連接 second, minute, hour, day, month, year 的 counter, 設定 second 從 0 數到 59 進位至 minute , minute 從 0 數到 59 進位至 hour , hour 從 day0 數到 23 進位至 day , day 從 1 數到 monthday(28or30or31) 進位至 month , month 從 1 數到 12 進位至 year , year 從 0 數到 99 。

I/O pin assignment:

```
## pin mapping
NET "clk"          LOC = "R10";
NET "rst_n"         LOC = "N3";

## LCD control signals
NET "LCD_RST"      LOC = "E3";
NET "LCD_CS[1]"     LOC = "E1";
NET "LCD_CS[0]"     LOC = "F4";
NET "LCD_DATA[7]"   LOC = "F3";
NET "LCD_DATA[6]"   LOC = "D2";
NET "LCD_DATA[5]"   LOC = "D1";
NET "LCD_DATA[4]"   LOC = "H7";
NET "LCD_DATA[3]"   LOC = "G6";
NET "LCD_DATA[2]"   LOC = "E4";
NET "LCD_DATA[1]"   LOC = "D3";
NET "LCD_DATA[0]"   LOC = "F6";
NET "LCD_EN"        LOC = "F5";
NET "LCD_RW"        LOC = "C2";
NET "LCD_DI"        LOC = "C1";
```

Discussion:

利用 RAM 自 counter 讀取資料並輸出在 LCD 上。

Conclusion:

只要結合 lab07 的 counter 與 RAM 便可製作簡易的電子鐘。