

Using Push Buttons

Hsi-Pin Ma


<http://lms.nthu.edu.tw/course/24953>

Department of Electrical Engineering

National Tsing Hua University

Switch Contact Bounce

 
- Push button contains a metal spring which will cause signal bounce when switching
 - A random number of unwanted signal pulses
 - Usually in μs range
 - FPGA is sensitive to pulses down to ns range



Debounce Circuits


- Spec

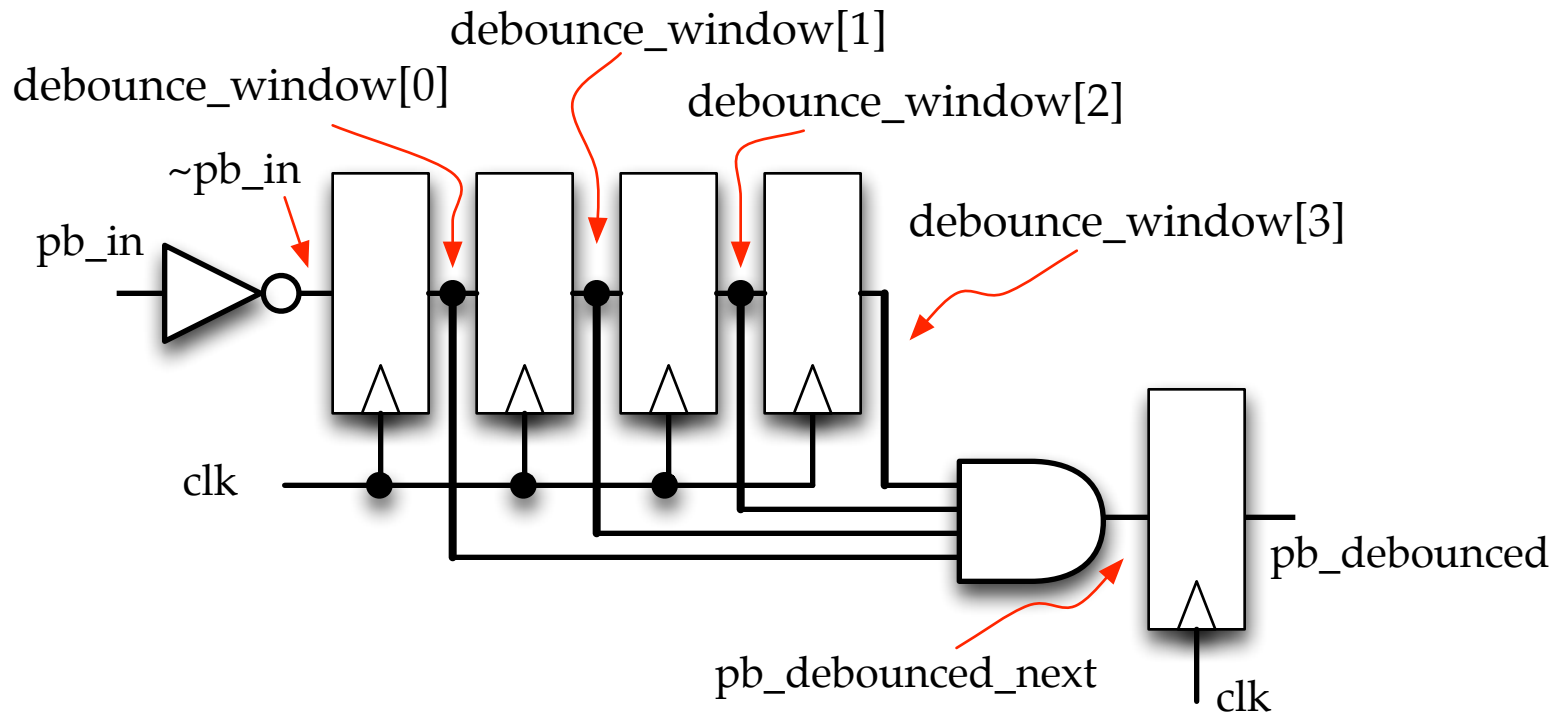- 4-bit shift register clocked at 100Hz
- Input is the push button input
- When all 4 bits of the registers are high the output of the debounce circuit changes to high




One-Pulse Generation


 
- When one presses the push button for a short moment, the time that the switch is closed (ms range) is usually much longer than one clock period (μs or ns range)




 
- The one-pulse circuit generates only a one-clock-period-long pulse every time the push button is hit, independent of the time one keeps the button pressed



One-Pulse Generation

  

Simulation

 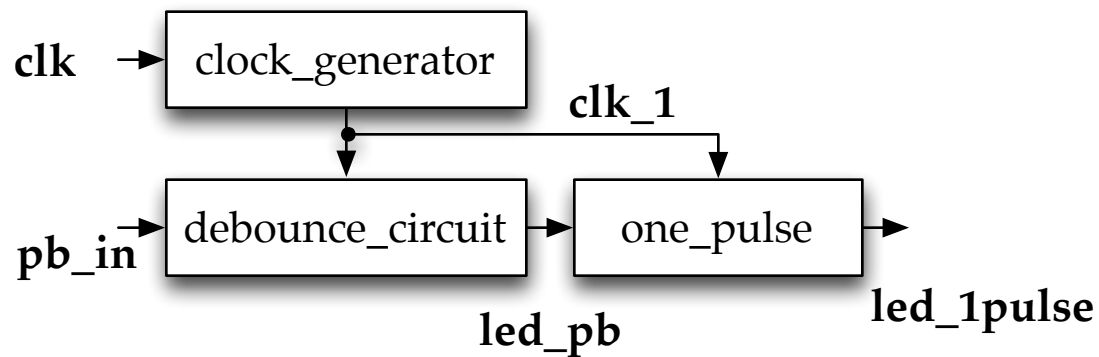

clock_generator.v

```

`include "global.v"
module clock_generator(
    clk, // clock from crystal
    rst_n, // active low reset
    clk_1, // generated 1 Hz clock
    clk_100 // generated 100 Hz clock
);

// Declare I/Os
input clk; // clock from crystal
input rst_n; // active low reset
output clk_1; // generated 1 Hz clock
output clk_100; // generated 100 Hz clock
reg clk_1; // generated 1 Hz clock
reg clk_100; // generated 100 Hz clock

// Declare internal nodes
reg [ `DIV_BY_20M_BIT_WIDTH-1:0 ]
count_20M, count_20M_next;
reg [ `DIV_BY_200K_BIT_WIDTH-1:0 ]
count_200K, count_200K_next;
reg clk_1_next;
reg clk_100_next;

```

```

// Clock Divider: Counter operation
always @*
    if (count_20M == `DIV_BY_20M-1)
        begin
            count_20M_next = `DIV_BY_20M_BIT_WIDTH'd0;
            clk_1_next = ~clk_1;
        end
    else
        begin
            count_20M_next = count_20M + 1'b1;
            clk_1_next = clk_1;
        end

// Counter flip-flops
always @(posedge clk or negedge rst_n)
    if (~rst_n)
        begin
            count_20M <= `DIV_BY_20M_BIT_WIDTH'b0;
            clk_1 <= 1'b0;
        end
    else
        begin
            count_20M <= count_20M_next;
            clk_1 <= clk_1_next;
        end
    ...
endmodule

```

Remember to use clk_100 in real design !!!

debounce_circuit.v

```

`include "global.v"
module debounce_circuit(
  clk, // clock control
  rst_n, // reset
  pb_in, //push button input
  pb_debounced // debounced push button output
);

// declare the I/Os
input clk; // clock control
input rst_n; // reset
input pb_in; //push button input
output pb_debounced; // debounced push button output
reg pb_debounced; // debounced push button output

// declare the internal nodes
reg [3:0] debounce_window; // shift register flip flop
reg pb_debounced_next; // debounce result
  
```

```

// Shift register
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    debounce_window <= 4'd0;
  else
    debounce_window <= {debounce_window[2:0],~pb_in};

// debounce circuit
always @*
  if (debounce_window == 4'b1111)
    pb_debounced_next = 1'b1;
  else
    pb_debounced_next = 1'b0;

always @(posedge clk or negedge rst_n)
  if (~rst_n)
    pb_debounced <= 1'b0;
  else
    pb_debounced <= pb_debounced_next;

endmodule
  
```


one_pulse.v

```

module one_pulse(
  clk, // clock input
  rst_n, //active low reset
  in_trig, // input trigger
  out_pulse // output one pulse
);

// Declare I/Os
input clk; // clock input
input rst_n; //active low reset
input in_trig; // input trigger
output out_pulse; // output one pulse
reg out_pulse; // output one pulse

// Declare internal nodes
reg in_trig_delay;

// Buffer input
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    in_trig_delay <= 1'b0;
  else
    in_trig_delay <= in_trig;

```


```

// Pulse generation
assign out_pulse_next = in_trig &
(~in_trig_delay);

always @(posedge clk or negedge rst_n)
  if (~rst_n)
    out_pulse <= 1'b0;
  else
    out_pulse <= out_pulse_next;

endmodule

```

 




Stopwatch Example

Stopwatch with FSM



- 1 • stopwatch function with 1-bit control for stop (S0), start(S1)

Inputs: pressed


Outputs: count_enable

 

stopwatch

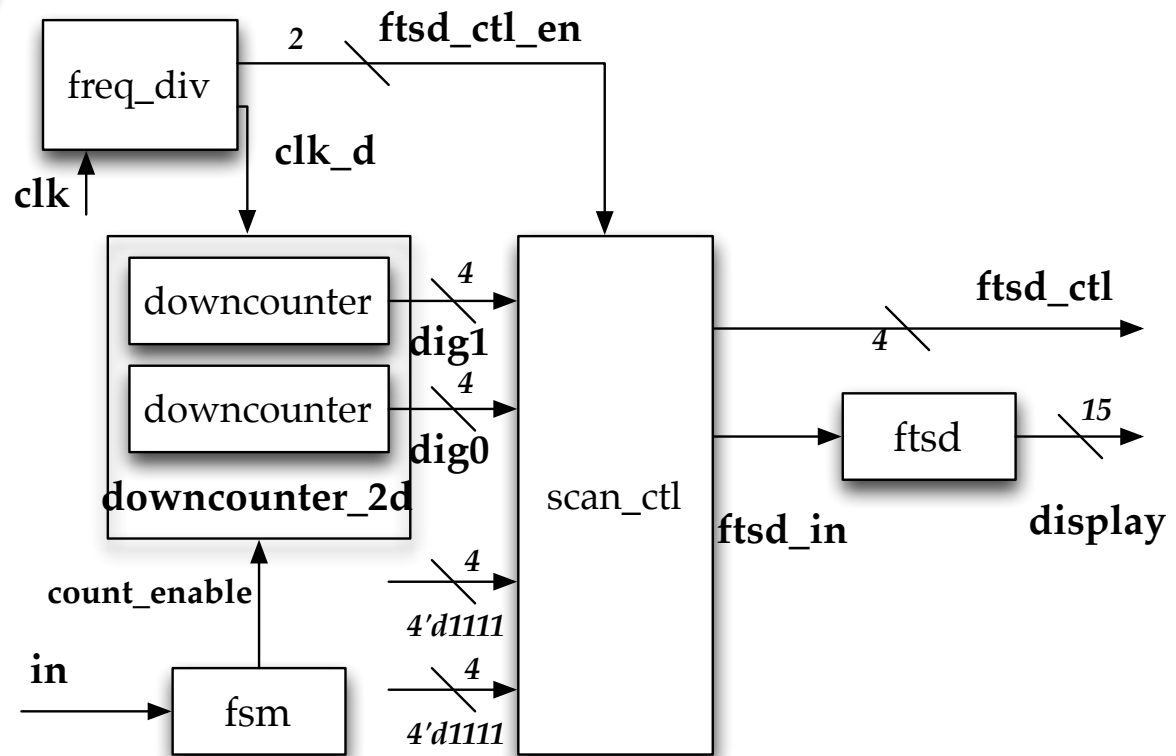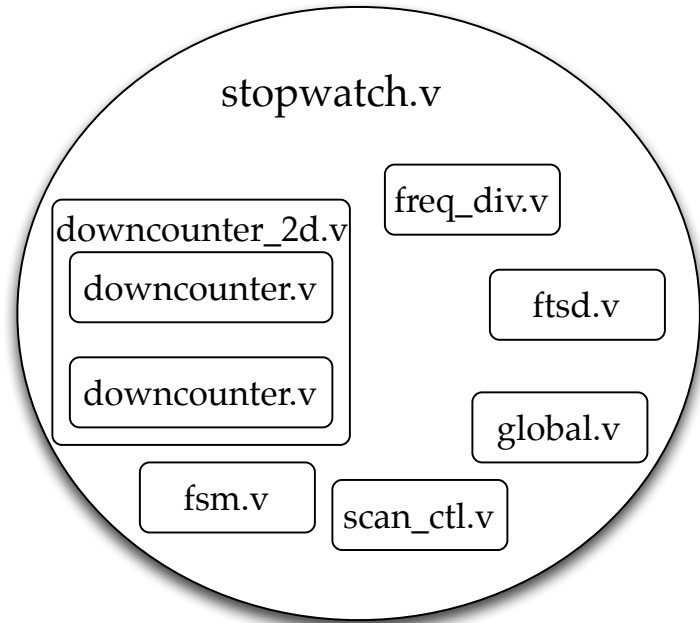

downcounter.v (1/2)

 

```

`define BCD_BIT_WIDTH 4
`define BCD_ZERO 4'd0
`define INCREMENT 1'b1
module downcounter(
    value, // counter value
    borrow, // borrow indicator for counter to next stage
    clk, // global clock
    rst_n, // active low reset
    decrease, // decrease input from previous stage of counter
    init_value, // initial value for the counter
    limit, // limit for the counter
    en // enable/disable of the counter
);

output [^BCD_BIT_WIDTH-1:0] value; // counter value
output borrow; // borrow indicator for counter to next stage
input clk; // global clock
input rst_n; // active low reset
input decrease; // decrease input from previous stage of counter
input [^BCD_BIT_WIDTH-1:0] init_value; // initial value for the counter
input [^BCD_BIT_WIDTH-1:0] limit; // limit for the counter
input en; // enable/disable of the counter

reg [^BCD_BIT_WIDTH-1:0] value; // output (in always block)
reg [^BCD_BIT_WIDTH-1:0] value_tmp; // input to dff (in always block)
reg borrow; // borrow indicator for counter to next stage


```

downcounter.v (2/2)


```
// Combinational logics
always @(value or decrease or en or limit)
  if (value==`BCD_ZERO && decrease && en)
    begin
      value_tmp = limit;
      borrow = `ENABLED;
    end
  else if (decrease && en)
    begin
      value_tmp = value - `INCREMENT;
      borrow = `DISABLED;
    end
  else if (en)
    begin
      value_tmp = value;
      borrow = `DISABLED;
    end
  else
    begin
      value_tmp = `BCD_ZERO;
      borrow = `DISABLED;
    end
end
```

```
// register part for BCD counter
always @(posedge clk or negedge rst_n)
  if (~rst_n) value <= init_value;
  else value <= value_tmp;

endmodule
```

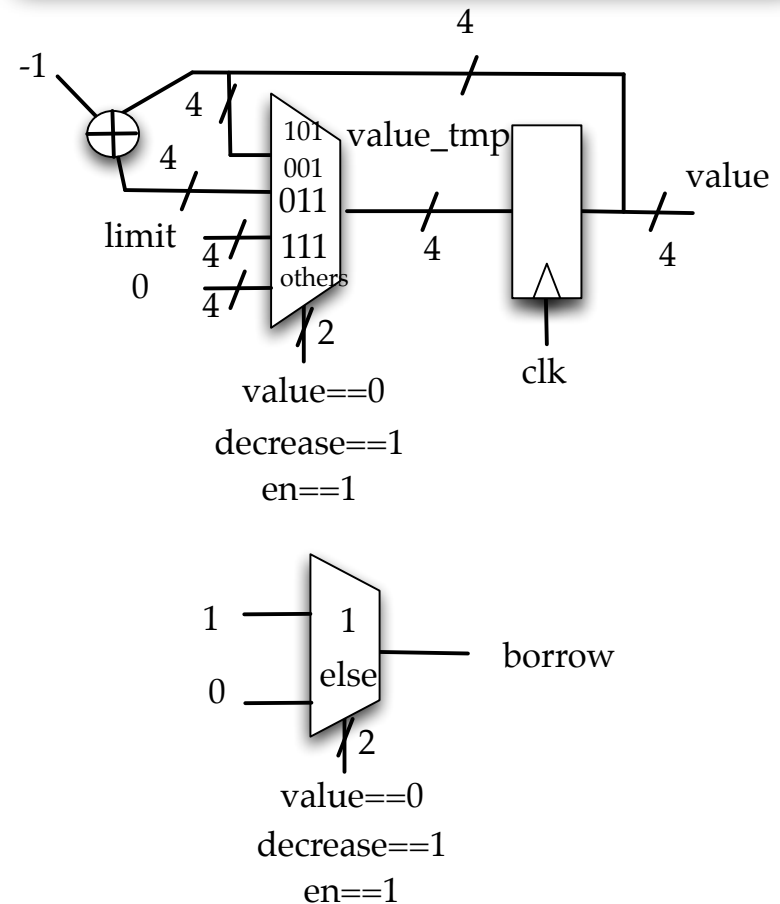

downcounter_2d.v (1/3)

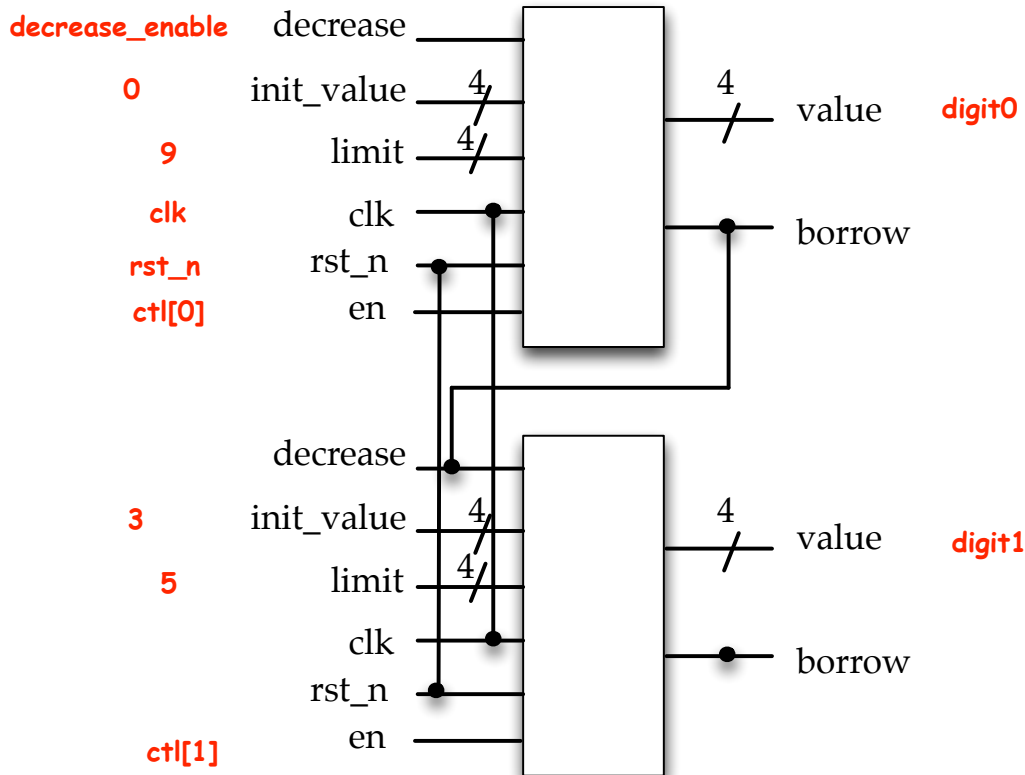

```

`define BCD_BIT_WIDTH 4
`define ENABLED 1
`define DISABLED 0
`define INCREMENT 1'b1
`include "global.v"
module downcounter_2d(
    digit1, // 2nd digit of the down counter
    digit0, // 1st digit of the down counter
    clk, // global clock
    rst_n, // active low reset
    en // enable/disable for stopwatch
);

    output [`BCD_BIT_WIDTH-1:0] digit1;
    output [`BCD_BIT_WIDTH-1:0] digit0;
    input clk; // global clock
    input rst_n; // active low reset
    input en; // enable/disable for stopwatch

    wire br0, br1; // borrow indicator
    wire decrease_enable;

    assign decrease_enable = en &&
        (~((digit0==`BCD_ZERO) &&
            (digit1==`BCD_ZERO) &&
            (digit2==`BCD_ZERO)));


```

downcounter_2d.v (2/2)

```
// 30 sec down counter
downcounter Udc0(
    .value(digit0), // counter value
    .borrow(br0), // borrow indicator for counter to next stage
    .clk(clk), // global clock signal
    .rst_n(rst_n), // low active reset
    .decrease(decrease_enable), // decrease input from previous stage of counter
    .init_value(`BCD_ZERO), // initial value for the counter
    .limit(`BCD_NINE), // limit for the counter
    .en(ctl[0]) // enable/disable of the counter
);

downcounter Udc1(
    .value(digit1), // counter value
    .borrow(br1), // borrow indicator for counter to next stage
    .clk(clk), // global clock signal
    .rst_n(rst_n), // low active reset
    .decrease(br0), // decrease input from previous stage of counter
    .init_value(`BCD_THREE), // initial value for the counter
    .limit(`BCD_FIVE), // limit for the counter
    .en(ctl[1]) // enable/disable of the counter
);
```


fsm.v

 

```

`include "global.v"
module fsm(
    count_enable, // if counter is enabled
    in, //input control
    clk, // global clock signal
    rst_n // low active reset
);

// outputs
output count_enable; // if counter is enabled

// inputs
input clk; // global clock signal
input rst_n; // low active reset
input in; //input control


reg count_enable; // if counter is enabled
reg state; // state of FSM
reg next_state; // next state of FSM
  
```

```
// FSM state decision
always @*
case (state)
`STAT_DEF:
  if (in)
  begin
    next_state = `STAT_COUNT;
    count_enable = `ENABLED;
  end
  else
  begin
    next_state = `STAT_DEF;
    count_enable = `DISABLED;
  end
`STAT_COUNT:
  if (in)
  begin
    next_state = `STAT_PAUSE;
    count_enable = `DISABLED;
  end
  else
  begin
    next_state = `STAT_COUNT;
    count_enable = `ENABLED;
  end
end
```

```
`STAT_PAUSE:
  if (in)
  begin
    next_state = `STAT_COUNT;
    count_enable = `ENABLED;
  end
  else
  begin
    next_state = `STAT_PAUSE;
    count_enable = `DISABLED;
  end
default:
  begin
    next_state = `STAT_DEF;
    count_enable = `DISABLED;
  end
endcase
```

```
// FSM state transition
always @(posedge clk or negedge rst_n)
if (~rst_n)
  state <= `STAT_DEF;
else
  state <= next_state;

endmodule
```

 

stopwatch.v

```
`include "global.v"
module stopwatch(
    display, // 14 segment display control
    ftsd_ctl, // scan control for 14-segment display
    clk, // clock
    rst_n, // low active reset
    in // input control for FSM
);

output [^FTSD_BIT_WIDTH-1:0] display; // 14 segment display control
output [^FTSD_DIGIT_NUM-1:0] ftsd_ctl; // scan control for ftsd
input clk; // clock
input rst_n; // low active reset
input in; // input control for FSM

wire [^FTSD_SCAN_CTL_BIT_WIDTH-1:0] ftsd_ctl_en; // divided output for ftsd ctl
wire clk_d; // divided clock

wire count_enable; // if count is enabled

wire [^BCD_BIT_WIDTH-1:0] dig0,dig1; // second counter output
```

stopwatch.v

```

//*****
// Functional block
//*****
// frequency divider 1/(2^25)
freq_div U_FD(
    .clk_out(clk_d), // divided clock
    .clk_ctl(ssd_ctl_en), // divided clock for scan control
    .clk(clk), // clock from the crystal
    .rst_n(rst_n) // low active reset
);

FSM U_fsm(
    .count_enable(count_enable), // if counter is enabled
    .in(in), //input control
    .clk(clk_d), // global clock signal
    .rst_n(rst_n) // low active reset
);

// stopwatch module
stopwatch U_sw(
    .digit1(dig1), // 2nd digit of the down counter
    .digit0(dig0), // 1st digit of the down counter
    .clk(clk_d), // global clock
    .rst_n(rst_n), // low active reset
    .en(count_enable) // enable/disable for the stopwatch
);

```

```

//*****
// Display block
//*****
// Scan control
scan_ctl U_SC(
    .ftsd_ctl(ftsd_ctl), // ftsd display control signal
    .ftsd_in(ftsd_in), // output to ftsd display
    .in0(4'b1111), // 1st input
    .in1(4'b1111), // 2nd input
    .in2(dig1), // 3rd input
    .in3(dig0), // 4th input
    .ftsd_ctl_en(ftsd_ctl_en) // divided clock for scan control
);

// binary to 14-segment display decoder
ftsd U_display(
    .display(display), // 14-segment display output
    .in(ftsd_in) // BCD number input
);

endmodule

```