

Lab 4: Shift Registers

Objective


- ✓ Review sequential circuits.
- ✓ Review shift registers.

Prerequisite

- ✓ Fundamentals of logic gates.
- ✓ Clocking concepts
- ✓ Logic modeling in Verilog HDL.


Pre-labs

- 1 Cascade eight DFFs together as the figure shown below with the input bits $D=(d)$, output $Q=(q_7, q_6, q_5, q_4, q_3, q_2, q_1, q_0)$, and tie all their Cs together as clk (the divided clock). This is a serial shift register circuit. By adding a multiplexer before the first DFF, we can choose the input from outside or from q_0 . As the clk changes 0,1,0,1,..., let the output of LEDs be (01010101), (10101010), (01010101), (10101010),
 - 1.1 Construct the Verilog RTL representation for the logics with verification

 

Experiments

 - 1 Implement pre-lab1 with the following pin assignments.
- 2 Use the idea from pre-lab1. We can do something on the seven-segment display. Assume we have the pattern of E, H, N, T, U for seven-segment display as shown below. Try to implement the scrolling pre-stored pattern NTHUEE with the four seven-segment displays.



- 3 (Bonus) Display 1010 in the seven-segment display. Use the DIP switch (one bit to indicate left/right shift, three bits with one hot to display the kind of shift operation) as the control input to implement the functional/arithmetic/barrel shifter. Use one push button to control the display of the number before/after the shift operation.

TA: _____