

Lab 2: FPGA Emulation

Objective

- ✓ Introduce BASYS 3 demo board emulation flow.

Prerequisite

- ✓ Fundamentals of logic gates.
- ✓ Verilog HDL representation of Logic components.

Experiments

- 1 Emulate exp1 in lab1 (a full adder $s+cout=x+y+cin$) with the following parameters.

I/O	x	y	cin	s	$cout$
LOC	V17	V16	W16	U16	E19

- 2 Derive a BCD ($i[3:0]$) to 7-segment display decoder ($D_ssd[7:0]$), and also use four LEDs ($d[3:0]$) to monitor the 4-bit BCD number. (Other values of i outside the range will show F).
- 3 (Bonus) Design a combinational circuit that compares two 4-bit unsigned numbers A and B to see whether A is greater than B. The circuit has one output X such that $X = 0$ if $A \leq B$ and $X = 1$ if $A > B$. (let A[3:0], B[3:0] be controlled by 8 DIP switches, the binary numbers are displayed on 8 LEDs. The result X is on another LED.)

TA: _____