 


邏輯設計實驗 preLab3

105060012 張育崧

1 Consider a 4-bit synchronous binary up counter.

1.1 Draw the logic diagram



1.2 Construct Verilog RTL representation for the logics with verification.

```
input rst, clk;  
output reg [3:0]q; //q 為一 4-bit 的數  
always@(posedge clk or negedge rst) //clk=1 時加法&讀值  
    if(~rst) //rst = 0 時 reset  
        q<=4'b0000;  
    else  
        q<=q+4'd1;
```

