

Finite State Machine

Hsi-Pin Ma

<http://lms.nthu.edu.tw/course/43639>


Department of Electrical Engineering
National Tsing Hua University

Clocks

- Use signal (100MHz) from crystal (W5)
- Do not use gated clock
 - ex: en & clk (X)
 - For large blocks, use PLL IP
- Various clock frequencies in labs
 - 100-Hz for Debounce circuits
 - 1-Hz for second clock display
 - faster clock for push-button-controlled FSM (~10-Hz) - one pulse generation


“Turn off” a Block

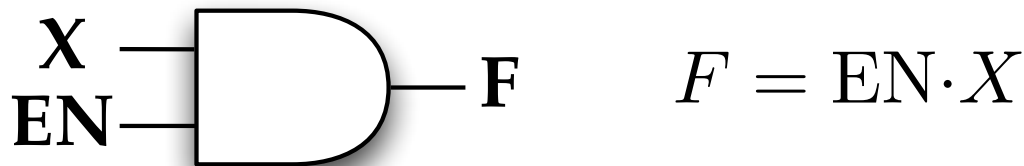- Enable control (with AND gate) for combinational logics (block input)



E	X	F
0	0	0
0	1	0
1	0	0
1	1	1

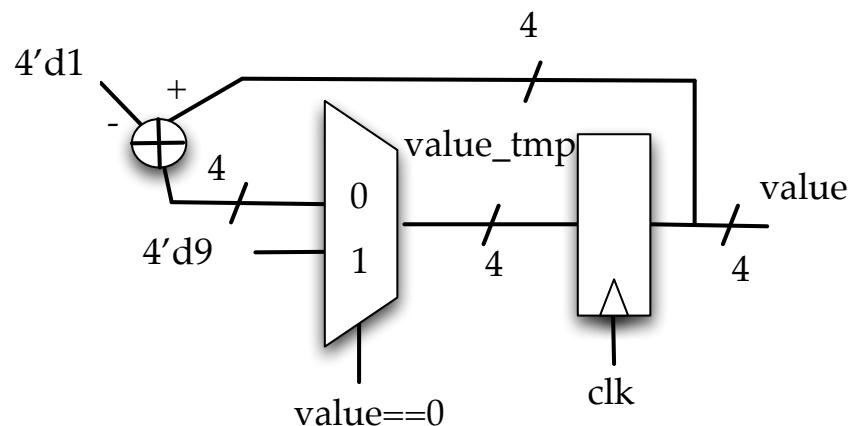- Use MUXs in front of DFFs for unchanged states
 - Clock gating is NOT preferred



Finite State Machine


- Derive the state diagram
- Determine # of DFFs (for N states)
 - Use $\lceil \log_2 N \rceil$ numbers of DFFs for binary-coded state
 - If FSM is Moore model, use DFFs for outputs
 - Write Verilog codes for DFFs
- Use combinational logics for state transitions and output functions (Use *case* statement)

Bad Coding Style:

Inferred Latches in Combinational Logics

- Incomplete case statement
- To avoid
 - Make sure to have *default* case
 - Or always specify the default value in the beginning of the always block

```
always @*  
begin  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
  endcase  
end
```




```
always @*  
begin  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
    default: y = 0;  
  endcase  
end
```

```
always @*  
begin  
  y=0;  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
  endcase  
end
```

Bad Coding Style:

Inferred Latches in Combinational Logics
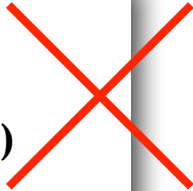
```
always @*  
begin  
  if (alu_control==2'b00)  
    y=x+z;  
  else if (alu_control==2'b01)  
    y=x-z;  
  else if (alu_control==2'b10)  
    y=x*z;  
end
```



```
always @*  
begin  
  y=0;  
  if (alu_control==2'b00)  
    y=x+z;  
  else if (alu_control==2'b01)  
    y=x-z;  
  else if (alu_control==2'b10)  
    y=x*z;  
end
```

```
always @*  
  if (alu_control==2'b00)  
    y=x+z;  
  else if (alu_control==2'b01)  
    y=x-z;  
  else if (alu_control==2'b10)  
    y=x*z;  
  else  
    y=0;
```