

1. Design and implement a full adder. ($s + \text{cout} = x + y + \text{cin}$)

From the specifications, determine the inputs, outputs, and their symbols.

Inputs: x , (augend)
 y , (addend)
 cin (carry in)

Outputs: s , (sum)
 cout (carry out)

Derive the truth table (functions) from the relationship between the inputs and outputs.

x	y	cin	s	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


1.1 Write the logic equation.

Derive the simplified Boolean functions for each output function.

$$s = x \oplus y \oplus \text{cin}$$

$$\text{cout} = x \times y + y \times \text{cin} + \text{cin} \times x$$

1.2 Draw the related logic diagram.

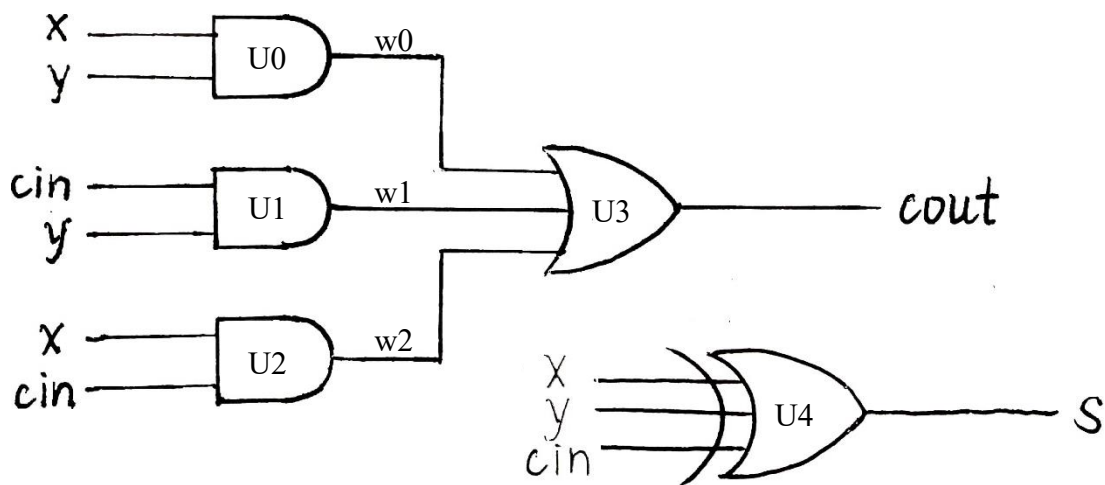


1.3 Verilog RTL representation with verification.

Construct the Verilog code according to the logic diagram.

```
module fulladder(  
    output s,      // sum  
    output cout,  // carry out  
    input  x,     // augend  
    input  y,     // addend  
    input  cin    // carry in  
);  
  
    assign cout = x & y | y & cin | cin & x;  
    assign s = x ^ y ^ cin;  
  
endmodule          //fulladder
```

Write the test bench and verify the design.

```
module fulladder_test();  
    // outputs  
    wire s;      // sum  
    wire cout;   // carry out  
  
    // inputs  
    reg  x;      // augend  
    reg  y;      // addend  
    reg  cin;    // carry in  
  
    // DUT  
    fulladder fa0(  
        .s(s),      // sum  
        .cout(cout), // carry out  
        .x(x),      // augend  
        .y(y),      // addend  
        .cin(cin)   // carry in  
    );  
  
    // stimulus  
    always #10 {cin, y, x} = {cin, y, x} + 1;  
    initial {cin, y, x} = 0;  
  
endmodule          //fulladder_test
```

 

2. Design a 3-to-8-line decoder with enable (input in[2:0], enable, output d[7:0]).

From the specifications, determine the inputs, outputs, and their symbols.

Inputs: in[2:0], en

Outputs: d[7:0]

Derive the truth table from the relationship between the inputs and outputs.

en	in[2]	in[1]	in[0]	d[7]	d[6]	d[5]	d[4]	d[3]	d[2]	d[1]	d[0]
0	×	×	×	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

2.1 Logic equation.

Derive the simplified Boolean functions for each output function.

$$d[0] = en \times in[2]' \times in[1]' \times in[0]'$$

$$d[1] = en \times in[2]' \times in[1]' \times in[0]$$

$$d[2] = en \times in[2]' \times in[1] \times in[0]'$$

$$d[3] = en \times in[2]' \times in[1] \times in[0]$$


$$d[4] = en \times in[2] \times in[1]' \times in[0]'$$

$$d[5] = en \times in[2] \times in[1]' \times in[0]$$

$$d[6] = en \times in[2] \times in[1] \times in[0]'$$

$$d[7] = en \times in[2] \times in[1] \times in[0]$$

2.2 Logic schematic.

 


Construct the Verilog code according to the logic diagram.

```
module decoder_3_to_8(  
    output [7:0] d,      // one-hot  
    input  [2:0] in,     // binary  
    input          en    // enable  
);  
  
    assign d[0] = en & ~in[2] & ~in[1] & ~in[0];  
    assign d[1] = en & ~in[2] & ~in[1] & in[0];  
    assign d[2] = en & ~in[2] & in[1] & ~in[0];  
    assign d[3] = en & ~in[2] & in[1] & in[0];  
    assign d[4] = en & in[2] & ~in[1] & ~in[0];  
    assign d[5] = en & in[2] & ~in[1] & in[0];  
    assign d[6] = en & in[2] & in[1] & ~in[0];  
    assign d[7] = en & in[2] & in[1] & in[0];  
  
endmodule                                // decoder_3_to_8
```

 2.3 Verilog RTL representation with verification.

Write the test bench and verify the design.

```
module decoder_3_to_8_test();  
    // output  
    wire [7:0] d;      // one-hot  
  
    // input  
    reg  [2:0] in;     // binary  
    reg          en;   // enable  
  
    // DUT  
    decoder_3_to_8 U0(  
        .d(d),          // one-hot  
        .in(in),        // binary  
        .en(en)         // enable  
    );  
  
    // stimulus  
    always #10 {en, in} = {en, in} + 1;  
    initial {en, in} = 0;  
  
endmodule                                // decoder_3_to_8_test
```



3. For two 3-bit unsigned numbers a(a2a1a0) and b(b2b1b0), build a logic circuit to output the larger number.

From the specifications, determine the inputs, outputs, and their symbols.

Inputs: a[2:0], (a2a1a0)
 b[2:0] (b2b1b0)

Outputs: larger[2:0]

Derive the truth table (functions) from the relationship between the inputs and outputs.

MUX:

sel	a	b	Q
0	0	×	0
0	1	×	1
1	×	0	0
1	×	1	1

3-bit comparator:

a[2]	a[1]	a[0]	b[2]	b[1]	b[0]	a > b	a = b	a < b
1	×	×	0	×	×	1	0	0
0	1	×	0	0	×	1	0	0
1	1	×	1	0	×	1	0	0
0	0	1	0	0	0	1	0	0
0	1	1	0	1	0	1	0	0
1	0	1	1	0	0	1	0	0
1	1	1	1	1	0	1	0	0
0	×	×	1	×	×	0	0	1
0	0	×	0	1	×	0	0	1

1	0	×	1	1	×	0	0	1
0	0	0	0	0	1	0	0	1
0	1	0	0	1	1	0	0	1
1	0	0	1	0	1	0	0	1
1	1	0	1	1	1	0	0	1
0	0	0	0	0	0	0	1	0
0	0	1	0	0	1	0	1	0
0	1	0	0	1	0	0	1	0
0	1	1	0	1	1	0	1	0
1	0	0	1	0	0	0	1	0
1	0	1	1	0	1	0	1	0
1	1	0	1	1	0	0	1	0
1	1	1	1	1	1	0	1	0


Derive the simplified Boolean functions for each output function.

MUX: $Q = sel \times a + sel' \times b$

comparator: $(a > b) = (a[2] \times b[2]') +$

$(a[1] \times b[1]')(a[2] \odot b[2]') +$

 $(a[0] \times b[0]')(a[1] \odot b[1]')(a[2] \odot b[2]')$



Construct the Verilog code according to the logic diagram.

4 (Bonus) Design a single digit decimal adder with input $A(a_3a_2a_1a_0)$, $B(b_3b_2b_1b_0)$, $C_{in}(c_i)$, and output $S(s_3s_2s_1s_0)$ and $C_{out}(c_o)$.

