



Verilog HDL – II

黃元豪

Yuan-Hao Huang

國立清華大學電機工程學系

Department of Electrical Engineering

National Tsing-Hua University

Outline



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits



Introduction

- Verilog HDL是一種高階且模組化的硬體描述語言
 - 完整功能：整合電路描述、合成與模擬驗證之設計功能。
 - 彈性設計：模組化設計，易做重新組合，容易設計。
 - 多種描述型式：電路連接關係，順序性與共時性敘述，布林代數式等。
 - 跨平台可攜性：可用不同編譯軟體編譯，適用不同工作平台與製程。
 - 容易學習：語法與C語言相似。
- VHDL為另一個類似的硬體描述語言。



Verilog HDL

- Verilog 硬體描述語言 (Verilog Hardware Description Language)
 - 在積體電路設計（特別是超大型積體電路的計算機輔助設計）的電子設計自動化領域中，**Verilog HDL**是一種用於描述、設計電子系統（特別是數位電路的硬體描述語言）。
 - Verilog HDL是電力電子工程師學會（IEEE）1364號標準。
- Verilog 硬體描述語言在邏輯設計上的用途
 - 用途一: 邏輯電路設計的模擬與驗證
 - 用途二: FPGA邏輯電路(**IC電路)的設計與實作
 - ** IC電路的設計與實作在【EE4292積體電路設計實驗】教授。




Verilog HDL Utilization Scenario I

- Simulation and verification of logic circuits on PC.

Specification



Logic Design

 

Verilog HDL Coding

```

module SMUX(out, a, b, sel);
    output out;
    input a,b,sel;
    wire sel_n,t1,t2;

    not U0(sel_n,sel);
    and U1(t1,a,sel);
    and U2(t2,b,sel_n);
    or U3(out,t1,t2);

endmodule

```

Test Pattern

a, b, sel
000
001
010
...
111



Verilog HDL Simulator

- Imaging what happens when the circuit is as complex as a CPU or MP3 player processor.



Verilog HDL Utilization Scenario II

- Design and Implementation of logic circuits in FPGA (IC)

Specification

2-to-1 Multiplexer

Verilog HDL Coding


```

module SMUX(out, a, b, sel);
output out;
input a,b,sel;
wire sel_n,t1,t2;

assign out = sel ? a:b;
endmodule

```

Synthesized Logic Circuits

 

FPGA Implement Design and Programming



Now, it can work !

Verilog HDL Logic Synthesizer

Outline




- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits

Verilog Module Architecture



Device under Test (DUT)

 



Verilog Module

- `module module_name(port_names);`

- Port declaration

- Data type declaration

- Task & function declaration

- Module functionality or structure

- Timing Specification

- `endmodule`

```
module SMUX(out, a, b, sel);
```

```
output out;  
input a,b,sel;
```

```
wire sel_n,t1,t2;
```

```
not U0(sel_n,sel);  
and U1(t1,a,sel);  
and U2(t2,b,sel_n);  
or U3(out,t1,t2);
```

```
endmodule
```

Testbench (1/4)



- module testfixture;
- Declare signals
- Instantiate modules
- Applying stimulus
- Monitor signals
- endmodule

Testbench (2/4)





- Declare signals
 - Test pattern must be stored in storage elements first and then apply to DUT (Device under Test)
 - Use “reg” to declare the storage element
- Instantiate modules
 - Both behavioral level or gate level model can be used.



Testbench (3/4)

- Describing Stimulus

  - The testbench always be described behaviorally.
- Procedural blocks are bases of behavioral modeling.
- The simulator starts executing all procedure blocks at time 0 and executes them concurrently.
- Two types of procedural blocks
 - initial
 - always





Testbench (4/4)

```
• module test_SMUX;  
• reg      A,B,SEL;  
• wire    OUT;  
• SMUX U0(.out(OUT),.a(A),.b(B),.sel(SEL));  
• initial  
• begin  
•     A=0;B=0;SEL=0;  
•     #10  A=0;B=1;SEL=1;  
•     #10  A=1;B=0;  
•     #10  SEL=0;  
•     .....  
•     #10  SEL=1;  
• end  
• endmodule
```

Declare signals

Make an instance

Assign values to storage elements

#10 to specify 10 time unit delay

Example: always

```
initial clk = 0;  
always #10 clk = ~clk;
```

```
initial clk=0;  
always  
begin  
clk = 0;  
#10;  
clk = 1;  
#10;  
end
```

Outline



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits

Verilog HDL Coding Tokens




- Verilog HDL coding tokens
 - White space (空白)
 - Comments (註解)
 - Keyword (關鍵字)
 - Identifier (識別子)
 - Operator (運算子)
 - Number (數字)
 -

White Space and Comment



 - White space makes code more readable
 - Include blank space (`\b`), tabs (`\t`), and carriage return (`\n`).
- Comments
 - `/* ... */` : mark more than one line
 - `//` : mark only one line.



```
module SMUX(out,a,b,sel);
output    out;
input     a,b,sel;
// The following are logic gates
not       U0(sel_,sel);
and       U1(a1,a,sel_),
          U2(b1,b,sel_);
or        U3(out,a1,b1); /* This
                          comment marks more than one
                          line*/
endmodule
```

Keywords




- Pre-defined non-escaped identifiers that used to define the language construct.
- All keywords are defined in lower cases.
- Examples
 - module, endmodule
 - input, output, inout, wire
 - reg, integer, real, time
 - not, and, or, nand, nor, xor
 - parameter
 - begin, end
 - fork, join, assign
 - always, for, if, else
 - negedge, posedge
- Verilog is a case sensitive language.
 - Use “-u” option in command line option for case-insensitive.



Identifiers

 - Names of modules, ports, and instances are identifiers.
- Identifiers are **user-defined** names for Verilog objects within a description.
- Legal characters in identifiers:
 - a-z, A-Z, 0-9, `_`, `$`
- The first character of an identifier must be an alphabetical character (a-z, A-Z) or an underscore (`_`).
- Identifiers can be up to 1023 characters long.






Operators (1/3)

Bitwise Operators		
OP	Usage	Description
\sim	$\sim m$	Invert each bit of m
$\&$	$m \& n$	AND each bit of m with each bit of n
$ $	$m n$	OR each bit of m with each bit of n
\wedge	$m \wedge n$	Exclusive OR each bit of m with n
$\sim\wedge$ or $\wedge\sim$	$m \sim\wedge n$ or $m \wedge\sim n$	Exclusive NOR each bit of m with n

Unary Reduction Operators		
OP	Usage	Description
$\&$	$\&m$	AND all bits in m together (1-bit result)
$\sim\&$	$\sim\&m$	NAND all bits in m together (1-bit result)
$ $	$ m$	OR all bits in m together (1-bit result)
$\sim $	$\sim m$	NOR all bits in m together (1-bit result)
\wedge	$\wedge m$	Exclusive OR all bits in m (1-bit result)
$\sim\wedge$ or $\wedge\sim$	$\sim\wedge m$ or $\wedge\sim m$	Exclusive NOR all bits in m (1-bit result)

Operators (2/3)

 

Arithmetic Operators		
OP	Usage	Description
+	$m + n$	Add n to m
-	$m - n$	Subtract n from m
-	$-m$	Negate m (2's complement)
*	$m * n$	Multiply m by n
/	m / n	* Divide m by n
%	$m \% n$	* Modulus of m / n

* **Synthesis not supported** : The divisor for divide operator may be restricted to constants and a power of 2

Logical Operators		
OP	Usage	Description
!	$!m$	Is m not true? (1-bit True/False result)
&&	$m \&\& n$	Are both m and n true? (1-bit True/False result)
	$m n$	Are either m or n true? (1-bit True/False result)

Equality Operators (compares logic values of 0 and 1)		
OP	Usage	Description
==	$m == n$	Is m equal to n? (1-bit True/False result)
!=	$m != n$	Is m not equal to n? (1-bit True/False result)

Identity Operators (compares logic values of 0, 1, x, and z)		
OP	Usage	Description
===	$m === n$	* Is m identical to n? (1-bit True/False result)
!==	$m !== n$	* Is m not identical to n? (1-bit True/False result)

Synthesis not supported
Synthesis not supported

Operators (3/3)



Relational Operators		
OP	Usage	Description
<	$m < n$	Is m less than n? (1-bit True/False result)
>	$m > n$	Is m greater than n? (1-bit True/False result)
<=	$m \leq n$	Is m less than or equal to n? (True/False result)
>=	$m \geq n$	Is m greater than or equal to n? (True/False result)

Logical Shift Operators		
OP	Usage	Description
<<	$m \ll n$	Shift m left n-times
>>	$m \gg n$	Shift m right n-times

Misc Operators		
OP	Usage	Description
?:	$sel?m:n$	If sel is true, select m: else select n
{}	$\{m,n\}$	Concatenate m to n, creating larger vector
{}	$\{n\{m\}\}$	Replicate m n-times

Integer and Real Numbers



- Numbers can be integer or real numbers.
- Integer can be sized or unsized. Sized integer can be represented as
 - `<size>'<base><value>`
 - size : size in bits
 - base : can be b(binary), o(octal), d(decimal), or h(hexadecimal)
 - value : any legal number in the selected base and x, z, ?.
- Real numbers can be represented in decimal or scientific format.

Integer and Real Numbers



- 16 : 32 bits decimal
- 8'd16
- 8'h10
- 8'b0001_0000
- 8'o20
- 32'bx : 32 bits x
- 2'b1? : ? represents a high impedance bit
- 6.3
- 5.3e-4
- 6.2e3

Concatenation and Replication Operators



- Bit replication for 01010101
 - assign byte = {4{2'b01}};
- Sign extension
 - wire [7:0] byte;
 - assign word = {{8{byte[7]}},byte};



Input/Output Ports Declaration


- Input/output port declaration
 - **input** : 輸入埠
 - **output** : 輸出埠
 - **inout** : 雙向埠具輸出輸入特性

Input/Output Ports

```
module MUXS(out,a,b,sel);  
  output out;  
  input a,b,sel;  
  // The following are logic gates  
  not U0(sel_,sel);  
  and U1(a1,a,sel_),  
  U2(b1,b,sel);  
  or U3(out,a1,b1);  
endmodule
```

Inout Ports
 
```
module bidir(rw, din, da, iop);  
  input rw, din, da;  
  inout iop;  
  assign iop = rw ? ((din) ? da : iop): 1'bz;  
endmodule
```





Data Types and I/O Ports

- Verilog basic data types
 - **wire**: 一條接線(只能被動顯示硬體運算結果，無法設定特定值)
 - **wand**: wired AND 接線 (FPGA not support)
 - **wor**: wired OR 接線 (FPGA not support)
 - **reg**: 暫存接線(主要來用來儲存設定特定值)
 - **integer (32-bit signed), real, float, time**: 特性如reg，但只能用於test bench module的運算。
- 使用於所設計的邏輯模組內的通常只有**wire (net property)**與**reg (reg property)**。
- input/output/inout 輸出入埠預設為**wire**的特性。

Characteristics of reg and wire



- wire

- 資料型態為wire 的變數為連接硬體元件之連接線。
- 變數必須被驅動，才能改變它的內容。
- 除非被宣告為一向量，否則wire 型態的變數內定為一個位元的值，且其內定值為z。
- 使用wire 所宣告的變數必須配合assign 敘述來改變其值，不能在always 區塊中作為敘述的等號左值。





- reg

- 宣告為資料型態reg 之變數的功能和一般程式語言中的變數類似，可以直接給定一個數值。
- 除非被宣告為一向量，否則reg 型態的變數內定為一個位元的值，且其值為X。
- 使用reg 所宣告的變數必須使用在always 區塊中作為敘述的等號左值。

Value Sets



    - 4-value logic system in Verilog
 - 0: Logic 0, Zero, False, Ground, V_{ss} , Negative
 - 1: Logic 1, One, True, Power, V_{dd} , Positive
 - X: Unknown value
 - Z: High Impedance, Floating State, Tri-State, Disable driver.



Behavior Modeling



- Behavior model concerns only the function of the module without considering the operation of the circuits.
- Verilog is an event-driven timing control language.
 - Events:
 - Value change of reg or wire
 - Value change of input port
 - Synthesizable description of event control
 - Positive edge, negative edge, and value of changes of signals



always Description

- **always** monitors the change of input signals and update the output signals once the input changes.
 - **begin/end** are used when multiple statements respond to a specific event.

```
always@(event description)  
logic statement;
```

```
always@(event description)  
begin  
logic statement 1;  
logic statement 2;  
end
```

- Event description

- Single signal (level trigger)

```
always@(in1)
```

- Multiple signals (level trigger)

```
always@(in1 or in2 or in3)
```

- Edge trigger event (edge trigger)

```
always@(posedge clk)
```

```
always@(posedge clk or negedge reset)
```



if or if-else Description

- **if** is a conditional operation that checks the logic value (1 or 0)(true or false) to perform the following statement.
- **if** must be placed inside the **always** statement.
 - If always@(event) is level-triggered, if(expression) is level-triggered.
 - If always@(event) is edge-triggered, if(expression) is edge-triggered.
- **begin/end** are used when multiple statements are determined by a specific expression.

```
if(expression)
statement;
```

```
if(expression)
begin
statement1;
statement2;
end
```

```
if(expression)
statement1_true;
else
statement1_false;
```

```
if(expression)
begin
statement1_true;
statement2_true;
end
else
begin
statement1_false;
statement2_false;
end
```



case Description

- **case** is a conditional operation that checks multiple cases for perform the multiple statements in a tabular form.
 - If all conditions are stated, it is called “full case”; otherwise, it is not “full case”
 - The **default** case and statement are optional, but should be always included for circuit stability even if it is “full case”.

```
case (signal)
case0: statement0;
case1: statement1;
...
default: def_statement;
endcase
```

```
module decoder(X, out);
input [0:1] X;
output [0:3] out;
reg [0:3] out;
always@(X) begin
case (X)
2'b00: out = 4'b0001;
2'b01: out = 4'b0010;
2'b10: out = 4'b0100;
default: out = 4'b0000;
endcase
end
endmodule
```


```
module decoder(X, out);
input [0:1] X;
output [0:3] out;
reg [0:3] out;
always@(X) begin
case (X)
2'b00: out = 4'b0001;
2'b01: out = 4'b0010;
2'b10: out = 4'b0100;
2'b11: out = 4'b1000
default: out = 4'b0000; → instable
endcase
end
endmodule
```



 Example (1/3)

- **Continuous Assignment**
 - ? : ; Conditional operators (multiplexer)

```
module SMUX(out,a,b,sel);  
output out;  
input a,b,sel;  
  
assign out = (sel) ? a : b ;  
  
endmodule
```






Example (2/3)

- **if-else** statements
 - Not for large multiplexers

```
module SMUX(out,a,b,sel)
output out;
input a,b,sel;
reg out;

always @(sel or a or b)
  if (sel)
    out = a;
  else
    out = b ;

endmodule
```

 




 Example (3/3)

- case statements
 - Usually for large multiplexers

```
module SMUX(out,a,b,sel);  
output out;  
input a,b,sel;  
  
reg output;  
always @(sel or a or b)  
case (sel)  
1'b0: out = b;  
1'b1: out = a;  
endcase  
  
endmodule
```





Declaration of Vectors

- Vector declarations
 - `reg <range> <name> ,...,<name>;`
 - `Wire <range> <name>, ..., <name>;`
 - Example
 - `reg [3:0] a,b;`
 - `reg [0:3] c;`
 - `wire [7:0] in1;`
 - `wire [0:7] in2;`

Bit/Partial Bits Selection



- Bit Selection

```
wire [7:0] a, b, c;  
assign c[0] = a[0] & b[0];
```

- Partial Bits Selection


```
wire [7:0] a, b, c;  
assign c[3:0] = a[5:2] & b[7:4];
```

- Replication

```
wire [7:0] a, b, c;  
assign c = {{2{a[7:6]}},{4{b[2]}}};
```


- Concatenation

 
```
wire [7:0] a, b, c;  
assign c = {a[3:0],b[5:2]};
```



Port Connection Between Modules

 - An **input** or **inout** port must be a net (wire).
- An **output** port can be a register.
- A signal assigned a value in a procedural block (always, initial) must be a register data type.



 

Common Mistakes in Choosing Data Types

- Make a procedural assignment to a net
 - wire [7:0] databus;
 - always @(read or addr) databus=read ? mem[addr] : 'bz;
 - **Illegal left-hand-side assignment**
- Connect a register to an instance output
 - reg myreg;
 - and (myreg, net1, net2);
 - **Illegal output port specification**
- Declare a module **input** port as a register
 - input myinput;
 - reg myinput;
 - **Incompatible declaration**

Procedural Assignments



```
module assignment_test;
reg [3:0] a,b;
wire [4:0] sum1;
reg [4:0] sum2;

assign sum1 = a + b ;

initial
begin
    a=4'b1010;b=4'b0110;
    sum2 = a + b;
    $display("a b sum1 sum2");
    $monitor(a,b,sum1,sum2);
    #10 a=4'b0001;
end
endmodule
```

Continuous assignment

Procedural assignment

```
module FA(s,co,a,b,ci);
input a,b,ci;
output s,co;
reg s;

s=a^b^ci;

always @(a or b or ci)
begin
    assign co=(a&b)|(b&ci)|(a&ci);
end
endmodule
```

Error! Illegal left-hand-side continuous assignment.

Error! Illegal left-hand-side in assign statement.



Parameter

- parameter敘述可用於定義一個常數供模組用來定義輸出入埠的寬度、向量的大小等
 - parameter name = number;

```
module add8(a, b, c);  
parameter width=8;  
input [width-1:0] a, b;  
output [width-1:0] c;  
  
assign c = a + b;  
  
endmodule
```



Compiler Directives

- Verilog 語言跟 C 語言一樣提供編譯命令 (compiler directives) 供使用者利用，指示編譯程式進行編譯的前置作業。

- `define
- `include

```
`define LEN 4
module buf4(in, out, clock);
input  [^LEN-1:0] in;
input  clock;
output [^LEN-1:0] out;
reg    [^LEN-1:0] out;
...
```

fa1.v

```
module fa1(a, b, ci, s, co);
input  a, b, ci;
output s, co;
assign {co, s} = a + b + ci;
endmodule
```

fa2.v

```
`include "fa1.v"
module fa2(a, b, ci, s, co);
input  [1:0] a, b;
input  ci;
output [1:0] s;
output co;
wire   c1;
fa1 fa0(a[0],b[0],ci,s[0],c1);
fa1 fa1(a[1],b[1],c1,s[1],co);
endmodule
```

- `define 用來定義模組中使用到的常數。
- `include 用來引入其他verilog檔案一起編譯與合成。
- 如果已經在proj list已經都加入fa1.v fa2.v，就沒有必要使用`include fa1.v

Module Connections



- Module connection can be called by **port order** or **port names**.
- **call-by-name** can ignore the port order defined in the module.

```
module ha(a,b,sum,co)
input a,b;
output sum,co;
wire sum,co;
assign sum = a^b;
assign co=a&b;
endmodule
```

call by port order

```
module adder(a_in,b_in,sum_out,carry_cout)
input a_in,b_in;
output sum_out,co_out;
wire sum_out,co_out;
ha adder0(a_in,b_in,sum_out,carry_out);
endmodule
```

call by port names

```
module adder(a_in,b_in,sum_out,carry_cout)
input a_in,b_in;
output sum_out,co_out;
wire sum_out,co_out;
ha adder0(.b(b_in),
           .a(a_in),
           .sum(sum_out),
           .co(carry_out));
endmodule
```

Outline




- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits



MUX 1

```
module mux(  
    out, // output  
    a, // input a  
    b, // input b  
    c, // input c  
    d, // input d  
    sel // selection control signal  
);  
  
output out; // output  
input a; // input a  
input b; // input b  
input c; // input c  
input d; // input d  
input [1:0] sel; // selection control signal  
reg out; // output (in always block)  
  
always @(sel or a or b or c or d)  
    if (sel==2'b00) out = a;  
    else if (sel==2'b01) out = b;  
    else if (sel==2'b10) out=c;  
    else out=d;  
endmodule
```


Final "else ---;" is required

 

MUX 2



```
module mux(  
    out, // output  
    a, // input a  
    b, // input b  
    c, // input c  
    d, // input d  
    sel // selection control signal  
);  
  
output out; // output  
input a; // input a  
input b; // input b  
input c; // input c  
input d; // input d  
input [1:0] sel; // selection control signal  
reg out; // output (in always block)  
  
always @(sel or a or b or c or d)  
    case (sel)  
        2'b00: out = a;  
        2'b01: out = b;  
        2'b10: out = c;  
        2'b11: out = d;  
        default: out = 0;  
    endcase  
endmodule
```

 


Final "default: ---;" is required

Design Procedure




- 1 • From the *specifications*, determine the inputs, outputs, and their symbols.
- 2 • Derive the *truth table (functions)* from the relationship between the inputs and outputs
- 3 • Derive the *simplified Boolean functions* for each output function.
- 4 • Draw the logic diagram.
- 5 • Construct the Verilog code according to the logic diagram.
- 6 • Write the testbench and verify the design.



Seven-Segment Display Decoder (1/2)

 

 1 input: `bcd[3:0]`
output: `display[7:0]`



2

  

3

- BCD → 7-segment_star_dot
- 0000 → 0000001_1
- 0001 → 1001111_1
- 0010 → 0010010_1
- 0011 → 0000110_1
- 0100 → 1001100_1
- 0101 → 0100100_1
- 0110 → 0100000_1
- 0111 → 0001111_1
- 1000 → 0000000_1
- 1001 → 0000100_1
- others → 0111000_1 (F)

Seven-Segment Display Decoder (2/2)




5

```
module ssd(  
    display, // SSD display output  
    bcd // BCD input  
);  
  
output [7:0] display; // SSD display output  
input [3:0] bcd; // BCD input  
  
reg [7:0] display; // SSD display output (in always)  
  
// Combinational logics:  
always @(bcd)  
    case (bcd)  
        4'd0: display = 8'b 0000001_1; //0  
        4'd1: display = 8'b 1001111_1; //1  
        4'd2: display = 8'b 0010010_1; //2  
        4'd3: display = 8'b 0000110_1; //3  
        4'd4: display = 8'b 1001100_1; //4  
        4'd5: display = 8'b 0100100_1; //5  
        4'd6: display = 8'b 0100000_1; //6  
        4'd7: display = 8'b 0001111_1; //7  
        4'd8: display = 8'b 0000000_1; //8  
        4'd9: display = 8'b 0000100_1; //9  
        default: display = 8'b 0111000_1 ; //F  
    endcase  
  
endmodule
```




2-bit Absolute Value Calculator (1/3)


1 input: $z[1:0]$
output: $z_abs[2:0]$

 

 2 If z is negative (MSB is 1), complement every bit and add 1.
If z is positive (MSB is 0), output remains the same as input.
Use XOR for MSB and every bit.



2-bit Absolute Value Calculator (2/3)

 

module : abs.v

5


```
module abs(  
  z_abs, // absolute value of z  
  z // original value  
);  
  
output [2:0] z_abs; // absolute value of z  
input [1:0] z; // original value  
  
reg [1:0] z_tmp; // XOR output  
reg [2:0] z_abs; // register for Z  
  
// Combinational logics:  
always @(z)  
begin  
  z_tmp[1]=z[1]^z[1];  
  z_tmp[0]=z[0]^z[1];  
  z_abs={z_tmp[1],z_tmp}+{2'b0,z[1]};  
end  
  
endmodule
```

testbench module : t_abs.v


6

```
module t_abs;  
  
wire [2:0] z_abs; // absolute value of z  
reg [1:0] z; // original value  
  
abs U0(.z_abs(z_abs),.z(z));  
  
initial  
begin  
  z=2'b00;  
  #5 z=2'b01;  
  #5 z=2'b10;  
  #5 z=2'b11;  
  #5 z=2'b00;  
end  
  
endmodule
```

2-bit Absolute Value Calculator (3/3)

 

6

 

Outline



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits

Sequential Logic Circuits




- Memory Devices
 - Latch
 - Flip-flop
 - Register
- Sequential Circuits
 - Synchronous Counters
 - General Synchronous Sequential Circuits
- Finite State Machine
 - Moore Machine
 - Mealy Machine



Latch

- Latch is an level-triggered storage with a trigger signal enable.
- It is suggested not to use the level-triggering latch in the experiment.
 - Transparent Q
 
```
module latch_d(Enable, D, Q);  
input Enable, D;  
output Q;  
reg Q;  
  
always@(Enable or D)  
if (Enable)  
Q = D;  
  
endmodule
```





Flip-Flop

- Flip-flop with synchronous clock and asynchronous reset
 - Opaque flip-flop



```
module D_FF_SR(clock, reset, D, Q);  
input clock, reset, D;  
output Q;  
reg Q;
```

```
always @(posedge clock or negedge reset)  
begin
```

```
if (reset == 1'b0)  
Q = 1'b0; // reset
```

```
else  
Q = D;  
end
```

```
endmodule
```

  





register

- 16-bit synchronous register with clear

```
module reg_16(clear, clock, in, out);  
input  clear, clock;  
input  [0:15] in;  
output [0:15] out;  
reg    [0:15] out;
```
 
```
always@(posedge clock or posedge clear)  
begin  
if (clear == 1'b1)  
out = 16'b0;  
else out = in;  
end  
endmodule
```



 

Synchronous Counter

- It is recommended that the logic circuits and the flip-flops are coded separately.

Logic circuits and flip-flops are jointly coded.

```
module counter1(direct, clk, reset, out);
input  direct, clk, reset;
output [0:3] out;
reg    [0:3] out;

always@(posedge clk or negedge reset) begin
if (~reset)
out <= 4'b0000;
else
begin
if (direct)
out <= out + 1;
else
out <= out - 1;
end
end
endmodule
```

Logic circuits and flip-flops are separately coded.


```
module counter1(direct, clk, reset, out);
input  direct, clk, reset;
output [0:3] out;
reg    [0:3] out;
wire  [0:3] out_temp;

// Logic circuits
assign out_temp = (direct) ? out+1 : out-1;


// Flip-flops
always@(posedge clk or negedge reset) begin
If(~reset)
out <= 4'b0000;
else
out <= out_temp;
end

endmodule
```

Generalized Sequential Circuits

 

 - Recommended coding styles
 - Separate coding of combinational logics and flip-flops



```
reg    [0:LEN-1] out;  
reg    [0:LEN-1] out_temp;
```

```
// Logic circuits
```

```
always @(in1 or in2 or ...)
```

```
out_temp <= combinational_circuits_codes;
```

```
// Flip-flops
```

```
always@(posedge clk or nedge reset) begin
```

```
if(~reset)
```

```
out <= 0;
```

```
else
```

```
out <= out_temp;
```

```
end
```

```
reg    [0:LEN-1] out;
```

```
wire   [0:LEN-1] out_temp;
```

```
// Logic circuits
```

```
assign out_temp = combinational_circuits_codes;
```

```
// Flip-flops
```

```
always@(posedge clk or nedge reset) begin
```

```
if(~reset)
```

```
out <= 0;
```

```
else
```

```
out <= out_temp;
```


```
end
```




Finite State Machine

- Moore Machine

 - Output y depends on the current state, not input x .
- Output y is synchronized with the state s .



Current State	Next State		output y
	Input $x=0$	Input $x=1$	
s0	s2	s1	0
s1	s0	s2	0
s2	s1	s0	1

 

Moore Machine

- Moore Machine Coding Style

```
module moore(reset, clk, x, y);  
input reset, clk, x;  
output y;  
reg y;  
parameter s0=2'b00, s1=2'b01, s2=2'b10;  
reg [0:1] ps, ns;  
  
always@(reset or ps)  
begin  
    if (reset)  
        begin  
            ns = s0; y = 0;  
        end  
    else  
        begin  
            case(ps)  
                0: ns = s0; y = 0;  
                1: ns = s1; y = 0;  
                2: ns = s2; y = 0;  
            end  
        end  
    end  
end
```


```
s0: begin  
    if (x == 0)  
        ns = s2;  
    else ns = s1;  
    y = 0;  
end  
s1: begin  
    if (x == 0)  
        ns = s0;  
    else ns = s2;  
    y = 0;  
end  
.....  
endcase  
end end // else & always  
  
always@(posedge clk or negedge reset)  
if (~reset)  
    ps<= s0;  
else  
    ps<= ns;  
endmodule
```



Finite State Machine

- Mealy Machine

 - Output y depends on both the current state and input x .
- Output y is synchronized with the input x .



Current State	Next State		Output y	
	Input $x=0$	Input $x=1$	Input $x=0$	Input $x=1$
s0	s2	s1	0	0
s1	s0	s2	0	0
s2	s1	s0	1	1



Mealy Machine

- Mealy Machine Coding Style

```
module mealy(reset, clk, x, y);
input reset, clk, x;
output y;
reg y;
parameter s0=2'b00, s1=2'b01, s2=2'b10;
reg [0:1] ps, ns;
always@(reset or ps)
begin
    if (reset)
        begin
            ns = s0; y = 0;
        end
    else
        begin
```

```
        case(ps)
            s0: begin
                if (x == 0)
                    ns = s2;
                else ns = s1;
                if (x == 0)
                    y = 0;
                else y = 0;
            end
            s1: begin
                .....
            endcase
        end end // else & always

always@(posedge clk or negedge reset)
if (~reset)
    ps<= s0;
else
    ps<= ns;
endmodule
```

Outline



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- **Behavior Modeling**
- Examples of Sequential Circuits

Behavior Modeling





- In behavior modeling, you must specify your circuit's
 - Action
 - How to model the circuit's behavior
 - Timing control
 - Timing
 - Condition
- Verilog supports the following structures for behavior modeling
 - Procedural block
 - Procedural assignment
 - Timing control
 - Control statement



Procedural Blocks

  - In Verilog, procedural blocks are basis of behavior modeling
- Procedural blocks are of two types
 - initial procedural block, which executes only once
 - always procedural block, which executes in a loop






Procedural Blocks


- All procedural blocks are activated at simulation time 0.
 - The block will not be executed until the enabling condition evaluates TRUE.
 - Without the enabling condition, the block will be executed immediately.

Activated at simulation time 0

 

Statement will not be executed until the condition *c* is TRUE.

Procedural Blocks

 

```
• module clock_gen(phi1,phi2);
• output phi1,phi2;
• reg phi1,phi2;

• initial
• begin
• phi1=0;phi2=0
• end

• always
• #100 phi1=~phi1;

• always @(posedge phi1)
• begin
• phi2=1;
• #50 phi2=0;
• #50 phi2=1;
• #50 phi2=0;
• end
• endmodule
```

This procedural block is activated and executed at simulation time 0

This procedural block is activated at simulation time 0 and is always executed

This procedural block is activated at simulation time 0 but executed at positive edge of phi1

Procedural Blocks



- Three components
 - Procedural assignment statements
 - High-level programming language constructs
 - Timing controls
- Using the first two components to model the actions of the circuit.
- Using **timing controls** to model when should these actions happen.

Procedural Timing Control



- Three types
 - Simple delay control
 - #50 clk=~clk;
 - Event control
 - @(a or b or ci) sum=a+b+ci;
 - @(posedge clk) q=d;
 - Level-sensitive timing control



Block Statements

- Group two or more statements together
 - Sequential blocks
 - Enclosed by keyword **begin** and **end**
 - Parallel blocks
 - Enclosed by keyword **fork** and **join**

```
begin
  #10 out='d10;
  #10 out='d43;
  #10 out='d25;
  #10 out='d86;
end
```

Equivalent

```
fork
  #10 out='d10;
  #20 out='d43;
  #30 out='d25;
  #40 out='d86;
join
```



Blocking and Non-blocking Assignments

- Procedural assignments update the value of register under the control of the procedure flow constructs.
- Blocking procedure assignment
Basic form : `<lvalue> = <timing_control> <expression>`
- Non-Blocking procedure assignment
Basic form : `<lvalue> <=> <timing_control> <expression>`

<pre>initial begin a=0; b=1; c=0; end always c = #5 ~c;</pre>	<pre>always @(posedge c) begin a=b; // 1 b=a; // 1 end</pre>	<pre>always @(posedge c) begin a<=b; // 1 b<=a; // 0 end</pre>
	Blocking	Non-Blocking





Blocking and Non-blocking Assignments

- Blocking assignments

- Evaluate the RHS expression and **stores** the value in the LHS register immediately
  
```
initial begin
  a = #10 1;
  $display("current time = %t a = %b", $time, a);
end
```







Blocking and Non-blocking Assignments

- Non-blocking assignments
 - It evaluate the RHS expression and **schedules** to update the value in the LHS register
 - It updates the LHS only after evaluating all the RHS
  
```
initial begin
  a <= #10 1;
  $display("current time = %t a = %b", $time, a);
end
```




Blocking and Non-blocking Assignments




Bad: Circuit from blocking assignment.
 
```
always @(posedge clk)
begin
    b=a;
    a=b;
end
```



Good: Circuit from nonblocking assignment.
 
```
always @(posedge clk)
begin
    b<=a;
    a<=b;
end
```



Outline




- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits
- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits

D-type Flip Flop


 
```
module dff(  
    q, // output  
    d, // input  
    clk, // global clock  
    rst_n // active low reset  
);  
  
output q; // output  
input d; // input  
input clk; // global clock  
input rst_n; // active low reset  
  
reg q; // output (in always block)  
  
always @(posedge clk or negedge  
rst_n)  
    if (~rst_n)  
        q<=0;  
    else  
        q<=d;  
  
endmodule
```



Binary Up Counter



```
`define BCD_BIT_WIDTH 4
`define BCD_ZERO 4'd0
`define BCD_ONE 4'd1
`define BCD_NINE 4'd9
module bcdcounter(
  q, // output
  clk, // global clock
  rst_n // active low reset
);


output [BCD_BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [BCD_BIT_WIDTH-1:0] q; // output (in always block)
reg [BCD_BIT_WIDTH-1:0] q_tmp; // input to dff (in always block)

// Combinational logics
always @(q)
  q_tmp = q + `BCD_ONE;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n) q<=`BCD_BIT_WIDTH'd0;
  else q<=q_tmp;

endmodule
```

 

Frequency Divider



```
`define FREQ_DIV_BIT 24
module freq_div(
  clk_out, // divided clock output
  clk, // global clock input
  rst_n // active low reset
);


output clk_out; // divided output
input clk; // global clock input
input rst_n; // active low reset

reg clk_out; // clk output (in always block)
reg [FREQ_DIV_BIT-2:0] cnt; // remainder of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

// Combinational logics: increment, neglecting overflow
always @(clk_out or cnt)
  cnt_tmp = {clk_out,cnt} + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n) {clk_out, cnt}<=`FREQ_DIV_BIT'd0;
  else {clk_out,cnt}<=cnt_tmp;

endmodule
```

 

cnt_tmp[23:0]



cnt[22:0]



Modularized Shift Register Design



Shift Register

  

shifter.v




```
`define BIT_WIDTH 4
module shifter(
  q, // shifter output
  clk, // global clock
  rst_n // active low reset
);

output [^BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [^BIT_WIDTH-1:0] q; // output

 // Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    begin
      q<=`BIT_WIDTH'b0101;
    end
  else
    begin
      q[0]<=q[3];
      q[1]<=q[0];
      q[2]<=q[1];
      q[3]<=q[2];
    end
  end
endmodule
```



Initial value $q = 0101$

shiftreg.v



```
`define BIT_WIDTH 4
module shift_reg(
  q, // LED output
  clk, // global clock
  rst_n // active low reset
);

output [^BIT_WIDTH-1:0] q; // LED output
input clk; // global clock
input rst_n; // active low reset

wire clk_d; // divided clock
wire [^BIT_WIDTH-1:0] q; // LED output
```

```
// Insert frequency divider (freq_div.v)
freq_div U_FD(
  .clk_out(clk_d), // divided clock output
  .clk(clk), // clock from the crystal
  .rst_n(rst_n) // active low reset
);

// Insert shifter (shifter.v)
shifter U_D(
  .q(q), // shifter output
  .clk(clk_d), // clock from the frequency divider
  .rst_n(rst_n) // active low reset
);

endmodule
```