



Shifter

黃元豪
Yuan-Hao Huang



國立清華大學電機工程學系
Department of Electrical Engineering
National Tsing-Hua University



Modularized Shift Register Design



Shift Register

  

Frequency Divider



```
`define FREQ_DIV_BIT 27
module freq_div(
    clk_out, // divided clock output
    clk, // global clock input
    rst // active high reset
);

output clk_out; // divided output
input clk; // global clock input
input rst; // active high reset

reg [FREQ_DIV_BIT-1:0] cnt; // remainder of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)



wire clk_out;

// Dividied frequency
assign clk_out = cnt[FREQ_DIV_BIT-1];

// Combinational logics: increment, neglecting overflow
always @(cnt)
    cnt_tmp = cnt + 1'b1;

// Sequential logics: Flip flops
always @ (posedge clk or posedge rst)
    if (rst)
        cnt<= `FREQ_DIV_BIT'd0;
    else
        cnt<=cnt_tmp;

endmodule
```

  

shifter.v




```
`define BIT_WIDTH 4
module shifter(
    q, // shifter output
    clk, // global clock
    rst // active high reset
);

output [`BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst; // active high reset

reg [`BIT_WIDTH-1:0] q; // output

 // Sequential logics: Flip flops
always @(posedge clk or posedge rst)
if (rst)
begin
    q<=`BIT_WIDTH'b0101;
end
else
begin
    q[0]<=q[3];
    q[1]<=q[0];
    q[2]<=q[1];
    q[3]<=q[2];
end
endmodule
```



Initial value q = 0101

shiftreg.v



```
`define BIT_WIDTH 4
module shiftreg(
    q, // LED output
    clk, // global clock
    rst // active high reset
);

output [BIT_WIDTH-1:0] q; // LED output
input clk; // global clock
input rst; // active high reset

wire clk_d; // divided clock
wire [BIT_WIDTH-1:0] q; // LED output
```

```
// Insert frequency divider (freq_div.v)
freq_div U_FD(
    .clk_out(clk_d), // divided clock output
    .clk(clk), // clock from the crystal
    .rst(rst) // active high reset
);

// Insert shifter (shifter.v)
shifter U_D(
    .q(q), // shifter output
    .clk(clk_d), // clock from the frequency divider
    .rst(rst) // active high reset
);

endmodule
```

FAQ: Module Reuse



```
/// combinational circuits
new N0(.c(Q_temp), .a(A) , .b(B));

/// sequential flip-flops
always @(posedge clk or posedge rst)
If(rst)
Q<=0;
else
Q<=Q_temp;

module new(a,b,c);
input a,b;
output c;
.....
endmodule
```

```
/// combinational circuits
/// sequential flip-flops
always @(posedge clk or posedge rst)
If(rst)
Q<=0;
else
new N0(.c(Q), .a(A) , .b(B));  
  
X

module new(a,b,c);
input a,b;
output c;
.....
endmodule
```



FAQ: Black Box

- Your module is reported as “black box” if the module is redundant.
 - Example : a module without output port.

```
`define FREQ_DIV_BIT 24
module freq_div(
    clk_out, // divided clock output
    clk, // global clock input
    rst // active high reset
);

output clk_out; // divided output
input clk; // global clock input
input rst; // active high reset

reg [FREQ_DIV_BIT-1:0] cnt; // remainder of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

wire clk_out;

// Dividied frequency
assign clk_out = cnt[23], →

// Combinational logics: increment, neglecting overflow
always @(cnt)
    cnt_tmp = cnt + 1'b1;

// Sequential logics: Flip flops
always @ (posedge clk or posedge rst)
    if (rst)
        cnt<=`FREQ_DIV_BIT'd0;
    else
        cnt<=cnt_tmp;

endmodule
```