



Electronic Clock - Display Control

黃元豪

Yuan-Hao Huang

國立清華大學電機工程學系

Department of Electrical Engineering

National Tsing-Hua University

Timer




- Timer is a counter with carry propagation.
 - Hour : 0~23
 - Date: 0~28/30/31
 - Month:
Jan(0)/Feb(1)/March(2)/...../November(10)/December(11)
 - Year: 00~99
- The carry propagation is determined not only by lower counter but also upper counters.
 - Leap month
 - Leap year

Display Control of Timer



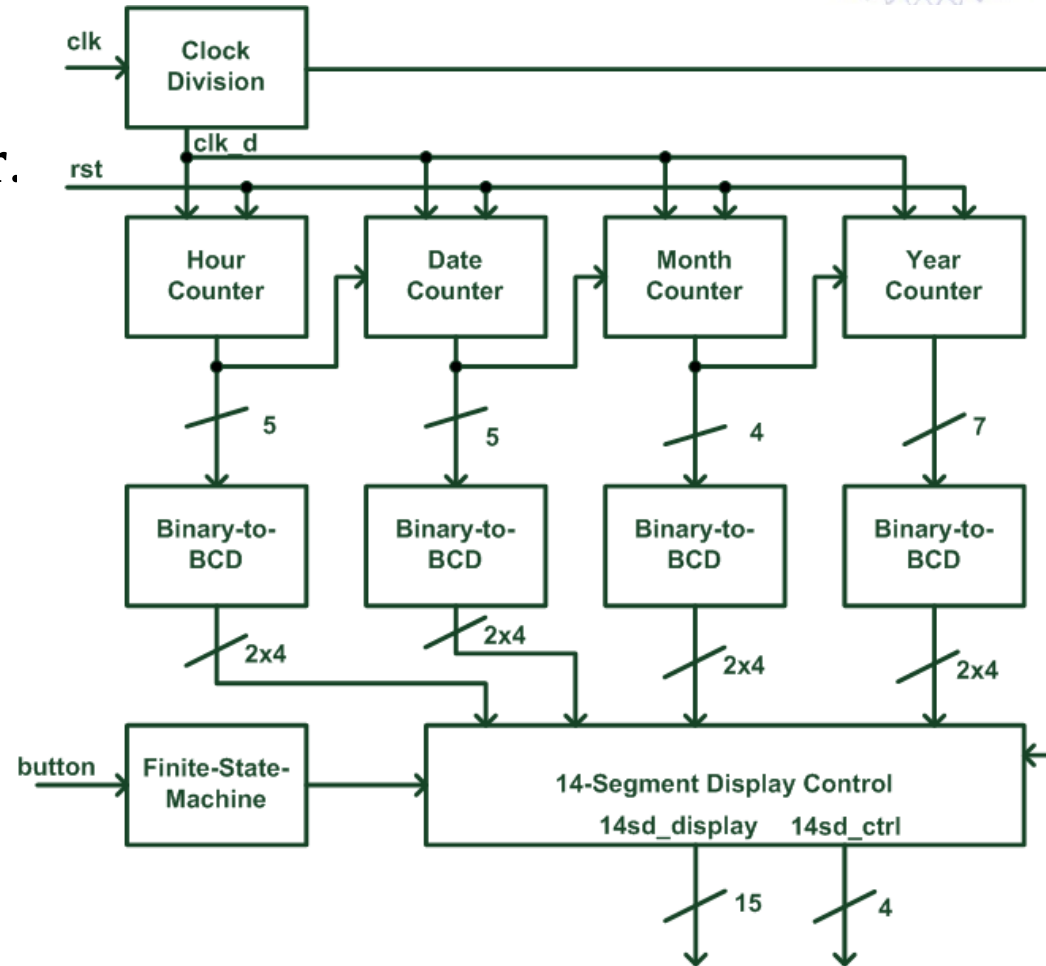
- Finite-state-Machine
 - State determines the display modes of Timer.
 - 24hr or AM/PM
 - Month + Year
 - Date + Month
 - Year






Switch Contact Bounce

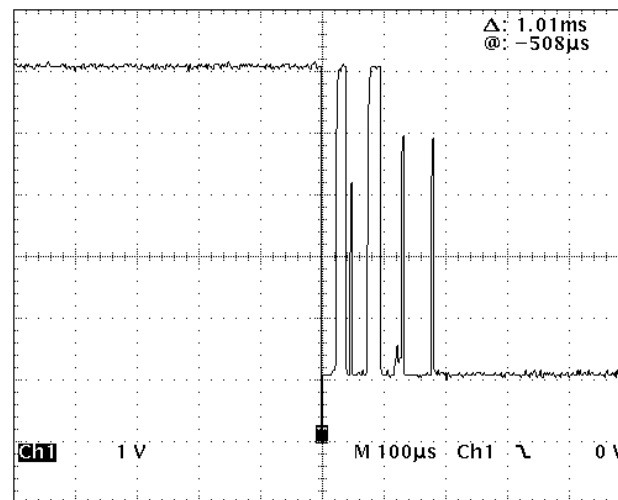- Pushbutton contains a metal spring
 - The switch contact will bounce several times before stabilization when buttons are pressed and released.
 - The random pulses causes instable results to the design.
 - The random pulses ranges in μs , but the FPGA is sensitive to pulses down to ns range.



Debounce Circuit

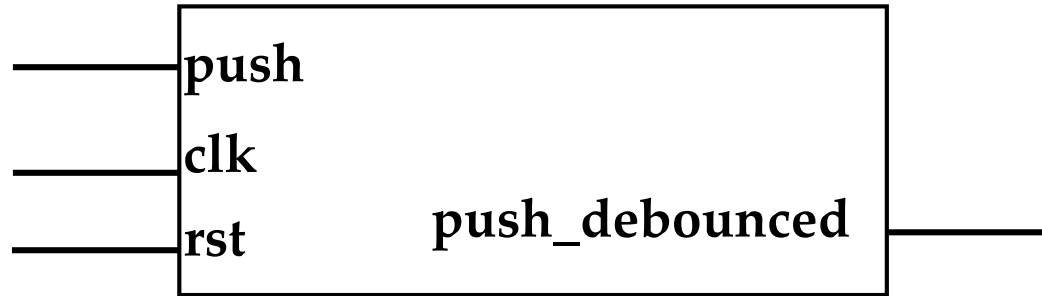

- N-bit shift register triggered with clock can be used as debounce circuit.
- When all 4 bits of the register are high (low), the output of the debounce circuit changes to high (low).

Debounce Design



```
module debounce (  
  rst, clk, push, push_debounced );
```

```
input rst;  
input clk;  
input push;  
output push_debounced;
```

```
// declare the outputs
```

```
reg push_debounced;
```

```
// declare the shifting registers
```


```
reg[3:0] push_window;
```

```
always @(posedge clk or posedge rst)  
begin  
  if (rst) begin  
    push_window <= 4'b0;  
    push_debounced <= 1'b0;  
  end else begin  
    push_window <= {push, push_window[3:1]};  
  
    if (push_window[3:0] == 4'b1111) begin  
      push_debounced <= 1'b1;  
    end else begin  
      push_debounced <= 1'b0;  
    end  
  end  
end  
endmodule
```




One-Pulse Generation

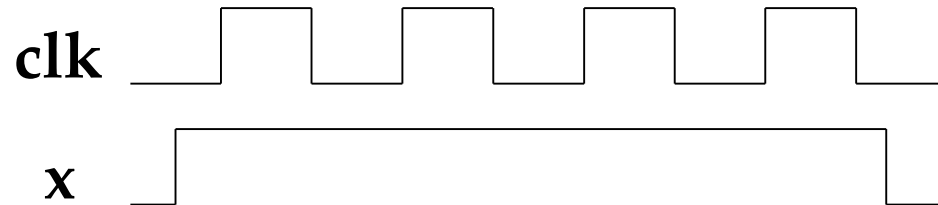- Since the state of pressed is much longer than one clock period, the push-button usually recognizes one “pressed” event as successive cycles of “pressed”.



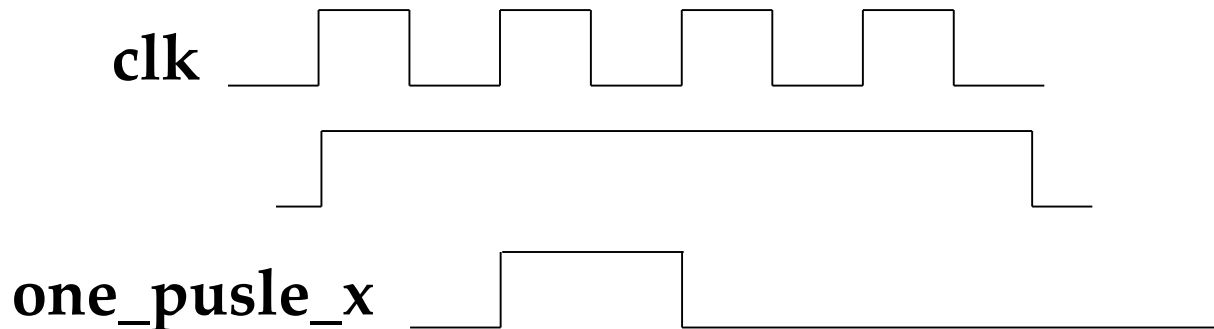- Once a pushbutton is pressed (long or short), the one-pulse circuit generates only a one-clock-period-long pulse.



One-Pulse Generation



- Inputs
 - `clk, rst` : system clock and reset.
 - `push_debounced`: debounced pushbutton signal
- Output
 - `push_onepulse`: one-clock-cycle impulse when pushbutton is pressed.

One-Pulse Design



```
module onepulse (  
rst, clk, push_debounced, push_onepulse  
);  
input clk, rst;  
input push_debounced;  
output push_onepulse;  
  
// internal registers  
reg push_onepulse_next;  
reg push_debounced_delay;  
  
always @* begin  
push_onepulse_next = push_debounced  
& ~push_debounced_delay;  
end
```

```
always @(posedge clk or posedge rst)  
begin  
if (rst) begin  
  
push_onepulse <= 1'b0;  
push_debounced_delay <= 1'b0;  
  
end else begin  
  
push_onepulse <= push_onepulse_next;  
push_debounced_delay <= push_debounced;  
  
end  
end  
endmodule
```