

Pre-Lab3 Report

I . Pre-Lab3_1 (4-bit synchronous binary up counter)

Design Specification

IO:


Input: clk, rst_n.

Output: [3:0] q.

Design Implementation

First, according to binary up counter, output add 1 after passing D-flip flop. So I declare a variable [3:0] q_tmp to store the result temporarily after adding 1. Then I can construct the logic diagram:


Logic diagram:

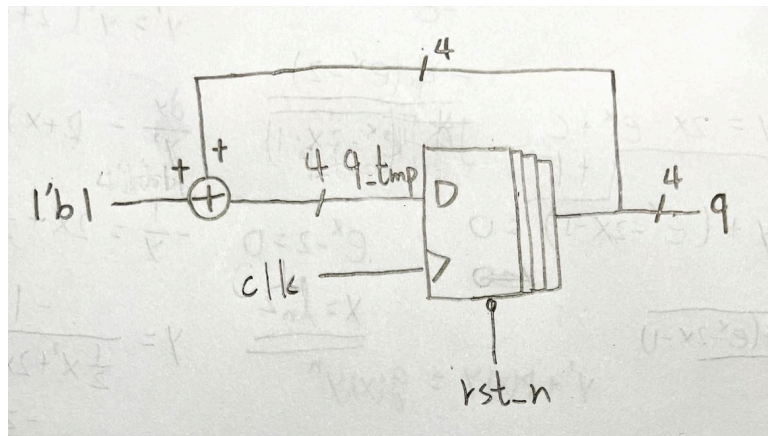

Finally, construct Verilog RTL code for the binary up counter:

```
22
23 module counter(
24     output reg [3:0] q,
25     input clk,
26     input rst_n
27 );
28     reg [3:0] q_tmp;
29     always@*
30         q_tmp = q + 1'b1;
31     always@(posedge clk or negedge rst_n)
32         if(~rst_n)
33             q <= 4'd0;
34         else
35             q <= q_tmp;
36 endmodule
37
```

Simulation:

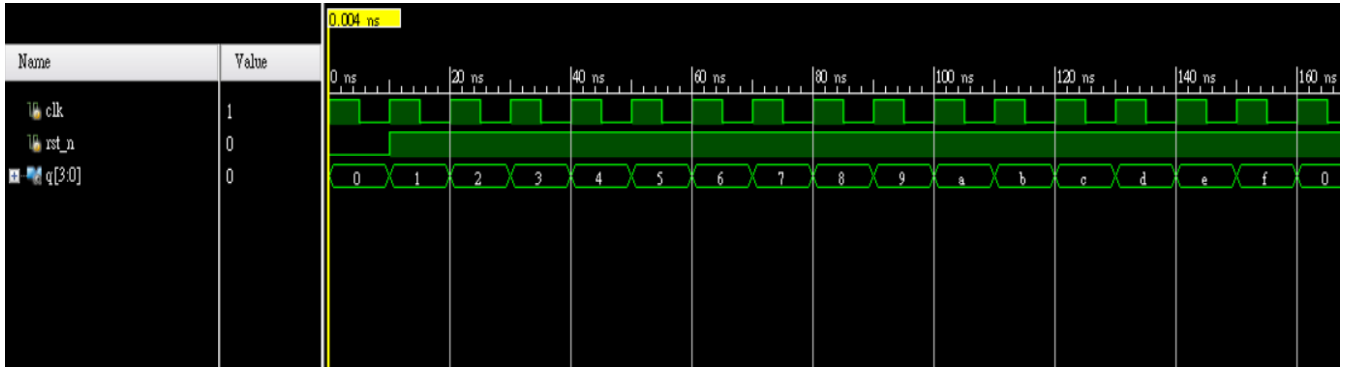

II. Pre-Lab3_2 (ringer counter)

Design Specification

IO:

Input: clk, rst_n.

Output: [7:0] q.


Design Implementation

Because this is a ring counter, I connect each flip flop by following method

```
q[6] <= q[7];  
q[5] <= q[6];  
q[4] <= q[5];  
q[3] <= q[4];  
q[2] <= q[3];  
q[1] <= q[2];  
q[0] <= q[1];  
q[7] <= q[0];
```

and if rst_n = 1, D-flip flop should be 10010110.

Logic diagram:

 

Finally, construct Verilog RTL code for the ring counter:

```
module shifter(  
    output reg [7:0] q,  
    input clk,  
    input rst_n  
);  
  
always@(posedge clk or negedge rst_n)  
    if(~rst_n)  
        q <= 8'b10010110;  
    else  
        begin  
            q[6] <= q[7];  
            q[5] <= q[6];  
            q[4] <= q[5];  
            q[3] <= q[4];  
            q[2] <= q[3];  
            q[1] <= q[2];  
            q[0] <= q[1];  
            q[7] <= q[0];  
        end  
endmodule
```

Simulation:

