

Lab 4: Counters and Shift Registers II

Objective

- ✓ Review sequential circuits.
- ✓ Review counters and shift registers.

Prerequisite

- ✓ Fundamentals of logic gates.
- ✓ Clocking concepts
- ✓ Logic modeling in Verilog HDL.

Experiments

- 1 Construct a 4-bit synchronous binary up counter ($b_3b_2b_1b_0$) with the 1-Hz clock frequency from lab2 and use 4 LEDs for display.

I/O	$f_{crystal}$	b_3	b_2	b_1	b_0
Site	W5	V19	U19	E19	U16

- 2 Combine the 4-bit synchronous binary up counter from exp1 with a binary-to-seven-segment-display decoder (from lab2-exp2) to display the binary counting in 7-segment display.
- 3 Construct a single digit BCD up counter with a 5-Hz clock as the clock frequency and display on the seven-segment display.
 - 3.1 Construct a BCD up counter.
 - 3.2 Construct a BCD-to-seven-segment display decoder.
 - 3.3 Combine the above two together.
- 4 Construct a 2-digit BCD up counter with a 1-Hz clock as the clock frequency and display on the seven-segment display.