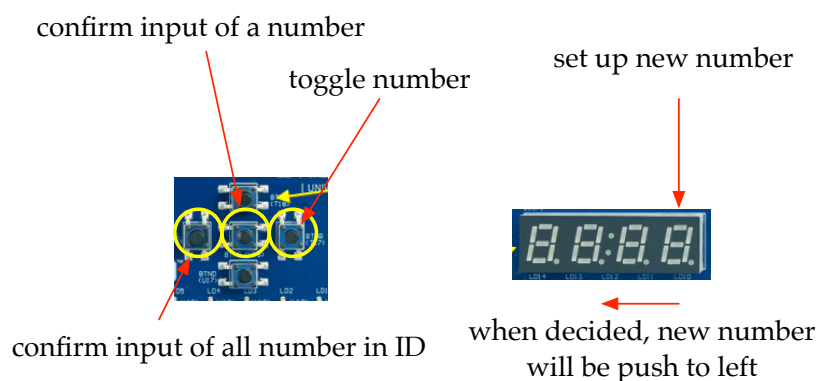


Final Exam

Exams

1. Use your 9-digit student ID to form the display pattern described below
 - 1.1. To set each number in the ID, push right button to toggle the number in the sequence of 0, 1, 2, 3, ..., 7, 8, 9, and then back to 0 to continue counting up. Each push of the right button will increase the number by 1. The number to be determined is display in the right most digit of the seven-segment display. When the number is decided, push center button to confirm and the number will be push to left.



- 1.2. When all the numbers in the ID are input completely, push the left button to confirm.
- 1.3. After all the numbers in the ID have been input, the numbers will display as a marquee.
- 1.4. Construct a frequency divider to provide frequency of 1 Hz (exact 1 Hz) for the marquee.
- 1.5. Use push button to set the number into the ID.
- 1.6. Your results will be the following two
 - 1.6.1. Your student ID will be display on the 7-segment display as a marquee.
 - 1.6.2. Use the last four digits of your student ID as the initial 16 bits into to the LED.
- 1.7. You will have the two operation modes as
 - 1.7.1. mode 1: input your student ID
 - 1.7.2. mode 2: start the student ID marquee on 7-segment display.
- 1.8. Use DIP switches as 'reset' and 'mode selection'.

You can use all the resources in the FPGA board to implement the above mentioned functions.

Score:

1. Frequency divider: 5%
2. push button input:
 - a. BCD up counter and display: 5%
 - b. FSM for push button input: 20%

- c. whole integration: 10%
- 3. 7-segment display (9-digit marquee shift register, any pattern): 20%
- 4. 7-segment display (student ID marquee): 20%
- 7. All (include FSM control) 20%