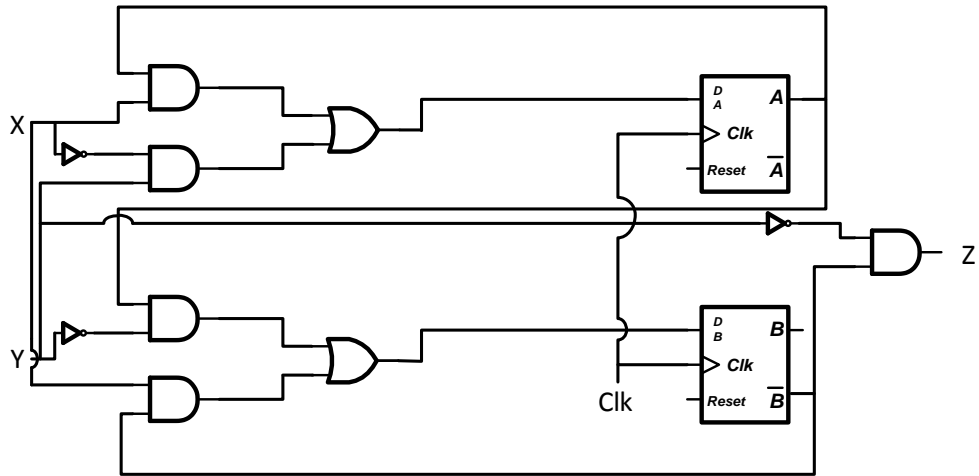


1.


a.)



b.)

Present state		Input		Next Stage		Output
A	B	X	Y	A+1	B+1	Z
0	0	0	0	0	0	1
0	0	0	1	1	0	0
0	0	1	0	0	1	1
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	0	1	1
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	1	0
1	1	0	0	0	1	0
1	1	0	1	1	0	0
1	1	1	0	1	1	0
1	1	1	1	1	0	0

c.)

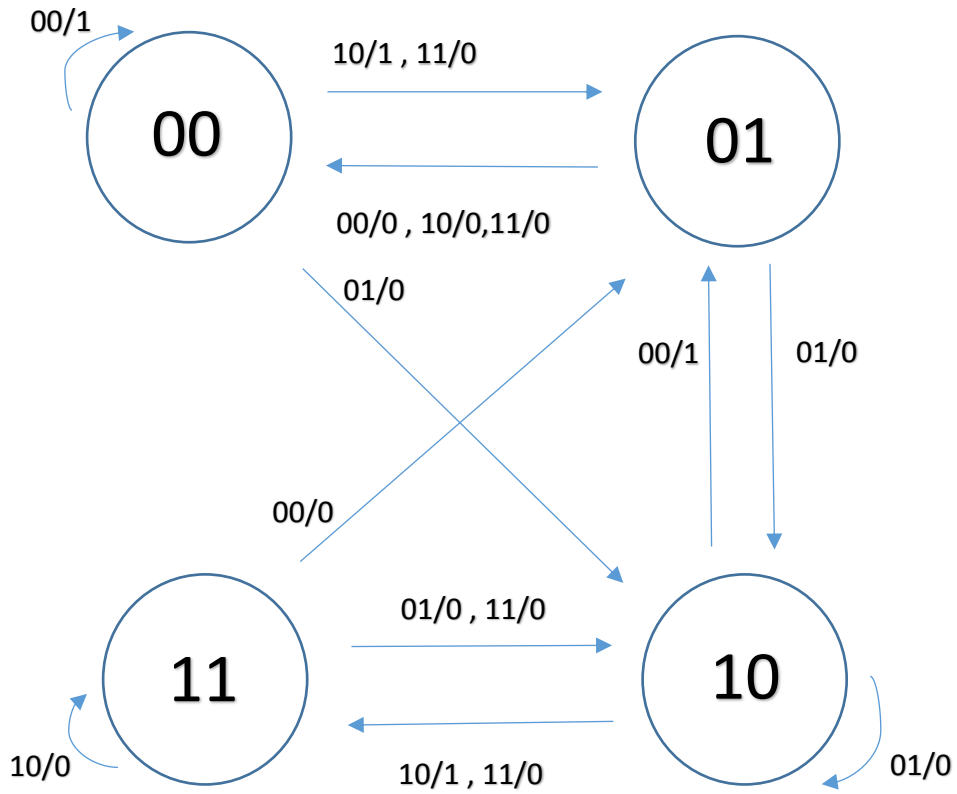

2.


Present state		Input	Next state	
A	B	x	A+1	B+1
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

D_A		AB			
	X	00	01	11	10
0		1			1
1				1	1


$$D_A = B'X' + AX$$

D_B		AB			
	X	00	01	11	10
0				1	1
1			1	1	

$$D_B = AX' + BX$$

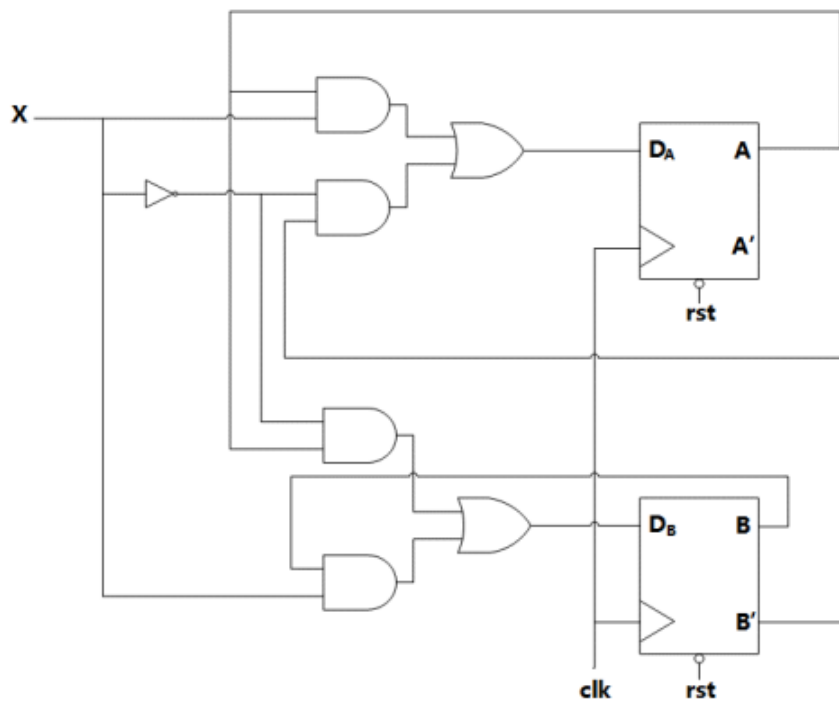

3.

 

4.

00 → 1000 01 → 0100 10 → 0010 11 → 0001

Present state				Input	Next state				Output
A	B	C	D	x	A+1	B+1	C+1	D+1	Y
1	0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0	1
0	1	0	0	0	0	1	0	0	0
0	1	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0
0	0	1	0	1	0	0	1	0	0
0	0	0	1	0	0	0	0	1	0
0	0	0	1	1	1	0	0	0	0

AB \ CD	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$X=0$

AB \ CD	00	01	11	10
00	x	0	x	1
01	1	x	x	x
11	x	x	x	x
10	0	x	x	x

$X=1$

$$D_A = B'C'X$$

AB \ CD	00	01	11	10
00	x	1	x	1
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$X=0$

AB \ CD	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$X=1$

$$D_B = C'D'X'$$

AB \ CD	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$X=0$

AB \ CD	00	01	11	10
00	x	1	x	0
01	0	x	x	x
11	x	x	x	x
10	1	x	x	x

$X=1$

$$D_C = A'D'X'$$

AB \ CD	00	01	11	10
00	x	0	x	0
01	1	x	x	x
11	x	x	x	x
10	1	x	x	x

$X=0$

AB \ CD	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x


$X=1$

$$D_D = A'B'X'$$


AB \ CD	00	01	11	10
00	x	0	x	1
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

AB \ CD	00	01	11	10
00	x	0	x	1
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$$Y = A$$

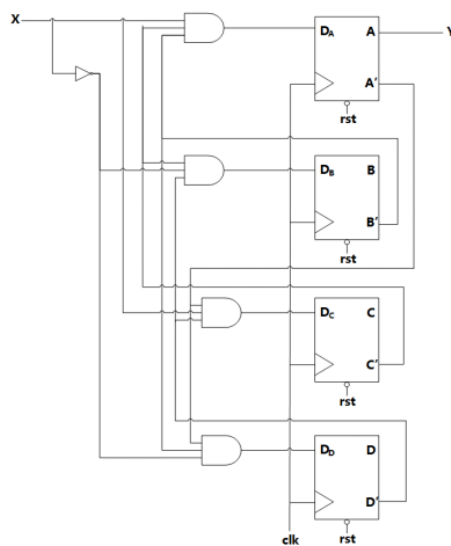


5.

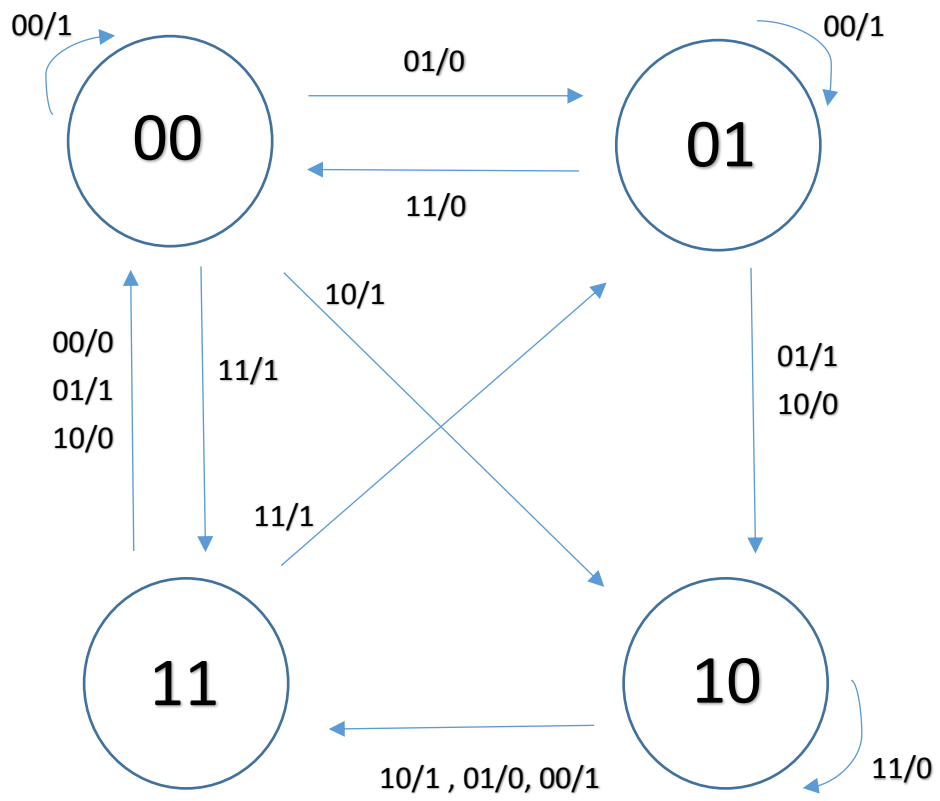


6.
(a)

Case1: 連續的 1

 

Case2: 不連續的 1

 

(b)

Case1


Present state		Input	Next state		output
A	B	x	A+1	B+1	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	x	x	1

Case2


Present state		Input	Next state		output
A	B	x	A+1	B+1	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

(c)

Case1

 

Case2

 

7.

```
module Hw7_7 (DA, DB, A, B, x);  
output DA, DB;  
input A, B, x;  
assign DA = ((~B) & (~x)) | (A & x);  
assign DB = (A & (~x)) | (B & x);  
endmodule
```

.v檔

```
module test_Hw7_7;  
wire DA, DB;  
reg A, B, x;  
  
Hw7_7 U0 (.DA (DA), .DB (DB), .A (A), .B (B), .x (x));  
initial  
begin  
    A=0; B=0; x=0;  
    #10 A=0; B=0; x=1;  
    #10 A=0; B=1; x=0;  
    #10 A=0; B=1; x=1;  
    #10 A=1; B=0; x=0;  
    #10 A=1; B=0; x=1;  
    #10 A=1; B=1; x=0;  
    #10 A=1; B=1; x=1;  
end  
endmodule
```

testbench檔

8.

Reduced state table

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
a	f	b	0	0
b	d	b	1	0
d	d	a	1	0
f	f	b	1	1
h	d	a	0	0

Original table

state	a	b	d	a	b	d	a	f	b	d	g
Input	1	0	1	1	0	1	0	1	0	0	1
Output	0	1	0	0	1	0	0	1	1	1	0

Reduced table

state	a	b	d	a	b	d	a	f	b	d	d
Input	1	0	1	1	0	1	0	1	0	0	1
Output	0	1	0	0	1	0	0	1	1	1	0