

2016 Logic Design HW8

8.1

Shift 1: 01011

Shift 2: 10110


Shift 3: 01101

Shift 4: 11010


Shift 5: 10101


8.2

2.

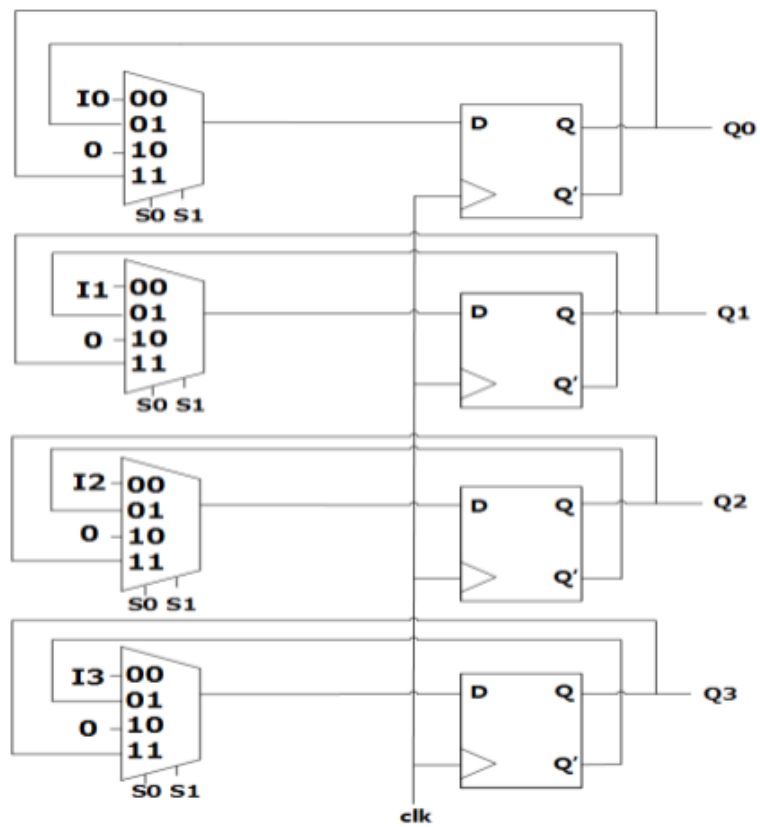

8.3

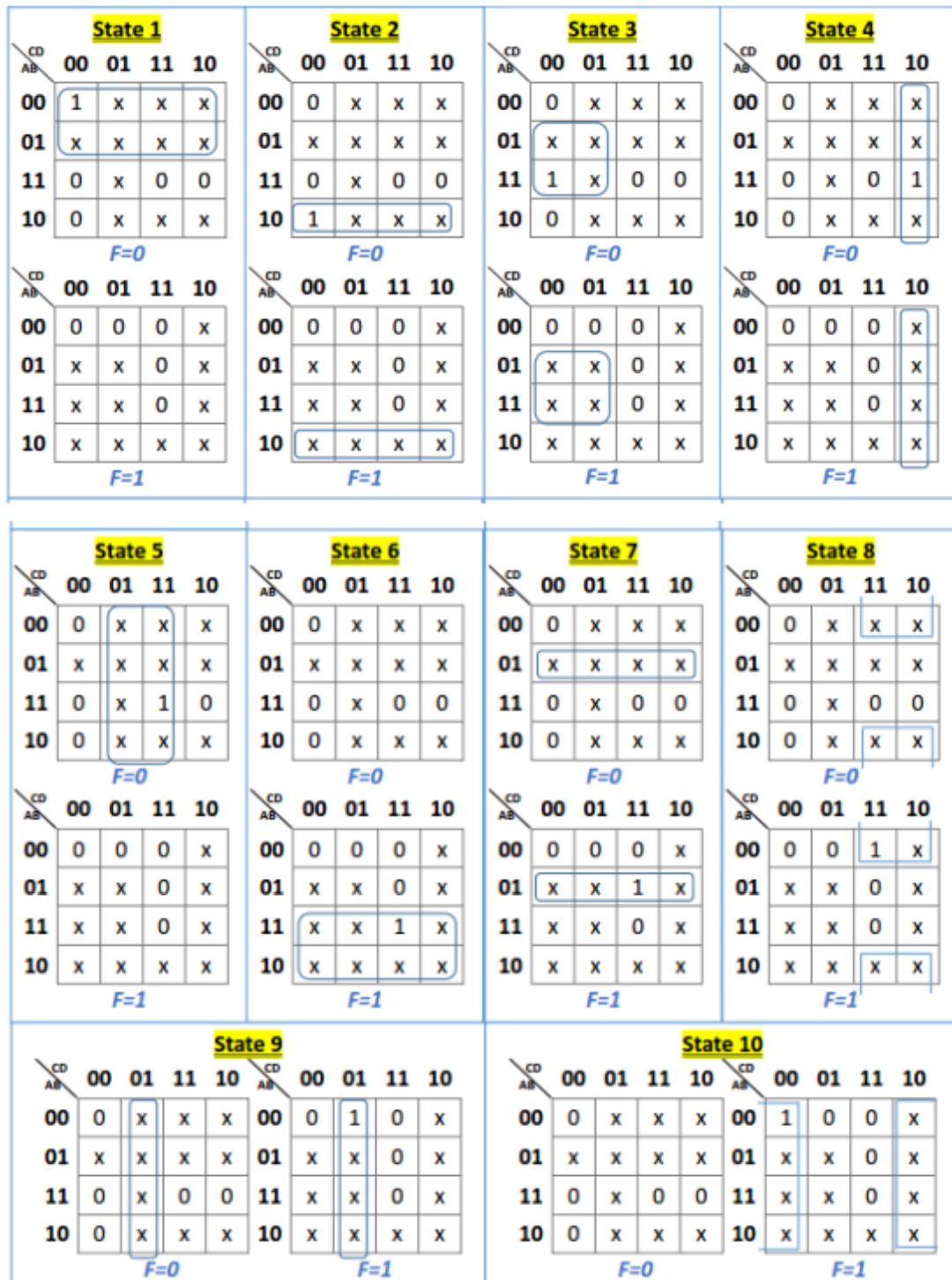

 

Sequence Number	A	B	C	D	F	AND gate for output
1	0	0	0	0	0	$A'F'$
2	1	0	0	0	0	AB'
3	1	1	0	0	0	BC'
4	1	1	1	0	0	CD'
5	1	1	1	1	0	DF'
6	1	1	1	1	1	AF
7	0	1	1	1	1	$A'B$
8	0	0	1	1	1	$B'C$
9	0	0	0	1	1	$C'D$
10	0	0	0	0	1	$D'F$

8.4

(a)1,4,7

A	B	C	D_A	D_B	D_C
0	0	0	X	X	X
0	0	1	1	0	0
0	1	0	X	X	X
0	1	1	X	X	X
1	0	0	1	1	1
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	0	0	1

D_A :

A \ BC	00	01	11	10
0	X	1	X	X
1	1	X	0	X

$D_A=B'$

D_B :


A \ BC	00	01	11	10
0	X	0	X	X
1	1	X	0	X

$D_B=C'$

D_C :

A \ BC	00	01	11	10
0	X	0	X	X
1	1	X	1	X

$D_C=A$

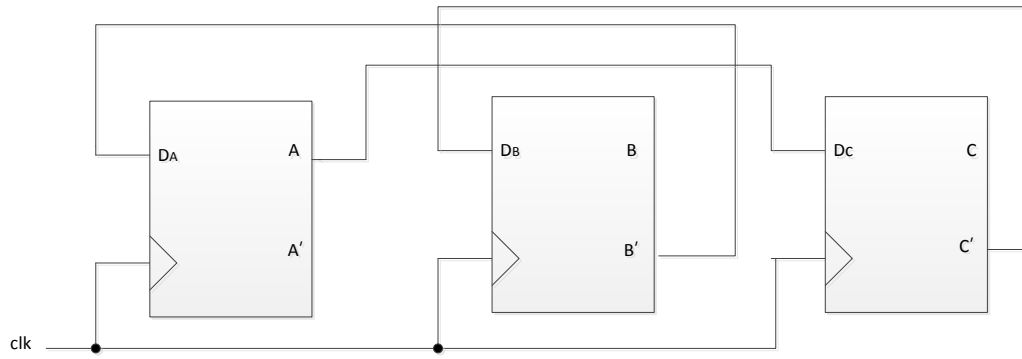

(b) 0,2,4,6,7

A	B	C	DA	DB	DC
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	1	0	0
0	1	1	X	X	X
1	0	0	1	1	0
1	0	1	X	X	X
1	1	0	1	1	1
1	1	1	0	0	0

DA:

A \ BC	00	01	11	10
0	0	X	X	1
1	1	X	0	1

$$D_A = BC' + AC'$$

D_B:


A \ BC	00	01	11	10
0	1	X	X	0
1	1	X	0	1

$$D_B = B' + AC'$$

D_C:


A \ BC	00	01	11	10
0	0	X	X	0
1	0	X	0	1

$$D_C = ABC'$$

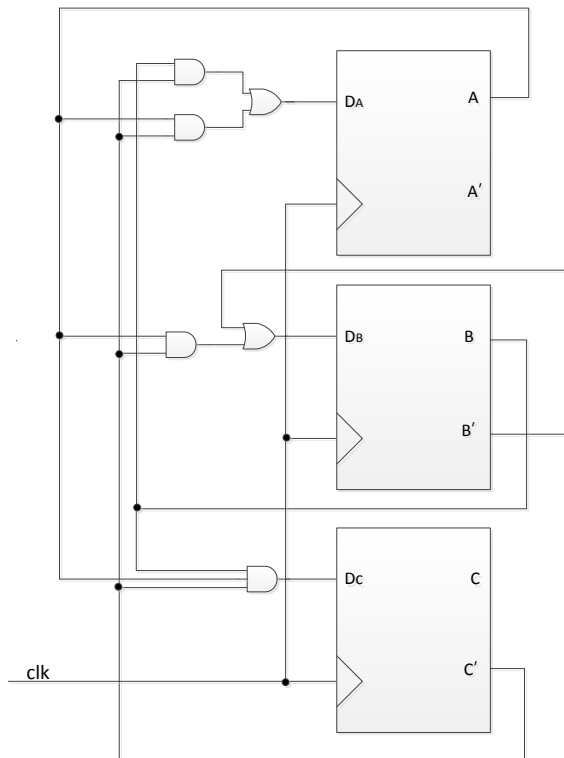

8.5


Solution 1 (鎖在 1101):

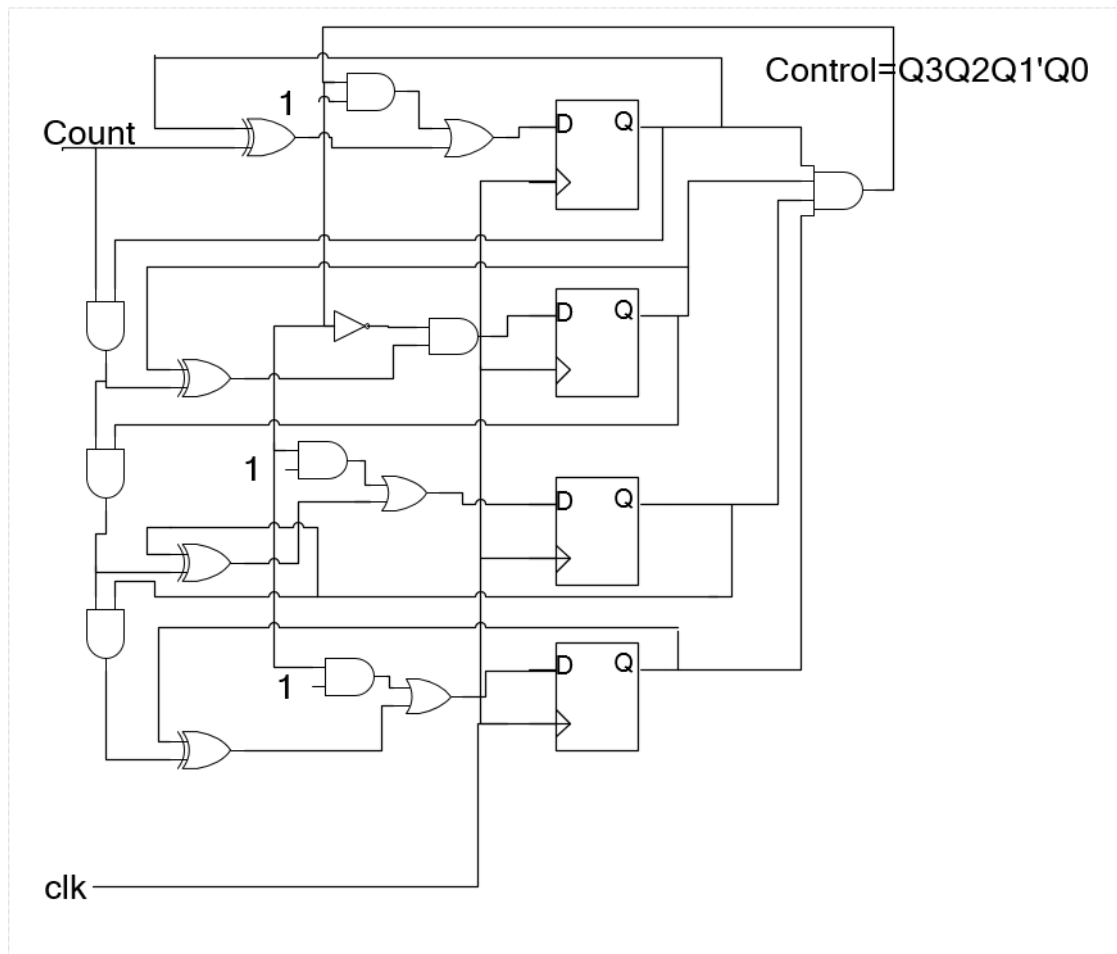


Q3	Q2	Q1	Q0	D3	D2	D1	D0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1

Solution 2 (1101 後重新數):


Q_A	Q_B	Q_C	Q_D	D_A	D_B	D_C	D_D
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	1
1	1	0	1	0	0	0	0

 

 
$$D_A = Q_A Q_B' + Q_A Q_D' + Q_B Q_C Q_D$$



 
$$D_B = Q_B Q_D' + Q_A' Q_B Q_C' + Q_B' Q_C Q_D$$


 
$$D_C = Q_C Q_D' + Q_A' Q_C' Q_D + Q_B' Q_C' Q_D$$




$$D_D = Q_D'$$

 

8.6


(1)

 

(2)


方法 1.

說明: 前半段累加器, 每個周期加一, 加到 4(0100)後, XOR gate 的輸出會為零。此時第一個 MUX 選擇 0 而不是加法器的輸出。形成 0000、0001、0010、0011、0100、0000、0001...循環。第二個多功器則會每五個週期反向一次, 形成 1/10 的除頻器。

 


方法 2.


Q _A	Q _B	Q _C	Q _D	D _A	D _B	D _C	D _D	Out
0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	1	0
0	0	1	1	0	1	0	0	0
0	1	0	0	0	1	0	1	0
0	1	0	1	0	1	1	0	1
0	1	1	0	0	1	1	1	1
0	1	1	1	1	0	0	0	1
1	0	0	0	1	0	0	1	1
1	0	0	1	0	0	0	0	1

 


$$D_A = Q_A Q_D' + Q_B Q_C Q_D$$

 

 
$$D_B = Q_B Q_D' + Q_B Q_C' + Q_B' Q_C Q_D$$




$$D_C = Q_C Q_D' + Q_A' Q_C' Q_D$$

 

$$D_D = Q_D'$$

 


$$D_E = Q_A + Q_B Q_C + Q_B Q_D$$

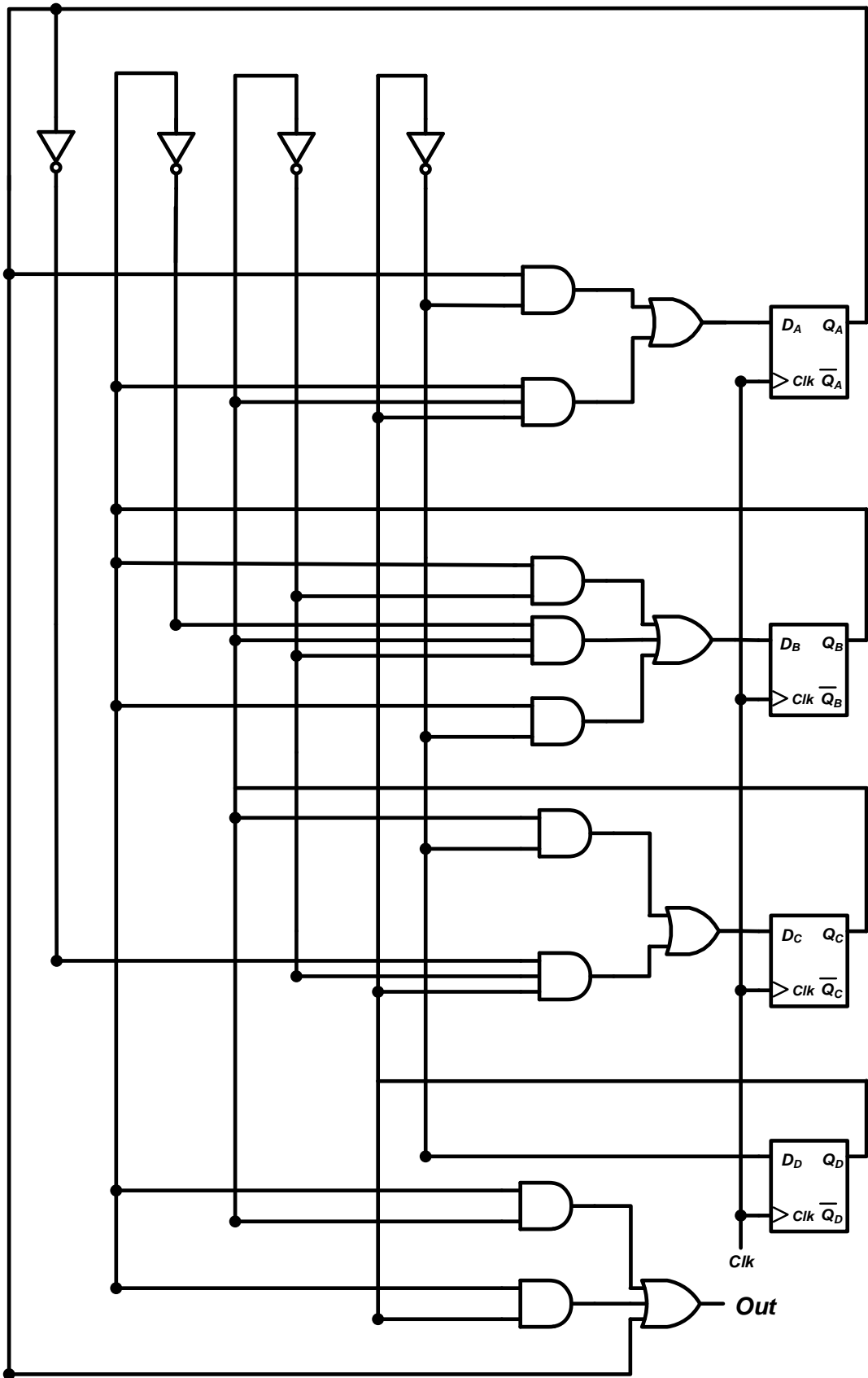


8.7

(a)

 

(b)

 

8.8

8,(a)

Shift	State
0	1000
1	0100
2	0010
3	0001
4	1000

8(b)

Shift	State
0	10.....0
1	010.....0
2	0010....0
⋮	⋮
n-1	00.....1

∴ n states