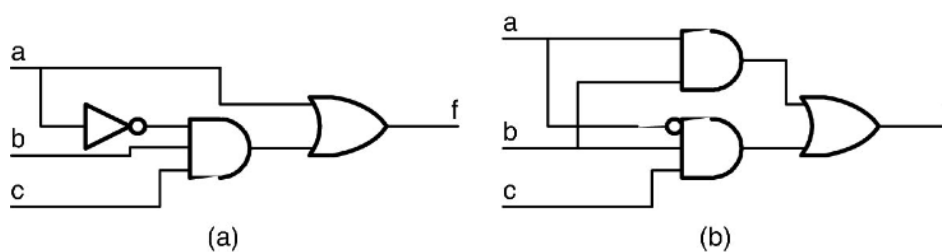


## HW4

---

1. Majority Indicator: Design a voting machine for three people. When there is more than one person agree on some case (with input 1), the case will be passed (with output 1); otherwise, the case will be rejected (with output 0). (10%)
  - (a) Derive the truth table.
  - (b) Derive the simplified Boolean expressions for A, B, and C using maps in sum-of-products and product-of-sum forms, respectively.
  - (c) Draw the related logic diagram.

2. Fix the hazard that may occur in the following figures: (10%)



3. Design a combinational circuit with three inputs, x (MSB), y, and z (LSB), and three outputs, A (MSB), B, and C (LSB). When the binary input is 0, 1, or 2, the binary output is three greater than the input ( $xyz=001(1) \Rightarrow ABC=100(4)$ ,  $xyz=010(2) \Rightarrow ABC=101(5)$ ). When the binary input is 3, 4, 5, 6, or 7, the binary is two less than the input ( $xyz=110(6) \Rightarrow ABC=100(4)$ ,  $xyz=100(4) \Rightarrow ABC=010(2)$ ). (10%)
  - (a) Derive the truth table.
  - (b) Derive the simplified Boolean expressions for A, B, and C using maps.
  - (c) Draw the related logic diagram.
4. Design an excess-3-to-binary decoder using the unused combinations of the code as don't-care conditions. (10%)
5. Simplify the following Boolean expressions to a minimum number of literals, and implement with two-level NAND-NAND and NOR-NOR gates, respectively. (10%)
  - (a)  $xy'z + xy'z' + xyz'$ ,
  - (b)  $(y'z + xw')(xw + y'z)$ .

6. Simplify the following expression. Do not use k-map but use cube method. (10%)

$$F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

7. A half adder is a circuit that takes in one-bit binary numbers  $a$  and  $b$ , and outputs a sum  $s$  and a carry out  $co$ . The concatenation of  $co$  and  $s$ , is the two-bit value that results from adding  $a$  and  $b$  (e.g. if  $a=1, b=1, s=0$ , and  $co=1$ ). (10%)
- Derive the truth table of a half adder.
  - Derive the Boolean expression of  $co$  and  $s$  in the simplest sum-of-product form.
  - Find the prime implicants and essential prime implicants of  $co$  and  $s$ .
8. Use Verilog to simulate the half adder in problem 7. (10%)
9. Use Verilog to simulate the majority detector in problem 1. (10%)
10. Which of the following circuits are combinational? Each box in the figure is itself a combinational circuits. (10%)

