

HW5

1. Design a three-way magnitude comparator that outputs true if its three inputs are in strict order: $a > b > c$.
2. Design an arbiter with programmable priority – a binary input selects which bit is highest priority. The priority rotates rightward from that bit position. The input/output bit number of the arbiter is 4.
3. Design an 8- \rightarrow 1 multiplexer using a 3- \rightarrow 8 decoder and 8x2 AND-OR (eight 2-input AND-OR logic).
4. Draw the logic diagram of a 3- \rightarrow 8 decoder using only NOR and NOT gates.
5. Design a 4- \rightarrow 2 priority encoder with input $D[3:0]$ and output $A[1:0]$ where D_0 has the highest priority and D_3 has the lowest priority.