

HW2

1. Convert F and G to the other canonical form and standard forms of sum of products and product of sums. (10%)
 $F(a, b, c) = \sum(0,1,3,4,7)$
 $G(w, x, y, z) = \prod(1,3,5,8,9,11,13,15)$
2. Simplify the following Boolean expressions (do not use K-map) to a minimum number of literals as less as possible. After simplification, draw the logic diagrams of the circuits that implement the original and simplified expressions, respectively. (10%)
 - (a) $(x+y'z')(w+xy')$,
 - (b) $w'x'y+wyz+wx'z'+x'yz$.
3. Use DeMorgan's theorem to remove the complement outside the braces. (12%)
 - (a) $((x+w')'+w'y'z+(x+z)'(x+y))'$,
 - (b) $(x(yz'+y'z)'+wy(y'+x'z))'$,
 - (c) $(x+y)'+z'(x'+z)'$,
 - (d) $(xy'+z)'(w+y'z)$.
4. Reformulate the function $F=x'+x(x'+y)(y'+z)$ using (15%)
 - (a) AND, OR, and inverter (NOT) gates,
 - (b) AND and inverter (NOT) gates,
 - (c) OR and inverter (NOT) gates.
5. For the function $F(w, x, y, z) = \prod(2,3,4,5,6,7,9,11,14)$
 - (a) Obtain its truth table, (3%)
 - (b) Express F in sum-of-minterms and product-of-maxterms forms, (6%)
 - (c) Draw the logic diagram of F, (5%)
 - (d) Use Boolean algebra to simplify the function F to a new function G, with minimum number of literals, (5%)
 - (e) Obtain the truth table of G and compare it with that of F, (5%)
 - (f) Draw the logic diagram of G and compare the number of literals of F and G. (5%)
6. For the Gray code sequence of 16 code words $(g_3g_2g_1g_0)$, use a 4-bit binary code $(b_3b_2b_1b_0)$ as inputs
 - (a) Derive the related truth table, (6%)
 - (b) Find the logic functions for each g_i . (8%)
7. Write the Boolean functions with one canonical form (f_1 and f_2) and draw the logic diagrams of the circuit whose outputs are defined by the truth table. (10%)

a	b	c	f ₁	f ₂
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0

1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1