

1. (30%) Design a 4-bit two parameter comparator (input A and B, A:a₃a₂a₁a₀, B:b₃b₂b₁b₀ are both in 2's complement representation) and output the smaller one S(s₃s₂s₁s₀).

(賴聖耘)

先用 comparator，當(A<B)時，輸出 1，若是(A>=B)，則輸出 0。

再使用 MUX，以 comparator 的輸出作為 select，

當 select==1(A<B)時，輸出 A₃A₂A₁A₀，

當 select==0(A>=B)時，輸出 B₃B₂B₁B₀。

By algorithm to build a regular circuit


$$A = A_3A_2A_1A_0, B = B_3B_2B_1B_0$$

因為是 2's-complement，MSB 為 0 代表正數，MSB 為 1 代表負數，且因為規定是 A,B 都是 4-bit，所以 MSB 也會因 sign extension 而補上 1 或是 0。在判斷大小時，就可以使用 A₃B₃'，其他位置則是使用課本上的 bit equality。


$$\text{equality } x_i = A_i B_i + A_i' B_i'$$

$$(A < B) = A_3 B_3' + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$


Block diagram:

 

4-bit comparator logic diagram:

 

4-bit 2:1 MUX logic diagram:

 

MUX function table:

E(enable)	A<B(select)	Output
0	0	Select B
0	1	Select A


2. (10%) Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder.

陳冠霖

inputs: A0 to A4

outputs: D0 to D31

 Since we have four 3-to-8-lines decoders with enable, we may consider deriving enable signals from part of our inputs; with the 2-to-4-line decoder, we obtain E0 to E3 and use them as enable signals to the four 3-to-8-line decoders.



Visual Paradigm Online Free Edition