


1. (20%) A sequential circuit with two *D* flip-flops A and B, two inputs *x* and *y*, and one output *z* is specified by the following next state equations and output equation:

$$A(t+1)=x'B(t)+xy', B(t+1)=A'(t)+y'B(t), z=yA'B$$

(林致佑)

- (a) Draw the logic diagram of the circuit.
 (b) Derive the state table.
 (c) Derive the state diagram.


(a) logic diagram:

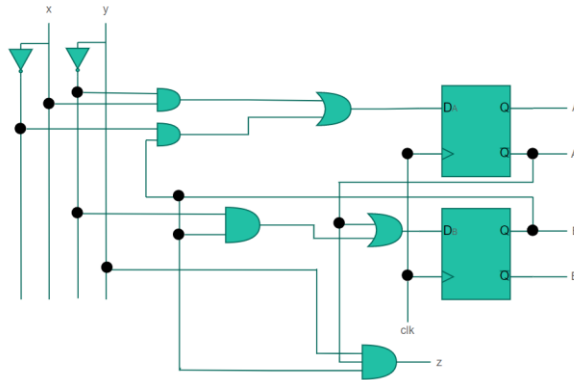

(b) state table:

A(t)	B(t)	x	y	A(t+1)	B(t+1)	z
0	0	0	0	0	1	0
0	0	0	1	0	1	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	0
0	1	0	1	1	1	1
0	1	1	0	1	1	0
0	1	1	1	0	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	0	1	1	0	0	0
1	1	0	0	1	1	0
1	1	0	1	1	0	0
1	1	1	0	1	1	0
1	1	1	1	0	0	0

(c) state diagram:

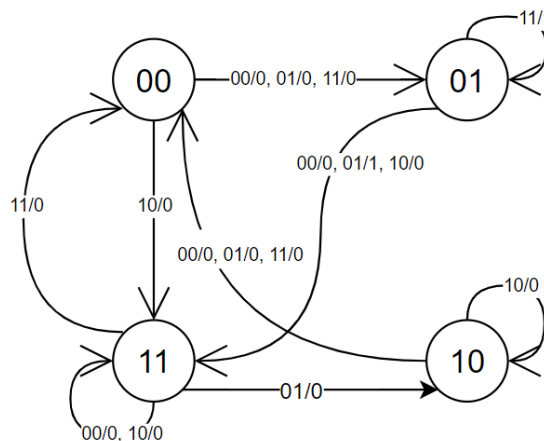


2. (20%) Design a synchronous finite state machine whose output is the sequence 0, 1, 3, 5, 7, 9, 0, 1, 3, 5, 7, 9, 0, The machine is controlled by a single input, *Run*, so that counting occurs while *Run* is 1, suspends while *Run* is 0, and resumes the count when *Run* is 1 again. Clearly state any assumptions that you make.

(陳冠霖)

Follow the design procedure:

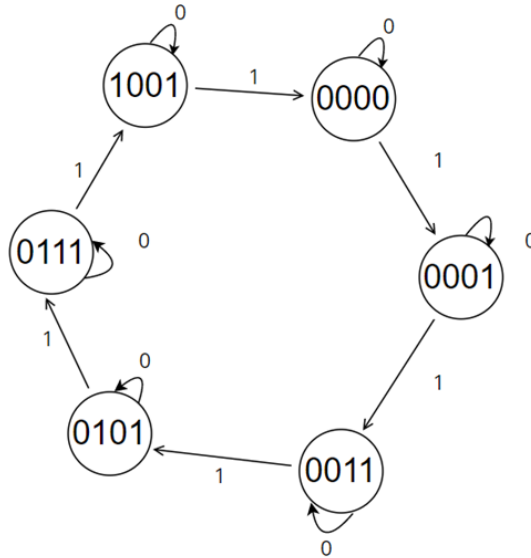- 1) Only one input Run; we may try to use the states to be the outputs (A3A2A1A0).
- 2) Determine the states. The states are the outputs.



3) 4) 5) Derive the next state table

	Input	Present state				Next State			
	Run	A3(t)	A2(t)	A1(t)	A0(t)	A3(t+1)	A2(t+1)	A1(t+1)	A0(t+1)
0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	1
2	0	0	0	1	0	x	x	x	x
3	0	0	0	1	1	0	0	1	1
4	0	0	1	0	0	x	x	x	x
5	0	0	1	0	1	0	1	0	1
6	0	0	1	1	0	x	x	x	x
7	0	0	1	1	1	0	1	1	1
8	0	1	0	0	0	x	x	x	x
9	0	1	0	0	1	1	0	0	1
10	0	1	0	1	0	x	x	x	x
11	0	1	0	1	1	x	x	x	x
12	0	1	1	0	0	x	x	x	x

13	0	1	1	0	1	x	x	x	x
14	0	1	1	1	0	x	x	x	x
15	0	1	1	1	1	x	x	x	x
16	1	0	0	0	0	0	0	0	1
17	1	0	0	0	1	0	0	1	1
18	1	0	0	1	0	x	x	x	x
19	1	0	0	1	1	0	1	0	1
20	1	0	1	0	0	x	x	x	x
21	1	0	1	0	1	0	1	1	1
22	1	0	1	1	0	x	x	x	x
23	1	0	1	1	1	1	0	0	1
24	1	1	0	0	0	x	x	x	x
25	1	1	0	0	1	0	0	0	0
26	1	1	0	1	0	x	x	x	x
27	1	1	0	1	1	x	x	x	x
28	1	1	1	0	0	x	x	x	x
29	1	1	1	0	1	x	x	x	x
30	1	1	1	1	0	x	x	x	x
31	1	1	1	1	1	x	x	x	x

6)

$$A3(t + 1) = D_{A3}(Run, A3(t), A2(t), A1(t), A0(t)) = \sum(9,23)$$

$$A2(t + 1) = D_{A2}(Run, A3(t), A2(t), A1(t), A0(t)) = \sum(5,7,19,21)$$

$$A1(t + 1) = D_{A1}(Run, A3(t), A2(t), A1(t), A0(t)) = \sum(3,7,17,21)$$

$$A0(t + 1) = D_{A0}(Run, A3(t), A2(t), A1(t), A0(t)) = \sum(1,3,5,7,9,16,17,19,21,23)$$

All equations at above have the same don't-care condition,

$$d = \sum(2, 4, 6, 8, 10 \sim 15, 18, 20, 22, 24, 26 \sim 31).$$

7) Choose D FFs (default).

8)

For D_{A_3}

		Run'				Run								
		A1A0	00	01	11	10	00	01	11	10				
A3A2	00	0	1	3	2	X	16	17	19	18	X			
	01	4	X	5	7	6	X	20	21	23	22	X		
	11	12	X	13	X	15	X	14	X	31	X	30	X	
	10	8	X	9	1	11	X	10	X	24	25	27	X	26

$$D_{A_3} = \text{Run}(A_2A_1) + \text{Run}'(A_3)$$

For D_{A_2}

		Run'				Run								
		A1A0	00	01	11	10	00	01	11	10				
A3A2	00	0	1	3	2	X	16	17	19	18	X			
	01	4	X	5	7	6	X	20	21	23	22	X		
	11	12	X	13	X	15	X	14	X	31	X	30	X	
	10	8	X	9	1	11	X	10	X	24	25	27	X	26

$$D_{A_2} = \text{Run}(A_2'A_1) + \text{Run}'(A_2) + A_2A_1'$$

For D_{A1}

		Run'				Run			
		00	01	11	10	00	01	11	10
A3A2	00	0	1	3	2	16	17	19	18
	01 <td>4</td> <td>5</td> <td>7</td> <td>6</td> <td>20</td> <td>21</td> <td>23</td> <td>22</td>	4	5	7	6	20	21	23	22
	11 <td>12</td> <td>13</td> <td>15</td> <td>14</td> <td>28</td> <td>29</td> <td>31</td> <td>30</td>	12	13	15	14	28	29	31	30
	10 <td>8</td> <td>9</td> <td>11</td> <td>10</td> <td>24</td> <td>25</td> <td>27</td> <td>26</td>	8	9	11	10	24	25	27	26
			1	X		1		X	
	X		1	X	X	1		X	
	X	X	X	X	X	X	X	X	
	X		X	X	X		X	X	


$$D_{A1} = \text{Run}(A3'A1'A0) + \text{Run}'(A1)$$

For D_{A0}

		Run'				Run			
		00	01	11	10	00	01	11	10
A3A2	00	0	1	3	2	16	17	19	18
	01 <td>4</td> <td>5</td> <td>7</td> <td>6</td> <td>20</td> <td>21</td> <td>23</td> <td>22</td>	4	5	7	6	20	21	23	22
	11 <td>12</td> <td>13</td> <td>15</td> <td>14</td> <td>28</td> <td>29</td> <td>31</td> <td>30</td>	12	13	15	14	28	29	31	30
	10 <td>8</td> <td>9</td> <td>11</td> <td>10</td> <td>24</td> <td>25</td> <td>27</td> <td>26</td>	8	9	11	10	24	25	27	26
		1	1	X		1	1	X	
	X	1	1	X	X	1	1	X	
	X	X	X	X	X	X	X	X	
	X	1	X	X	X		X	X	

$$D_{A0} = \text{Run}(A3') + \text{Run}'(A0)$$

9)

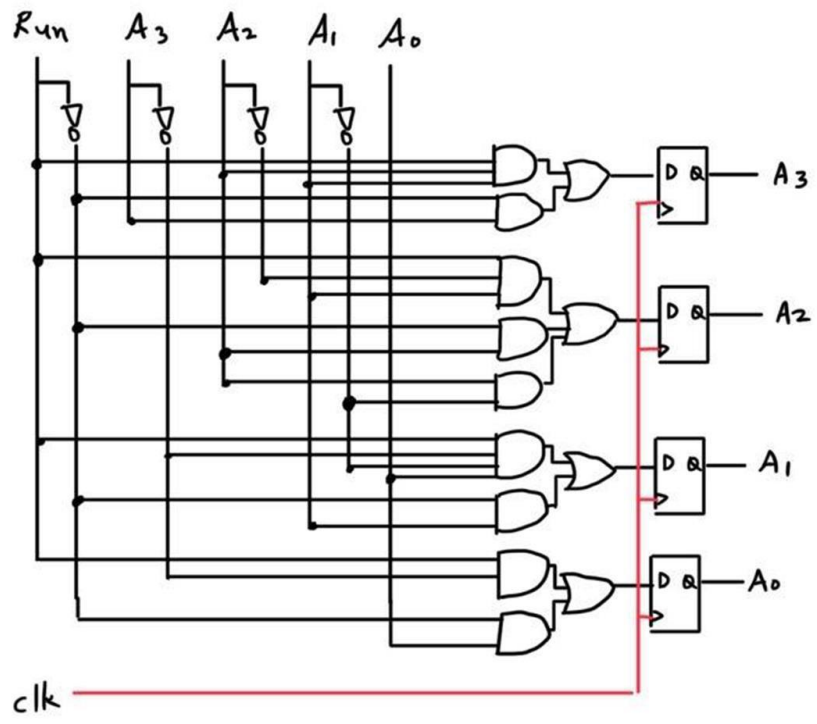

3. (20%) For the state table below:

- (a) Reduce the number of states in the following state table and tabulate the reduced state table. Assume the initial state is A.
- (b) Draw the state diagram using the reduced state table.
- (c) Draw the logic diagram of the logic.
- (d) Show the output sequence when the input sequence is 111010101.


(呂易縉)

Present state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
A	F	B	0	0
B	D	E	1	0
C	F	E	0	0
D	G	A	1	0
E	D	E	1	0
F	F	B	1	1
G	G	A	1	0
H	G	C	0	0

(a)

Present state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
A	F	B	0	0
B	D	B	1	0
C	F	E	0	0
D	D	A	1	0
E	D	E	1	0
F	F	B	1	1
G	G	A	1	0
H	G	C	0	0

(b)

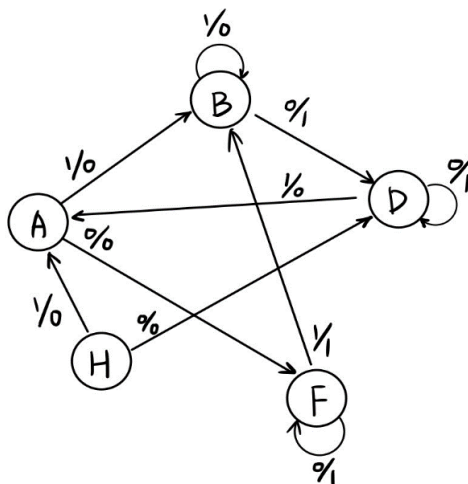

(c)

Present State				Input	Next State				Output
	A(t)	B(t)	C(t)	x		A(t+1)	B(t+1)	C(t+1)	y
A	0	0	0	0	F	0	1	1	0
	0	0	0	1	B	0	0	1	0
B	0	0	1	0	D	0	1	0	1
	0	0	1	1	B	0	0	1	0
D	0	1	0	0	D	0	1	0	1
	0	1	0	1	A	0	0	0	0
F	0	1	1	0	F	0	1	1	1
	0	1	1	1	B	0	0	1	1
H	1	0	0	0	D	0	1	0	0
	1	0	0	1	A	0	0	0	0




Next state equations


$$B(t+1) = D_B(A(t), B(t), C(t), x) = \Sigma(0,2,4,6,8) , d = \Sigma(10,11,12,13,14,15)$$

$$C(t+1) = D_C(A(t), B(t), C(t), x) = \Sigma(0,1,3,6,7) , d = \Sigma(10,11,12,13,14,15)$$

Output equation
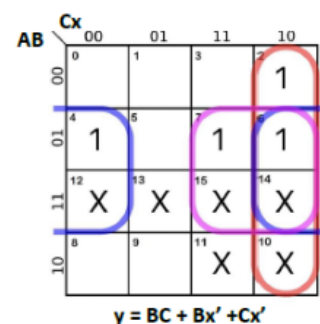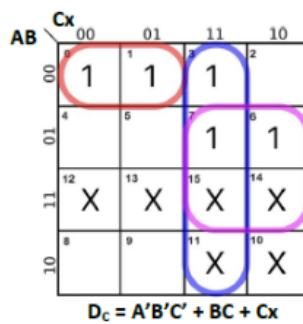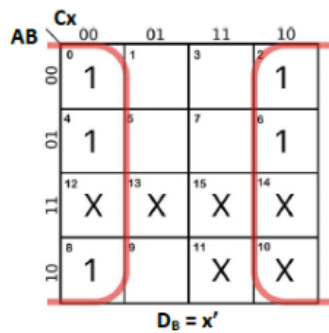
$$y(A(t), B(t), C(t), x) = \Sigma(2,4,6,7) , d = \Sigma(10,11,12,13,14,15)$$



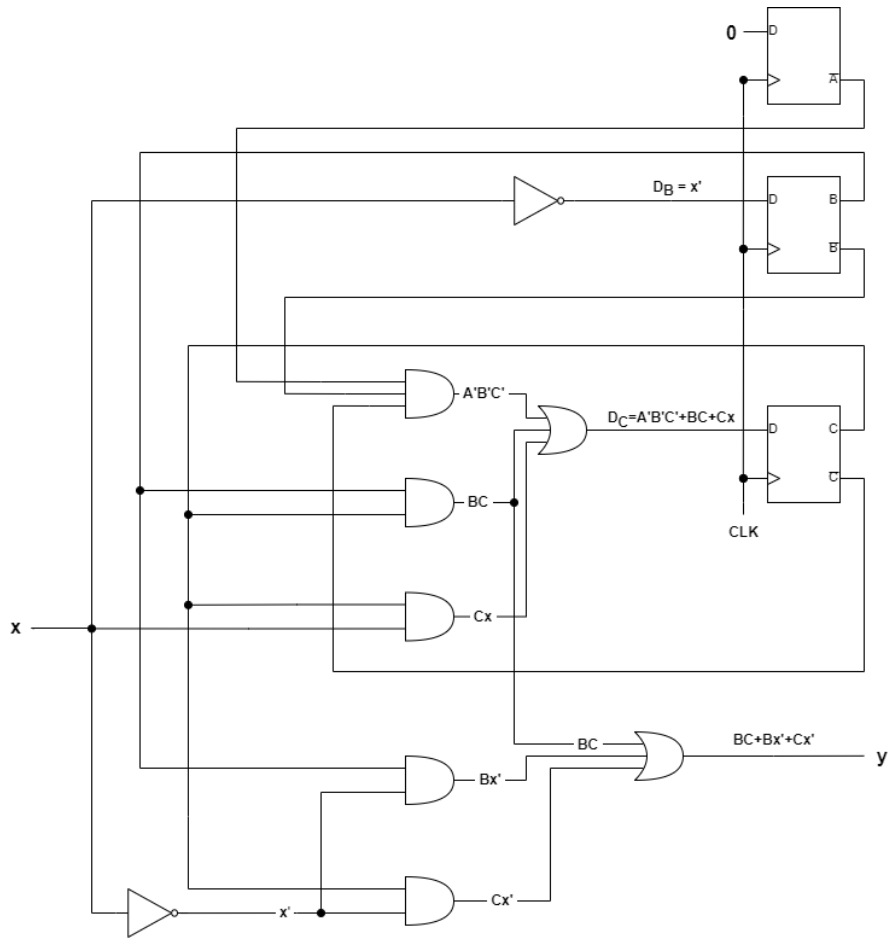

(d)

Input : 111010101


Initial State : A

State : A \rightarrow B \rightarrow B \rightarrow B \rightarrow D \rightarrow A \rightarrow F \rightarrow B \rightarrow D \rightarrow A

Output : 000100110

4. (20%) Derive the timing diagram of the following circuit. Draw Q_3 , Q_2 , Q_1 , and Q_0 .


(林彦岑)

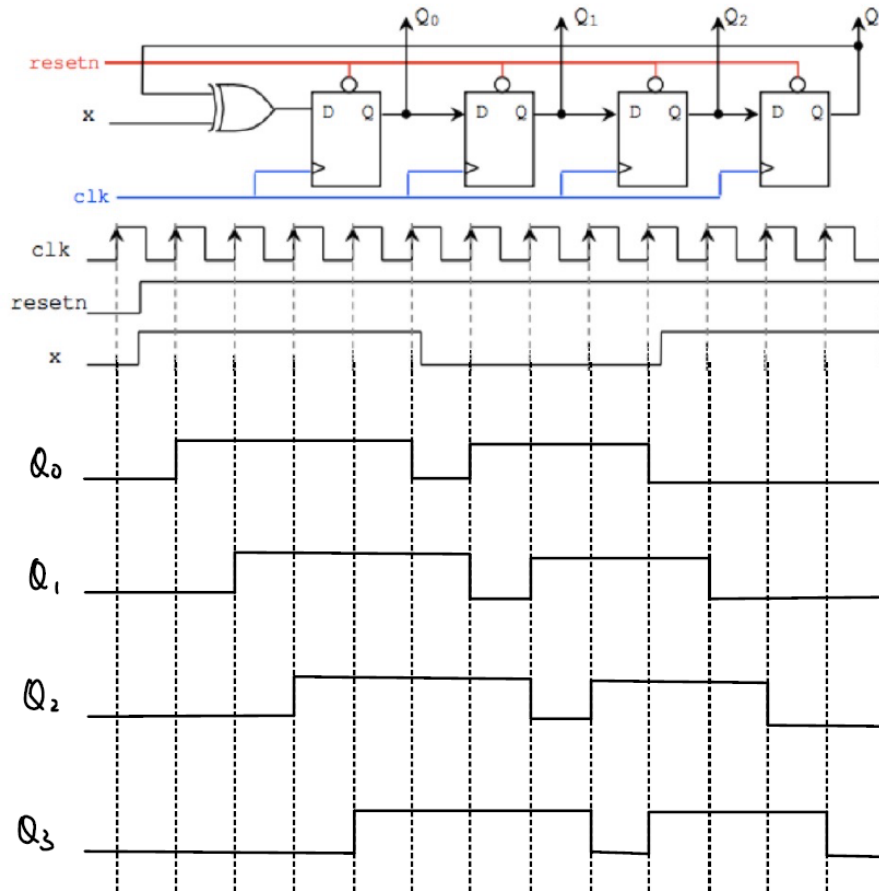

5. (20%) Design a sequential circuit with two D flip-flops A and B and two inputs X and Y . When $X = Y$, the state of the circuit remains the same. When $X \neq Y$, the circuit goes through the state transitions from 00 to 11 to 01 to 10, back to 00, and then repeats.

(徐浩庭)

State diagram

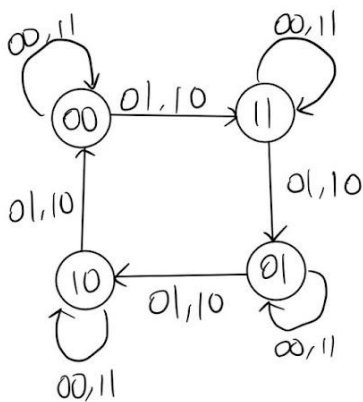

State table

Present state		Next State	
A	B	$X=Y$ (00 or 11)	$X \neq Y$ (01 or 10)
0	0	00	11
1	1	11	01
0	1	01	10
1	0	10	00

Truth table

A(t)	B(t)	X	Y	A(t+1)	B(t+1)
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	1

A(t+1)

AB ^{XY}	00	01	11	10
00		1		1
01		1		1
11	1		1	
10	1		1	

$$D_A = AX'Y' + AX'Y + AX + A'XY'$$

B(t+1)

AB ^{XY}	00	01	11	10
00		/		/
01	1		1	
11	1		1	
10				

$$D_B = BX'Y' + BXY + AB + A'BX'Y + A'BX'Y'$$

Logic Diagram

