

1 呂依凡

(a)

index	input				computing process	output			
	x	y	z	w		A	B	C	D
0	0	0	0	0	0000 + 0011	0	0	1	1
1	0	0	0	1	0001 + 0011	0	1	0	0
2	0	0	1	0	0010 + 0011	0	1	0	1
3	0	0	1	1	0011 + 0011	0	1	1	0
4	0	1	0	0	0100 + 0011	0	1	1	1
5	0	1	0	1	1 equals to input	0	1	0	1
6	0	1	1	0	0 equals to input	0	1	1	0
7	0	1	1	1	1 equals to input	0	1	1	1
8	1	0	0	0	0 equals to input	1	0	0	0
9	1	0	0	1	1 equals to input	1	0	0	1
10	1	0	1	0	0 equals to input	1	0	1	0
11	1	0	1	1	1011 - 0101 = 1011 + 1010 + 1	0	1	1	0
12	1	1	0	0	1100 - 0101 = 1100 + 1010 + 1	0	1	1	1
13	1	1	0	1	1101 - 0101 = 1101 + 1010 + 1	1	0	0	0
14	1	1	1	0	1110 - 0101 = 1110 + 1010 + 1	1	0	0	1
15	1	1	1	1	1111 - 0101 = 1111 + 1010 + 1	1	0	1	0

(b)

A	$\Sigma(8,9,10,13,14,15)$			
xy \ zw	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$\Rightarrow A = xy'w' + xz'w + xy z$

B	$\Sigma(1, 2, 3, 4, 5, 6, 7, 11, 12)$			
xy \ zw	00	01	11	10
00		1	1	1
01	1	1	1	1
11	1			
10			1	

$\Rightarrow B = x'w + x'z + y'zw + yz'w'$



C	$\Sigma(0, 3, 4, 6, 7, 10, 11, 12, 15)$			
xy \ zw	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1		1	1
10			1	1



$\Rightarrow C = zw + x'z'w' + x'y'z + yz'w'$

D	$\Sigma(0, 2, 4, 5, 7, 9, 12, 14)$				
	$xy \backslash zw$	00	01	11	10
	00	1			1
	01	1	1	1	
	11	1			1
	10		1		


$\Rightarrow D = x'yz' + x'y'w' + x'yzw + xyw' + xy'z'w$

(c)

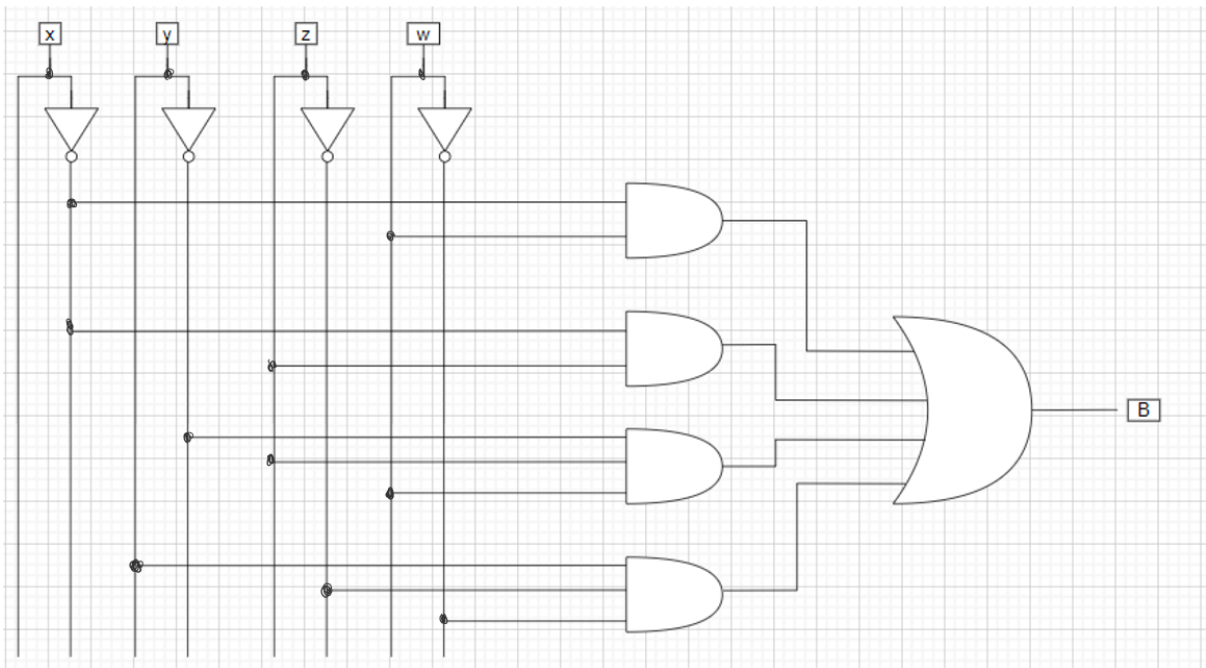 

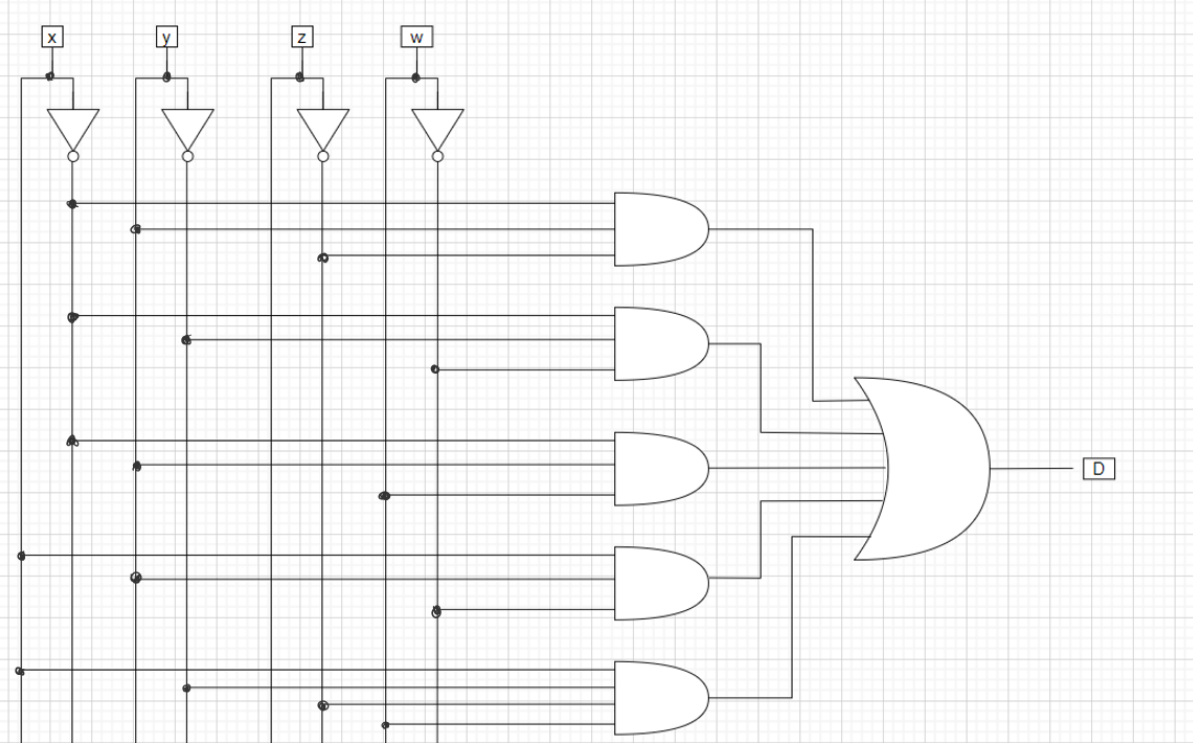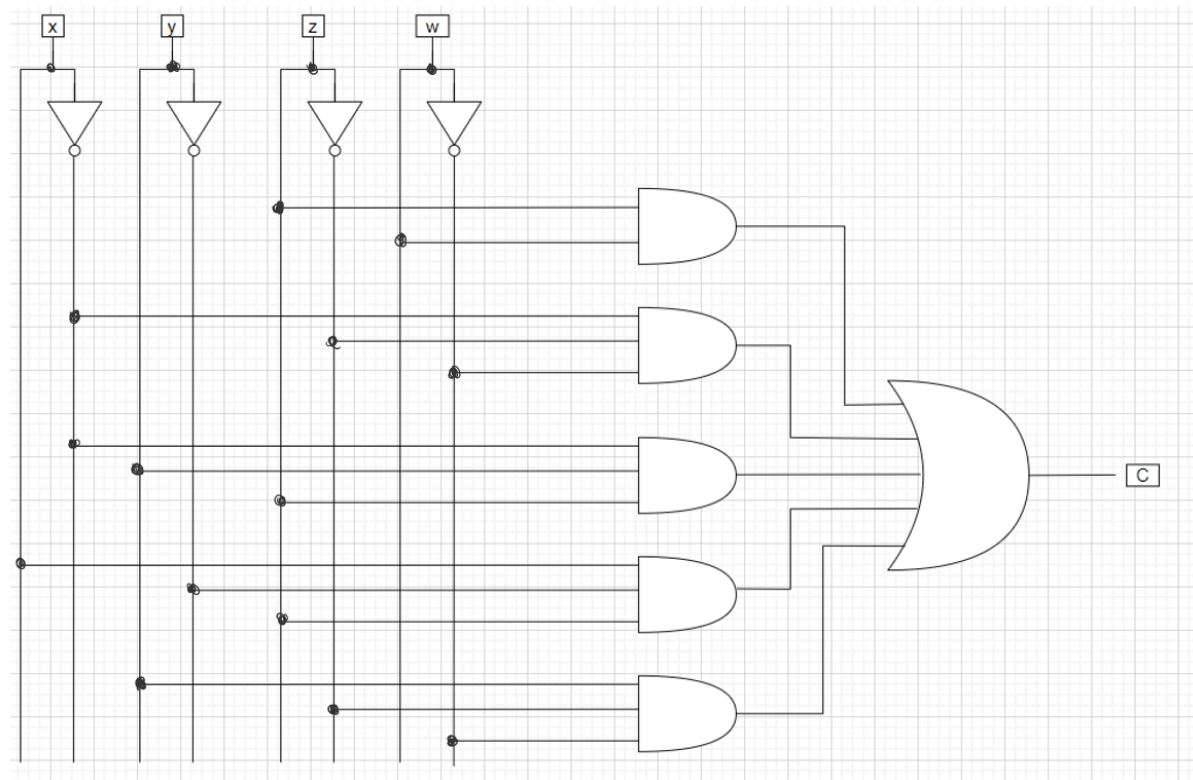

2 陳謙謙

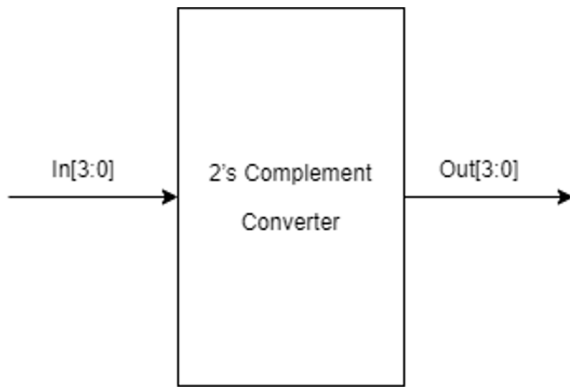

Truth Table of 2's Complement (For signed-input)

decimal	In[3]	In[2]	In[1]	In[0]	Out[3]	Out[2]	Out[1]	Out[0]	decimal
0	0	0	0	0	0	0	0	0	0
+1	0	0	0	1	1	1	1	1	-1
+2	0	0	1	0	1	1	1	0	-2
+3	0	0	1	1	1	1	0	1	-3
+4	0	1	0	0	1	1	0	0	-4
+5	0	1	0	1	1	0	1	1	-5
+6	0	1	1	0	1	0	1	0	-6
+7	0	1	1	1	1	0	0	1	-7
-8	1	0	0	0	1	0	0	0	-8
-7	1	0	0	1	0	1	1	1	+7
-6	1	0	1	0	0	1	1	0	+6
-5	1	0	1	1	0	1	0	1	+5
-4	1	1	0	0	0	1	0	0	+4
-3	1	1	0	1	0	0	1	1	+3
-2	1	1	1	0	0	0	1	0	+2
-1	1	1	1	1	0	0	0	1	+1


Special Case: Since the 2's complement of 1000 is 1000, we the signed input 1000 is decimal -8; however, the 2's complement output 1000 represents decimal -8 rather than +8

K-map

Out[3]

In[3:2] \ In[1:0]	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	0	0	0	0
10	1	0	0	0

 
$$\text{Out}[3] = \text{In}[3]' \text{In}[0] + \text{In}[3]' \text{In}[1] + \text{In}[3]' \text{In}[2] + \text{In}[3] \text{In}[2]' \text{In}[1]' \text{In}[0]'$$



Out[2]

In[3:2] \ In[1:0]	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	1	0	0	0
10	0	1	1	1

 
$$\text{Out}[2] = \text{In}[2]' \text{In}[0] + \text{In}[2]' \text{In}[1] + \text{In}[2] \text{In}[1]' \text{In}[0]'$$



Out[1]

In[3:2] \ In[1:0]	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

 
$$\text{Out}[1] = \text{In}[1]' \text{In}[0] + \text{In}[1] \text{In}[0]' = \text{In}[1] \oplus \text{In}[0]$$





Out[0]

In[3:2] \ In[1:0]	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

Out[0] = In[0]

 


3. 林彦岑

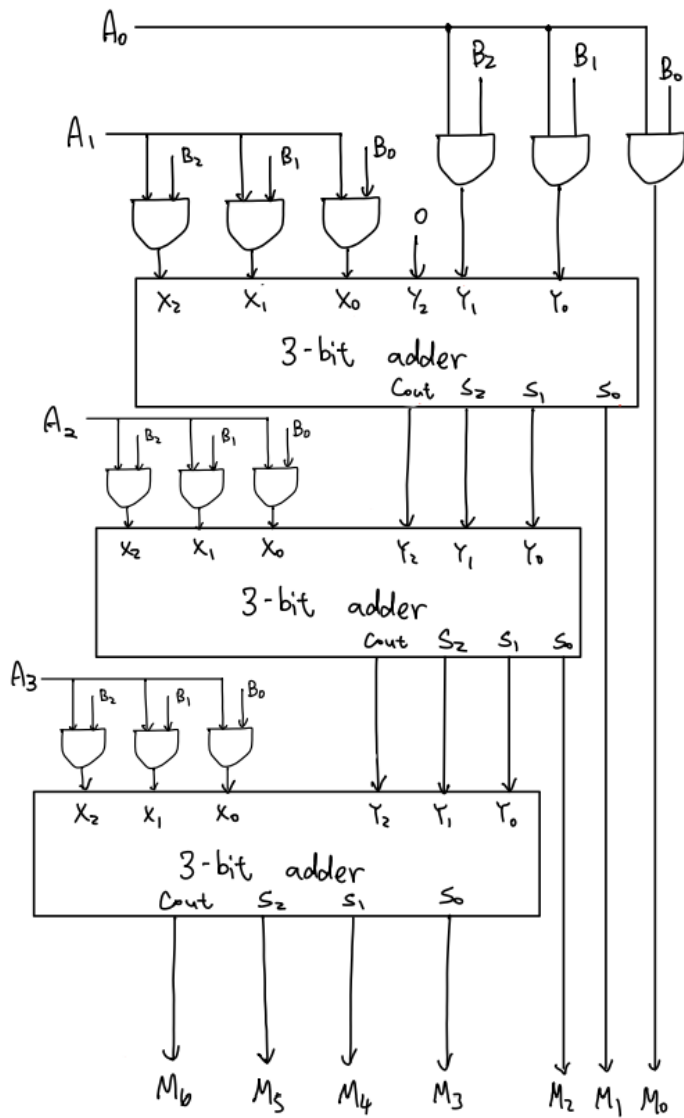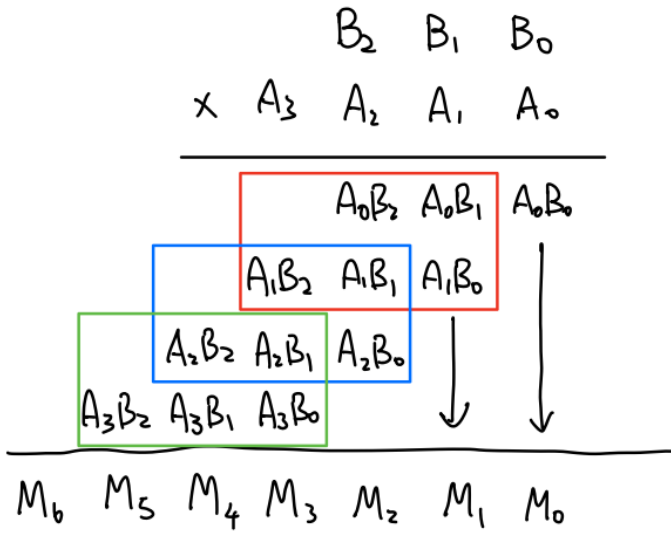

NOTE:


3-bit adder (以 ripple carry adder 實現)

 

Full adder

$$S_i = A_i \oplus B_i \oplus C_i$$
 
$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$



3-bit adder logic gate:

