

1 林致佑

(a) 2M x 16

1. $2^{10} = 1024 \rightarrow$ take 2^{10} as the binary approximation of kilo- (1000 multiplier)
 $2M = 2 * 2^{20} = 2^{21}$, so 2M x 16 takes **21 address lines** and **16 input and 16 output lines**
2. Number of bits stored in the memories:
 2M x 16: $2M = 2^{21} = 2,097,152$ words. Each word is 2 bytes = 16 bits, so the total number of bits is **$2^{21} * 16$**

(b) 32K x 4


1. $32K = 2^5 * 2^{10} = 2^{15}$, so 32K x 4 takes **15 address lines** and **4 input and 4 output lines**
2. Number of bits stored in the memories:
 32K x 4: $32K = 2^{15} = 32,768$ words. Each word is 4 bits, so the total number of bits is **$2^{15} * 4$**

2 徐浩庭

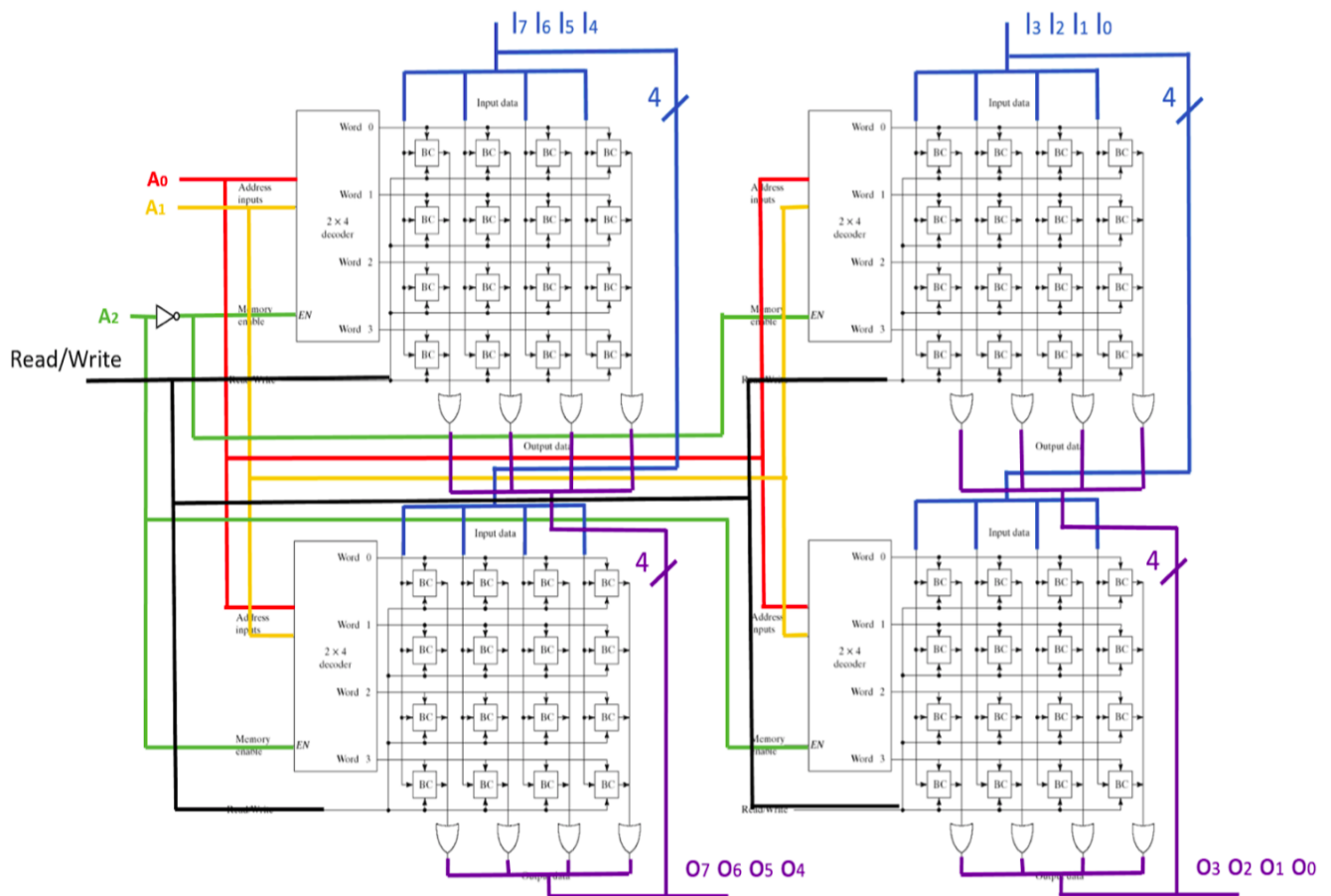題目要求為 8X8 => I0~I7 為 Inputs, O0~O7 為 outputs

4X4 RAM 為 2-to-4-lines decoder

因此有兩個 Address inputs (A0, A1), 而 A2 為 Memory enable 用於控制 A0 及 A1, 當 A2=0 時 Address inputs (A0, A1)=0, A2=1 時 Address inputs (A0, A1)=1。



3 呂政和

3. (a) bit position 1 2 3 4 5 6 7 8 9 10 11 12

0 1 1 0 0 1 0 0 0 1 1 0

$$C_1 = \text{XOR of bits } (1, 3, 5, 7, 9, 11)$$

$$= 0 \oplus 1 \oplus 0 \oplus 0 \oplus 0 \oplus 1 = 0$$

$$C_2 = \text{XOR of bits } (2, 3, 6, 7, 10, 11)$$

$$= 1 \oplus 1 \oplus 1 \oplus 0 \oplus 1 \oplus 1 = 1$$

$$C_4 = \text{XOR of bits } (4, 5, 6, 7, 12)$$

$$= 0 \oplus 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

$$C_8 = \text{XOR of bits } (8, 9, 10, 11, 12)$$

$$= 0 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 0$$

$$C = C_8 C_4 C_2 C_1 = 0110 = 6 \Rightarrow \text{error in bit 6}$$

$$\Rightarrow 011000000110$$

$$\Rightarrow \text{Original data} = 10000110$$

(b) bit position 1 2 3 4 5 6 7 8 9 10 11 12
 1 0 1 1 1 0 1 1 0 1 0 0

$$C_1 = \text{XOR of bits } (1, 3, 5, 7, 9, 11) \\ = 1 \oplus 1 \oplus 1 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$C_2 = \text{XOR of bits } (2, 3, 6, 7, 10, 11) \\ = 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 1$$

$$C_4 = \text{XOR of bits } (4, 5, 6, 7, 12) \\ = 1 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$C_8 = \text{XOR of bits } (8, 9, 10, 11, 12) \\ = 1 \oplus 0 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$C = C_8 C_4 C_2 C_1 = 0110 = 6 \Rightarrow \text{error in bit } 6$$

$$\Rightarrow 10111110100$$

$$\text{original data} = 11110100$$

4.

$$\begin{aligned}\text{The number of words} &= 64 \text{ k} \\ &= 2^6 \cdot 2^{10} \\ &= 2^{16} \\ &= 2^8 \cdot 2^8 \\ &= 256 \cdot 256\end{aligned}$$

(a)

decoder size : $8\text{-to-}2^8\text{-line decoder}$

for row / column decoder

256 8-input AND gates for row decoder
and column decoder

\therefore 256×2 8-input AND gates are required

for RAM cell

2^{16} 2-input AND gates are required

*

(b)


$$\begin{array}{r} 2 \overline{) 880} \\ 2 \overline{) 440} - 0 \\ 2 \overline{) 220} - 0 \\ 2 \overline{) 110} - 0 \\ 2 \overline{) 55} - 0 \\ 2 \overline{) 27} - 1 \\ 2 \overline{) 13} - 1 \\ 2 \overline{) 6} - 1 \\ 2 \overline{) 3} - 0 \\ 1 - 1 \end{array}$$

$$\begin{aligned} (880)_{10} &= (110110000)_2 \\ &= \underbrace{(00000011)}_{\text{row}} \underbrace{(0110000)}_{\text{column}})_2 \end{aligned}$$

$$\text{column} = (0110000)_2$$

$$\text{row} = (00000011)_2$$

#

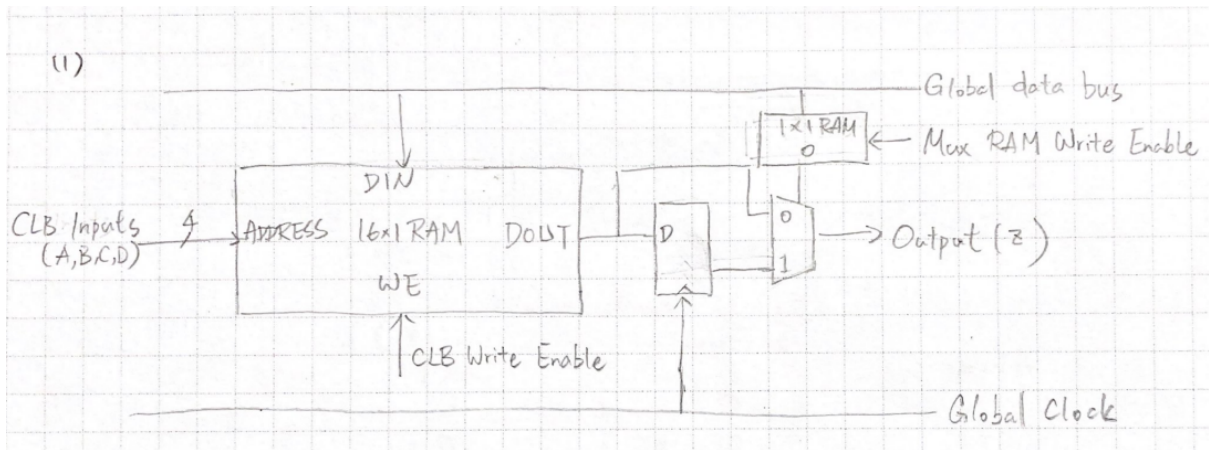


Inputs A, B, C would first send to the "16x1 RAM". There is also a lookup table (LUT) inside that RAM to determine the output "DOUT". The LUT (16-1 mux) is shown below.

LOGIC CELL 1

Address	ABCD	carry DOUT(Z[1])
0	000X	0
1	000X	0
2	001X	0
3	001X	0
4	010X	0
5	010X	0
6	011X	1
7	011X	1
8	100X	0
9	100X	0
10	101X	1
11	101X	1
12	110X	1
13	110X	1
14	111X	1
15	111X	1

LOGIC CELL 2

Address	ABCD	Sum DOUT(Z[0])
0	000X	0
1	000X	0
2	001X	1
3	001X	1
4	010X	1
5	010X	1
6	011X	0
7	011X	0
8	100X	1
9	100X	1
10	101X	0
11	101X	0
12	110X	0
13	110X	0
14	111X	1
15	111X	1

 


Since we have two functions ($f(A,B,C) = Z[1]$, $f(A,B,C) = Z[0]$), we need two FPGA logic cells for carry and sum respectively.

Full adder is a combinational logic so the "1x1 RAM" would select "0". Finally, we can get the output $Z[0]$ or $Z[1]$.

During the process, "CLB Write Enable" is off.

 "CLB Write Enable" = 1 only happens if we wanna change the RAM CLB function.




The LUT of TFF is shown below.

ADDRESS	(T) $Q(t)$				$Q(t+1)$ DOUT
	A	B	C	D	
0	0	0	x	x	0
1	0	0	x	x	0
2	0	0	x	x	0
3	0	0	x	x	0
4	0	1	x	x	1
5	0	1	x	x	1
6	0	1	x	x	1
7	0	1	x	x	1
8	1	0	x	x	1
9	1	0	x	x	1
10	1	0	x	x	1
11	1	0	x	x	1
12	1	1	x	x	0
13	1	1	x	x	0
14	1	1	x	x	0
15	1	1	x	x	0

Connect T to CLB Input A, $Q(t+1)$ to DOUT, CLB output (Z) to CLB input B.

 The whole process is similar to (1), but this time the "1x1 RAM" is "1" order to create a sequential circuit.



6呂依凡

b.

$8 \times 4 \text{ ROM} \Rightarrow 2^3 \times 4 \text{ ROM}$

$$A(X, Y, Z) = \sum m(1, 3, 5) = m_1 + m_3 + m_5$$

$$D(X, Y, Z) = \sum m(2, 3, 5, 6, 7) = m_2 + m_3 + m_5 + m_6 + m_7$$

	X	Y	Z	A	D	f_0	f_1
m_0	0	0	0	0	0	0	0
m_1	0	0	1	1	0	0	0
m_2	0	1	0	0	1	0	0
m_3	0	1	1	1	1	0	0
m_4	1	0	0	0	0	0	0
m_5	1	0	1	1	1	0	0
m_6	1	1	0	0	1	0	0
m_7	1	1	1	0	1	0	0
						↑	↑
						not	use

登記分數: 陳謙謙