

1. Consider the timing diagram in Figure 1(a). D and Clock are the inputs to the circuits in Figure 1(b). Draw the waveforms of the Q_a , Q_b , and Q_c . (15%)

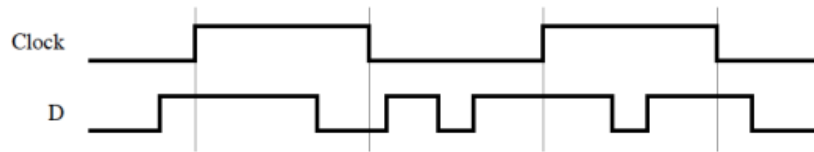


Figure 1(a)



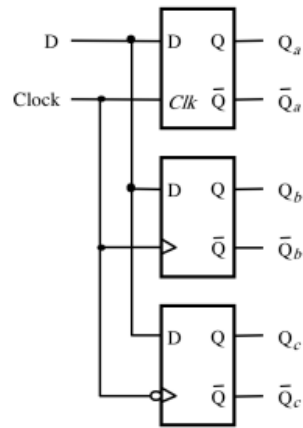


Figure 1(b)

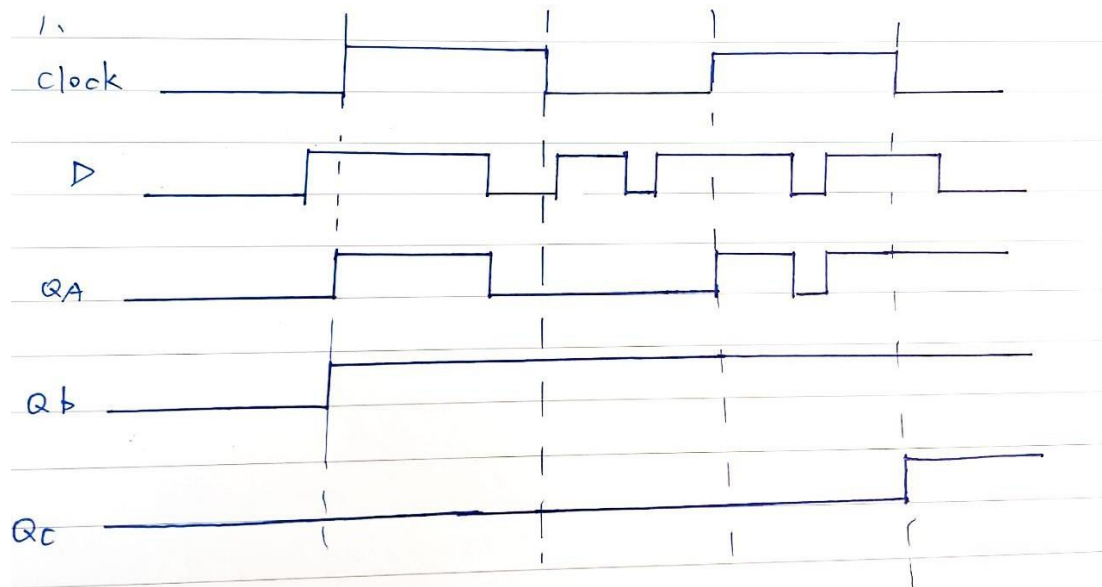

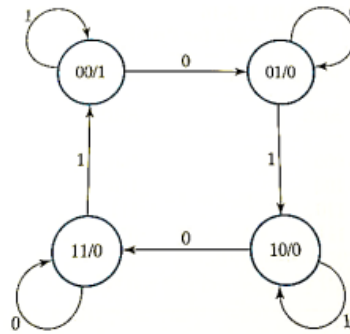2. A sequential circuit has two flip-flops A and B, one input x and one output z. The state diagram is shown in the following figure. Design the circuit with D flip-flops using one-hot state assignment. (15%)



Truth table						D3	D2	D1	D0	Z
	Y3	Y2	Y1	Y0	X					
1	0	0	0	0	0	x	x	x	x	x
2	0	0	0	1	0	0	0	1	0	1
3	0	0	1	0	0	0	0	1	0	0
4	0	0	1	1	0	x	x	x	x	x
5	0	1	0	0	0	1	0	0	0	0
6	0	1	0	1	0	x	x	x	x	x
7	0	1	1	0	0	x	x	x	x	x
8	0	1	1	1	0	x	x	x	x	x
9	1	0	0	0	0	1	0	0	0	0
10	1	0	0	1	0	x	x	x	x	x
11	1	0	1	0	0	x	x	x	x	x
12	1	0	1	1	0	x	x	x	x	x
13	1	1	0	0	0	x	x	x	x	x
14	1	1	0	1	0	x	x	x	x	x
15	1	1	1	0	0	x	x	x	x	x
16	1	1	1	1	0	x	x	x	x	x
17	0	0	0	0	1	x	x	x	x	x
18	0	0	0	1	1	0	0	0	1	1
19	0	0	1	0	1	0	1	0	0	0
20	0	0	1	1	1	x	x	x	x	x
21	0	1	0	0	1	0	1	0	0	0
22	0	1	0	1	1	x	x	x	x	x
23	0	1	1	0	1	x	x	x	x	x
24	0	1	1	1	1	x	x	x	x	x
25	1	0	0	0	1	0	0	0	1	0
26	1	0	0	1	1	x	x	x	x	x
27	1	0	1	0	1	x	x	x	x	x
28	1	0	1	1	1	x	x	x	x	x
29	1	1	0	0	1	x	x	x	x	x
30	1	1	0	1	1	x	x	x	x	x
31	1	1	1	0	1	x	x	x	x	x
32	1	1	1	1	1	x	x	x	x	x

KMAP

$D_{0,x=0}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$D_{0,x=1}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	1	x	0
01	0	x	x	x
11	x	x	x	x
10	1	x	x	x

$D_{1,x=0}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	1	x	1
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$D_{1,x=1}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$D_{2,x=0}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$D_{2,x=1}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	1
01	1	x	x	x
11	x	x	x	x
10	0	x	x	x

$D_{3,x=0}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	0
01	1	x	x	x
11	x	x	x	x
10	1	x	x	x

$D_{3,x=1}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	0	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$Z_{x=0}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	1	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x

$Z_{x=1}$

Y3Y2	Y1Y0			
	00	01	11	10
00	x	1	x	0
01	0	x	x	x
11	x	x	x	x
10	0	x	x	x


$$D_0 = X(Y_0 + Y_3)$$

$$D_1 = \bar{X}(Y_0 + Y_1)$$

$$D_2 = X(Y_1 + Y_2)$$

$$D_3 = \bar{X}(Y_2 + Y_3)$$

$$Z = Y_0$$

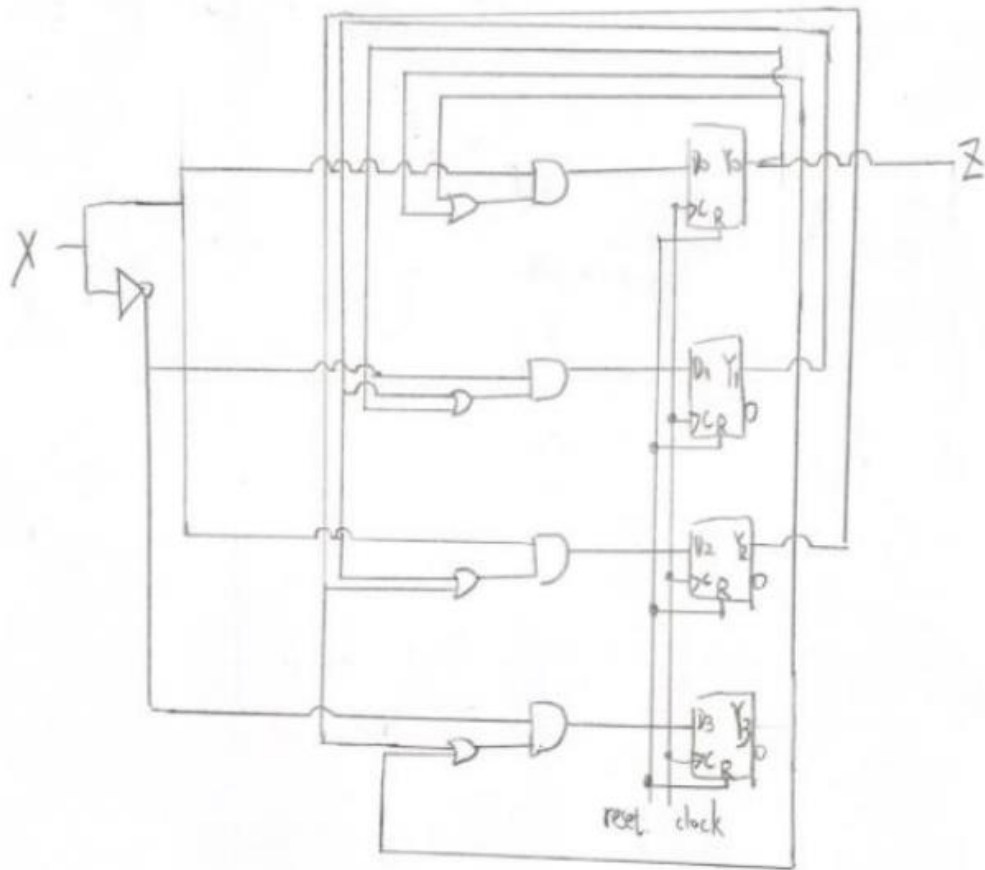

3. Design a sequential circuit with two D flip-flops A and B and one input X . When $X = 1$, the state of the circuit remains the same. When $X = 0$, the circuit goes through the state transitions from 00 to 10 to 11 to 01, back to 00, and then repeats. (15%)

3. present state input Next state

A	B	X	A+1	B+1
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

A+1:



A \ Bx	00	01	11	10
0	1			
1		1	1	

$$D_A = B'x' + Ax$$


B+1:

A \ Bx	00	01	11	10
0			1	
1	1			1

$$D_B = Bx + Ax'$$

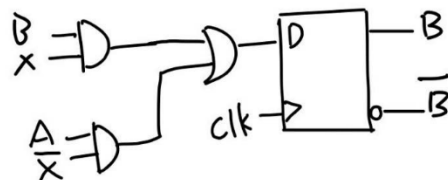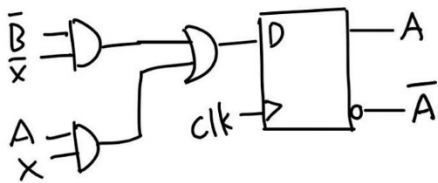

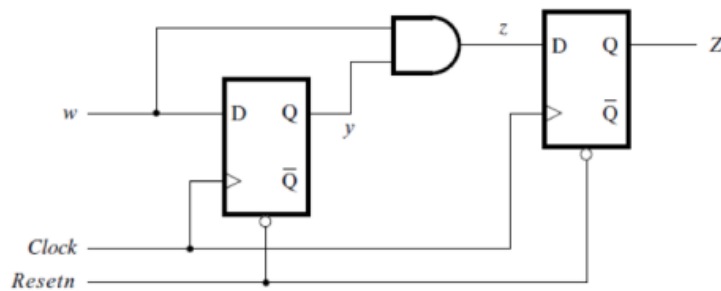
4. Derive the state table, state diagram, and next-state and output equations (y, z, Z) of the following figure. (20%)



① state table :

$z = wy$ $y(t+1) = w$ $z(t+1) = z = wy$	Present state		next state				output
	y	z	$w=0$		$w=1$		z
	y	z	y	z	y	z	
	0	0	0	0	1	0	0
	0	1	0	0	1	0	1
	1	0	0	0	1	1	0
	1	1	0	0	1	1	1

② state diagram :

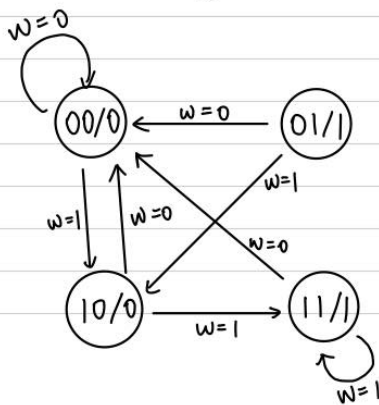

③ next state / output equation


$$y(t+1) = w$$

$$z(t+1) = wy$$

$$z, out = z$$

5. (a) Draw the gate level implementation of a gated (clocked) D latch using NORs or NANDs. Write its function table. (10%)
- (b) Use gated D latch as a block, draw the logic diagram of an edge-triggered D flip-flop. Indicate whether the D flip-flop is positive or negative edge triggered. (10%)

5. (a)

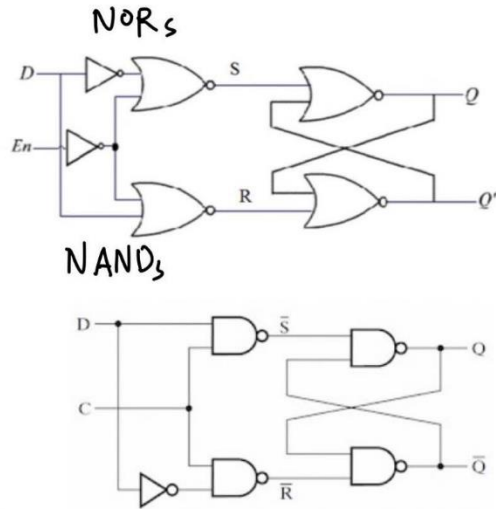


function table


Inputs		Outputs	
C	D	Q	Q̄
0	X	NC	NC
1	0	0	1
1	1	1	0

(b)

Negative edge triggered

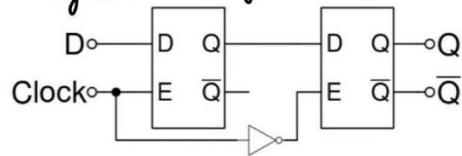


Positive edge triggered

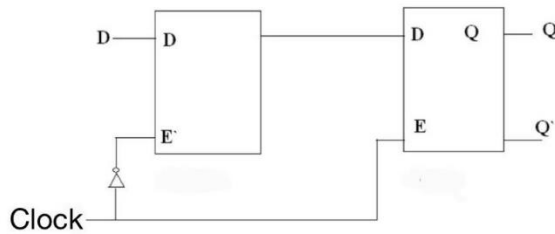

6. Design a sequential circuit that recognize the sequence 1001. (15%)

Mealy machine:

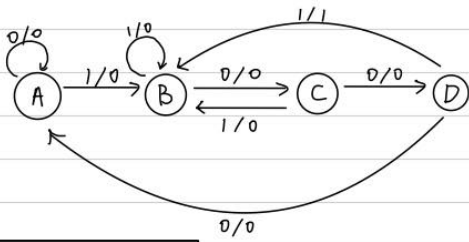

present state a b	next state		output (z)	
	X=0 a^+b^+	X=1 a^+b^+	X=0	X=1
A 0 0	0 0	0 1	0	0
B 0 1	1 0	0 1	0	0
C 1 0	1 1	0 1	0	0
D 1 1	0 0	0 1	0	1

A: reset
B: 1
C: 1 0
D: 1 0 0

a^+ :

X \ ab	00	01	11	10
0		1		1
1				

$$a^+ = \bar{x}\bar{a}b + \bar{x}a\bar{b}$$

b^+ :

X \ ab	00	01	11	10
0				1
1	1	1	1	1

$$b^+ = X + a\bar{b}$$

output: $z = xab$

