



EECS1010 Logic Design

Lecture 2

Boolean Algebra and Logic Gates

Jenny Yi-Chun Liu
jennyliu@gapp.nthu.edu.tw



Outline

- Digital systems and information
- Boolean algebra and logic gates
- Gate-level minimization
- Combinational logic
- Sequential circuits
- Registers and counters
- Memory



Chapter Outline

- Boolean algebra and logic gates *the most primitive logic element*
 - Binary logic
 - Basic theorems and properties of Boolean algebra
 - Normal and standard forms
 - Other logic functions



Binary Logic



Digital Circuits

- Digital circuits: hardware components that manipulate binary information.
- Each basic circuit is called *a logic gate*
- Each gate performs a specific logic function.



Binary Logic

- Binary logic deals with 0's and 1's.

Boolean expression

logic diagram

- Basic logic functions:

1. AND

•

$$a \cdot b = c$$



2. OR

+

$$a + b = c$$



3. NOT

,


-

$$a', \bar{a} = c$$



- Operation order: parentheses, NOT, AND, OR

$$F = (x + y) + z \cdot \bar{y}$$

 



Operator Definitions

- Binary logic operation vs. binary arithmetic
- Definitions of AND, OR, and NOT:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$



Truth Table

- Truth table: a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: truth tables for the basic logic operations

AND

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

x	\bar{x}
0	1
1	0



Example: Truth Table

Practice

° $F = (x+y) + z \cdot \bar{y}$. Truth table = ?



Boolean algebra



Logic Diagrams and Expressions

- Boolean algebra: algebra dealing with binary variables and logic operations.
- Boolean equations, truth tables and logic diagrams describe the same function!
- ✱ • Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.



Axioms of Boolean Algebra

- Axioms: a set of mathematical statements that we assert to be true.

- Identity $1 \cdot x = x$

$$0 + x = x$$

- Annihilation $0 \cdot x = 0$

$$1 + x = 1$$

- Negation $\overline{0} = 1$

$$\overline{1} = 0$$



Basic Identities of Boolean Algebra (1/2)

1. Commutative

$$x \cdot y = y \cdot x$$

$$x + y = y + x$$

2. Associative,

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$x + (y + z) = (x + y) + z$$

3. Distributive

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

4. Idempotence

$$x \cdot x = x$$

$$x + x = x$$

5. Absorption

$$x \cdot (x + y) = x$$



$$x + (x \cdot y) = x$$



Basic Identities of Boolean Algebra (2/2)

6. Combining, $(x \cdot y) + (x \cdot \bar{y}) = x$
 $(x + y) \cdot (x + \bar{y}) = x$

  7. DeMorgan's $\overline{(x \cdot y)} = \bar{x} + \bar{y}$
 $\overline{(x + y)} = \bar{x} \cdot \bar{y}$



8. Complementation, $x + \bar{x} = 1$
 $x \cdot \bar{x} = 0$

9. Involution, $\overline{\bar{x}} = x$



Duality


- Dual: interchanging AND and OR, 0's and 1's.
usually F^D (dual of F) $\neq F$

- Example:

$$1) \quad F = \underbrace{(A + \bar{C}) \cdot B + 0}_{\uparrow} \quad \Rightarrow \quad F^D = \left[(A \cdot \bar{C}) + B \right] \cdot 1 = A \cdot \bar{C} + B \neq F$$

$$2) \quad G = \overline{A \cdot B} + AC + BC, \quad \Rightarrow \quad G^D = G$$

Practice

 



Summary of Useful Theorems

- Boolean algebra is applied to reduce an expression to obtain a simpler circuit.

1. Minimization = combining (p.14)

2. Consensus: $xy + \bar{x}z + yz = xy + \bar{x}z$

$$(x+y)(\bar{x}+z)(y+z) = (x+y)(\bar{x}+z)$$

3. Simplification: $x + \bar{x}y = x + y$

$$x(\bar{x} + y) = xy$$



Example: Boolean Function

o Truth table

$$F_1 = x y \bar{z}$$

$$\begin{aligned} x &= 1 \\ y &= 1 \\ \bar{z} &= 1 \quad z = 0 \end{aligned}$$

$$F_2 = x + \bar{y} z$$

$$\begin{aligned} x &= 1 & \bar{y} z &= 1 \\ & & \bar{y} &= 1 \\ & & z &= 1 \end{aligned}$$

$$F_3 = \bar{x} \bar{y} \bar{z} + \bar{x} y z + x \bar{y} z$$

$$\begin{aligned} x &= 1 \\ y &= 0 \\ z &= 1 \end{aligned}$$

$$F_4 = x \bar{y} + \bar{x} z$$

$$\begin{cases} x=1 & \bar{x}=0 \\ y=0 & z=1 \end{cases}$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0	1	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

F3

Practice.

\bar{F}_3 , \bar{F}_4
" ? " ?

$$\bar{F}_1 = \overline{(x y \bar{z})} = \bar{x} + \bar{y} + z$$



NOT

Complementing Functions

- Complement: *interchanging 0's and 1's in the truth table*
- General rules: use DeMorgan's theorem to complement a function

- *Interchange AND and OR*

- Complement each literal ($x \rightarrow \bar{x}$, $\bar{y} \rightarrow y$) and constant ($0 \leftrightarrow 1$)

o Examples:

$$1) F = \bar{x}y\bar{z} + x\bar{y}\bar{z}, \quad \bar{F} = \overline{\bar{x}y\bar{z} + x\bar{y}\bar{z}} = (x + \bar{y} + z) \cdot (\bar{x} + y + z)$$

$$2) G = \underline{(\bar{x} + yz)} \cdot \bar{a} + b, \quad \bar{G} = \left[\left(x \cdot (\bar{y} + \bar{z}) \right) + a \right] \cdot \bar{b}$$

◦ Homework 1: average 90.5

◦ Quiz 1: solutions posted

◦ Midterm 1: 3/28 (Tue) 1:20pm. classroom to be announced.

◦ Homework 2: due 3/25 (Sat) 6pm, online

Lec1-Lec2.



Normal and standard forms



Boolean Function

- Can be represented by a truth table with 2^n rows. n is the number of variables in the function.
- There are many algebraic expressions to specify a given Boolean function. It is important to find the simplest one. $F(x, y, z) = xy + z$
- Any Boolean function can be transformed into a logic diagram with only AND, OR, and NOT gates.





Normal Forms

- It is useful to specify Boolean functions in a standard way.
- Common normal forms

1. ⁺Sum of minterms (SOM)

2. Product of maxterms (POM)

•



Minterms

AND

- Minterm: a product term in which all of the variables appear exactly once, either complemented or uncomplemented.
- Minterm represents exactly one combination of variables in the truth table.

◦ 2^n minterms for n variables.

◦ Example: 2 variables, x and y .

Truth table	x	y	minterm	symbol
	0	0	$\bar{x}\bar{y}$	m_0
	0	1	$\bar{x}y$	m_1
	1	0	$x\bar{y}$	m_2
	1	1	xy	m_3



★ Maxterms

OR

- Maxterm: a sum term in which all of the variables appear exactly once, either complemented or uncomplemented.
- 2^n maxterms for n variables.

Example: 2 variables, x and y

Truth table	x	y	maxterm	symbol
	0	0	$x + y$	M_0
	0	1	$x + \bar{y}$	M_1
	1	0	$\bar{x} + y$	M_2
	1	1	$\bar{x} + \bar{y}$	M_3



Standard Minterms and Maxterms

- Minterms and maxterms are designated with a subscript, corresponding to a binary pattern
- All variables are presented in a minterm or maxterm and will be listed in the same order (usually alphabetically)
- Example: For variables a, b, c:

– Maxterm

$$a + \bar{b} + c$$

$$b + a + c \quad \times$$

$$\times \underline{a} b + c$$

$$\times b +$$

– Minterm

$$a \bar{b} c,$$

$$\times b a c$$

$$\times b a$$



Minterm and Maxterm Relationship


- Each maxterm is the complement of its corresponding minterm and vice versa.
- Use DeMorgan's Theorem

$$m_2 = x \bar{y}$$

$$M_2 = \bar{x} + y$$

$$\bar{m}_2 = (\overline{x \bar{y}}) = \bar{x} + y = M_2$$

 • For n variables, $m_i = \bar{M}_i$, $i = 0, 1, \dots, 2^n - 1$



Minterms and Maxterms with Three Variables

	x y z	minterms	notation	maxterms	notation
0	0 0 0	$x'y'z'$	m_0	$x+y+z$	M_0
1	0 0 1	$x'y'z$	m_1	$x+y+z'$	M_1
2	0 1 0	$x'yz'$	m_2	$x+y'+z$	M_2
3	0 1 1	$x'yz$	m_3	$x+y'+z'$	M_3
4	1 0 0	$xy'z'$	m_4	$x'+y+z$	M_4
5	1 0 1	$xy'z$	m_5	$x'+y+z'$	M_5
6	1 1 0	xyz'	m_6	$x'+y'+z$	M_6
7	1 1 1	xyz	m_7	$x'+y'+z'$	M_7



Sum of Minterms (SOM)

- A Boolean function can be represented algebraically from a given truth table by forming the logical sum of all the minterms that produce 1 in the function.



SOM Example 1

- Given a truth table.
Find som .

x	y	z	F(x,y,z)	minterm
0	0	0	1	m ₀
0	0	1	0	m ₁
0	1	0	1	m ₂
0	1	1	0	m ₃
1	0	0	0	m ₄
1	0	1	1	m ₅
1	1	0	0	m ₆
1	1	1	1	m ₇

$$\begin{aligned}F(x,y,z) &= m_0 + m_2 + m_5 + m_7 \\ &= \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}z + xyz \\ &= \sum m(0, 2, 5, 7) \\ &= \Sigma(0, 2, 5, 7)\end{aligned}$$



SOM Example 2

o Given $F(x, y, z) = m_1 + m_4 + m_7$.

Find truth table.

	<u>x y z</u>	<u>$F(x, y, z)$</u>	<u>\bar{F}</u>
m_0	0 0 0	0	1
m_1	0 0 1	1	0
m_2	0 1 0	0	1
m_3	0 1 1	0	1
m_4	1 0 0	1	0
m_5	1 0 1	0	1
m_6	1 1 0	0	1
m_7	1 1 1	1	0

$$\bar{F}(x, y, z) = \Sigma(0, 2, 3, 5, 6)$$

$$F + \bar{F} = 1$$



SOM Example 3

Practice

Given $F(A, B, C, D, E) = m_2 + m_9 + m_{17} + m_{23}$

1) Derive its truth table

2) Find the SOM Boolean expression (with literals)




Properties of SOM

- There are 2^n minterms for n Boolean variables.
- Any Boolean function can be expressed as a logical sum of minterms.
- The complement of a function contains those minterms not included in the original function.
- A function that include all the 2^n minterms is equal to 1.
- A function not in the sum-of-minterms form can be converted to that form by a truth table. $F(x, y, z) = x + \bar{y}z$

• **Implementation** of this form is a two-level network of gates such that:

$$\underline{x}y\underline{z} + \underline{x}\bar{y}\bar{z}$$

 - The first level consists of n-input AND gates
- The second level is a single OR gate (with fewer than 2^n inputs)





Product of Maxterms (POM)

- A Boolean function can be represented algebraically from a given truth table by forming the logical product of all the maxterms that produce 0 in the function =>

Practice

=

• Example.

Given $F(x, y, z) = x + \bar{x}\bar{y}$. Find its POM expression

1) By truth table

2) By Boolean algebra



POM Example 1

Given truth table. Find its POM.

x	y	z	F(x, y, z)	maxterm.
0	0	0	0	M ₀
0	0	1	1	M ₁
0	1	0	0	M ₂
0	1	1	0	M ₃
1	0	0	1	M ₄
1	0	1	0	M ₅
1	1	0	0	M ₆
1	1	1	1	M ₇

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$= (x+y+z) \cdot (x+\bar{y}+z) \cdot (x+\bar{y}+\bar{z}) \cdot (\bar{x}+y+\bar{z}) \cdot (\bar{x}+\bar{y}+z)$$

$$= \prod M(0, 2, 3, 5, 6)$$

$$= \prod (0, 2, 3, 5, 6)$$

$$\bar{F}(x, y, z) = \prod (1, 4, 7) \text{ POM}$$

$$SOM \quad F(x, y, z) = \sum (1, 4, 7)$$



$$x=1$$
$$z=0$$

POM Example 2

• $F(x, y, z) = x\bar{z} + yz + \bar{x}\bar{y}$. Find its POM.

① By truth table

② By Boolean algebra

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

SOM, $F = \Sigma(0, 1, 3, 4, 6, 7)$

$$F = M_2 \cdot M_5$$

Use Boolean algebra

$$\circ F(x, y, z) = \underline{x\bar{z}} + \underline{y\bar{z}} + \underline{\bar{x}\bar{y}}$$

SOM.

(p.11)

$$\underline{x \cdot 1 = x}$$

$$= \underline{x\bar{z}} \cdot (y + \bar{y}) + y\bar{z}(x + \bar{x}) + \bar{x}\bar{y} \cdot (z + \bar{z}) \quad \begin{matrix} \uparrow \\ (y + \bar{y}) \end{matrix}$$

$$= xy\bar{z} + x\bar{y}\bar{z} + xy\bar{z} + \bar{x}y\bar{z} + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$$

Practice

POM. $F(x, y, z) = x\bar{z} + y\bar{z} = (x\bar{z} + y)(x\bar{z} + z)$

distributive

$$= (x + y) \cdot (\bar{z} + y) \cdot (x + z) \cdot \underline{(\bar{z} + z)}$$

$$= (x + y) \cdot (y + \bar{z}) \cdot (x + z)$$

$$x + 0 = x$$

$$= (x + y + z \cdot \bar{z}) \cdot (y + \bar{z} + x\bar{x}) \cdot (x + z + y\bar{y})$$

$$= (x + y + \check{z}) \cdot (x + y + \check{\bar{z}}) \cdot (\check{y} + \bar{z} + x) (y + \bar{z} + \check{\bar{x}}) \cdot (x + \check{z} + y)$$

$$(x + \bar{y} + z)$$

$$= (x + y + z) \cdot (x + y + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (x + \bar{y} + z)$$



POM Example 3

Practice

$$F(A, B, C, D, E) = \Pi M(3, 8, 11, 14)$$

Find its truth table and SOM.



SOM and POM Conversion

- Any Boolean function can be represented by either SOM or POM normal forms.
 - To convert from one normal form to another, interchange Σ and Π , and list the index that are excluded from the original form.

o Example.

$$F(x, y, z) = \overset{\text{SOM}}{\Sigma}(1, 4, 7) = \overset{\text{POM}}{\Pi}(0, 2, 3, 5, 6)$$
$$\bar{F}(x, y, z) = \overset{\text{SOM}}{\Sigma}(0, 2, 3, 5, 6) = \overset{\text{POM}}{\Pi}(1, 4, 7)$$



Conversion to Normal Form

- Convert any Boolean expression into normal form
 - ✓ — By truth table
 - ✓ — By expanding the missing variables in each term using $x + x' = 1$, $xx' = 0$

$$xy(z + \bar{z}) = xy z + xy \bar{z}$$

$$(x + y) = (x + y + z \cdot \bar{z}) = (x + y + z) \cdot (x + y + \bar{z})$$




Complement of Function

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms normal forms.
- Alternatively, the complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices.




Standard Forms

 1. ⁺ Sum-of-products (SOP)
 - Has fewer literals than SOM



 2. ⁺ Product-of-sums (POS)
 - Has fewer literals than POM



- The corresponding circuit may be simpler than that of the normal form.
- Standard forms are not unique.



$$(x+y) \cdot (\bar{y}+z)$$

pos

Standard Sum-of-Products (SOP)

- Standard Sum-of-Products (SOP) form: equations are written as an OR of AND (product) terms.

Example:


$$\begin{aligned}
 F(x, y, z) &= \sum m(1, 4, 5, 6, 7) \\
 &= \bar{x}\bar{y}z + x\bar{y}\bar{z} + xy\bar{z} + x\bar{y}z + xyz \\
 &= \bar{x}\bar{y}z + x(\bar{y}\bar{z} + y\bar{z} + \bar{y}z + yz) \\
 &= \bar{x}\bar{y}z + x(y+\bar{y})(z+\bar{z}) \\
 &= \bar{x}\bar{y}z + x
 \end{aligned}$$

L=8

G=12


SOP

L=3
G=4

 

1 AND
1 OR

SOM implementation

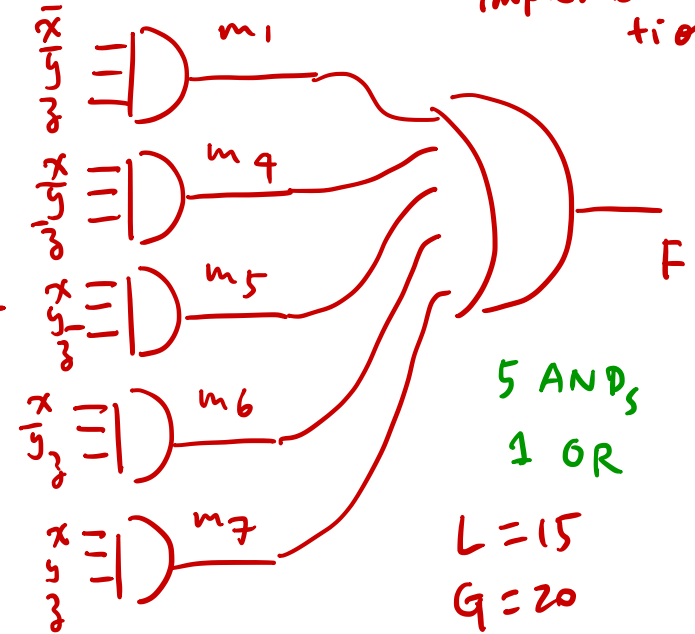

5 ANDs
1 OR

L=15
G=20
GN=23



Optimization



Circuit Optimization

- The complexity of a logic circuit directly related to the algebraic expression (literal count).
- Goal: to obtain the simplest implementation for a given function.
- Optimization is a formal approach to simplification that is performed using a specific procedure or algorithm.
- Simplest form is not necessarily unique.
- Optimization requires a cost criterion to measure the simplicity of a circuit.

Computer aided design

- CAD tools are commonly used today for optimization.

- Cost criteria we will use:

1. Literal cost (L)

* 2. Gate input cost (G)

* 3. Gate input cost with NOTs (GN)



Literal Cost

- Literal: a *variable* or its complement
- Literal cost: the number of the literals appeared in a Boolean expression.
 - Simple to count.
 - Not accurate in some cases.

Example.

$$F = \underline{ABC} + \underline{AC}\overline{D} + \underline{B}, \quad L = 7 \quad G = 9 \quad GN = 9 + 1 = 10$$

$$G = (\underline{A+B}) (\underline{C+D}) (\underline{\overline{B+C+D}}), \quad L = 7 \quad G = 10, \quad GN = 10 + 2 = 12$$



Gate Input Cost

- Gate input costs: the number of the inputs to the gates corresponding to a given Boolean expression.
 - Obtain from the logic diagram.
- For SOP and POS equations, it can be found from the equations by finding the sum of:
 - All literal appearances = L
 - The number of terms excluding single literal terms
 - The number of distinct complemented single literals (\underline{GN})
- Gate input cost is a good measure of logic implementation.
 - It is proportional to the number of transistors and wires in implementation.
 - It considers the internal inputs, particular important for circuits more than two levels.

$$\left. \begin{array}{l}) = G \\ = \\ \underline{GN} \end{array} \right) GN$$



Practice

Cost Criteria Example 1

- $F = AB' + BC + B'C'$

$L =$

$G =$

$G_N =$

- $G = (AC' + B)(B + C + D')(B' + C' + D)$

$L =$

$G =$

$G_N =$



Cost Criteria Example 2

• $F = \underbrace{ABC}_{\substack{\checkmark \checkmark \checkmark \\ \text{SOP, SOM}}} + \underbrace{A'B'C'}_{\substack{\checkmark \checkmark \checkmark \\ \text{SOP, SOM}}}, G = \underbrace{(A + C')}_{\text{POS}} \underbrace{(B' + C)}_{\text{POS}} \underbrace{(A' + B)}_{\text{POS}}$

$$L = 6$$

$$L = 6$$

$$G = 6 + 2 = 8$$

$$G = 6 + 3 = 9$$

$$G_N = 8 + 3 = 11$$

$$G_N = 9 + 3 = 12$$

$F = G$ same function, same L .

Function F has better G and G_N than function G .




Other gates



Other Gate Types

 - Why?
 - Implementation feasibility and low cost
NAND easier to fabricate than *AND, OR*
NOR
- Gate classifications
 - Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus inversions. *AND, OR, NOT, NAND, NOR, buffer*
 - Complex gate - a gate that requires more than one primitive operation type for its description.
XOR, XNOR, AOI, OAI, AO, OA



Buffer

- A buffer is a gate with the function: $F = x$



- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.





NAND Gate

- Digital circuits are more common to implement with NAND/NOR gates rather than AND/OR/NOT gates due to simple fabrication.
- NAND is an universal gate that any operation can be implemented by NAND gates.



NAND: $AND + NOT = \underline{NOT} + \underline{OR}$

x	y	$\overline{x \cdot y} = \bar{x} + \bar{y}$
0	0	1
0	1	1
1	0	1
1	1	0

  





NAND-NAND Implementation

- NAND-NAND implementation procedure:
 - Simplify the function in the sum-of-products form. (AND-OR)
 - Transfer it to a 2-level NAND-NAND expression by DeMorgan's Theorem.
 - Draw the corresponding NAND-NAND implementation. An 1-input NAND gate can be replaced by an inverter.



NAND-NAND Example

 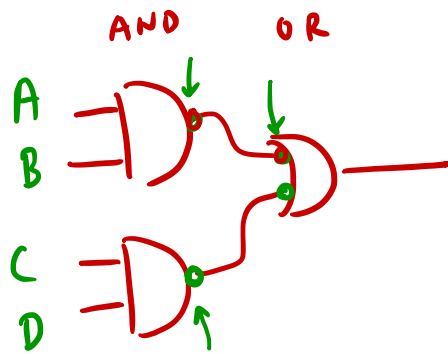- Given $F(A, B, C, D) = AB + CD$. use NAND



AND-OR(SOP) \longrightarrow NAND-NAND

$$F(A, B, C, D) = AB + CD = \overline{\overline{AB + CD}} = \overline{\overline{AB} \cdot \overline{CD}}$$



NOR Gate

o NOR: OR - NOT = NOT - AND

x	y	$\overline{x+y} = \bar{x} \cdot \bar{y}$
0	0	1
0	1	0
1	0	0
1	1	0

Symbol





o POS (OR - AND) \rightarrow NOR - NOR



NOR-NOR

- NOR-NOR is the dual of the NAND-NAND implementation
 - AND-OR => NAND-NAND
 - OR-AND => NOR-NOR

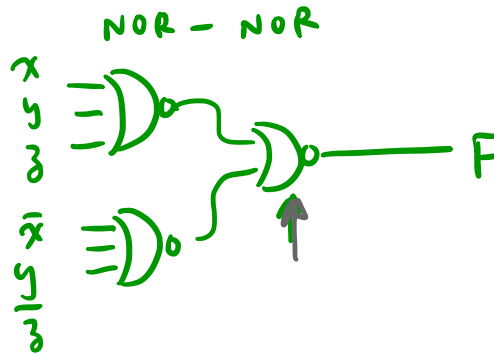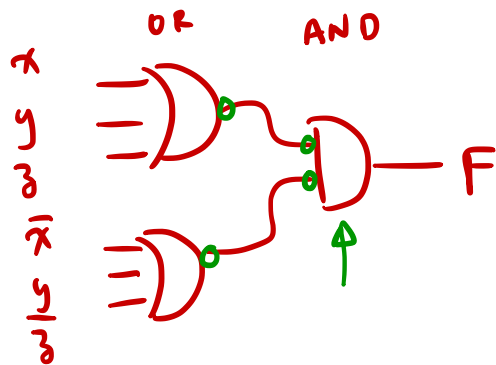• Example: $F(x, y, z) = (x+y+z)(\bar{x}+y+\bar{z})$. use NOR



$$F = \overline{\overline{(x+y+z)} + \overline{(\bar{x}+y+\bar{z})}} = \overline{\overline{(x+y+z)} + \overline{(\bar{x}+y+\bar{z})}}$$

↑ ↑ = ↓

NOR - NOR




exclusive

XOR/XNOR (1/3)



x	y	XOR $x \oplus y$	XNOR $\overline{x \oplus y}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 The eXclusive NOR (XNOR): $\overline{x \oplus y} = xy + \bar{x}\bar{y}$



- Definitions

- The XOR function: $x \oplus y = x\bar{y} + \bar{x}y$
- The eXclusive NOR (XNOR): $\overline{x \oplus y} = xy + \bar{x}\bar{y}$

- The eXclusive OR (XOR) function may be:
 - Implemented directly as an electronic circuit.
 - Implemented by interconnecting other gate types.

- The eXclusive NOR (XNOR) function is the complement of the XOR function.



XOR/XNOR (2/3)

- Uses for the XOR and XNOR gates:
 - Adders, subtractors, multipliers
 - Counters, incrementers, decrementers
 - Parity checkers, parity generators
- XOR and XNOR do not exist for more than two inputs. Instead, they are replaced by odd and even functions for more than two inputs.

x	y	z	$x \oplus y \oplus z$ (odd function)
1	0	0	1
0	1	0	1
0	0	1	1
1	1	1	1

Handwritten note: 奇函数 (odd function) 1



XOR/XNOR (3/3)

° XOR identities:

$$x \oplus 0 = x$$

$$x \oplus 1 = \bar{x}$$

$$x \oplus x = 0$$

$$x \oplus \bar{x} = 1$$

$$x \oplus y = y \oplus x$$

$$x \oplus y \oplus z = (x \oplus y) \oplus z = x \oplus (y \oplus z)$$



Parity Generators and Checkers (1/2)

- A parity bit is an extra bit added to n-bit code to produce and produce an (n+1) bit code for error detection and correction.
- Example:

$w=3$, generate a parity bit for even parity codewords. (4 bits)


x	y	z	(p)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(p x y z)
(1 0 0 1)


$$\text{SOM, } p = \Sigma(1, 2, 4, 7) = \Pi(0, 3, 5, 6)$$




$$p = x \oplus y \oplus z$$

 

Parity generator.

 


Parity Generators and Checkers (2/2)

 

$e=0$ no error (even "1"s)
 $e=1$ error (odd "1"s)

p	x	y	z	e
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

阻抗

High-Impedance Outputs (1/2)




- Logic gates introduced thus far
 - have 1 and 0 output values.
 - cannot have their outputs connected together.
 - transmit signals on connections in only one direction.
- Three-state logic adds a third logic value, High-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.



Hi-Impedance Outputs (2/2)

 
- What is a Hi-Z value?
 - The Hi-Z value behaves as an open circuit
 - Looking into the circuit, the output appears to be disconnected
- Hi-Z may appear on the output of any gate, but we restrict gates to:
 - ✓ A 3-state buffer
 - ✓ A transmission gate



Each of which has one data input and one control input.



The 3-State Buffer

 

control = 0, out = high-Z regardless of input

control = 1, out = in



不考








Gate implementation



MOSFET: metal-oxide-semiconductor field effect transistor


MOS Switches

cross section

       





NOT Gate Implementation

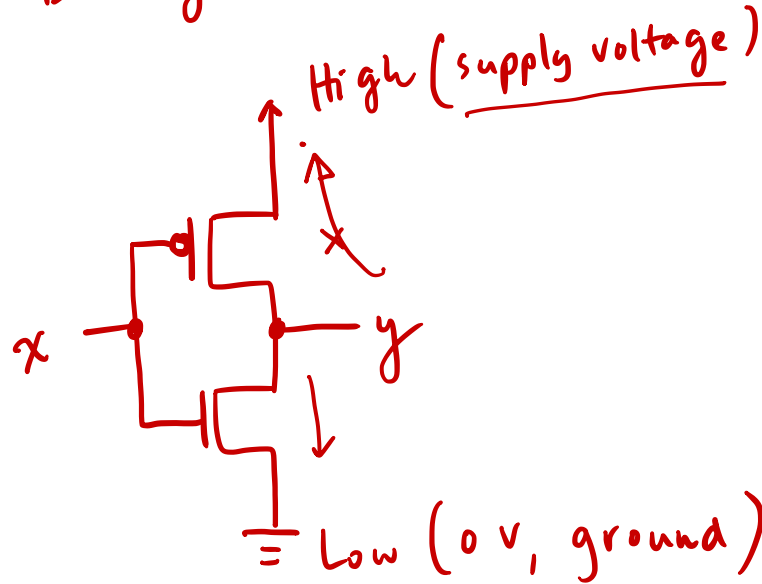

x = High

 


x = low


 




NAND and AND Implementations

 

NAND = AND - NOT

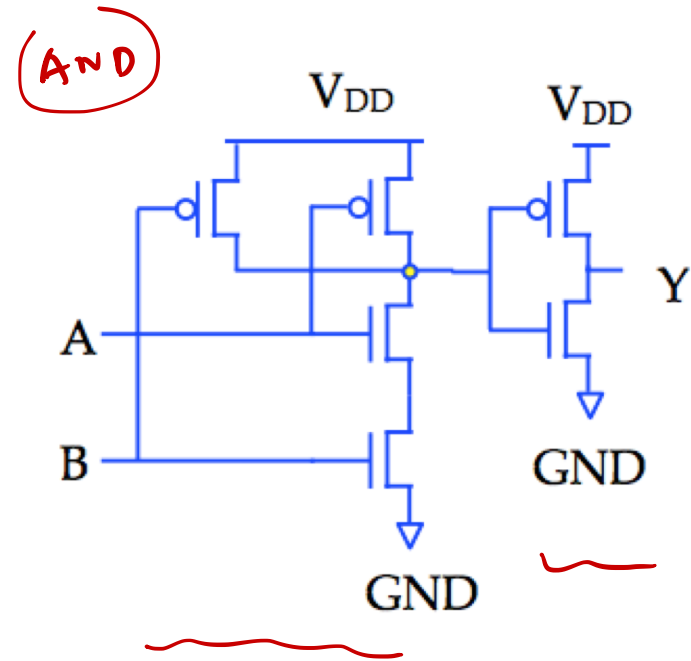 



Basic Gate Implementation

Type	Symbol	Function	# of transistors	Gate delay (ns)
NOT		$F = \bar{x}$	2 ✓	1 ✓
Buffer		$F = x$	4	2 ✓
AND		$F = x \cdot y$	6 ✓	2.4 ✓
OR		$F = x + y$	6 ✓	2.4 ✓
NAND		$F = \overline{x \cdot y}$	4 ✓	1.4 ✓
NOR		$F = \overline{x + y}$	4 ✓	1.4 ✓
XOR		$F = x \oplus y$	14 ✓	4.2
XNOR		$F = \overline{x \oplus y}$	12 ✓	3.2