



# EECS1010 Logic Design

## Lecture 3 Gate-Level Minimization

Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)



# Outline

- Digital systems and information
- Boolean algebra and logic gates
- **Gate-level minimization**
- Combinational logic
- Sequential circuits
- Registers and counters
- Memory



# Chapter Outline

- ✓ • The map method
- Technology mapping
- Hazards



# The Map Method





# Logic Simplification

- For a logic function, its truth-table representation is unique, while its algebraic expression is not unique.
- Complexity of digital circuit (gate count) is proportional to the complexity of algebraic expression (literal count).
- The simplest algebraic expression is one that has minimum number of terms with the smallest possible number of literals in each term.



# Merging Minterms

- The minterms in a function can be merged to form a simpler product term.
- Example:

–  $m_1$  and  $m_3$ :

$$d'c'b'a + d'c'ba = d'c'a(\underline{b'+b}) = \bar{d}\bar{c}a$$

–  $m_2$  and  $m_3$ :

$$\underbrace{d'c'ba'}_{L=8} + \underbrace{d'c'ba}_{L=3} = \underline{\bar{d}\bar{c}b}$$

$$L = 8$$

$$L = 3$$

$$G = 8 + 2 = 10$$

$$G = 3$$

$$G_N = 10 + 3 = 13$$

$$G_N = 3 + 2 = 5$$



# ★ Implicant

$$\begin{aligned} w &= 0 \\ x &= 0 \\ y &= 1 \end{aligned}$$

- Implicant of a function: a product term that is true implies the function is true.

- Example 1: for the prime detector,  $F = \sum m(1, 2, 3, 5, 7, 11, 13)$ .  
 $m_1 = \bar{w} \bar{x} \bar{y} z$

implicants:  $m_1, m_2, m_3, m_5, m_7, m_{11}, m_{13}, \bar{w} \bar{x} y, \dots$

$$m_2 + m_3 = \bar{w} \bar{x} y \bar{z} + \bar{w} \bar{x} y z = \bar{w} \bar{x} y (\bar{z} + z) = \bar{w} \bar{x} y \cdot 1$$

- Example 2:  $F(x,y,z) = \overline{x'yz} + \overline{xy'z} + \overline{xyz'} + \overline{xyz}$ .  
 $= \sum m(?)$

w	x	y	z	F	
0	0	0	0	0	$m_0$
0	0	0	1	1	$m_1$
0	0	1	0	1	$m_2$
0	0	1	1	1	$m_3$
0	1	0	0	0	

$F(x,y,z)$

implicants:  $\bar{x}y\bar{z}, x\bar{y}\bar{z}, xy\bar{z}, xyz, \bar{x}y, yz, xz$

Total: 7 implicants.



# Prime Implicant and Essential Prime Implicant

- Prime implicant (PI)
  - The implicant that cannot be merged into a larger one.
- Essential prime implicant (EPI)
  - The one and only one prime implicant that contains particular minterm of a function.

• Example:  $F(x,y,z)=m_3+m_5+m_6+m_7$

implicants :  $\underline{m_3}, \underline{m_5}, \underline{m_6}, \underline{m_7}, \underline{m_3+m_5}, \underline{m_5+m_7}, \underline{m_6+m_7}$   
(7)

PIs:  $\underline{m_3+m_5} (yz),$   
 3 PIs.  $\underline{m_5+m_7} (xz) \checkmark$   
 $\underline{m_6+m_7} (xy) \checkmark$

EPIs:  $yz, xz, xy$



# Karnaugh Map (K-Map)

- A K-map is a collection of squares.
  - Each square represents a *minterm/maxterm*
  - Each K-map is a graphical representation of a Boolean function.
  - ★ – Adjacent squares differ in the value of *one* variable.
    - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares.
- Each K-map defines a unique Boolean function.
- K-map is a visual diagram of all possible ways a function may be expressed.
  - Provide visual aid to identify PIs and EPIs.
  - Provide a means for finding optimum or near optimum of a Boolean function by combining squares.

# Two-Variable K-Map



$x \backslash y$	0	1
0	$x=0$ $m_0$ $y=0$	$x=0$ $m_1$ $y=1$
1	$x=1$ $m_2$ $y=0$	$x=1$ $m_3$ $y=1$

$x$	$y$	
0	0	$m_0$
0	1	$m_1$
1	0	$m_2$
1	1	$m_3$



# Three-Variable K-Map

	$yz$	00	01	11	10
$x$	0	$x=0$ $m_0$	$x=0$ $y=0, z=1$ $m_1$	$x=0$ $m_3$	$x=0$ $m_2$
	1	$x=1$ $m_4$	$x=1$ $y=0, z=1$ $m_5$	$x=1$ $m_7$	$x=1$ $m_6$

$xy/z$	0	1
00	$m_0$	$m_1$
01	$m_2$	$m_3$
11	$m_6$	$m_7$
10	$m_4$	$m_5$

$$m_0 + m_2 = \bar{x}\bar{z}$$

$$m_2 + m_3 = \bar{x}y$$

$$m_2 + m_6 = \bar{x}y\bar{z} + xy\bar{z} = y\bar{z}(\bar{x} + x) = y\bar{z} \cdot 1 = \underline{\underline{y\bar{z}}}$$

$\downarrow x=1, y=1, z=0$ , minterm  $m = xy\bar{z} = m_6$

maxterm  $m = \bar{x} + \bar{y} + z = M_6$



# Four-Variable K-Map

		yz		y	
	wx	00	01	11	10
	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z			

} x

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$





# Five-Variable K-Map

$A, B, C, D, E$

- For five variable problems, we use two adjacent K-maps. It becomes harder to visualize adjacent minterms for selecting. You can extend the problem to six variables by using four K-maps.

$A = 0$

		DE		D	
		00	01	11	10
BC	00	$m_0$ 0	1	3	2
	01	4	5	7	6
	11	12	13	$m_{15}$ 15	14
	10	8	9	11	10

$E$

$A = 1$

		DE		D	
		00	01	11	10
BC	00	$m_{16}$ 16	17	19	18
	01	20	21	23	22
	11	28	29	$m_{31}$ 31	30
	10	24	25	27	26

$E$



# Covering a Function

- Procedure to select an inexpensive set of implicants
  - Start with an empty cover.
  - Add all essential prime implicants.
  - For the remaining uncovered minterms, add the largest implicant that covers the minterms.
- The procedure results in a good cover, but no guarantee the lowest cost cover.



# K-Map Example 1

$$F(x,y,z) = \Sigma m(2,3,6,7) = \underbrace{(m_3 + m_7)}_{y\bar{z}} + \underbrace{(m_2 + m_6)}_{y\bar{z}} = y\bar{z} + y\bar{z} = y$$

$x \backslash yz$	00	01	11	10
0	0	0	1	1
1	0	0	1	1

Handwritten annotations: Circles around the 1s in the right two columns. A green arrow points to the right side of the map with the label  $y=1$ .

implicants:  $m_2, m_3, m_6, m_7, y\bar{z}, y\bar{z}, y$ .  
 (9)  
 $m_2 + m_3 (\bar{x}y), m_6 + m_7 (xy)$

PIs:  $y$   
 EPIs:  $y$

$$G(x,y,z) = \Sigma m(3,4,6,7)$$




# K-Map Example 1

$$F(x,y,z) = \sum m(2,3,6,7) = \underline{(m_3 + m_7)} + \underline{(m_2 + m_6)} = y\bar{z} + yz = y$$

$x \backslash yz$	00	01	11	10
0	0	0	1	1
1	0	0	1	1

$y=1$

implicants:  $m_2, m_3, m_6, m_7, y\bar{z}, yz, y$   
 (9)  $m_2+m_3(\bar{x}y), m_6+m_7(xy)$

PIs:  $y$   
 EPIs:  $y$

W

Practice

$$G(x,y,z) = \sum m(3,4,6,7)$$


$$F = m_3 + m_4 + m_6 + m_7$$


---



# K-Map Example 2

$$F(w,x,y,z) = \Sigma m(0,2,4,5,6,7,8,10,11,15)$$

	00	01	11	10
00	1 <sup>m<sub>0</sub></sup>	0 <sup>m<sub>1</sub></sup>	0 <sup>m<sub>3</sub></sup>	1 <sup>m<sub>2</sub></sup>
01	1 <sup>m<sub>4</sub></sup>	1 <sup>m<sub>5</sub></sup>	1 <sup>m<sub>7</sub></sup>	1 <sup>m<sub>6</sub></sup>
11	0 <sup>m<sub>12</sub></sup>	0 <sup>m<sub>13</sub></sup>	1 <sup>m<sub>15</sub></sup>	0 <sup>m<sub>14</sub></sup>
10	1 <sup>m<sub>8</sub></sup>	0 <sup>m<sub>9</sub></sup>	1 <sup>m<sub>11</sub></sup>	1 <sup>m<sub>10</sub></sup>

$$F = \bar{w}x(\bar{y}\bar{z} + \bar{y}z + y\bar{z} + yz) + \bar{x}\bar{z}$$

$$+ wyz$$

$$= \bar{w}x + \bar{x}\bar{z} + wyz$$

$$L = 7$$

$$G = 7 + 3 = 10$$

$$GN = 10 + 3$$

$$= 13$$

implicants:  $m_0, m_2, \dots, m_{11}, m_{15}, \bar{w}\bar{y}\bar{z}, \dots$

Prime implicants:  $\bar{w}x, \bar{x}\bar{z}, wyz, \bar{w}\bar{z}, xy\bar{z}, w\bar{x}y$

EP1:  $\bar{w}x, \bar{x}\bar{z}$



# K-Map Example 3

$B=0$   
 $C=1$   
 $D=0$

$$F(A,B,C,D) = \underline{B'CD'} + \underline{A'B'C'} + \underline{A'BCD'} + \underline{AB'C'}$$

Practice: optimize F using Boolean algebra.

AB \ CD	00	01	11	10
00	1	1	0	1
01	0	0	0	1
11	0	0	0	0
10	1	1	0	1

$$F = \bar{B}\bar{D} + \bar{B}\bar{C} + \bar{A}C\bar{D}$$

Prime implicants:  $\bar{B}\bar{D}$ ,  $\bar{B}\bar{C}$ ,  $\bar{A}C\bar{D}$


EPIs:  $\bar{B}\bar{D}$ ,  $\bar{B}\bar{C}$ ,  $\bar{A}C\bar{D}$



# Cube Method

- Implicants can be visualized on a cube.
  - Vertex: Gray-coded minterm
  - Edge: product (implicant) consisting of 2 minterms
  - Shaded face: product (implicant) consisting of 4 minterms

$$f = \sum m(1,2,3,5,7)$$

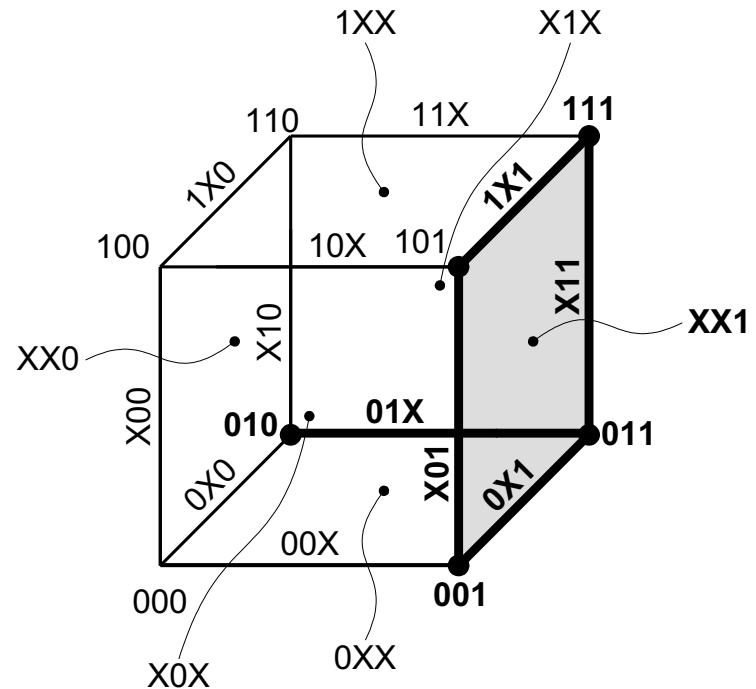




Practice

# 4D Hypercube for 4-Bit Input

$$f = \sum_{dcba} m(1,2,3,5,7,11,13)$$



- Shaded face:

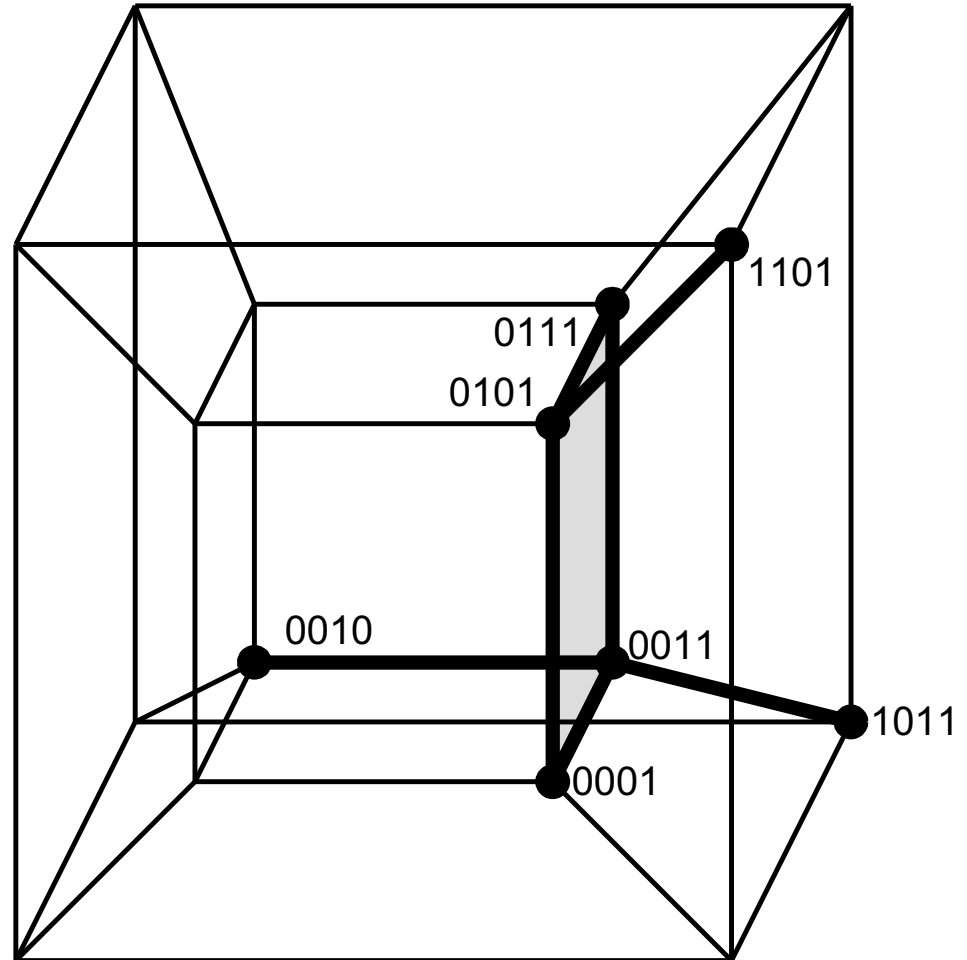





## Example: PIs and EPIs

- $F = \Sigma m(0,1,4,5,7,10)$



# Non-Unique Minimum Covering

- When there is no essential prime implicants, more than one solution exist.

		a			
		00	01	11	10
c	0	1 <sub>0</sub>	0 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
	1	1 <sub>4</sub>	1 <sub>5</sub>	1 <sub>7</sub>	0 <sub>6</sub>
		b			

$$F = \bar{b}\bar{a} + ca + \bar{c}b$$

		a			
		00	01	11	10
c	0	1 <sub>0</sub>	0 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
	1	1 <sub>4</sub>	1 <sub>5</sub>	1 <sub>7</sub>	0 <sub>6</sub>
		b			

$$F = \bar{c}\bar{a} + c\bar{b} + ba$$

- All product terms are not EPIs.



# K-Map Summary

- Any  $2^k$  adjacent squares,  $k = 0, 1, \dots, n$ , in an  $n$ -variable map represent an area that gives a product term of  $n-k$  literals.

K	# of adjacent squares	# of literals in a term in an n-variable map			
		n=2	n=3	n=4	n=5
0	1	2	3	4	5
1	2	1	2	3	4
2	4	0	1	2	3
3	8		0	1	2
4	16			0	1
5	32				0



## Example: From Cover to Gates

$$f(d, c, b, a) = d'a + d'c'b + cb'a + c'ba$$

Practice .



# Don't Care

- The output value need not be defined:
  - The input values for the minterm will never occur, or
  - The output value for the minterm is not used
  - Instead, the output value is defined as a “don't care”
- By placing “don't cares” (“x”) in the map, the cost of the logic circuit may be lowered.
- Example: A logic function using BCD digits as its inputs.

A hand-drawn Karnaugh map for BCD digits. The vertical axis is labeled 'w' and 'x' with values 00, 01, 11, 10. The horizontal axis is labeled 'y' and 'z' with values 00, 01, 11, 10. The map contains the following values: 0000 is 0, 0001 is 0, 0011 is 1, 0010 is 1, 0100 is x, 0101 is x, 0111 is x, 0110 is x, 1100 is x, 1101 is x. A green circle highlights the 1s in the 0011 and 0010 cells. A red circle highlights the 'x' in the 0111 cell.

w \ x	yz	00	01	11	10
00		0			0
01	0			1	1
11	x	x	x	x	
10			x	x	






# Example: Boolean Function with Don't Cares

- $F = \Sigma m(1,2,3,5,7) + \underline{\underline{d}}(10, 11, 12,13, 14, 15).$

$w \backslash yz$	00	01	11	10
00	0	1	1	1
01	0	1	1	0
11	x	x	x	x
10	0	0	x	x

$$F = \bar{w}z + \bar{x}y$$

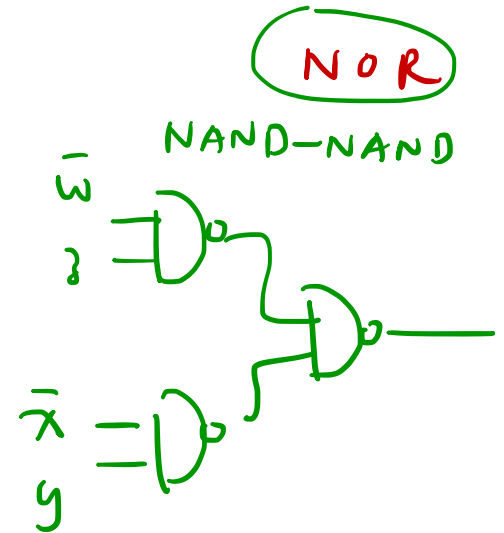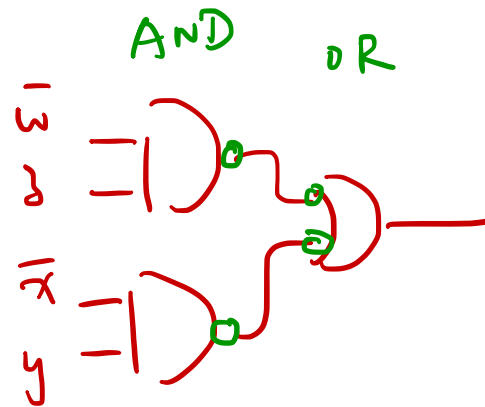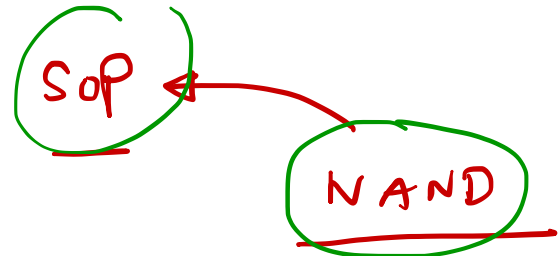



# Product of Sums Simplification



- Based on DeMorgan's Theorem  $\bar{F} : \text{SOP} \Rightarrow \bar{\bar{F}} = \overline{\text{SOP}} =$ 
  - Choose 0's in the k-map: simplified  $F'$  in the form of sum of products
  - Apply DeMorgan's theorem
  - $F'$ : sum of products
  - $F$ : product of sums



# Example: Product of Sums Simplification

$$F(w,x,y,z) = \sum m(0,1,2,5,8,9,10)$$

$wx \backslash yz$	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

POS (cover 0's)

$$\bar{F} = yz + x\bar{z} + wx$$

$$F = \bar{\bar{F}} = \overline{(yz + x\bar{z} + wx)}$$

$$= (\bar{y}\bar{z}) \cdot (\bar{x}\bar{z}) \cdot (\bar{w}\bar{x})$$


$$= (\bar{y} + \bar{z}) \cdot (\bar{x} + z) \cdot (\bar{w} + \bar{x}) \quad \text{POS}$$





# Simplification Example 1


$F(w, x, y, z) = \pi(13, 15)$

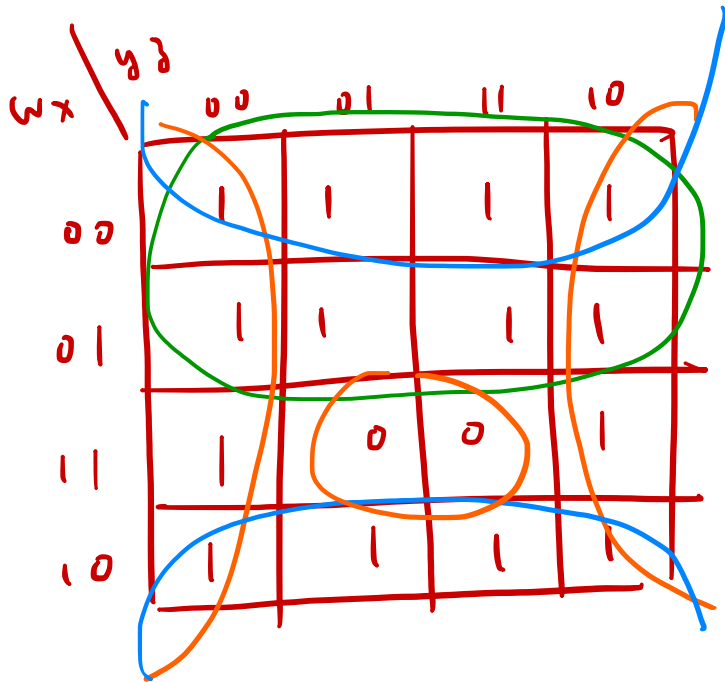


SOP

$$F = \bar{w} + \bar{z} + \bar{x}$$
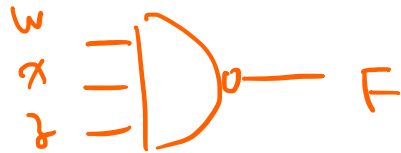
$$\bar{F} = w x z \quad \bar{\bar{F}} = (\bar{w} \bar{x} \bar{z}) = \bar{w} + \bar{x} + \bar{z}$$



NAND

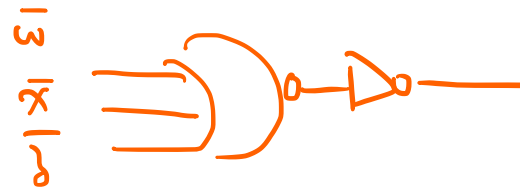

NOR