



# EECS1010 Logic Design

## Lecture 7 Memory 不考


Jenny Yi-Chun Liu

[jennyliu@gapp.nthu.edu.tw](mailto:jennyliu@gapp.nthu.edu.tw)


 
# Outline

- Digital systems and information
- Boolean algebra and logic gates
- Gate-level minimization
- Combinational logic
- Sequential circuits
- Registers and counters
- **Memory**



# Memory Definitions (1/3)



- Memory: a collection of cells capable of storing binary information together with necessary circuits to transfer information.
- Read operation: transfers the stored information out of memory.
- Write operation: stores new information into memory.
- Random Access Memory (RAM): a memory that can transfer data to or from any cell with the same access time.

16 bits

32 bits

64 bits



# Memory Definitions (2/3)

- Memory address: a vector of bits that identifies a particular memory element.

G  $10^9$   $2^{30}$   
M  $10^6$   $2^{20}$   
K  $10^3$   $2^{10}$

- Typical data elements are:

- Bit: a single digit
- Byte: a collection of 8 bits
- Word: a collection of binary bits whose size is a typical unit of access for the memory.

$2^{30} \times 8$   
↓  
8GB




## Memory Definitions (3/3)

- RAM: random-access memory
  - Volatile (information lost when power is off)
  - Read/write operation
- ROM: read-only memory
  - Nonvolatile
  - Information in ROM cannot be re-written.


 
# Memory Block Diagram

- I/Os:
  - n data inputs
  - n data outputs
  - k address lines
  - 2 control inputs
- $2^k * n$  (depth\*width) memory




$2^2 \times 6$  memory

k Address Lines

Read  
Write

Read/Write  
= 1 Read  
= 0 Write

n Data Input Lines

 

n Data Output Lines



# Basic Memory Operations (1/2)

- Address of a memory:  $k$  bits ( $0 \sim 2^k - 1$  words)

$k \rightarrow 2^k$

- Decoder accepts the address and opens the path selected.
- A memory has two parts:
  - Memory cells that store data.
  - Decoding circuits that select the word.

# Basic Memory Operations (2/2)



- Read memory – an operation that reads a data value stored in memory.
  - Apply the binary address to the address line.
  - Activate the read control input.
- Write memory – an operation that writes a data value to memory.
  - Apply the binary address to the address line.
  - Apply the data to the data input lines.
  - Activate the write control input.





# Memory Integrated Circuits

- Types of random access memory (RAM)
  - Static: information stored in latches. (SRAM)
  - Dynamic: information stored as electrical charges on capacitors. (DRAM)
- Dependence on power supply
  - Volatile: information is lost when power turns off. RAM
  - Non-volatile: retains information when power is off. ROM, Flash






# Timing of Memory

- The operation of a memory unit is controlled by an external device such as a CPU.
- The access time is the time required to select a word and read it.
- The write cycle time is the time required to complete a write operation.
- Read and write operations are controlled by a CPU and synchronized with a clock.



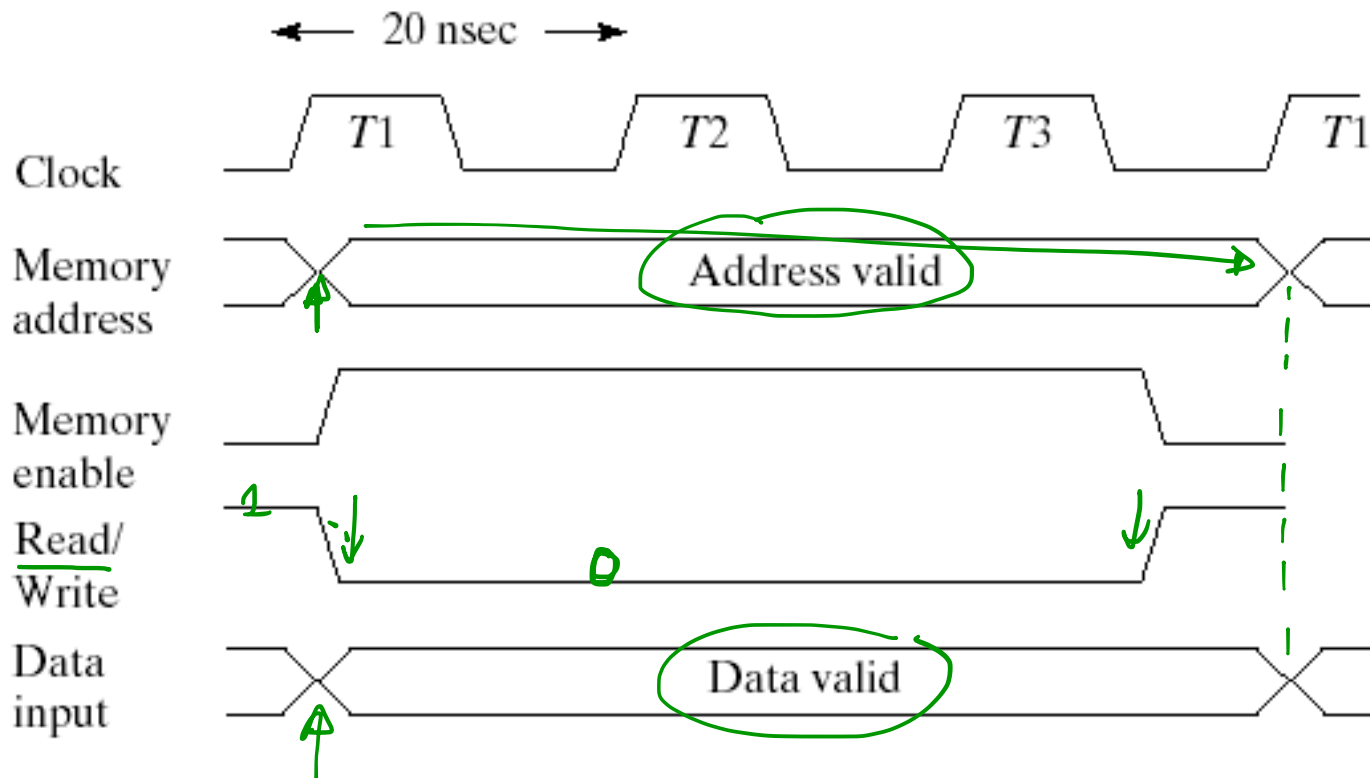
# The Write Cycle

- At T1: provides the address and input data to the memory and the read/write control signal.






# The Read Cycle

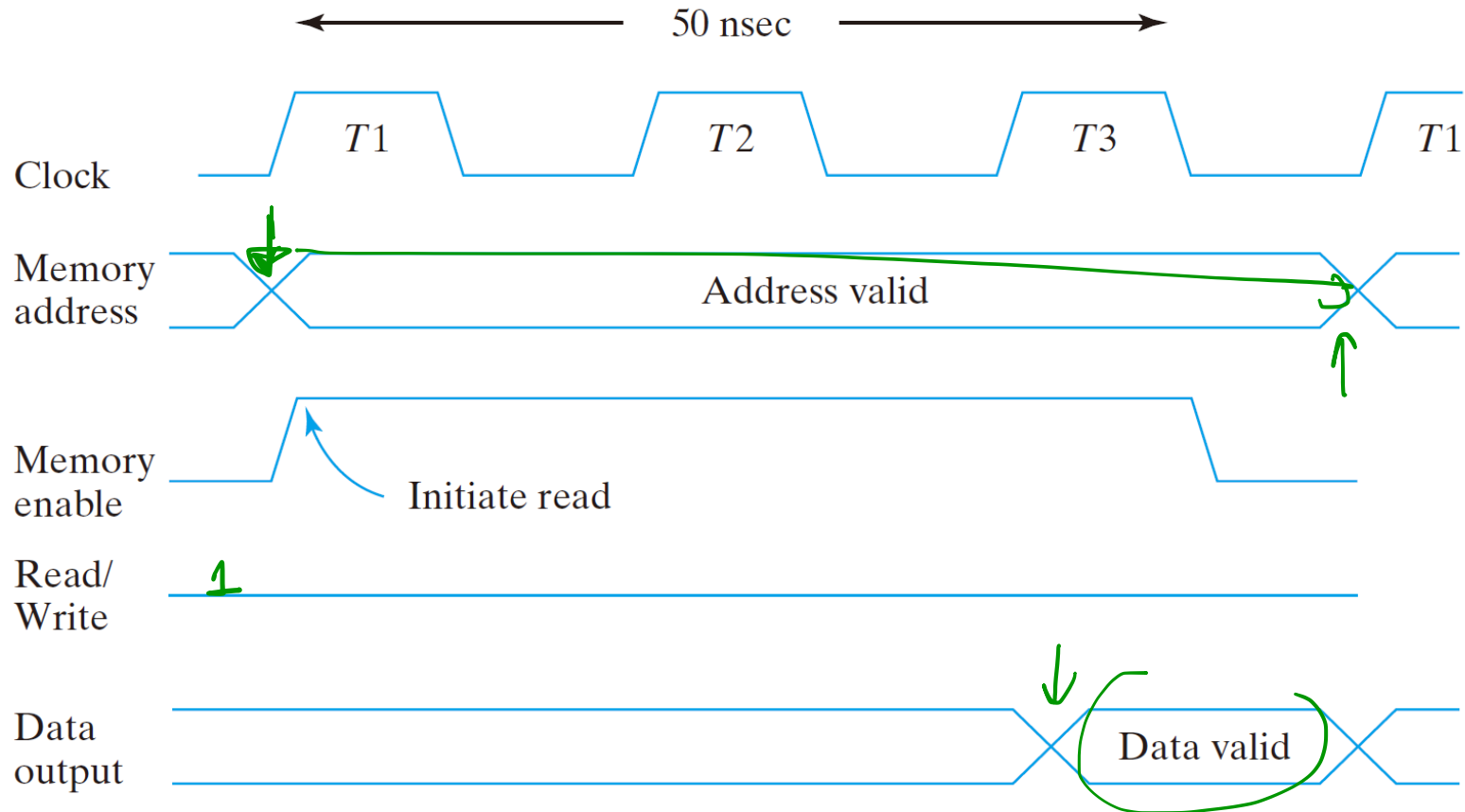



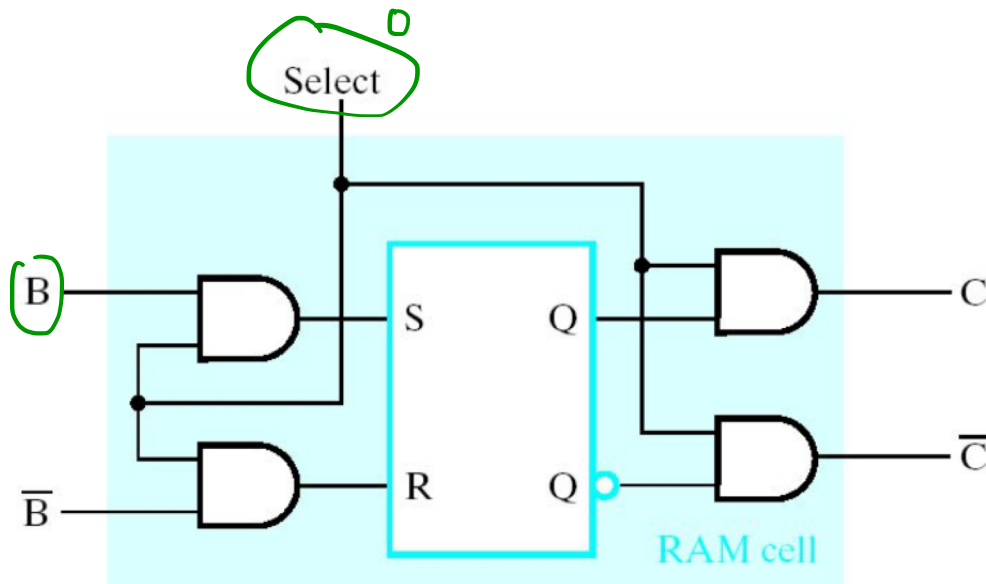
# Static RAM Cell

- Array of storage cells used to implement static RAM.
- Storage cell : SR latch, ANDs




Function table

Select	B	C	$\bar{C}$	
0	X	0	1	
1	0	0	1	reset
1	1	1	0	set

 
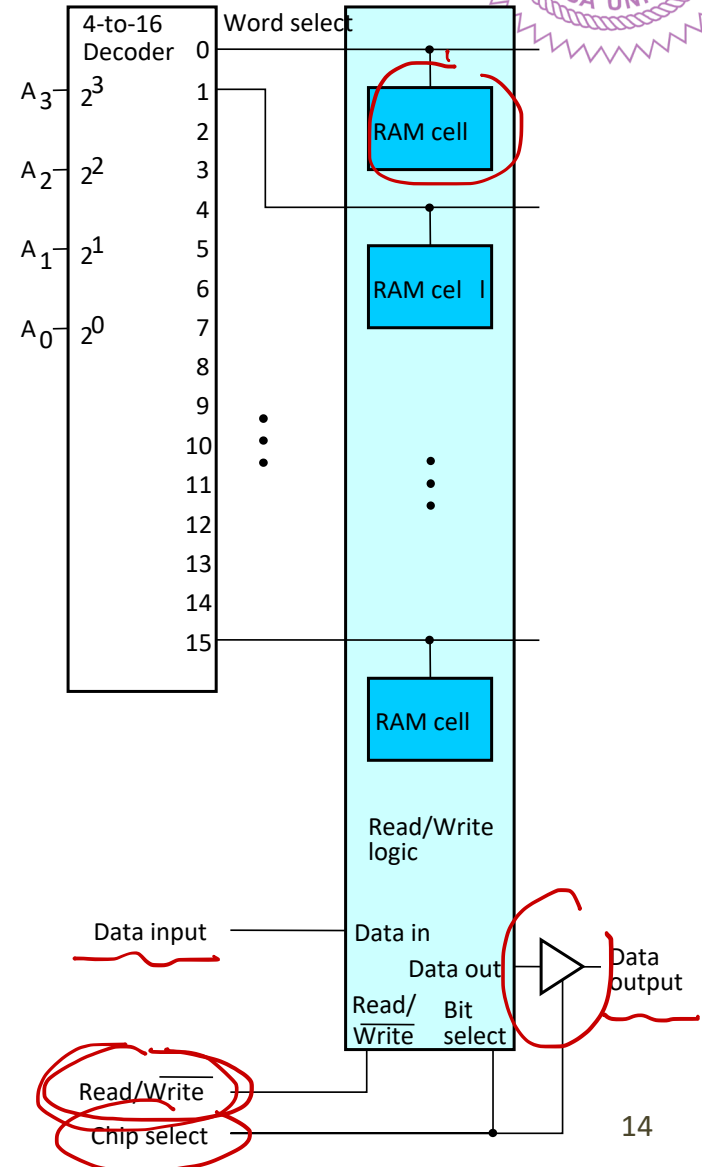
# $2^4 \times 1$ 16-Word $\times$ 1-Bit RAM IC


- I/Os:
  - 4 address inputs ( $A_3, A_2, A_0, A_1$ )
  - Data input (1 bit)
  - Data output (1 bit)
  - Read/write control input
  - 4-to-16 decoder
  - 16 RAM cells




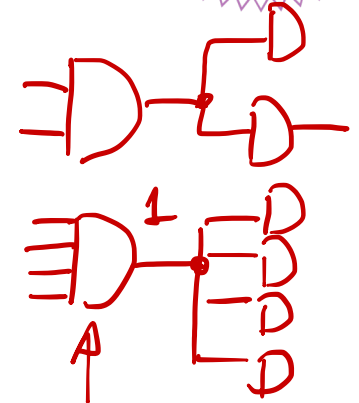
# Cell Arrays and Coincident Selection (1/2)

- Memory arrays can be very large
  - Large decoder:  $K$ -to- $2^K$
  - Read/write shared by many RAM cells




- The decoder size and the number of inputs per gate can be reduced by using a coincident selection in a 2D array.


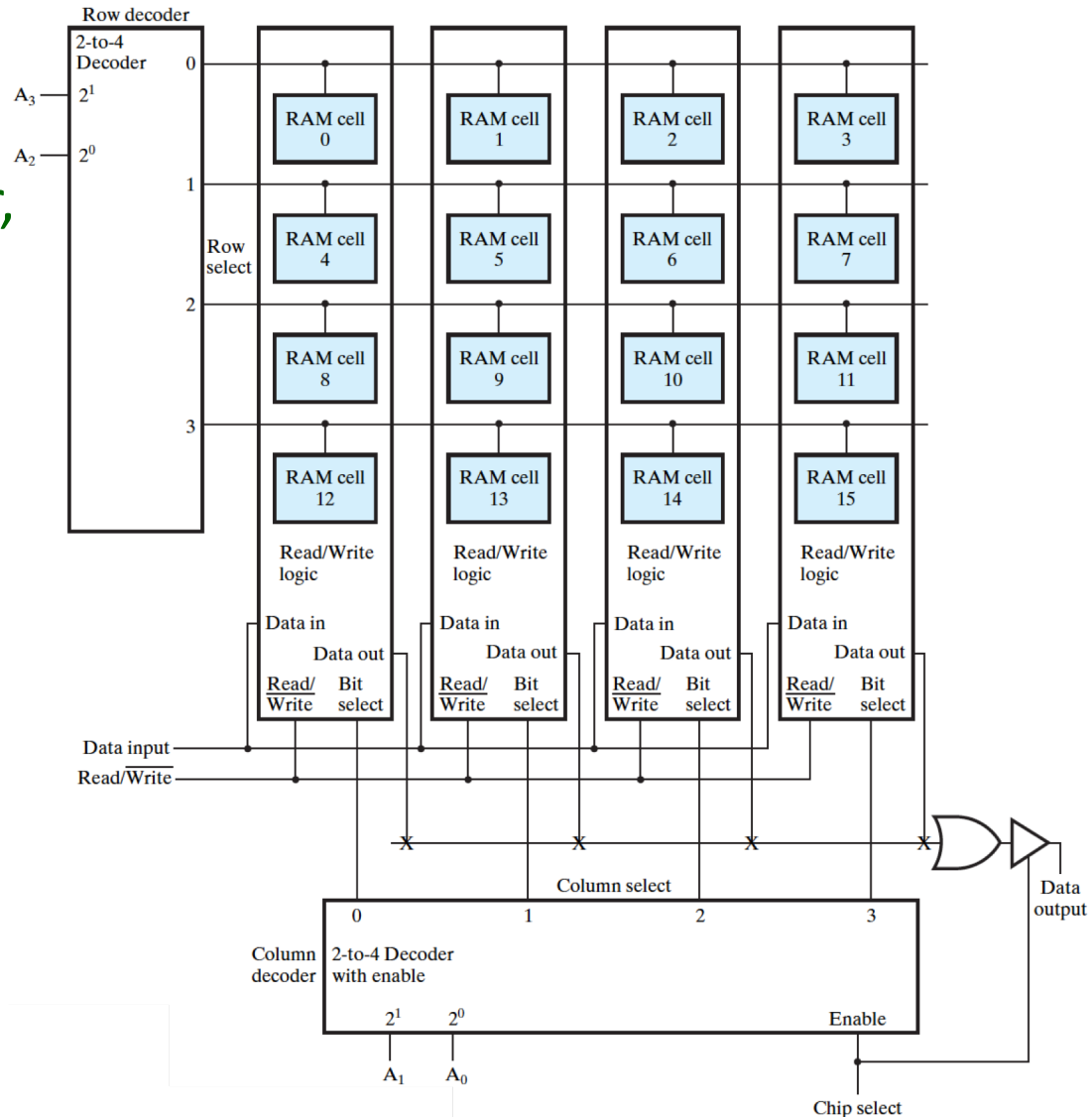
# Cell Arrays and Coincident Selection (2/2)

- Instead of one 4-to-16 line decoder, use two 2-to-4 line decoders.








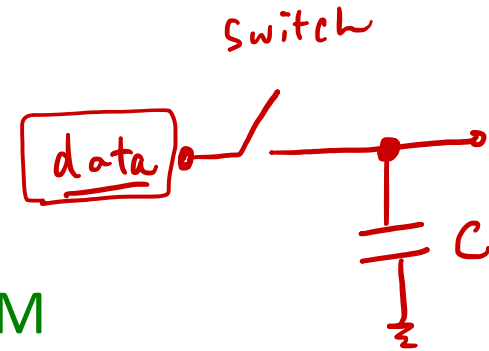
# Dynamic RAM (1/2)

- DRAM: stores information temporarily
  - High storage capacity
  - Low cost
  - Design is more challenging than SRAM
  - Needs periodically refresh
- Basic principle: charge and discharge the capacitor





# Dynamic RAM (2/2)

 




# SRAM vs. DRAM

- SRAM
  - 6 transistors
  - Faster access time
- DRAM
  - 1 transistor + 1 capacitor
  - Slower access time
  - Smaller area
  - Smaller power
  - Higher storage capacity
  - ~~– Destructive read~~



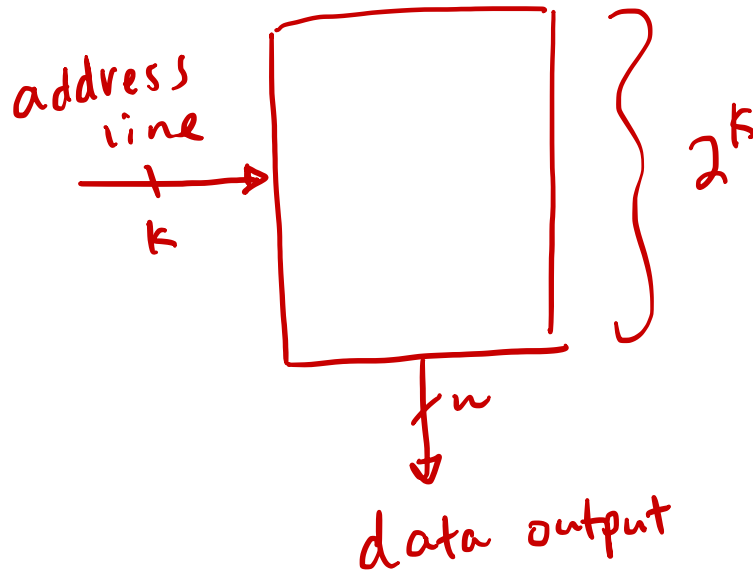
# ROM


- Read-only memory: stores the information permanently.
- The data stores in ROM whether the power is on or off.
- $2^k * n$  ROM



ROM: decoder + OR gates.

# ROM Example $2^5 \times 8$ bits

 

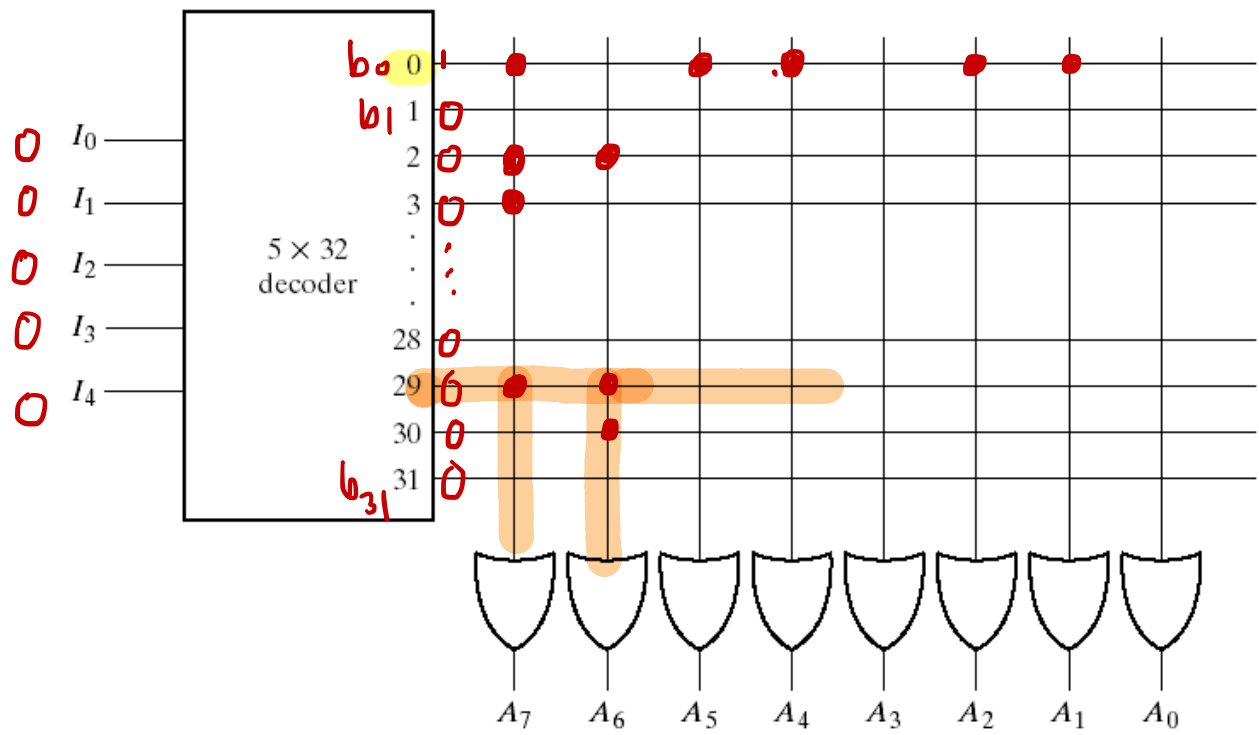

$b_0 + \dots$

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮					⋮					
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1



# Combinational Circuit Implementation

- ROM: decoder + OR gates
- For n-input, m-output combinational circuit, we can use  $2^n \times m$   
( $n$ -to- $2^n$  decoder,  $m$  OR gates)